

LAPLACE TRANSFORMS FOR ELECTRONIC ENGINEERS

by

JAMES G. HOLBROOK

Senior Engineer

Varian Associates, Palo Alto, California

SECOND (REVISED) EDITION



PERGAMON PRESS

OXFORD · LONDON · EDINBURGH · NEW YORK
TORONTO · SYDNEY · PARIS · BRAUNSCHWEIG

Pergamon Press Ltd., Headington Hill Hall, Oxford
4 & 5 Fitzroy Square, London W.1

Pergamon Press (Scotland) Ltd., 2 & 3 Teviot Place, Edinburgh 1

Pergamon Press Inc., Maxwell House, Fairview Park, Elmsford,
New York 10523

Pergamon of Canada Ltd., 207 Queen's Quay West, Toronto 1

Pergamon Press (Aust.) Pty. Ltd., 19a Boundary Street,
Rushcutters Bay, N.S.W. 2011, Australia

Pergamon Press S.A.R.L., 24 rue des Écoles, Paris 5^e

Vieweg & Sohn GmbH, Burgplatz 1, Braunschweig

Copyright © 1959 and 1966 Pergamon Press Ltd.

First edition 1959

Second (revised) edition 1966

Reprinted 1969

Library of Congress Catalog Card No. 59-12607

Printed in Great Britain by A. Wheaton & Co., Exeter

PREFACE TO THE FIRST EDITION

THIS book is written primarily for the practicing electronics engineer. It will be of most interest and benefit to those who devote a portion of their leisure time to self-study and improvement. The material covers a rather wide area of modern ideas, concepts, methods, and logic, but is arranged and presented in a manner which will allow the conscientious electronics engineer to advance gradually and consistently to a thorough and practical knowledge of Laplace transform theory.

Laplace transform theory is difficult to express in a brief, clear, concise definition. Its purposes are many and varied. Perhaps a good starting definition for the electronics engineer is to observe that:

Laplace transform theory is a philosophy of logic and analytical reasoning which allows one to analyze and synthesize electronic circuitry, networks, filters, oscillators, servo-systems, etc., with much less effort and far more accuracy and depth of understanding than most engineers can develop when using older methods.

It will be assumed at the outset that the electronic engineers who study this text will have completed the usual college level courses in differential and integral calculus, as well as the usual B.S. courses in circuit analysis.

There is today a growing tendency in many colleges and universities to present a course in Laplace transform theory in the undergraduate program, and the relative merits are being argued for and against such an undergraduate course. It is true that a good background in Laplace transform theory gives one far more insight into the useful and interesting phases of advanced circuitry and networks than the usual introductory work with the j -operator alone; however, it must also be admitted that the usual college courses in classical steady-state circuit analysis are presented while the student is still in the process of finishing his studies of the calculus, and certainly long before he has had the advantages of any graduate courses in subjects such as vector analysis or complex variable theory. It would seem that to inject a Laplace transform course at such a period would deprive the student of the more firm development that he could attain were he to receive the classical circuit

analysis courses (adequate for his undergraduate level work) and then to study the more advanced Laplace transform theory after having had a chance to digest his calculus, and gain some measure of practical experience with it. The writer will not attempt to take sides, except to observe that time will eventually tell at what scholastic level the Laplace transform theory should be introduced for maximum effectiveness.

Laplace transform theory allows one to perform a complete analysis of electronic network problems, in contrast with the "steady-state" solution arrived at by classical network analysis using the j -operator. When the reader recalls that the terms "inductive reactance," and "capacitive reactance" are only valid when speaking strictly of sine wave excitation, and become meaningless when applied to any of the many waveshapes we use today, he should see the vital necessity of devoting a moderate amount of time to the study of more general methods and ways of thinking. The Laplace transform is a general method, and permits the introduction of any waveshape into the network being analyzed.

To begin the text directly with a derivation of the Laplace integral would be to assume a good working knowledge of functions of a complex variable. This would make the book unreadable to a large number of highly skilled engineers who entered the electronic industry after receiving their first degree, but who have not had occasion to acquire a complex variable course as background. I have therefore chosen to begin the book with a review of complex variable theory as applicable to the Laplace transform. By the time he is finished with Chapter I, the reader will be speaking casually of poles, zeros, residues of functions and integration in the complex plane. The actual Laplace transform theory begins in Chapter II and occupies the remainder of the book.

The emphasis throughout has been on a clear, free style of writing. It is rigorous and thorough, but devoid of the heavily abstract terminology of pure mathematics which so often defeats self-study. Symbolism and definitions are explained in simple terms as they are introduced, and some proofs of theorems, unless germane to the discussion, are omitted. The real purpose of the text is to allow the practicing electronics engineer to develop and expand his knowledge of circuitry and networks by a careful program of study of the modern method of Laplace transform theory and applications.

I am most indebted to numerous friends and associates who have

contributed to the text in one way or another. My special interest began while attending a semester of lectures given by Dr. Charles R. Hausenbauer, of the University of Arizona. His superb presentation of Laplace transform theory was truly outstanding, and notes taken from his lectures served as a basis for much of Chapter II.

Many of the concepts presented throughout the text have evolved gradually during the past century, and it is doubtful if the origin of most of them is properly known. The writer, therefore, must express general thanks to one and all whose original work has been sampled, and must, of course, assume full responsibility for such errors in presentation as may occur.

Thanks are due also to Dorothy Deuel, who typed much of the manuscript, and to numerous engineers who assisted in editing and checking equations at various times. The writer will feel amply rewarded if the book provides someone with a few pleasant weeks of suggestive thought. Best wishes to you as you begin your trip into the new world of the s -domain.

JAMES G. HOLBROOK

Santa Maria, California
September, 1958.

PREFACE TO THE SECOND EDITION

LAPLACE transform theory has become a basic part of electronic engineering study. Its influence is apparent in almost every area of network analysis and synthesis. In addition to its theoretical value, the Laplace transformation is immediately applicable to everyday engineering problems which arise in the design of oscillators, amplifiers, filters, and other electronic networks.

The objectives of this book are twofold: First, to provide a substantial theoretical background in the Laplace transformation. This includes applicable introductory material on complex variable theory, and treatment of the various Laplace transform theorems. The second objective is to offer a broad introduction to practical applications of the theory. In almost every case the applications have been chosen from electronic engineering problems. Thus, a large number of applications deal with amplifiers, oscillators, and both passive and active wave filters.

For engineering applications, an attempt has been made to choose

contributed to the text in one way or another. My special interest began while attending a semester of lectures given by Dr. Charles R. Hausenbauer, of the University of Arizona. His superb presentation of Laplace transform theory was truly outstanding, and notes taken from his lectures served as a basis for much of Chapter II.

Many of the concepts presented throughout the text have evolved gradually during the past century, and it is doubtful if the origin of most of them is properly known. The writer, therefore, must express general thanks to one and all whose original work has been sampled, and must, of course, assume full responsibility for such errors in presentation as may occur.

Thanks are due also to Dorothy Deuel, who typed much of the manuscript, and to numerous engineers who assisted in editing and checking equations at various times. The writer will feel amply rewarded if the book provides someone with a few pleasant weeks of suggestive thought. Best wishes to you as you begin your trip into the new world of the s -domain.

JAMES G. HOLBROOK

Santa Maria, California
September, 1958.

PREFACE TO THE SECOND EDITION

LAPLACE transform theory has become a basic part of electronic engineering study. Its influence is apparent in almost every area of network analysis and synthesis. In addition to its theoretical value, the Laplace transformation is immediately applicable to everyday engineering problems which arise in the design of oscillators, amplifiers, filters, and other electronic networks.

The objectives of this book are twofold: First, to provide a substantial theoretical background in the Laplace transformation. This includes applicable introductory material on complex variable theory, and treatment of the various Laplace transform theorems. The second objective is to offer a broad introduction to practical applications of the theory. In almost every case the applications have been chosen from electronic engineering problems. Thus, a large number of applications deal with amplifiers, oscillators, and both passive and active wave filters.

For engineering applications, an attempt has been made to choose

subjects which have not been widely discussed in the popular literature. It is hoped that most readers will discover at least one or two applications which they find completely new and stimulating. Examples might be the use of Pascal's triangle in finding the transfer functions of iterated networks, the treatment of single-band wide range oscillators, and charge amplifiers.

Although not intended as a substitute for a formal course in either network analysis or synthesis, the book provides the reader with a substantial background in several of the more useful classes of filter networks. It is expected that the reader will be able to make profitable and immediate use of these filter concepts in his practical engineering work.

The plan of the book remains as in the first edition. Some of the material has been rewritten, much new material has been added, and many original articles have been expanded to provide more complete and detailed treatment. As in the first edition, it will be assumed that the reader has completed the initial courses in differential and integral calculus.

In preparing this second edition, the writer is indebted to the many readers who have taken the time to comment on parts of the book and to point out errors. I have tried to minimize errors by having the manuscript carefully reviewed by numerous people, but I know that a few errors will inevitably creep in. Hopefully these will be limited to minor misprints which the reader will spot in following details of the text.

I would particularly like to express appreciation to Dr. Robert Codrington, and to James Jacobsen, John Larson, William Simons, and other scientists and engineers on the Varian staff for their assistance. Miss Margaret Little has provided most welcomed secretarial and photo-reproduction services. A special thank-you must also go to Dr. Kazuo Miyawaki, Professor of Engineering at Osaka University, who has translated the first edition into Japanese. Miss Michiko Ichibara merits thanks for her assistance in preparation of the manuscript for the Japanese edition.

JAMES G. HOLBROOK

Palo Alto, California

CHAPTER I
FUNCTIONS OF A COMPLEX VARIABLE

1.1. Introduction

AN introductory course on the functions of complex variables usually lasts for one semester and takes one through the major part of a sizeable text devoted exclusively to that subject. We must therefore limit our objective in this first chapter to presenting only those elements of complex variable theory which are actually necessary for the logical development of the Laplace transform material which will occupy the remainder of the book.

From Chapter II on, we will do most of our traveling in the complex world of the s -domain, carrying out the major part of the work in this new and interesting territory, and returning home to our real world of the familiar time, or t -domain, only to convert the results into suitable form for practical use. Fortunately, as the reader spends more and more time in the new world of the s -plane, he begins first to gradually take up the speech, and later to actually think in the new language of the s -world. Of course, when one actually thinks in a new language it is no longer necessary to translate back into the original. This is the real goal of the text, to enable the reader to visualize his circuitry and networks in the s -domain.

It is strongly recommended that the reader does not hurry in studying the material to follow. A good rule for self-study would be to set a definite, self-enforced limit of one numbered article per day. Self-study at a faster rate will most likely cause the reader to start neglecting fine points and missing new concepts as they are presented. With this mild word of caution, we now proceed to work.

1.2. Complex numbers

Algebra, of course, has been studied for centuries, and the early mathematicians who encountered the square roots of negative numbers merely labeled such quantities as imaginary, because

no one in those days had assigned any meaning to such numbers. It was not until 1797 that the Norwegian surveyor, Casper Wessel, in a paper read before the Royal Academy of Denmark, brought out the fact that since

$$(\sqrt{-1})^2 = -1 \quad (1.1)$$

and since the -1 could be looked upon as a unit vector which had been rotated through 180° from the standard position shown in

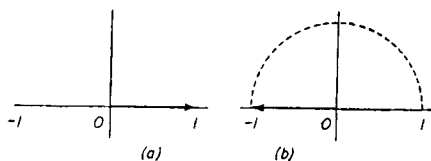


Fig. 1.1

Fig. 1.1(a), then the $\sqrt{-1}$ could be considered as a unit vector which had been rotated only half-way around from the standard position, and stopped as shown in Fig. 1.2.

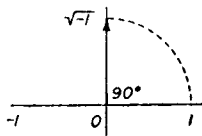


Fig. 1.2

Now the idea of negative numbers had already been long accepted, as they were relatively easy to picture along a one-dimensional line as a magnitude to the right or left of some arbitrary zero reference, as in Fig. 1.3. Using the new concept of Wessel, one could then

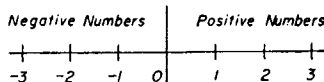


Fig. 1.3

suppose that any positive number in Fig. 1.3 might be considered as a simple vector from 0 to the number, and that this vector could be rotated half-way around by multiplying it by $(\sqrt{-1})^2$, or one-quarter way around by multiplying only by $\sqrt{-1}$. Thus the positive number 3, Fig. 1.4(a), can be rotated 90° by multiplying it by

$\sqrt{-1}$, and shown in Fig. 1.4(b). This special rotating property leads us to call the $\sqrt{-1}$ an operator, and we assign the symbol j to represent it.

The symbol j allows us to mark off a vertical line at right angles to the horizontal line of Fig. 1.3, thereby creating a two-dimensional

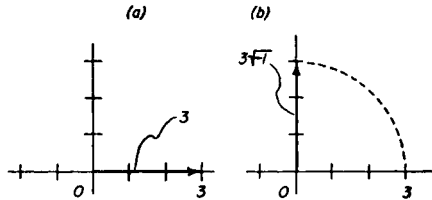


Fig. 1.4

surface, rather than a single line. This surface will be called the complex plane. We note in passing that

$$\left. \begin{aligned} j^2 &= -1 \\ j^3 &= -j \\ j^4 &= 1 \\ j^5 &= j, \text{ etc.} \end{aligned} \right\} \quad (1.2)$$

The complex plane may be thought of as a map whereon it is possible to locate any number (point) by specifying its distances x and y , measured from zero in the horizontal and vertical directions.

The complex number p , $4 + j3$, is shown in the complex plane as the sum of two components 4 and $j3$ (Fig. 1.5(a)), and as a single

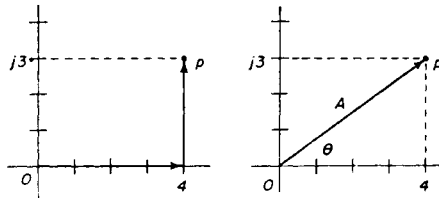


Fig. 1.5

vector $(4 + j3)$ in Fig. 1.5(b). The complex number p is of course the same quantity, or point, either way.

There are two basic ways of describing the location of a complex

number such as p in the complex plane. The first, called the rectangular, or algebraic form, locates the complex number by giving its xy components as

$$p = 4 + j3$$

or in general

$$p = x + jy \quad (1.3)$$

The second way of describing the location of a complex number is to give its magnitude A as well as its direction, or angle θ . It is noted that in Fig. 1.5(b)

$$A = \sqrt{4^2 + 3^2} = 5$$

$$\theta = \tan^{-1} \frac{3}{4} = 36.9^\circ$$

so that

$$p = 5 \angle 36.9^\circ$$

or in general

$$p = A \angle \theta \quad (1.4)$$

which is read “ p equals the magnitude A at an angle of θ degrees”. This is called the polar form.

The rectangular form and the polar form are equally useful, although there are advantages to using one form or the other in a given case. It is easy to convert from one form to the other, because we see from Fig. 1.5(b) and equation (1.3) that

$$x = A \cos \theta \quad (1.5)$$

and

$$y = A \sin \theta \quad (1.6)$$

thus equation (1.3) may be re-written as

$$p = A(\cos \theta + j \sin \theta) \quad (1.7)$$

Now the factor $(\cos \theta + j \sin \theta)$ may be simplified by the use of Euler's theorem, which says

$$\cos \theta + j \sin \theta = e^{j\theta} \quad (1.8)$$

This identity is shown to be true by adding the infinite series for $\cos \theta$ to the infinite series for $\sin \theta$ multiplied by j , and noting that the sum is the same as the infinite series for $e^{j\theta}$. Using Euler's theorem, we may re-write equation (1.7) as

$$p = A e^{j\theta} \quad (1.9)$$

Equation (1.9) is called the exponential form, and is most useful for raising a complex number to a power or extracting a root, as we may apply the usual rules of exponents and logarithms. In summary then, we may express any complex number in four ways:

$$p = x + jy \quad (1.10)$$

$$p = A \angle \theta \quad (1.11)$$

$$p = A(\cos \theta + j \sin \theta) \quad (1.12)$$

$$p = A e^{j\theta} \quad (1.13)$$

The form (1.11) has little use except in description, while form (1.12) is used chiefly to convert from form (1.10) algebraic to form (1.13) exponential. Almost all of our work will be carried out using either the algebraic or the exponential form.

1.3. Complex planes

In art. 1.2 the complex number $4 + j3$ was pictured as a point located four units to the right and three units up from the zero point. Thus any complex number whose component real and imaginary parts are given can be located as a point in the xy -plane. It has become a tradition in mathematics to call the variables x and y , and to call z the resulting complex number. That is, by definition

$$z = x + jy \quad (1.14)$$

therefore, any specific complex number z consists of a real part x and imaginary part y , and occupies a definite point in the complex plane. The particular plane used to plot z -values will therefore be called the z -plane. The z -plane is adequate for plotting a wide variety of relations between the variables x and y . The y -dimension is used to plot any function of x and is therefore called a function of x . Thus to say that

$$y = x^2 - 2$$

or

$$y = \sin x$$

is the same as saying

$$f(x) = x^2 - 2$$

or

$$f(x) = \sin x$$

which is read "the function f of x equals $\sin x$ ", etc. Such functions are readily graphed in the z -plane, as shown in Fig. 1.6.

Note that any line in the z -plane is actually a chain of connected points, each point having a particular value of x and y . Thus if the function $f(x)$ is known, the graph of the function can be presented in the z -plane.

Now each of us is familiar with the Mercator projection used for making maps, wherein the graticule is composed of vertical lines, representing x -values of longitude, and horizontal lines, showing y -values of latitude. This graticule of lines is very similar to our

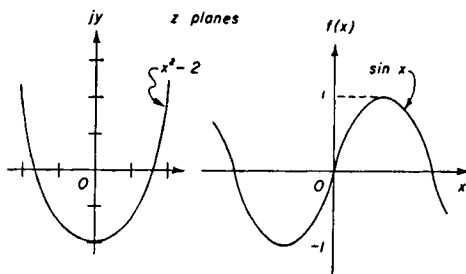


Fig. 1.6

z -plane, and curves in the z -plane could possibly be coast lines on the Mercator map.

Ordinarily the Mercator map might serve our needs, but perhaps the need arises for some accurate information about the northern coast of Greenland. In this case a polar projection map would probably be better.

We note at once that coast lines are not at all familiar in the two projections, in fact, at some points the familiar areas are so different and striking that it is hard to think of them as being the same. Of course we learned early that it was not really a difference in land shape, but only a difference in the nature of the plane.

Seeing the desirability of more than one type of geographical plane, let us grant for the time being that there is need for other mathematical planes in addition to the z -plane. We will call such an additional plane the s -plane.

This new s -plane will be drawn with vertical and horizontal lines the same as the z -plane, but here the co-ordinates of the point locations will be given as σ (sigma) units to the right and ω (omega) units up from the zero reference.

At this point the pure mathematician may object, saying that it is customary and traditional to introduce this second plane as the w mapping, with the real and imaginary components u and v . To this my reply is that ordinarily it is good to keep to tradition, but two facts lead me to prefer the term “ s -plane” here.

First, the reader who is highly versed in complex variable theory will find little of value in this chapter and will have begun directly with Chapter II.

Second, to the reader not acquainted with the details of complex variable theory, one name is as good as another, and I prefer to

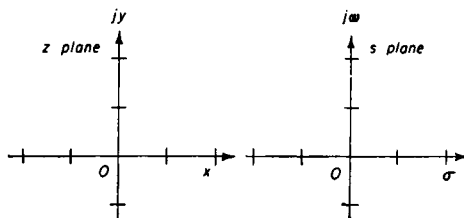


Fig. 1.7

start with the term “ s -plane” because this is the nomenclature used throughout in the literature on the Laplace transformation, and it would seem especially confusing to become familiar with certain symbols in this chapter and then to change abruptly at the start of Chapter II.

Let us not for the moment give any special significance to the component variables σ and ω . Think of them simply as co-ordinates of the various complex numbers s which may be plotted in the s -plane. That is, by definition

$$s = \sigma + j\omega \quad (1.15)$$

In summary, we now have two planes available, the z -plane and the s -plane. Functions of x , such as

$$f(x) = x^3 - 2x + 3$$

will be graphed in the z -plane as in Fig. 1.6, while functions of s will be plotted only in the s -plane.

As in the case of the two map projections, it will not be likely that a function plotted in the z -plane will resemble the corresponding function graphed in the s -plane.

1.4. Relations between the z - and s -planes

Suppose we make the statement that s is a function of z , that is to say

$$s = f(z) \quad (1.16)$$

This is a general statement and tells little except that there will be some complex point in the s -plane corresponding to some complex point in the z -plane. To say more than this we need to choose a specific $f(z)$ and say, perhaps, that

$$s = z^2 \quad (1.17)$$

By the definitions (1.14) and (1.15) therefore

$$\sigma + j\omega = (x + jy)^2 \quad (1.18)$$

or

$$\sigma + j\omega = x^2 + 2jxy - y^2 \quad (1.19)$$

and if we group real and imaginary terms,

$$\sigma + j\omega = x^2 - y^2 + j2xy \quad (1.20)$$

then, equating reals to reals, and imaginaries to imaginaries, we have

$$\sigma = x^2 - y^2 \quad (1.21)$$

and

$$\omega = 2xy \quad (1.22)$$

Now this is specific information relating the function of s to the function of z . As an example of its use, let us take as a "coast line"

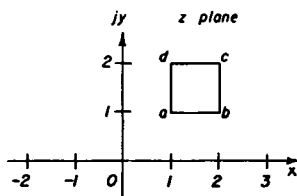


Fig. 1.8

the square in Fig. 1.8, bordered by the lines $x = 1$, $x = 2$, $y = 1$, $y = 2$; and transform this square into the s -plane.

The transformation may be carried out one point at a time, choosing first the corner points a , b , c and d .

The four corners of the area in the s -plane may now be located at a' , b' , c' and d' , as in Fig. 1.10, and if we transform intermediate

points between a and b , etc., we note that there is actually a slight curve to the sides in the s -plane, as shown. If we now pick one general point inside the z -plane square, we see that it transforms into a point inside the border of the s -plane figure. Hence we may say that all points inside the square, and thus the interior region of the square, transforms into the entire region inside the new figure in the

point	z		$\sigma = x^2 - y^2$	$\omega = 2xy$	s
	x	y			$\sigma + j\omega$
a	1	1	0	2	$0 + j2$
b	2	1	3	4	$3 + j4$
c	2	2	0	8	$0 + j8$
d	1	2	-3	4	$-3 + j4$

Fig. 1.9

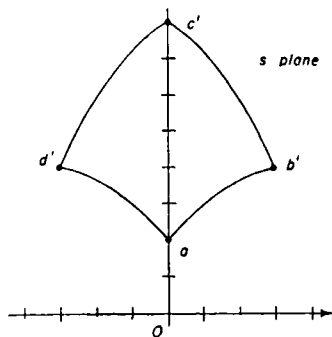


Fig. 1.10

s -plane. As was the case with the map projections, there is little resemblance between the two figures.

Let us examine several more transformations in art. 1.5, and then we shall work a practical problem to demonstrate the value of such transformations.

1.5. Additional transformations between the z - and s -planes

The reason for future transformation between planes will be to effect extreme simplification in solving problems. Fortunately, transformations of the type we will be using from Chapter II on, follow a very straightforward and standardized procedure. However, to develop a feeling for operation in the complex plane, it will be desirable at this time to examine a few of the more common transformations.

(a) Let us look at a very interesting and useful transformation between the z -plane and the s -plane. This transform is

$$z = e^s \tag{1.23}$$

This transform tells us that every point in the s -plane can be mapped into the z -plane by the use of (1.23). As a matter of fact, note

carefully that since any line is merely a collection of points, any line in the s -plane can also be redrawn in the z -plane by using (1.23).

To draw anything in the z -plane, it is of course necessary to solve for the values of x and y , which are the components of the complex number z . We replace the s and z in (1.23) by their component parts as a first step:

$$x + jy = \varepsilon^{(\sigma + j\omega)} \quad (1.24)$$

Now observe that the $\sigma + j\omega$ follows the usual rule of exponents and the expression can thus be rewritten as

$$x + jy = \varepsilon^\sigma \varepsilon^{j\omega} \quad (1.25)$$

On the left, the x and y values are seen to be the usual co-ordinates of points in the z -plane. On the right, the ε^σ is a magnitude and the $\varepsilon^{j\omega}$ is an angle. Looking back at (1.11), (1.12) and (1.13) it is seen that the $\varepsilon^{j\omega}$ term can be rewritten as

$$x + jy = \varepsilon^\sigma \underline{\varepsilon^{j\omega}} \quad (1.26)$$

or

$$x + jy = \varepsilon^\sigma (\cos \omega + j \sin \omega) \quad (1.27)$$

where ε^σ is the magnitude of a vector reaching from zero to the point in the s -plane, and ω is the angle of the vector. Since real terms must equal real terms on each side, we have from (1.27)

$$x = \varepsilon^\sigma \cos \omega \quad (1.28)$$

and

$$y = \varepsilon^\sigma \sin \omega \quad (1.29)$$

Therefore, if we are given any point, or set of points in the s -plane, we can place the σ and ω values of the point into (1.28) and (1.29) and learn the values of x and y for the location of the point in the z -plane.

PROBLEM. We are given a straight line, $\sigma = 0$ in the s -plane, reaching from $\omega = 0$ to $\omega = 2\pi$. Plot the path of this line in the z -plane.

HINT. Use (1.28) and (1.29) and choose values of ω such as $\omega = 0^\circ$, $\omega = 30^\circ$, $\omega = 60^\circ$, etc., which are easily looked up in tables or found by observation, and plot the xy points carefully. Draw a smooth curve through the points.

ANS. The s -plane line becomes a circle of radius 1 in the z -plane.

The results of this problem will be used in art. 1.6 to work a practical electronics problem. For the moment, however, let us examine one more transformation.

(b) Suppose one is given the function

$$z = \ln s \quad (1.30)$$

then for every point in the z -plane there will be a value corresponding to the natural logarithm of the complex variable s . As usual, it is necessary to solve for the individual values of x and y in order to plot a given point or curve.

$$x + jy = \ln(\sigma + j\omega) \quad (1.31)$$

By the definition of a logarithm, namely the power to which ϵ must be raised to equal the number

$$\epsilon^{x+jy} = \sigma + j\omega \quad (1.32)$$

or

$$\epsilon^x \epsilon^{jy} = \sigma + j\omega \quad (1.33)$$

or

$$\epsilon^x / \underline{y} = \sqrt{(\sigma^2 + \omega^2)} / \underline{\tan^{-1} \frac{\omega}{\sigma}} \quad (1.34)$$

and we see that the magnitude on the left must equal the magnitude on the right, thus

$$\epsilon^x = \sqrt{(\sigma^2 + \omega^2)} \quad (1.35)$$

from which

$$x = \ln \sqrt{(\sigma^2 + \omega^2)} \quad (1.36)$$

It is noted that the phase angle on both sides must also be equal, hence

$$y = \tan^{-1} \frac{\omega}{\sigma} \quad (1.37)$$

Therefore, with the last two equations we can transform any equation or curve in the s -plane into its corresponding curve in the z -plane.

PROBLEM. Show that the circle of radius 2.718 in the s -plane transforms into the straight line of 6.28 units length, at $x = 1$, as shown in Fig. 1.11.

(c) Transformation of a region. Thus far we have talked about transforming points, and have noted that lines were merely chains of points placed side by side. The thought now occurs that the

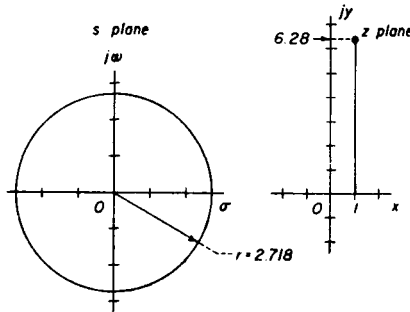


Fig. 1.11

region inside a closed curve in a plane is also only a collection of more points, and thus we may say that it is possible to transform regions in one plane to corresponding regions in the other plane. More will be said later of regions, but for the moment, merely

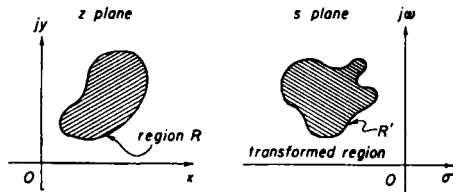


Fig. 1.12

observe that Fig. 1.12 represents a transformation of a region, similar to our practice here in transforming lines and points.

1.6. Simplification of problems by transforming into the complex s -plane

In this article we shall see the advantages of transforming a problem from the original plane into a new plane for solution. The procedure can best be illustrated by means of a sample problem.

PROBLEM. Calculate the capacity of a 1 m length section of coaxial cable, whose inner conductor is a m in radius, and whose outer thin conductor is b m in radius; b is greater than a .

First, the cross-section of the cable is shown in the z -plane, Fig. 1.13. The values of points making up the inner circle may be easily expressed by writing z in polar form,

$$z_a = a\varepsilon^{j\theta} \tag{1.38}$$

and it is seen that as θ goes from 0 to 2π , the z -points will trace out the inner circle. It is also noted that for the outer circle

$$z_b = b\varepsilon^{j\theta} \tag{1.39}$$

where again θ varies from 0 to 2π rad.

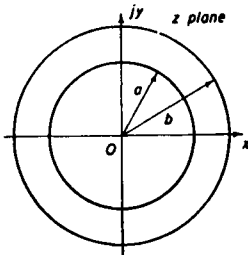


Fig. 1.13

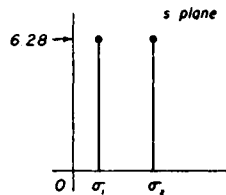


Fig. 1.14

Now let us transform these two circles into the s -plane by use of the transformation

$$z = \varepsilon^s \tag{1.40}$$

For the inner circle only,

$$a\varepsilon^{j\theta} = \varepsilon^\sigma \varepsilon^{j\omega} \tag{1.41}$$

from which it is seen that

$$\varepsilon^\sigma = a \tag{1.42}$$

or

$$\sigma_1 = \ln a \tag{1.43}$$

and also

$$\omega = \theta \tag{1.44}$$

Plotting the inner circle first, it is found from (1.43) that we have a straight vertical line $\sigma_1 = \ln a$, and that (1.44) shows this line to extend from $\omega = 0$ to $\omega = 2\pi$. Thus the inner z -plane circle has been transformed into a straight line segment in Fig. 1.14.

Next, let us repeat this process, and transform the outer circle into the s -plane. For the z -points making up the outer circle,

$$b\varepsilon^{j\theta} = \varepsilon^\sigma \varepsilon^{j\omega} \tag{1.45}$$

and we see that

$$b = e^{\sigma} \quad (1.46)$$

or

$$\sigma_2 = \ln b \quad (1.47)$$

and again

$$\omega = \theta \quad (1.48)$$

Therefore, the outer circle transforms into the s -plane as a line segment, $\sigma_2 = \ln b$, going from $\omega = 0$ to $\omega = 2\pi$.

The length dimension was not transformed, so we now have our coaxial cable in the shape of two identical, flat strips, 1 m long, of width 2π m, and separation $\ln b - \ln a$ m.

If we cared to plot the radial flux lines between conductors a and b in the z -plane, we would find that the corresponding flux in the s -plane was exactly uniform between the flat sheets, and that there is no fringing at the edges. We may therefore use the simple formula for the capacity of parallel plate condensers, which is:

$$C = \frac{\epsilon A}{d} \quad (1.49)$$

where $C =$ capacity (F)

$\epsilon =$ permittivity (F/m)

$A =$ area of plates (m^2)

$d =$ distance apart (m)

Thus, our two plates in the s -plane have a capacity

$$C = \frac{\epsilon 6.28}{\ln b - \ln a} \quad (1.50)$$

which is simplified to

$$C = \frac{2\pi\epsilon}{\ln \left(\frac{b}{a} \right)} \quad (1.51)$$

Now (1.51) is the general formula for capacity per unit length of a coaxial transmission line of radii a and b . It is an exact solution. Those of you who have calculated the formula by other methods will agree, I am sure, that this simple transformation into the s -plane is a very simple means of solution.

We note in passing that there is no reason to think of transforming anything back into the z -plane, as the problem is identical in either plane. In future work, it may or may not be necessary to transform a solution back into the original plane for use.

1.7. Functions in the complex plane

It has been previously stated that if the equation of a z -plane curve is given, then y is a function of x and is usually written $f(x)$. The x is a real variable, and thus the y , or $f(x)$ is called a function of a real variable. In a particular work, different functions of x may be called $f(x)$, $g(x)$, $h(x)$, etc. The graphs of functions of x can be plotted in two dimensions.

Now instead of having a function of only one real variable x , it is possible to define a function of the complex variables z or s , for example, one may have given the function* of s

$$F(s) = \frac{1}{s} \quad (1.52)$$

It is seen here that instead of being merely a curve above the real axis, as was the case for $f(x)$, this function $F(s)$ has a value for every point in the s plane.

Thus the magnitude of $F(s)$ may be thought of as a surface. For much of our work with the Laplace transform, the surface will be adequate, and if necessary to consider phase angle, the situation will be analyzed at that time.

Suppose we wish to draw a picture of the $F(s)$ in (1.52). The first steps would be to get it into the form of an absolute magnitude.

$$F(s) = \frac{1}{\sigma + j\omega} \quad (1.53)$$

or

$$|F(s)| = \frac{1}{\sqrt{\sigma^2 + \omega^2}} \quad (1.54)$$

To plot the $F(s)$, it is best to select a line $\sigma_1 = \text{constant}$, and then find the values of $F(s)$ along this line as ω varies. The procedure can be repeated along another line $\sigma_2 = \text{constant}$, etc., so that eventually the entire surface is created. For the $F(s)$ of (1.52) it is noted that the value becomes infinite at one point only, at $s = 0$.

* From now on, functions of s will use capital F , or other capital letters, while functions of z , functions of time, etc., will use lower case letters.

A portion of the surface may be sketched in three dimensions as suggested in Fig. 1.15, where it is seen that the surface is an infinitely high peak at $s = 0$ and falls off rapidly in both the σ and ω directions.

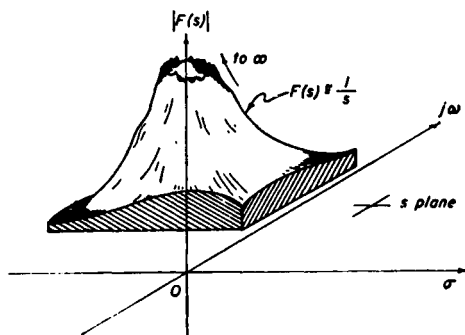


Fig. 1.15

1.8. Poles of complex functions

In the last article a simple function

$$F(s) = \frac{1}{s} \quad (1.55)$$

was shown in Fig. 1.15 to resemble a steep mountain peak reaching up to infinity. This peak is of such major importance in future work that a special name has been assigned to it. It is called a "pole". We speak of the function $F(s)$ as having poles at certain values of s , wherever the magnitude $F(s)$ goes to infinity.

EXAMPLE 1. Poles of the function

$$F(s) = \frac{1}{s(s+2)} \quad (1.56)$$

occur at

$$s = 0 \quad (1.57)$$

$$s = -2 \quad (1.58)$$

since at either of these two points the surface rises up to infinity.

EXAMPLE 2. The function

$$F(s) = \frac{1}{s(s+2)(s-2j+2)} \quad (1.59)$$

has poles at

$$s = 0$$

$$s = -2$$

$$s = -2 + 2j$$

because at each of these three points the $F(s)$ becomes infinite.

It is customary to indicate the location of poles in the s -plane with small crosses. The poles of (1.59) are thus illustrated as in Fig. 1.16.

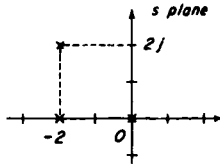


Fig. 1.16

We will merely hint at interesting things to come by saying that later on we will express entire complicated electronic networks as groups of poles in the s -plane, analyze them in the s -domain, and then transform the results back into the time plane for use.

PROBLEMS. Find the poles of the following functions of s , and indicate by crosses in the s -plane.

$$(a) \quad F(s) = \frac{1}{s(s-1)(s-4)}$$

$$(b) \quad F(s) = \frac{1}{s(s^2-1)}$$

$$(c) \quad F(s) = \frac{1}{(s-1)(s^2+1)}$$

ANS. (a) $s = 0, s = 1, s = 4$; (b) $s = 0, s = 1, s = -1$;

(c) $s = 1, s = j, s = -j$.

Poles are found one at a time by taking each individual factor in the denominator, setting it equal to zero, and solving for s . A pole is associated with a particular factor creating it. Thus in problem (a) the pole at 0 is caused by the factor s , the pole at $s = 1$ is created by the factor $(s - 1)$, etc.

We will digress for a few moments on the subject of zeros, and then return to discuss the general subject of poles and zeros at greater length.

1.9. Zeros of complex functions

A zero of a complex function is defined as a value of s which makes the entire function equal zero, thus

$$F(s) = \frac{(s - 2)(s + 1)}{(s - 4)} \quad (1.60)$$

has zeros at $s = 2$ and $s = -1$, because if $s = 2$ the first factor in the numerator becomes zero, making the entire $F(s)$ zero, and if $s = -1$ the second factor is zero and makes the entire $F(s)$ zero.

The zeros of a function are found then, by setting each factor in the numerator to zero, and solving for s . The zeros are located in the s plane by using small circles as markers. Equation (1.60) therefore has its zeros shown in the s -plane as in Fig. 1.17.

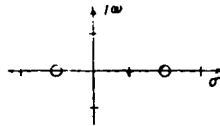


Fig. 1.17

PROBLEMS. Find the zeros of the following functions, and plot in the s -plane. Use small circles as in Fig. 1.17

(a) $F(s) = \frac{s}{s + 1}$

(d) $F(s) = s + \frac{1}{s}$

(b) $F(s) = \frac{s - 13}{s}$

(e) $F(s) = \frac{(s^2 + 1)s}{(s^2 - 1)}$

(c) $F(s) = \frac{(s - 1)(s + j)}{s^2 + 2}$

(f) $F(s) = \frac{(s - 3 - j4)}{(s + j)^2}$

ANS. (a) $s = 0$; (b) $s = 13$; (c) $s = 1, s = -j$; (d) $s = j, s = -j$;

(e) $s = 0, s = j, s = -j$; (f) $s = 3 + j4$.

Functions will often appear as the ratio of two polynomials, as in the following example:

$$F(s) = \frac{s^3 + as^2 + bs + c}{s^2 + ds + e} \quad (1.61)$$

In such a case it is necessary to set the numerator equal to zero and solve the resulting higher order equation. In this case the roots of the cubic equation would then be used to form the same $F(s)$ rewritten as a product of factors. Thus, if the roots are a_1 , a_2 , and a_3 , the function can be expressed as

$$F(s) = \frac{(s - a_1)(s - a_2)(s - a_3)}{s^2 + ds + e} \tag{1.62}$$

1.10. The pole-zero diagram

A given function of s can always be drawn as a pole-zero diagram. This is merely a picture of the small crosses and circles in the s plane which locate the poles and zeros. The function

$$F(s) = \frac{(s + 3)}{(s^2 + 4)} \tag{1.63}$$

has a zero at $s = -3$, and poles at $j2$ and $-j2$. Thus the pole-zero diagram appears as in Fig. 1.18.

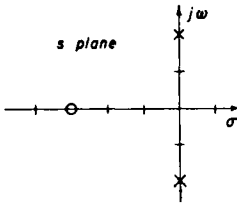


Fig. 1.18

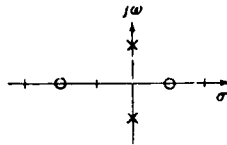


Fig. 1.19

Conversely, if one is given the pole-zero diagram, it is easy to write the corresponding function of s . As an example, suppose we are given Fig. 1.19. Taking the zeros first, the zero at $s = 1$ creates a factor $(s - 1)$ to be placed in the numerator. The zero at $s = -2$ creates a factor $(s + 2)$ to be placed as a second factor in the numerator, while the pole at $s = j$ gives a factor $(s - j)$, and the pole at $s = -j$ gives the factor $(s + j)$, both of which go into the denominator. Collecting the factors gives:

$$F(s) = \frac{(s - 1)(s + 2)}{(s - j)(s + j)} \tag{1.64}$$

which can also be expressed as

$$F(s) = \frac{s^2 + s - 2}{s^2 + 1} \tag{1.65}$$

Pole-zero diagrams are of special importance in the analysis of R - L - C networks, and we shall be using them throughout the remainder of the book.

PROBLEM. Write the function $F(s)$ corresponding to the pole-zero diagram in Fig. 1.20.

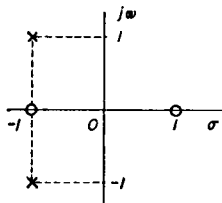


Fig. 1.20

Ans.

$$F(s) = \frac{s^2 - 1}{s^2 + 2s + 2}$$

1.11. Integration along a curve in the s -plane

The objective in this and other articles in Chapter I is to present only the parts of complex variable theory necessary to prepare the reader for the study of Laplace transforms. It would be highly desirable to have everyone complete a formal course in complex variables before beginning the study of Laplace transformations, but actually this is neither possible nor necessary. If the reader will master one or two more definitions and concepts, he will have ample background to begin Chapter II with confidence. One such concept is the subject of integration of a function $F(s)$ in the complex s -plane.

The reader will recall that in his earlier days of studying the calculus, integration was always carried out along the real or x -axis only, usually between specific upper and lower limits. It is not difficult to generalize this procedure.

First of all, let us examine, or review the procedure used in setting up a real integral for the area under a curve (see Fig. 1.21). It is recalled that the elementary, or differential area is length times width

$$\Delta A = y \Delta x \tag{1.66}$$

and a specific elementary area is

$$\Delta A_n = y_n \Delta x_n \tag{1.67}$$

The subscript may be dropped from the Δx since all Δx 's are identical, and y is known at any specific point $y_2, y_3, \text{etc.}$, because y is a $f(x)$ and this function is known. Now if the individual small areas are summed up, the total area is

$$A = y_1\Delta x + y_2\Delta x + y_3\Delta x + \dots + y_n\Delta x \tag{1.68}$$

or since $y = f(x)$

$$A = f(x_1)\Delta x + f(x_2)\Delta x + f(x_3)\Delta x + \dots + f(x_n)\Delta x$$

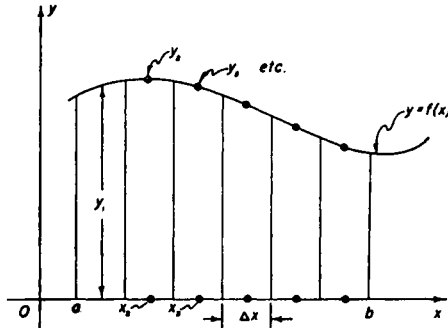


Fig. 1.21

Fortunately, this series simplifies to the basic integral

$$A = \int_a^b f(x) dx \tag{1.69}$$

which represents exactly the sum of the elementary areas from $x = a$ to $x = b$, as Δx approaches zero.

Note that in the above discussion, we merely divided the x -axis segment from a to b into n equal parts of Δx width each. We then took the value of $f(x)$ at the particular segment center times Δx to get the product $f(x)\Delta x$. It was not particularly important that the product was an area, and many useful products such as force times distance, voltage times current, etc., are not usually thought of as areas when integrating. Let us therefore look at Fig. 1.22. This is a plan view of the s -plane, and the path over which we wish to integrate is shown as the line from $s = a$ to $s = b$; a and b are of course both complex numbers, or limits. Note that this path follows a devious course through the s -plane, and that all points s on the path are complex. Thus the path itself requires a plane (two dimensions) rather than merely the x -axis.

Of course we must be given a formula for $F(s)$, so that we know $F(s_1)$, $F(s_2)$, etc., at the center of each of the small segments Δs . The integral, then, is of exactly the same form as (1.68) and (1.69), or

$$\int_a^b F(s) ds = F(s_1)\Delta s + F(s_2)\Delta s + F(s_3)\Delta s + \dots + F(s_n)\Delta s \quad (1.70)$$

if Δs approaches zero and n approaches infinity.

Note very carefully the major difference between Figs. 1.21 and 1.22. In Fig. 1.22 a third dimension is required (up and out of the

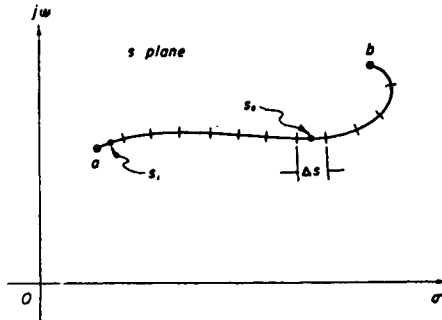


Fig. 1.22

page) to show the value $F(s)$, because both the σ and ω directions are used to show the path of integration in the plane, whereas in Fig. 1.21 only two dimensions are required, one to show the path of integration and one to show the value $f(x)$.

Note further that $F(s)$ is actually a surface, weaving above, in, and under the s -plane. If the s -plane is thought of as terrestrial sea level, then $F(s)$ will appear somewhat like the surface of the earth, i.e. some parts of the surface are above, and some are below sea level.

The magnitude of $F(s)$ can usually be drawn as a surface as shown in Fig. 1.15 in three dimensions, but for most of our work this will not be necessary.

We will be particularly interested in cases where the integral is around a complete closed loop, from one point, around an area, and back to the same point. Thus we will not take space to discuss integration from one point a to another point b as in Fig. 1.22, but will use this merely to visualize the setting up of the integral. We mention in passing that the value of the integral is a function only of the end points a and b , the same as for real integrals.

This last statement requires one qualification to be correct, and this is that the function in question must be analytic. We will avoid discussing the difference between analytic and non-analytic functions by saying that all of the functions we will normally deal with in our electronics work will be analytic, and we will leave the discussion of function analyticity to a formal text on complex variables. If the student is particularly curious, he may read up on the subject of analytic or non-analytic functions, and learn how to apply the Cauchy-Riemann criteria to determine whether or not the given function meets the requirements for analyticity. This subject is discussed in all complex variable texts.

1.12. Integration around a pole

In this article we will examine a procedure for integrating around a pole in the complex plane. This topic is of fundamental importance. Suppose we are interested in the function

$$F(s) = \frac{1}{s - a}$$

This factor, taken n times, and with different complex constants for a , can be used to represent the denominator of any $F(s)$. That

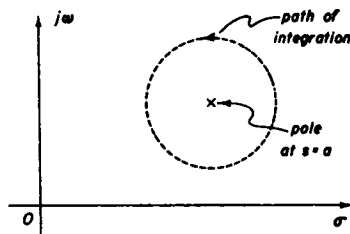


Fig. 1.23

is, the poles of any $F(s)$ are created by just such factors as this. It is vital then, to be able to integrate $F(s)$ around a path enclosing the pole at $s = a$. A typical path of integration is shown in Fig. 1.23, and a may be anywhere in the plane.

Now if we select a general point s on the circular path of integration shown in Fig. 1.23, we may draw vectors from the origin to this general point s , and also to the pole at a . These are the vectors s and a . It is seen then, that the radius vector reaching from the pole

to the point s is $s - a$, shown together with s and a in Fig. 1.24. Our specific problem then is to integrate the function $F(s)$ around the dotted, circular path.

$$\oint F(s) ds = \oint \frac{ds}{s - a} \quad (1.71)$$

where the small circle on the integral sign indicates that the integration begins at one point on a closed path, and goes around once,

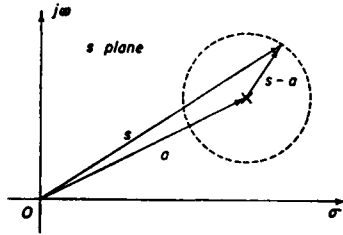


Fig. 1.24

ending at the same point. Let the $s - a$ vector shown in Fig. 1.24 be replaced by a magnitude A at an angle θ :

$$s - a = A e^{j\theta} \quad (1.72)$$

then, differentiating,

$$ds = jA e^{j\theta} d\theta \quad (1.73)$$

and if we replace s and ds in (1.71) by these substitutions

$$\oint \frac{ds}{s - a} = \int \frac{jA e^{j\theta} d\theta}{A e^{j\theta}} \quad (1.74)$$

which after simplification becomes

$$\oint \frac{ds}{s - a} = j \int_0^{2\pi} d\theta \quad (1.75)$$

and where we have added the limits, noting that the $s - a$, or A vector travels once around during the integration. Continuing,

$$\oint \frac{ds}{s - a} = j[\theta]_0^{2\pi} \quad (1.76)$$

and inserting limits gives

$$\oint \frac{ds}{s - a} = 2\pi j \quad (1.77)$$

Now the radius vector A could have been any assumed value to accommodate any circular path around the pole. Thus the actual size of the circle of integration is not important, and we can say that (1.77) is a general result valid for any circle, large or small.

Observe one point very carefully. It appears trivial, but we remark that if the original $F(s)$ had had a constant multiplier K , then the constant could have been carried as such through the entire process and the answer would have been K times the $2\pi j$. This point will be expanded upon later, when we discuss integration around multiple poles of functions of s .

1.13. Integration around a path not containing a pole

We saw in the previous article that different paths of integration around a pole gave the same value of the integral. It is stated now without proof that the path of integration is of no importance, and that integration around any path (uniform, or irregular) which encloses the pole will have the same value, $2\pi j$. The question now arises as to what the value of the integral would be if there is no pole enclosed within the integration path.

Suppose we redraw Fig. 1.24, but keep the pole outside the path of

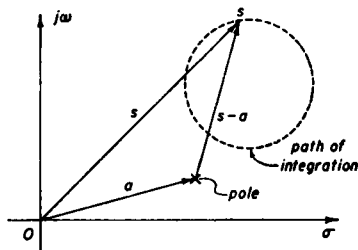


Fig. 1.25

integration (see Fig. 1.25). Using the same $F(s)$, we again set up the integral

$$\oint F(s) ds = \oint \frac{ds}{s - a} \tag{1.78}$$

and if we keep a circular path of integration, the magnitude of the $s - a$ vector will vary, and we may merely write it as a function of θ . Thus

$$s - a = f(\theta)e^{j\theta} \tag{1.79}$$

and differentiating,

$$ds = jf(\theta)\varepsilon^{j\theta}d\theta + \varepsilon^{j\theta}df(\theta) \quad (1.80)$$

then (1.78) becomes

$$\oint \frac{ds}{s-a} = \int \frac{jf(\theta)\varepsilon^{j\theta}d\theta}{f(\theta)\varepsilon^{j\theta}} + \int \frac{\varepsilon^{j\theta}df(\theta)}{f(\theta)\varepsilon^{j\theta}} \quad (1.81)$$

We note that the angle θ merely starts at some value, oscillates once as the point s goes around the path, and ends at the same angle as at the start. Thus the upper and lower limits can be the same general angle. Using ψ for this angle, and simplifying, (1.81) becomes

$$\oint \frac{ds}{s-a} = j \int_{\psi}^{\psi} d\theta + \int_{\psi}^{\psi} \frac{df(\theta)}{f(\theta)} = [\ln f(\theta)]_{\psi}^{\psi} \quad (1.82)$$

or

$$\oint \frac{ds}{s-a} = \ln \left[\frac{f(\psi)}{f(\psi)} \right] = \ln(1) \quad (1.83)$$

and finally

$$\oint \frac{ds}{s-a} = 0 \quad (1.84)$$

Equation (1.84) is a general result, and tells us that the value of any integral of $F(s)$ taken around a closed path not enclosing poles is zero.

As in the last article, if there is a constant multiplier for $F(s)$, it is brought out and carried through the entire procedure, until it can be dropped, upon being multiplied by the zero value of the integral. Suppose for example that one is given the function

$$F(s) = \frac{6}{s-a} \quad (1.85)$$

to be integrated around a path such as in art. 1.12, around a pole, or around a particular path not including a pole, as we have done in this article. One might be tempted to divide by 6, as

$$F(s) = \frac{1}{s/6 - a/6} \quad (1.86)$$

Note, however, that it is not possible to write this denominator as a vector from a to s , as shown in Figs. 1.24 and 1.25, and thus the substitutions as we have made them would not be valid. One must

therefore remove the constant multiplier before performing the substitutions, and keep the factor which creates the pole in exactly the same form as in the worked out procedure.

1.14. Residues

The present article on the subject of residues of functions will serve to bring together several seemingly unrelated topics which have been discussed in previous articles. The residues of functions of s are extremely important to our later study of the Laplace transform, and therefore it is well at this time to attain a clear, physical picture of what residues are and how they are used.

We have noted previously that an $F(s)$ could be visualized as a surface, with the s -plane itself corresponding to sea level, and the height from the s -plane (sea level) to the surface being the magnitude of $F(s)$. For the particular function

$$F(s) = \frac{1}{s - a} \tag{1.87}$$

it is seen that there will be a pole at $s = a$, which can be visualized as a high mountain peak where the surface rises to infinity at a point directly over the pole location.

For purposes of developing the concept of residues, let us at the moment confine our pole locations to the σ -axis in the s -plane. This

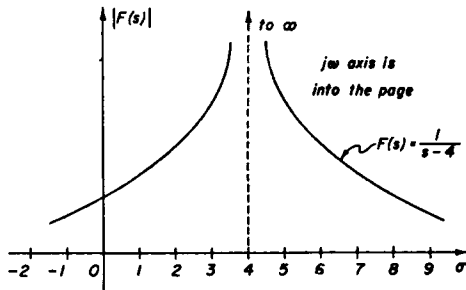


Fig. 1.26

will allow us to use a two-dimensional graph to show the σ -axis cross-section of the s -plane and the magnitude of $F(s)$ as well. It will not be difficult afterwards to enlarge the concept to three dimensions, so that the pole may be anywhere in the s -plane. If (1.87) is drawn for $a = 4$ we have Fig. 1.26.

Note again that Fig. 1.26 represents magnitude only, and thus all of the surface will be above the σ -axis. We will take actual numerical values from the equations, and therefore it will not be necessary to calibrate the vertical scale.

Let us now look at a slightly more elaborate function of s , composed of the two factors,

$$F(s) = \frac{1}{(s - 4)(s - 7)} \quad (1.88)$$

where we have used specific, real pole locations. It will be apparent that this function can be thought of as the product of two surfaces, or rewritten slightly as

$$F(s) = \frac{1}{(s - 4)} \times \frac{1}{(s - 7)} \quad (1.89)$$

where the first factor creates the same surface as in Fig. 1.26, while the second factor creates a second identical surface, except that the second surface rises to infinity above the pole located at $s = 7$, rather than 4. Both surface cross-sections are shown in Fig. 1.27.

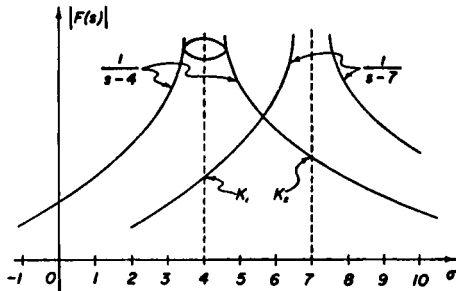


Fig. 1.27

Of course the over-all function $F(s)$ is the product of these two surfaces for each point in the s -plane, as in Fig. 1.28, but there are advantages to be had by considering the over-all $F(s)$ as the product of the two surfaces shown in Fig. 1.27 rather than as a single surface, as we shall now see.

Let us climb up rather high on the side of the $1/(s - 4)$ mountain which rises over the pole at $\sigma = 4$. If we climb up a moderate distance, we will be able to reach around the peak and draw a small circle, as shown in Fig. 1.27 also. Now observe carefully that if we keep the radius of the circle very small, the value of the second surface will be almost constant within the interior of the same circular

region in the s plane. As a matter of fact, if we let the radius approach zero, the value of the other surface $1/(s - 7)$ becomes the constant value K_1 . Within the small circle in Fig. 1.27, then, we may consider the over-all surface $F(s)$ to consist of the product of the two surfaces, or factors

$$F(s) = K_1 \times \frac{1}{(s - 4)} \tag{1.90}$$

Now we have seen previously that an integral around a pole is independent of the path of integration, as long as the path of

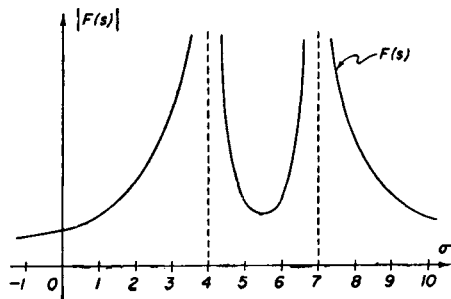


Fig. 1.28

integration encloses the pole. Thus to integrate around the pole at $s = 4$, it is perfectly valid to make the radius of the path of integration very small, so that (1.90) holds. Then

$$\oint F(s) ds = \oint \frac{ds}{(s - 4)(s - 7)} = \oint \frac{K_1 ds}{(s - 4)} \tag{1.91}$$

but the K_1 , being a constant, can be brought outside the integral, i.e.

$$\oint F(s) ds = K_1 \oint \frac{ds}{s - 4} \tag{1.92}$$

and it was found in art. 1.12 that the integral around such a pole was equal to $2\pi j$. Therefore

$$\oint F(s) ds = K_1 2\pi j \tag{1.93}$$

K_1 of course can be found by inspecting Fig. 1.27 and evaluating the surface $1/(s - 7)$ at the pole $s = 4$. So that

$$K_1 = \frac{1}{s - 7} \Big|_{s=4} = -\frac{1}{3} \tag{1.94}$$

Therefore

$$\oint F(s) ds = -\frac{2\pi j}{3} \quad (1.95)$$

If it is desired to integrate around the pole at $s = 7$, the procedure is exactly the same, except that within a small circle around the second mountain peak, we replace the surface $1/(s - 4)$ by the constant K_2 . Thus the value of the integral around the pole at $s = 7$ is

$$\oint F(s) ds = K_2 \cdot 2\pi j \quad (1.96)$$

We see then, that it is possible to simplify the $F(s)$ within a small circle surrounding each pole. Since the $F(s)$ may always be written as a product of factors, and since only one of the factors can contribute a particular pole, we may say that within a very small area surrounding any pole of any $F(s)$, the given $F(s)$ may be simplified as

$$F(s) = K \times \frac{1}{(s - a)} \quad (1.97)$$

where K is the product $K_1 K_2 K_3 \dots$ of all the values of the surfaces created by all the terms of $F(s)$ except the surface $1/(s - a)$, which creates the actual pole at a .

DEFINITION. The constant that, when multiplied by the one factor that creates a pole, causes the product to be a valid simple substitution for the more elaborate $F(s)$ within an infinitely small diameter circle around the pole at $s = a$, is called the residue of the function at the pole $s = a$. By this definition, it is seen that the constant K_1 in Fig. 1.27 is the residue of $F(s)$ at the pole $s = 4$. Similarly, for this same function (1.88) K_2 is the residue at the pole $s = 7$.

Using the concept of the residue then, a complicated function of s can be replaced within a very small circle of integration around a pole by the residue at the pole times the one factor which creates the pole. This makes it possible to integrate very complex functions of s around poles. Using a previous example, where

$$F(s) = \frac{6}{s - a} \quad (1.98)$$

one notes that by the above definition, 6 is a residue of $F(s)$ at the pole $s = a$. The 6 can be considered as a constant surface 6 units above the s -plane "sea level".

In the brief art. 1.15 to follow, it will be found that the value of an integral taken around two or more poles is the same as the sum of the integrals taken around each pole separately. After this statement is proved, a summary of all the ideas and concepts up to this point should enable us to integrate any $F(s)$ around any number of poles in the s -plane. For the moment, however, let us take the statement on faith, and as a last topic in this article, show how to find the residue at a given pole. If the given function is:

$$F(s) = \frac{1}{(s-a)(s-b)(s-c)} \quad (1.99)$$

then each of the three factors will create a pole. In particular, if we are interested first in the pole at $s = a$.

$$F(s) = \frac{1}{(s-b)(s-c)} \times \frac{1}{(s-a)} \quad (1.100)$$

we may consider the $1/(s-a)$ in the usual way, as a surface rising to infinity at $s = a$, and the remainder of the function surfaces to be constant within the very small circle of integration. We may thus substitute the value $s = a$ into the first of the above factors on the right-hand side to give

$$F(s) = \frac{1}{(a-b)(a-c)} \times \frac{1}{(s-a)} \quad (1.101)$$

or

$$F(s) = K_a \times \frac{1}{(s-a)} \quad (1.102)$$

where K_a is the residue of $F(s)$ at the pole $s = a$. For the residue at the pole $s = b$, one would write

$$F(s) = \frac{1}{(s-a)(s-c)} \times \frac{1}{(s-b)} \quad (1.103)$$

and evaluate

$$\left. \frac{1}{(s-a)(s-c)} \right|_{s=b} \quad (1.104)$$

to find the residue

$$\frac{1}{(b-a)(b-c)} = K_b \quad (1.105)$$

Stated in another way, one finds the residue of a function at a pole by removing the factor creating the pole, and evaluating the remainder of s at the pole. As an example, let

$$F(s) = \frac{3}{(s-1)(s+2)} \quad (1.106)$$

To evaluate the residue at the pole $s = -2$, remove this factor, and evaluate the remainder for $s = -2$.

$$K_{-2} = \frac{3}{s-1} \Big|_{s=-2} = \frac{3}{-2-1} = -1 \quad (1.107)$$

We also speak of this as "removing a pole".

PROBLEMS

- (1) Show that the sum of the residues at the poles of (1.88) is zero.
- (2) (a) Find the residue of the function

$$F(s) = \frac{s^2}{(s-3)(s+6)}$$

at the pole $s = -6$.

ANS. $K_{-6} = -4$.

(b) Show that the sum of the two residues is not zero for this function.

- (3) Show that the sum of all residues of the function

$$F(s) = \frac{s}{s^2 + 1}$$

is unity.

- (4) Show that the sum of all residues of

$$F(s) = \frac{s^2}{s^2 + 1}$$

is zero.

1.15. Integration around two or more poles in the s -plane

Let us look again at the equation

$$F(s) = \frac{1}{(s-4)(s-7)} \quad (1.108)$$

which we examined earlier in art. 1.14 and Fig. 1.27. The poles are at $s = 4$ and $s = 7$ and are shown in the usual pole-zero diagram as

in Fig. 1.29. Suppose that for our path of integration about the pole at $s = 4$ we choose the circular path beginning at point a . In actual practice we would choose a much smaller radius, but we merely illustrate the procedure here. It will be recalled that the integral around this particular type of path is the sum of the incremental products of $F(s)\Delta s$ (see Fig. 1.22).

Now if we sum up these small quantities from point a all the way around the pole to point b , where b is close to, but not quite touching

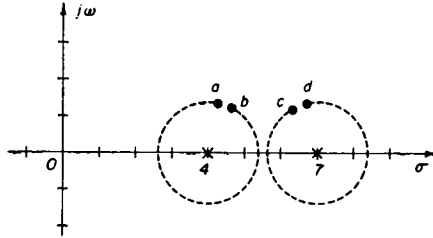


Fig. 1.29

point a , then the value of the integral from a to b is essentially the same as the circular integral completely around the pole. Our only inaccuracy is to leave off the last small term $F(s)\Delta s$ where the Δs reaches from b to a . As Δs approaches zero in the limit anyway, we say that in this case, around the pole $s = 4$

$$\oint F(s) ds = \int_a^b F(s) ds \tag{1.109}$$

By the same line of reasoning, around the pole $s = 7$

$$\oint F(s) ds = \int_c^d F(s) ds \tag{1.110}$$

It may not be obvious, and thus we point out that if a and b are close enough together, for practical purposes the value of $F(s)$ is the same at both points.

Now let us add the two paths from d to a , and from b to c , as in Fig. 1.30. We keep the paths very close together, but not actually touching. Thus, as we divide the total path up into the elementary sections Δs as shown, the value $F(s)$ at the center point e of such an element is essentially the same on both lines, or, for these two segments

$$F(s)_e \Delta s \text{ from } d \text{ to } a = F(s)_e \Delta s \text{ from } c \text{ to } b \tag{1.111}$$

As the same situation will be valid for each increment, we may sum along the entire path from d to a and from c to b

$$\sum_d^a F(s) \Delta s = \sum_c^b F(s) \Delta s \quad (1.112)$$

or in the limit, as $s \rightarrow 0$

$$\int_d^a F(s) ds = \int_c^b F(s) ds \quad (1.113)$$

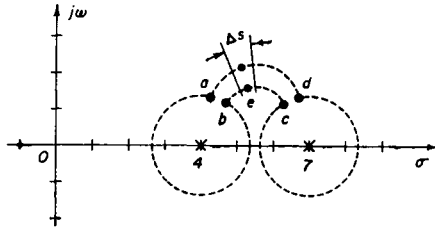


Fig. 1.30

Note carefully now that if we reverse the limits on the right-hand integral, we must also reverse the sign, i.e.

$$\int_d^a F(s) ds = - \int_b^c F(s) ds \quad (1.114)$$

We are now in a position to integrate around a complete path enclosing both poles. The complete integral may be written as the sum of the four sections starting at point a and returning to the same point. Thus

$$\oint F(s) ds = \int_a^b F(s) ds + \int_b^c F(s) ds + \int_c^d F(s) ds + \int_d^a F(s) ds \quad (1.115)$$

The last term on the right may be replaced by its equivalent from (1.114) as

$$\oint F(s) ds = \int_a^b F(s) ds + \int_b^c F(s) ds + \int_c^d F(s) ds - \int_b^c F(s) ds \quad (1.116)$$

The second and last terms on the right side cancel, leaving

$$\oint F(s) ds = \int_a^b F(s) ds + \int_c^d F(s) ds \quad (1.117)$$

Let us now close the small gap between b and a , and between d and c , Fig. 1.30, so that (1.117) becomes

$$\underbrace{\oint F(s) ds}_{\text{integral around both poles}} = \underbrace{\oint F(s) ds}_{\text{integral around one pole}} + \underbrace{\oint F(s) ds}_{\text{integral around other pole}} \quad (1.118)$$

Thus we say that the integral of a function of s taken around all poles equals the sum of the separate integrals around each pole. If the residue at each pole is K_n , the integral around all poles then is the sum of all residues times $2\pi j$.

$$\oint F(s) ds = 2\pi j [K_1 + K_2 + \dots] \quad (1.119)$$

We shall make good use of this result in the evaluation of inverse Laplace transforms later in the book.

PROBLEMS. Integrate the functions shown around all poles:

(a) $\oint \frac{s^2 ds}{(s - 3)(s + 6)}$

(c) $\oint \frac{s^2 ds}{s^2 + 1}$

(b) $\oint \frac{s ds}{s^2 + 1}$

(d) $\oint \frac{(4js - 2) ds}{s^2 + 1}$

ANS. (a) $-j6\pi$; (b) $j2\pi$; (c) 0; (d) -25.13 .

1.16. Summary of Chapter I

As the reader is without doubt anxious to move on to more interesting and practical things, let us take just a few moments to summarize the more important points in this chapter.

(a) Complex numbers were introduced and illustrated in several forms useful for analytical work. The j -operator was defined, and it was pointed out that there are advantages to be had by thinking of complex numbers as vectors.

(b) Complex planes were introduced and it was shown that a function plotted in one plane could be transformed or transferred on to another plane by the use of transformations as (1.17) and (1.23). In complex variable theory this is called conformal mapping, and is most useful for simplifying functions or more properly, for making intricate functions more symmetrical.

(c) Functions in the complex plane were introduced and it was suggested that the magnitude of $F(s)$ be thought of as a surface,

much like the irregular surface of the earth, over the s -plane itself, which was compared to sea level.

(d) Poles of complex functions were treated and their location in the s -plane pictured. Poles are especially important and the reader should develop the habit of making a rough sketch of the s -plane and poles of functions with which he is working. This concept will be used throughout the material on the Laplace transform and should eventually become second nature. After finishing this text, one should be able to deduce the behavior of rather complicated electrical networks merely by looking at their pole-zero diagrams. Zeros, although of importance, do not concern us much when they are in the numerator of functions of s . Zeros of the denominator, of course, are poles of the over-all function.

(e) Art. 1.11 discussed ways of forming line integrals, or integrals along a curve in the s -plane. It was shown that one extra dimension was necessary to illustrate this procedure, but that the path of integration could be shown in a plan view of the complex plane if $F(s)$ is thought of as coming out of the page toward the reader.

It was mentioned that the value of a line integral was a function of the end points only and thus the path of integration from one end to the other was not ordinarily of importance.

(f) The line integral was extended to reach completely around a pole, and with $F(s)$ as a simple factor it was shown that the integral around the pole was $2\pi j$. It was also brought out that the particular size of the path around the pole was not important. Art. 1.13 brought out the fact that integration along the closed path not containing a pole was zero.

(g) The previous ideas were extended in art. 1.14 to include the subject of residues. It was shown that rather complex functions of s could be represented as a product of surfaces, and that the entire function could be written inside a very small circle around the pole as simply the product of the residue and the one factor that created the pole.

(h) It was finally shown in art. 1.15 that the integral of $F(s)$ around all poles in the plane was the same as the sum of the integrals around each pole separately. This gave us a simple way to evaluate all such circular integrals, namely that the integral of $F(s)$ around all poles is equal to $2\pi j$ times the sum of the residues at all poles.

CHAPTER II
THE FOURIER SERIES AND INTEGRAL

2.1. The Fourier Series

THE electronics engineer will have already studied some material on the subject of Fourier Series. Actually, almost everyone who works with electricity and radio has a fair idea of the qualitative relations between fundamental frequencies and the harmonics which make up complicated waveshapes. However, since our work in the present

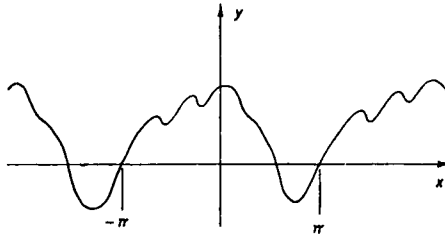


Fig. 2.1

chapter and those to follow grows increasingly complex, it is well to begin with the basic steps to make sure that we will all be using the same symbols and terminology.

Suppose we are given a function $p(x)$ which repeats itself exactly at regular intervals of x . Such a function is said to be periodic, where the period is defined as the interval shown in Fig. 2.1 between $-\pi$ and π .

The complex waveform in Fig. 2.1 can be shown to consist of the sum of a fundamental component and various harmonics, where the fundamental occupies the period from $-\pi$ to π . Therefore,

$$p(x) = a_0 + a_1 \cos x + a_2 \cos 2x + a_3 \cos 3x + \dots + b_1 \sin x + b_2 \sin 2x + b_3 \sin 3x + \dots \quad (2.1)$$

The a_0 term is the only constant quantity and is immediately found to be the average of $p(x)$ over the interval, thus

$$a_0 = \frac{1}{2\pi} \int_{-\pi}^{\pi} p(x) dx \quad \blacktriangleleft \quad (2.2)$$

For ease in writing, we may restate (2.1) in the following form:

$$p(x) = \sum_{n=0}^{\infty} (a_n \cos nx + b_n \sin nx) \quad (2.3)$$

which will be found to contain the a_0 term when $n = 0$, since $\sin(0) = 0$, and $\cos(0) = 1$. Let us now multiply (2.3) by the term $\cos n'x$.

$$p(x) \cos n'x = \cos n'x \sum_{n=0}^{\infty} a_n \cos nx + \cos n'x \sum_{n=0}^{\infty} b_n \sin nx \quad (2.4)$$

We now integrate this expression from $-\pi$ to π

$$\begin{aligned} \int_{-\pi}^{\pi} p(x) \cos n'x \, dx &= \int_{-\pi}^{\pi} \cos n'x \sum_{n=0}^{\infty} a_n \cos nx \, dx + \\ &+ \int_{-\pi}^{\pi} \cos n'x \sum_{n=0}^{\infty} b_n \sin nx \, dx \end{aligned} \quad (2.5)$$

This looks rather formidable. However, it really is not too difficult to handle, as we now show. Suppose we examine the first integral on the right. This is observed to consist of a summation of an infinite number of integrals of the form

$$a_n \int_{-\pi}^{\pi} \cos n'x \cos nx \, dx \quad (2.6)$$

Fortunately, this integral is found to be zero for all cases where n' does not equal n . For the one term where n' does equal n , the value is π . Thus,

$$a_n \int_{-\pi}^{\pi} \cos n'x \cos nx \, dx = \begin{cases} \pi a_n & \text{if } n = n' \\ 0 & \text{if } n \neq n' \end{cases} \quad (2.7)$$

The second term on the right of (2.5) also creates an infinite number of integrals of the form

$$b_n \int_{-\pi}^{\pi} \cos n'x \sin nx \, dx \quad (2.8)$$

By using the trigonometric identity

$$\cos n'x \sin nx = \frac{1}{2}[\sin(nx + n'x) + \sin(nx - n'x)] \quad (2.9)$$

it can easily be shown by integrating and substituting limits that (2.8) equals zero for all cases, whether $n' = n$ or not.

If we now let n' be the general n th term, we may rewrite (2.5), substituting for the intricate right-hand expressions the simple quantity πa_n from (2.7). That is

$$\int_{-\pi}^{\pi} p(x) \cos nx \, dx = \pi a_n \tag{2.10}$$

from which a_n may at last be found as

$$a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} p(x) \cos nx \, dx \quad \blacktriangleleft \tag{2.11}$$

The coefficients b_n may be found in exactly the same manner, by multiplying (2.3) by $\sin n'x$ and integrating from $-\pi$ to π . The final result is

$$b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} p(x) \sin nx \, dx \quad \blacktriangleleft \tag{2.12}$$

The formulas (2.2), (2.11) and (2.12) are marked with small triangles as an aid to future location.

If $p(x)$ is known, any of the coefficients, or “magnitudes” of the harmonic terms can be found simply by placing $p(x)$ into one of the desired formulas.

In our work with electronics, the independent variable is often time. We therefore define a fundamental frequency ω_1 as

$$\omega_1 = 2\pi f = \frac{2\pi}{T} \tag{2.13}$$

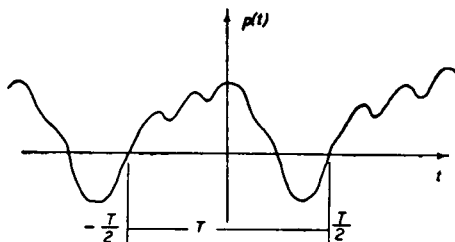


Fig. 2.2

where T is the period in seconds from $-\pi$ to π , as illustrated in Fig. 2.2. Any harmonic frequency ω will therefore be

$$\omega = n\omega_1 = \frac{n2\pi}{T} \tag{2.14}$$

We may now rewrite the Fourier series (2.3) in terms of frequency and time rather than the angle x . Thus

$$p(t) = \sum_{n=0}^{\infty} (a_n \cos n\omega_1 t + b_n \sin n\omega_1 t) \quad (2.15)$$

The corresponding formulas in x and t are collected in Table 2.1 for easy reference.

TABLE 2.1

<i>Variable x</i>	<i>Variable t</i>
$p(x) = \sum_{n=0}^{\infty} (a_n \cos nx + b_n \sin nx)$ <p>where</p> $a_0 = \frac{1}{2\pi} \int_{-\pi}^{\pi} p(x) dx$ $a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} p(x) \cos nx dx$ $b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} p(x) \sin nx dx$	$p(t) = \sum_{n=0}^{\infty} (a_n \cos n\omega_1 t + b_n \sin n\omega_1 t)$ <p>where</p> $a_0 = \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t) dt$ $a_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t) \cos n\omega_1 t dt$ $b_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t) \sin n\omega_1 t dt$

2.2. Exponential form of the Fourier series

It will be the purpose of this article to convert the Fourier series as written in (2.15) into exponential form. This is one of the numerous stages in the gradual development of the Laplace transform, and has considerable application in its own right, as we shall see in some later examples.

Let us begin by writing (2.15) with the following notation, as

$$p(t) = \sum_{n=0}^{\infty} z_n \quad (2.16)$$

where

$$z_n = a_n \cos n\omega_1 t + b_n \sin n\omega_1 t \quad (2.17)$$

Now by the use of Euler's theorem (see art. 1.2) we have the exponential form for a sine and cosine, namely:

$$\cos \theta = \frac{\varepsilon^{j\theta} + \varepsilon^{-j\theta}}{2}; \quad \sin \theta = \frac{\varepsilon^{j\theta} - \varepsilon^{-j\theta}}{2j} \quad (2.18)$$

Using these, the cosine and sine terms in (2.17) may be rewritten as

$$z_n = a_n \left(\frac{e^{jn\omega_1 t}}{2} + \frac{e^{-jn\omega_1 t}}{2} \right) + b_n \left(-j \frac{e^{jn\omega_1 t}}{2} + j \frac{e^{-jn\omega_1 t}}{2} \right) \quad (2.19)$$

which can be factored into the following form:

$$z_n = \frac{1}{2}[(a_n - jb_n)e^{jn\omega_1 t} + (a_n + jb_n)e^{-jn\omega_1 t}] \quad (2.20)$$

Note that the coefficients are complex conjugates. We take their actual values from Table 2.1. Therefore,

$$a_n + jb_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t) \cos n\omega_1 t \, dt + j \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t) \sin n\omega_1 t \, dt \quad (2.21)$$

This is simplified to

$$a_n + jb_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t)[\cos n\omega_1 t + j \sin n\omega_1 t] \, dt \quad (2.22)$$

Euler's theorem (1.8) is again used to simplify the bracketed term still further, to give

$$a_n + jb_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t)e^{jn\omega_1 t} \, dt \quad (2.23)$$

or, if we use both the plus and minus signs, we have both complex conjugates.

$$a_n \pm jb_n = \frac{2}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t)e^{\pm jn\omega_1 t} \, dt \quad (2.24)$$

We are now in a position to solve (2.20) for z_n , by using both values of (2.24), thus

$$z_n = \frac{1}{T} \left[\int_{-\frac{T}{2}}^{\frac{T}{2}} p(t)e^{-jn\omega_1 t} \, dt \, e^{jn\omega_1 t} + \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t)e^{jn\omega_1 t} \, dt \, e^{-jn\omega_1 t} \right] \quad (2.25)$$

Note carefully that the exponential term immediately following each dt is not part of the integral.

Equation (2.25) is now placed back into the original equation in this article, (2.16), which expresses the series. This gives

$$p(t) = \frac{1}{T} \sum_{n=0}^{\infty} \left[\begin{array}{c} \text{sum of the integral} \\ \text{terms in (2.25)} \end{array} \right] \quad (2.26)$$

Now note carefully that if we let n in (2.25) assume both plus and minus values, then we can omit the right-hand integral, as the values $\pm n$ placed in the left-hand integral will create both terms as shown. We can include all minus values of n by summing (2.26) from $-\infty$, rather than 0. Using this new limit of $-\infty$, (2.26) now becomes

$$p(t) = \frac{1}{T} \sum_{n=-\infty}^{\infty} \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t) \varepsilon^{-jn\omega_1 t} dt \varepsilon^{jn\omega_1 t} \quad (2.27)$$

Note again that the exponential term following the dt is not part of the integral. Let us now define a new expression $P(\omega)$ as

$$P(\omega) = \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t) \varepsilon^{-jn\omega_1 t} dt \quad (2.28)$$

(This is a definition, not a derivation) and it merely is defined to simplify the mathematics. If it proves useful as such then the definition is justified. Equation (2.27) therefore becomes

$$p(t) = \frac{1}{T} \sum_{n=-\infty}^{\infty} P(\omega) \varepsilon^{jn\omega_1 t} \quad (2.29)$$

As one last item in this article, we note again that ω_1 is the fundamental angular frequency, and that any harmonic may be simply expressed as

$$\omega = n\omega_1 \quad (2.30)$$

or

$$\omega = \frac{n2\pi}{T} \quad (2.31)$$

from which

$$\frac{T}{2} = \frac{n\pi}{\omega} \quad (2.32)$$

and

$$n = \frac{\omega T}{2\pi} \quad (2.33)$$

(2.29) is now recopied with these new quantities as

$$p(t) = \frac{1}{2\pi} \sum_{\omega=-\infty}^{\infty} P(\omega) \varepsilon^{j\omega t} \frac{\omega}{n} \quad \blacktriangleleft \quad (2.34)$$

and (2.28) is rewritten as

$$P(\omega) = \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t)\epsilon^{-j\omega t} dt \quad \blacktriangleleft \quad (2.35)$$

Equation (2.35) is called the direct Fourier transform of a function of time $p(t)$, and (2.34) is known as the inverse transform.

We have been using the term $p(t)$ and $P(\omega)$ to signify work with periodic functions. Therefore this work can later be distinguished from material dealing with non-periodic functions. For those functions we will use the expressions $f(t)$ and $F(\omega)$.

The results to be retained from this article are equations (2.34) and (2.35). Before finishing the article, however, it is desirable to present an example of their use in the form of a worked out typical problem.

PROBLEM 1 (art. 2.2). Given the periodic square wave shown in Fig. 2.3, find: (a) the frequency spectrum $P(\omega)$. (b) find $p(t)$.

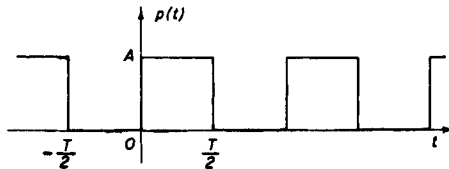


Fig. 2.3

(a) The frequency spectrum, may be found by direct application of (2.35). Thus

$$P(\omega) = \int_{-\frac{T}{2}}^{\frac{T}{2}} p(t)\epsilon^{-j\omega t} dt = \int_{-\frac{T}{2}}^0 (0)\epsilon^{-j\omega t} dt + A \int_0^{\frac{T}{2}} \epsilon^{-j\omega t} dt \quad (2.36)$$

$$P(\omega) = \left[\frac{-A\epsilon^{-j\omega t}}{j\omega} \right]_0^{\frac{T}{2}} = \frac{jA}{\omega} (\epsilon^{-\frac{j\omega T}{2}} - 1) \quad (2.37)$$

Using the trivial relations (2.30) to (2.33), we may rewrite this as

$$P(\omega) = \frac{jAT}{2\pi n} (\epsilon^{-jn\pi} - 1) \quad (2.38)$$

We now begin the seemingly endless task of evaluating this result for all values of n from $-\infty$ to ∞ . First, for $n = 0$, let us expand

the exponential term as a series, and retain the first two terms, i.e.

$$P(\omega) = \frac{jAT}{2\pi n} (1 - jn\pi + \dots - 1) \quad (2.39)$$

Canceling the one's and the n 's, we have

$$P(\omega)|_{\omega=0} = \frac{AT}{2} \quad (2.40)$$

This same result could also have been obtained by evaluating (2.38) by the use of l'Hospital's rule. Now for other values of n from $-\infty$ to ∞ , we may save several years time if we note that

$$(\varepsilon^{-jn\pi} - 1) = \begin{cases} 0 & \text{for } n \text{ even} \\ -2 & \text{for } n \text{ odd} \end{cases} \quad (2.41)$$

(see art. 1.2 for notation).

Retaining only odd values of n , we prepare a chart such as Table 2.2, using only odd values of n in (2.38).

TABLE 2.2

n	$P(\omega)$
0	$\frac{AT}{2}$
± 1	$\mp \frac{jAT}{\pi}$
± 3	$\mp \frac{jAT}{3\pi}$
± 5	$\mp \frac{jAT}{5\pi}$

The spectrum $P(\omega)$ is now plotted, using the values in Table 2.2, and is shown in Fig. 2.4. Fig. 2.4 is called the frequency spectrum, $P(\omega)$.

It is observed that the spectrum is discontinuous, having values only at certain discrete points $0, \omega_1, 3\omega_1$, etc. Later on we will find that certain other functions of time produce continuous spectra.

(b) The time function $p(t)$ may now be found by placing the coefficients of the frequency spectrum back into (2.29). That is

$$p(t) = F^{-1}(\omega) = \frac{1}{T} \sum_{n=-\infty}^{\infty} P(\omega) \varepsilon^{jn\omega_1 t} \tag{2.42}$$

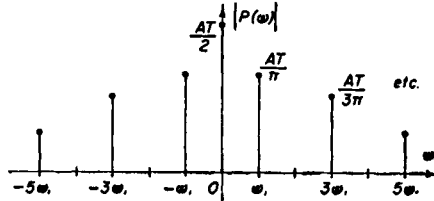


Fig. 2.4

We now insert the $P(\omega)$ values (both plus and minus) from Table 2.2, thus (2.42) becomes

$$p(t) = \frac{1}{T} \left[\underbrace{\frac{AT}{2}}_{n=0} - \underbrace{\frac{jAT\varepsilon^{j\omega_1 t}}{\pi}}_{n=1} + \underbrace{\frac{jAT\varepsilon^{-j\omega_1 t}}{\pi}}_{n=-1} - \underbrace{\frac{jAT\varepsilon^{j3\omega_1 t}}{3\pi}}_{n=3} + \underbrace{\frac{jAT\varepsilon^{-j3\omega_1 t}}{3\pi}}_{n=-3, \text{ etc.}} + \dots \right] \tag{2.43}$$

The T 's are all canceled, and each term except the first is multiplied by 2/2. The result is factored as follows:

$$P(t) = \frac{A}{2} + \frac{2A}{\pi} \left(\frac{\varepsilon^{j\omega_1 t} - \varepsilon^{-j\omega_1 t}}{2j} \right) + \frac{2A}{3\pi} \left(\frac{\varepsilon^{j3\omega_1 t} - \varepsilon^{-j3\omega_1 t}}{2j} \right) + \dots \tag{2.44}$$

and by Euler's theorem,

$$p(t) = \frac{A}{2} + \frac{2A}{\pi} \sin \omega_1 t + \frac{2A}{3\pi} \sin 3\omega_1 t + \dots \tag{2.45}$$

and the problem is solved.

The original square wave, Fig. 2.3, is thus seen to consist of a d.c. term, a fundamental, a third harmonic, and all odd harmonics following, with the magnitude of the harmonics given by the coefficients in (2.45).

Note that the above problem had only sine terms in the output. It is often advantageous to draw the original function so that it is perfectly symmetrical about $t = 0$. This will insure that only cosine terms are present.

Of course we should mention at this point that if one is merely interested in finding the magnitudes of the various harmonics which make up a given waveform, he may solve directly for the values a_n and b_n from the appropriate formulas. The definition of $P(\omega)$, and the concept of the frequency spectrum will be of great assistance to our future work, however, and it is for this reason that they are introduced in this way. Try to follow the same steps we have just illustrated when working the following exercise.

- PROBLEM 2 (a).** Find the frequency spectrum of $p(x)$ in Fig. 2.5.
(b) Find $p(x)$ from the frequency spectrum $P(\omega)$ in (a).

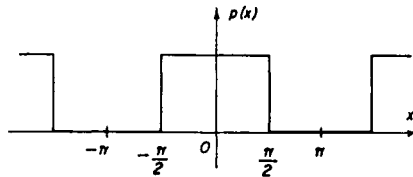


Fig. 2.5

2.3. The Fourier integral

All of the previous material has considered only periodic waveforms. It will now be interesting to see if we can generalize the foregoing ideas to include non-periodic waves as well.

We know that periodic non-sinusoidal waves give rise to a real, discrete, frequency spectrum. That is, the period of the waveform provides a knowledge of the fundamental frequency. The harmonics occupy discrete positions which are n times the fundamental frequency, where n is always integral.

Let us now examine Fig. 2.6, where ω_1 is the first division. Since the spacing between adjacent harmonics will be equal to ω_1 we may also define ω_1 as $\Delta\omega$. It is observed that if ω_1 is quite small, $\Delta\omega$ is very small and hence any frequency may be defined as

$$\omega = n\Delta\omega \quad (2.46)$$

Since ω_1 is inversely proportional to T , we see that it should be possible to let T approach infinity and accomplish this result. Thus

we might say that a non-periodic waveform could be considered to have an infinitely long period. Or looking at it another way, we see that

$$T = \frac{1}{f} = \frac{2\pi}{\omega_1} = \frac{2\pi}{\Delta\omega} \tag{2.47}$$

or

$$\frac{T}{2} = \frac{\pi}{\Delta\omega} \tag{2.48}$$

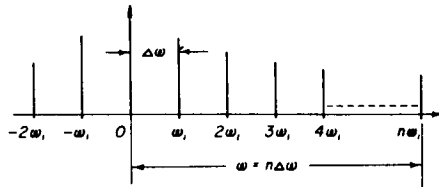


Fig. 2.6

If we now recopy (2.35) from the last article, but use the above value of $T/2$ for the limits, we have

$$F(\omega) = \int_{-\frac{\pi}{\Delta\omega}}^{\frac{\pi}{\Delta\omega}} f(t)\epsilon^{-j\omega t} dt \tag{2.49}$$

(note that when dealing with non-periodic waveforms we will use the letters F and f , rather than P and p). Also, we found earlier (2.34) that

$$f(t) = \frac{1}{2\pi} \sum_{\omega=-\infty}^{\infty} F(\omega)\epsilon^{j\omega t} \frac{\omega}{n} \tag{2.50}$$

Substituting (2.49) into (2.50) gives

$$f(t) = \frac{1}{2\pi} \sum_{\omega=-\infty}^{\infty} \left[\int_{-\frac{\pi}{\Delta\omega}}^{\frac{\pi}{\Delta\omega}} f(t)\epsilon^{-j\omega t} dt \right] \epsilon^{j\omega t} \Delta\omega \tag{2.51}$$

Note also from (2.48) that as $\Delta\omega \rightarrow 0$, $T \rightarrow \infty$, thus

$$\lim_{\Delta\omega \rightarrow 0} f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} \left[\int_{-\infty}^{\infty} f(t)\epsilon^{-j\omega t} dt \right] \epsilon^{j\omega t} d\omega \tag{2.52}$$

The quantity inside the bracket is defined as

$$F(\omega) = \int_{-\infty}^{\infty} f(t) \varepsilon^{-j\omega t} dt \quad \blacktriangleleft \quad (2.53)$$

and thus (2.52) reduces to

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) \varepsilon^{j\omega t} d\omega \quad \blacktriangleleft \quad (2.54)$$

Equation (2.53) will be called the direct Fourier integral, and (2.54) will be defined as the inverse Fourier integral. Equation (2.53) will be very useful in much future work, and is therefore illustrated here by a sample problem.

EXAMPLE. Fourier integral analysis of a simple rectangular pulse. Let us examine a symmetrical pulse as shown in Fig. 2.7, of T sec

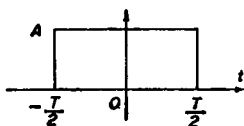


Fig. 2.7

duration and magnitude A . To find the frequency spectrum of this pulse, we use (2.53), and the integral will be broken down into three sections, as

$$F(\omega) = \int_{-\infty}^{-\frac{T}{2}} 0 \cdot \varepsilon^{-j\omega t} dt + A \int_{-\frac{T}{2}}^{\frac{T}{2}} \varepsilon^{-j\omega t} dt + \int_{\frac{T}{2}}^{\infty} 0 \cdot \varepsilon^{-j\omega t} dt \quad (2.55)$$

The first and last terms on the right are zero, therefore

$$F(\omega) = \frac{-A}{j\omega} \left[\varepsilon^{-j\omega t} \right]_{-\frac{T}{2}}^{\frac{T}{2}} \quad (2.56)$$

or

$$F(\omega) = \frac{-A}{j\omega} \left[\varepsilon^{-\frac{j\omega T}{2}} - \varepsilon^{\frac{j\omega T}{2}} \right] \quad (2.57)$$

Rearranging slightly

$$F(\omega) = \frac{2A}{\omega} \left(\frac{\varepsilon^{\frac{j\omega T}{2}} - \varepsilon^{-\frac{j\omega T}{2}}}{2j} \right) \quad (2.58)$$

which becomes finally

$$F(\omega) = \frac{2A}{\omega} \sin \frac{\omega T}{2} \tag{2.59}$$

To get the over-all curve, it is best to graph the numerator and denominator separately, and then divide the two curves at appropriate points (Fig. 2.8). The dotted curve shows the resulting

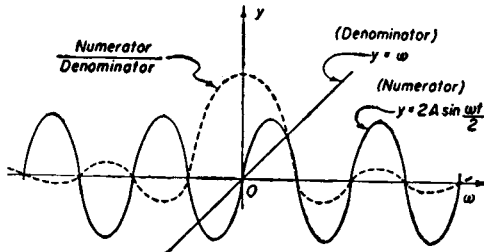


Fig. 2.8

function, which is redrawn in Fig. 2.9 for positive frequencies, and for magnitudes only. Compare Fig. 2.9 with Fig. 2.4, which was an analysis of the same rectangular pulse repeating itself at regular intervals.

We note that for the periodic case there were only certain harmonically related frequencies present, at discrete points in the

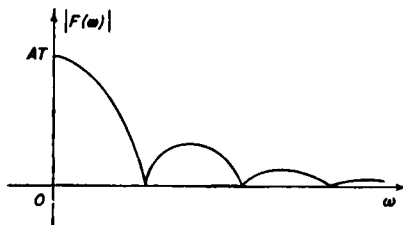


Fig. 2.9

spectrum. If we had tuned a receiver to frequencies other than those discrete points we would have received nothing.

In the case of the isolated, non-periodic pulse, however, note that the opposite is true. All frequencies are present except at discrete points, and unless our exploring receiver were accidentally tuned to one of the frequencies in Fig. 2.9 where a null occurs, there would be output when the pulse occurs. Such output would be created at the time of occurrence of the leading edge of the pulse, and would decay

gradually depending upon the Q of the receiver tuned circuits. When the trailing edge of the pulse occurred, energy would be delivered to or absorbed from the receiver tuned circuit, depending on its phase at the instant when the trailing edge occurred. This topic will be discussed later in the book when we talk about application of the Laplace transformation to shock spectrum analysis.

PROBLEM. Show that the spectrum in Fig. 2.9 has the magnitude AT at $\omega = 0$, i.e. evaluate (2.59) at $\omega = 0$.

2.4. The unit step function

One of the most useful functions in applied electronics is also the simplest. This function is called the *unit step*, and is shown in Fig. 2.10. Thus, the unit step function is seen to be a curve which

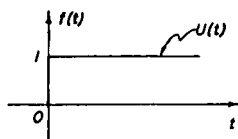


Fig. 2.10

has the value 0 at all points to the left of the origin, and is unity at all points to the right of the origin. The unit step function will be called $U(t)$.

One useful property of the unit step function $U(t)$ is that any other function multiplied by it will be zero for all values to the

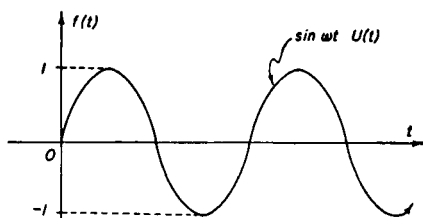


Fig. 2.11

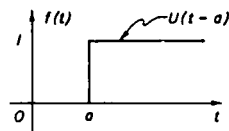


Fig. 2.12

left of the origin. This is illustrated in Fig. 2.11 for the product of a sine wave and a unit step.

The displaced unit step function is also used extensively, and is illustrated in Fig. 2.12. The discontinuity occurs at $t = a$ rather than

$t = 0$. The displaced unit step function will be called $U(t - a)$, where the time a is to the right of the origin.

As a typical introduction to the use of step functions, we see that a rectangular pulse of A volts magnitude, and a sec duration, such as shown in Fig. 2.13, can be completely described as

$$f(t) = A \cdot U(t) - A \cdot U(t - a) \quad (2.60)$$

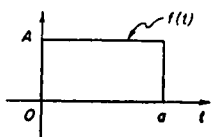


Fig. 2.13

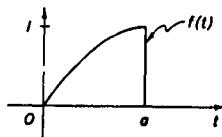


Fig. 2.14

As another example, suppose that one cycle of a sine wave has a period $4a$ sec. A unit rectangular pulse of length a sec can be used to sample the first 90° of the sine wave, resulting in Fig. 2.14, and the result is

$$f(t) = \sin\left(\frac{\pi t}{2a}\right) \cdot [U(t) - U(t - a)] \quad (2.61)$$

Further discussion could bring out the fact that any function could be broken down into a combination of step functions, in the same way that a complex periodic wave can be dissected into sine wave components. We shall return later to this topic, but the next step in our approach to our subject is to try to take the Fourier integral transform of the unit step function $U(t)$.

2.5. The Fourier transform of the unit step function

One of the conditions which a function must normally satisfy to be Fourier transformable is that the following integral must exist.

$$\int_{-\infty}^{\infty} |f(t)| dt \leq \infty \quad (2.62)$$

This automatically excludes all periodic functions such as sines, square waves, etc. Therefore if we try to transform the function $U(t)$ we must first see if it will pass the test given by (2.62).

$$\int_{-\infty}^{\infty} U(t) \cdot dt = \int_{-\infty}^0 0 \cdot dt + \int_0^{\infty} 1 \cdot dt = [t]_0^{\infty} = \infty \quad (2.63)$$

So that ordinarily we could not take the Fourier transform of the unit step function. However, suppose we multiply $U(t)$ by a decay factor to get the curve shown in Fig. 2.15, where c is any positive

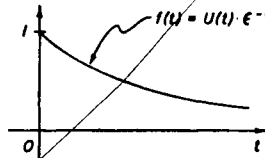


Fig. 2.15

constant. We then may write the Fourier transform of this new function as

$$F(\omega) = \int_{-\infty}^{\infty} f(t)e^{-j\omega t} dt \quad (2.64)$$

or

$$F(\omega) = \int_{-\infty}^0 0 \cdot e^{-j\omega t} dt + \int_0^{\infty} e^{-ct} e^{-j\omega t} dt \quad (2.65)$$

$$F(\omega) = \int_0^{\infty} e^{-(c+j\omega)t} dt = -\frac{1}{c+j\omega} [e^{-(c+j\omega)t}]_0^{\infty} \quad (2.66)$$

Therefore

$$F(\omega) = \frac{1}{c+j\omega}$$

or

$$|F(\omega)| = \frac{1}{\sqrt{c^2 + \omega^2}} \quad (2.67)$$

Now if we look back at Fig. 2.15, we see that if $c \rightarrow 0$, then $f(t)$ becomes our unit step function $U(t)$. The Fourier transform of $U(t)$ is therefore

$$|F(\omega)| = \frac{1}{\omega} \quad (2.68)$$

2.6. Convergence factors

We saw in art. 2.5 that it was possible to evaluate the Fourier transform of a step function by the artifice of making it appear to converge. Suppose that we are interested in functions which have values only after $t = 0$. If such a function $f_1(t)$ does not meet the requirement that

$$\int_0^{\infty} f_1(t) dt < \infty \quad (2.69)$$

it is often possible to multiply it by a convergence factor to form a new function $f(t)$

$$f(t) = f_1(t)e^{-ct} \tag{2.70}$$

which does satisfy (2.69). The value of c which just makes the entire function convergent is called σ_a , or in other words $\sigma_a =$ abscissa of absolute convergence.

EXAMPLE. Suppose we are given a diverging function

$$\left. \begin{aligned} f_1(t) &= 2e^{3t} \text{ for } t > 0 \\ f_1(t) &= 0 \quad \quad \quad t < 0 \end{aligned} \right\} \tag{2.71}$$

as shown in Fig. 2.16. To make this function converge, it is necessary to multiply $f_1(t)$ by a suitable convergence factor

$$f(t) = f_1(t)e^{-ct} \tag{2.72}$$

$$= 2e^{3t} \cdot e^{-ct} \tag{2.73}$$

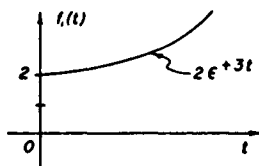


Fig. 2.16

We see by inspection that any value of c greater than 3 will make the over-all function convergent. In particular, (2.73) is convergent for

$$c > \sigma_a; \sigma_a = 3 \tag{2.74}$$

Now for functions such as (2.72), which have values only to the right of $t = 0$, we may write the Fourier integral transform as

$$F_1(\omega, c) = \int_0^\infty [f_1(t)e^{-ct}]e^{-j\omega t} dt \tag{2.75}$$

Suppose that we now move the convergence factor outside of the bracket, and remove the subscripts. Then the result becomes a function both of ω and c . That is

$$F(\omega, c) = \int_0^\infty f(t)e^{-ct}e^{-j\omega t} dt \tag{2.76}$$

In cases of most interest for our future work, the functions will always be made 0 to the left of the origin by multiplying all functions by $U(t)$. Removal of the integral to the left of the origin gives rise to the term *unilateral Fourier integral transform* for the above.

2.7. The complex Fourier integral transform

At this point the reader may begin to grow impatient and ask where we are going. Fortunately we are just on the verge of coming to the final form—the Laplace transform. This chapter will complete the actual formulation of the Laplace transform, and the remainder of the book will be devoted to practical theorems and engineering applications.

To continue, suppose we combine the exponents in (2.76) as follows, we thus have a specific function of $(c + j\omega)$,

$$F(c + j\omega) = \int_0^{\infty} f(t)\varepsilon^{-(c+j\omega)t} dt \quad \blacktriangleleft \quad (2.77)$$

The only condition here is that $c > \sigma_a$. Equation (2.77) is called the direct unilateral Fourier integral transform. We write (2.77) as follows

$$F(c + j\omega) = \int_0^{\infty} [f(t)\varepsilon^{-ct}]\varepsilon^{-j\omega t} dt \quad (2.78)$$

And going back to (2.54), we can write the inverse by inspection as

$$[f(t)\varepsilon^{-ct}] = \frac{1}{2\pi} \int_{\omega=-\infty}^{\infty} F(c + j\omega)\varepsilon^{j\omega t} d\omega \quad (2.79)$$

Now let us multiply both sides by ε^{ct}

$$f(t) = \frac{1}{2\pi} \int_{\omega=-\infty}^{\infty} F(c + j\omega)\varepsilon^{(c+j\omega)t} d\omega \quad (2.80)$$

The ε^{ct} on the right has been brought through the integral sign and combined with the other exponent. This is permissible as the integration is with respect to ω .

Let us now change our variable of integration from

$$\omega \text{ to } (c + j\omega) \quad (2.81)$$

which requires only that

$$d(c + j\omega) = j d\omega \quad (2.82)$$

We now re-write (2.80) in the new variable as

$$f(t) = \frac{1}{2\pi j} \int_{c-j\omega}^{c+j\omega} F(c+j\omega) \varepsilon^{(c+j\omega)t} d(c+j\omega) \quad (2.83)$$

Again, the only restrictions are that $c > \sigma_a$, and $t > 0$.

Note that the integration in (2.83) is performed in the complex plane as in Fig. 2.17. Note also that c is a real number, located on the real axis.

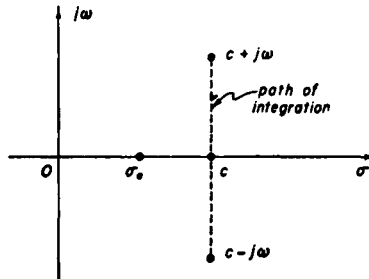


Fig. 2.17

2.8. The Laplace transform

Up to now we have treated c as a constant. We recognized, however, that it was necessary to use different values of c to make the over-all function convergent, and thus c might actually be called a parametric variable, i.e. compare this concept with the inductance L in a resonant L - C circuit. The inductance is usually considered a constant, as when one listens to a favorite radio program. When he wishes to change programs, however, the inductance becomes a variable while he is tuning in a new station, whereupon it resumes its constant characteristic. Such a quantity is called a parametric variable.

Letting c become a real variable σ , we can now define a complex variable s as

$$s = \sigma + j\omega \quad (2.84)$$

and with this new variable, (2.77) can be re-written as

$$F(s) = \int_0^{\infty} f(t) \varepsilon^{-st} dt \quad \blacktriangleleft \quad (2.85)$$

This will be called the direct Laplace transform. Here the restriction

on c has passed on to σ . Using the new complex variable s , (2.83) is also re-written as

$$f(t) = \frac{1}{2\pi j} \int_{c-j\omega}^{c+j\omega} F(s)\varepsilon^{ts} ds \quad (2.86)$$

We can leave the limits as shown for the time being, since they represent definite points in the s plane. The physical interpretation is this: one multiplies the quantity $F(s)\varepsilon^{ts}$ at a point on the path of integration by ds , and sums these quantities along the path from $\omega = -\infty$ to $\omega = \infty$. The only restriction on the path (the line $\sigma = c$) is that it be to the right of all poles of $F(s)\varepsilon^{ts}$.

It is shown in more advanced texts, and merely stated here without proof, that such an integration is equivalent to integrating around any closed path which includes all of the poles. We shall therefore write the definition of the inverse Laplace transform as

$$f(t) = \frac{1}{2\pi j} \oint F(s)\varepsilon^{ts} ds \quad \blacktriangleleft \quad (2.87)$$

where the small circle on the integral represents a line integral around all poles, as was discussed in detail in Chapter I. We shall issue a command, proclaiming $F(s)$ to be defined throughout the entire s -plane. Such a decree is enough justification at the moment to satisfy our electronic engineering readers.

CHAPTER III

THE LAPLACE TRANSFORMATION

3.1. Introduction

IN Chapter II the Fourier transforms were developed and progressively generalized into the Laplace integral. This development was necessary to understand and appreciate the origin of the Laplace transform. A number of texts omit the detailed material which we have just covered and begin directly with the definition of the Laplace integral. However, the student cannot help but have a much greater feeling and appreciation for the subject if he has followed carefully the material in the previous chapter.

In this chapter we will begin at last to work directly with Laplace transforms. Our first task will be to prepare a table of elementary Laplace transform pairs. This will be done by selecting various common functions of time, and transforming them into functions of s in accordance with the Laplace integral. The direct and inverse Laplace integrals are repeated here at the beginning of this chapter for future reference. The direct Laplace transform is:

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt \quad (3.1)$$

and the inverse transform is:

$$f(t) = \frac{1}{2\pi j} \oint F(s)e^{ts} ds \quad (3.2)$$

The reader will recall from his early work in mathematics that it was possible to simplify the process of multiplication by the use of logarithms. Each number was transformed into a corresponding logarithm and the multiplication was replaced by the simpler process of adding the logarithms. To use the method it was necessary to have a table of logarithms, but this was usually available.

Tables of integrals, trigonometric tables, and others are also common, as well as tables of Laplace transforms. However, it will be remembered that when studying the calculus, it was necessary to

do considerable work with the elementary forms before one could use the tables with any efficiency. In like manner it will be necessary here to develop a sufficient number of elementary Laplace transform pairs to have a feel for the subject. In much the same way that logarithms simplify the process of multiplication, so Laplace transforms will be found to simplify many types of operations.

As an example, it will be possible through the use of Laplace transforms to simplify the processes of differentiation and integration into simple algebraic operations. As another illustration, the solutions of complicated differential equations are often obtained with startling simplicity.

At this point we shall make use of the basic Laplace integral (3.1) to derive several important transform pairs. As they are derived, each pair will be numbered and listed in Table 3.1, which will serve as an elementary table of transforms for future work.

3.2. Transforms of constants

Perhaps the simplest function of time is a constant. For example, the voltage of a battery may be considered a constant for its useful life. In all of our work here, we will be concerned only with the value of the function after the time $t = 0$, as the defining Laplace integral has 0 as a lower limit.

Now any function of time which has a constant value from the time $t = 0$ can be written as A times the unit step function $U(t)$. See art. 2.4 for a review of $U(t)$. Suppose we begin by finding the Laplace transform of

$$f(t) = A \cdot U(t) \quad (3.3)$$

We can find $F(s)$, the transform, by using this value for $f(t)$ in (3.1), that is

$$F(s) = \int_0^{\infty} A \cdot U(t) \varepsilon^{-st} dt \quad (3.4)$$

The A , being a constant, can be brought through the integral sign as usual, and the $U(t)$ has the value unity between the limits of integration (see Fig. 2.10). Therefore (3.4) becomes

$$F(s) = A \int_0^{\infty} \varepsilon^{-st} dt \quad (3.5)$$

$$F(s) = \frac{A}{-s} [\varepsilon^{-st}]_0^{\infty} \quad (3.6)$$

and substituting the limits

$$F(s) = \frac{A}{s} \quad (3.7)$$

which is the Laplace transform of the constant A . If A should be unity, then (3.7) would give us the transform of unity, or the unit step function $U(t)$.

The operation of taking the Laplace transform is indicated by the symbol \mathcal{L} . This symbol placed in front of a quantity means that its Laplace transform is indicated. It is an operator, in the same manner that differential and integral symbols are operators. As an example:

$$\mathcal{L}[f(t)] = F(s) = \int_0^{\infty} f(t)\varepsilon^{-st} dt \quad (3.8)$$

From the results of this article therefore, we can also write

$$\mathcal{L}[A] = \frac{A}{s} \quad (3.9)$$

or

$$\mathcal{L}[U(t)] = \frac{1}{s} \quad (3.10)$$

This symbolism is read "the Laplace transform of U of t is one over s ." These forms are listed as #1 and #2 in Table 3.1 of "transform pairs".

3.3. The Laplace transform of exponentials

Probably the next form in order of complexity is the function

$$f(t) = \varepsilon^{-at} \quad (3.11)$$

which is a decaying exponential. It may be placed into the Laplace integral and transformed into a function of s as follows:

$$F(s) = \int_0^{\infty} \varepsilon^{-at}\varepsilon^{-st} dt \quad (3.12)$$

Performing the indicated integration, one first combines the exponents

$$F(s) = \int_0^{\infty} \varepsilon^{-(s+a)t} dt \quad (3.13)$$

$$F(s) = -\frac{1}{(s+a)} [\varepsilon^{-(s+a)t}]_0^{\infty} \quad (3.14)$$

and when the limits are inserted

$$F(s) = \frac{1}{s + a} \quad (3.15)$$

We could also say symbolically that

$$\mathcal{L}[e^{-at}] = \frac{1}{s + a} \quad (3.16)$$

This form is listed as #3 in Table 3.1.

It is easy to see that we can replace the a in (3.11) by $-a$, and merely change the sign of the resulting a in (3.15). We therefore have another form

$$\mathcal{L}[e^{at}] = \frac{1}{s - a} \quad (3.17)$$

which is listed as form #4 in Table 3.1.

3.4. The Laplace transform of imaginary exponents

To continue with the development of our table of Laplace transforms, suppose we have the function

$$f(t) = e^{j\omega t} \quad (3.18)$$

It would be easy enough to insert this function directly into the Laplace integral, and solve directly for $F(s)$. However, we should take advantage of the work already done. We note that we can let the $j\omega$ in (3.18) be represented by the constant a in form #4 which we have developed before. Using form #4 therefore, we can write the transform of (3.18) by inspection as

$$\mathcal{L}[e^{j\omega t}] = \frac{1}{s - j\omega} \quad (3.19)$$

By exchanging signs of the constants, we can also write by inspection

$$\mathcal{L}[e^{-j\omega t}] = \frac{1}{s + j\omega} \quad (3.20)$$

These two new forms are listed as pairs #5 and #6 in Table 3.1.

3.5. The Laplace transform of trigonometric terms

In future work with electronic networks and circuits it will often be necessary to take the Laplace transform of sine and cosine

waveforms. We will begin by assuming a function

$$f(t) = \cos \omega t \quad (3.21)$$

We may write this function as the sum of two conjugates as

$$\cos \omega t = \frac{1}{2} \varepsilon^{j\omega t} + \frac{1}{2} \varepsilon^{-j\omega t} \quad (3.22)$$

The coefficient $\frac{1}{2}$, being a constant, is not affected by the transformation, and we have already derived the transforms for both exponential terms (pairs #5 and #6). We therefore write the function of s by inspection as

$$\mathcal{L}[\cos \omega t] = \frac{1}{2} \cdot \frac{1}{(s - j\omega)} + \frac{1}{2} \cdot \frac{1}{(s + j\omega)} \quad (3.23)$$

We now find a least common denominator

$$F(s) = \frac{(s + j\omega) + (s - j\omega)}{2(s - j\omega)(s + j\omega)} \quad (3.24)$$

which simplifies nicely to

$$F(s) = \frac{s}{s^2 + \omega^2} \quad (3.25)$$

which is listed as pair #7 in Table 3.1.

If we are required to find the transform of $\sin \omega t$, the same procedure can be employed.

$$\sin \omega t = \frac{j\varepsilon^{-j\omega t}}{2} - \frac{j\varepsilon^{j\omega t}}{2} \quad (3.26)$$

The constant $j/2$ is not affected by the transformation, and pairs #5 and #6 can be used to write the transform of (3.26) by inspection.

$$\mathcal{L}[\sin \omega t] = \frac{j}{2} \cdot \frac{1}{(s + j\omega)} - \frac{j}{2} \cdot \frac{1}{(s - j\omega)} \quad (3.27)$$

We find the least common denominator to be

$$F(s) = \frac{j(s - j\omega) - j(s + j\omega)}{2(s + j\omega)(s - j\omega)} \quad (3.28)$$

and the resulting expression simplifies to

$$F(s) = \frac{\omega}{s^2 + \omega^2} \quad (3.29)$$

which is listed as transform pair #8 in Table 3.1.

It might be well at this time to mention the fact that the transform of a sum of terms is equal to the sum of the transforms of the individual terms. That is

$$\mathcal{L}[f_1(t) + f_2(t)] = \mathcal{L}[f_1(t)] + \mathcal{L}[f_2(t)] \quad (3.30)$$

This statement will be apparent upon recalling the integral definition of the Laplace transformation, and noting that the integral of a sum of terms is equal to the sum of the integrals of the individual terms.

3.6. The Laplace transform of hyperbolic functions

In developing a table of elementary transform pairs, it will be well to include the hyperbolic sine and hyperbolic cosine, as these functions play an important part in many branches of electronics. The hyperbolic cosine may be written

$$\cosh \omega t = \frac{e^{\omega t}}{2} + \frac{e^{-\omega t}}{2} \quad (3.31)$$

and by the use of transform pairs #3 and #4 we may write

$$\mathcal{L}[\cosh \omega t] = \frac{1}{2} \cdot \frac{1}{(s - \omega)} + \frac{1}{2} \cdot \frac{1}{(s + \omega)} \quad (3.32)$$

This expression is further simplified to give

$$\mathcal{L}[\cosh \omega t] = \frac{s}{s^2 - \omega^2} \quad (3.33)$$

The hyperbolic sine can be expressed as

$$\sinh \omega t = \frac{e^{\omega t}}{2} - \frac{e^{-\omega t}}{2} \quad (3.34)$$

and the same pairs may be used to write

$$\mathcal{L}[\sinh \omega t] = \frac{1}{2} \cdot \frac{1}{(s - \omega)} - \frac{1}{2} \cdot \frac{1}{(s + \omega)} \quad (3.35)$$

which simplifies into

$$\mathcal{L}[\sinh \omega t] = \frac{\omega}{s^2 - \omega^2} \quad (3.36)$$

These forms are listed as #9 and #10 in Table 3.1.

TABLE 3.1

#	$f(t)$	$F(s)$
1	$U(t)$	$\frac{1}{s}$
2	$A \cdot U(t)$	$\frac{A}{s}$
3	e^{-at}	$\frac{1}{s+a}$
4	e^{at}	$\frac{1}{s-a}$
5	$e^{j\omega t}$	$\frac{1}{s-j\omega}$
6	$e^{-j\omega t}$	$\frac{1}{s+j\omega}$
7	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
8	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cosh \omega t$	$\frac{s}{s^2 - \omega^2}$
10	$\sinh \omega t$	$\frac{\omega}{s^2 - \omega^2}$
11	$e^{(\alpha+j\omega)t}$	$\frac{1}{s-\alpha-j\omega}$
12	$e^{(\alpha-j\omega)t}$	$\frac{1}{s-\alpha+j\omega}$
13	$e^{-\alpha t} \sin \omega t$	$\frac{\omega}{(s+\alpha)^2 + \omega^2}$
14	$e^{-\alpha t} \cos \omega t$	$\frac{s+\alpha}{(s+\alpha)^2 + \omega^2}$
15	t	$\frac{1}{s^2}$
16	$\frac{df(t)}{dt}$	$sF(s) - f(0)$
17	$\int f(t) dt$	$\frac{1}{s} [F(s) + f^{-1}(0)]$

3.7. The Laplace transform of complex exponentials

Suppose one is given the time function

$$f(t) = e^{(\alpha+j\omega)t} \quad (3.37)$$

We may let the complex coefficient of t correspond to the a in pair #4. Whereupon the $F(s)$ may be written as

$$F(s) = \frac{1}{s - \alpha - j\omega} \quad (3.38)$$

Similarly, if

$$f(t) = e^{(\alpha-j\omega)t} \quad (3.39)$$

one can use the same form to obtain

$$F(s) = \frac{1}{s - \alpha + j\omega} \quad (3.40)$$

and these are listed as forms #11 and #12 in Table 3.1.

Other combinations of positive and negative real and complex exponentials can be transformed by similar reasoning.

3.8 Transforms of more complicated functions

A waveform often found in electronic equipment is the exponentially decaying sine wave, expressed as

$$f(t) = e^{-\alpha t} \sin \omega t \quad (3.41)$$

The sine wave factor can be expressed with exponentials and the entire function written as

$$f(t) = \frac{e^{-\alpha t} e^{j\omega t}}{2j} - \frac{e^{-\alpha t} e^{-j\omega t}}{2j} \quad (3.42)$$

and the exponents combined to give

$$f(t) = \frac{1}{2j} [e^{-(\alpha-j\omega)t} - e^{-(\alpha+j\omega)t}] \quad (3.43)$$

For the first exponential term, let $(\alpha - j\omega)$ correspond to the a in pair #3 of Table 3.1, and for the second term let $(\alpha + j\omega)$ be the a in the same pair. Thus we can write

$$F(s) = \frac{1}{2j} \left[\frac{1}{(s + \alpha - j\omega)} - \frac{1}{(s + \alpha + j\omega)} \right] \quad (3.44)$$

One can find a least common denominator, and then simplify this last quantity to

$$F(s) = \frac{\omega}{(s + \alpha)^2 + \omega^2} \quad (3.45)$$

This form is listed as pair #13 in Table 3.1.

PROBLEM

(1) Using any method, find the Laplace transform of

$$f(t) = e^{-\alpha t} \cos \omega t$$

Check your answer with pair #14 in Table 3.1.

(2) Using the Laplace integral, find the transform of

$$f(t) = t$$

and check your answer with pair #15 in Table 3.1.

3.9. Additional practice with sinewaves

As one last item before we finish with simple functions, let us examine the function

$$f(t) = \sin(\omega t + \phi) \quad (3.46)$$

We can expand the right-hand side trigonometrically to give

$$f(t) = \sin \omega t \cos \phi + \cos \omega t \sin \phi \quad (3.47)$$

and note that $\cos \phi$ and $\sin \phi$ are constants which we can call b and a , respectively. Therefore

$$f(t) = b \sin \omega t + a \cos \omega t \quad (3.48)$$

The transform may be written by pairs #7 and #8 as

$$F(s) = \frac{b\omega}{s^2 + \omega^2} + \frac{as}{s^2 + \omega^2} \quad (3.49)$$

which is combined to give

$$F(s) = \frac{as + b\omega}{s^2 + \omega^2} \quad (3.50)$$

where

$$\tan \phi = \frac{a}{b} \quad (3.51)$$

The result shows that if ϕ becomes 90° , for example, (3.51) requires that $b = 0$, and (3.50) becomes

$$F(s) = \frac{as}{s^2 + \omega^2} \quad (3.52)$$

which pair #7 shows to be a cosine wave. We can see by inspection that this is correct, as we know that a sine wave shifted 90° in phase would be the same as a cosine wave.

Another important fact to point out here is that the poles of this function of s do not depend upon the phase angle of the original function, that is, the poles of (3.50) occur at

$$\text{and } \left. \begin{array}{l} s = j\omega \\ s = -j\omega \end{array} \right\} \quad (3.53)$$

and the location of the poles in the s -plane will be fixed, regardless of phase angle in the time domain. This characteristic will be of considerable importance later.

3.10. The Laplace transform of a derivative

It will be remembered from the first courses in circuit analysis that voltages appearing across capacities and inductances involve derivatives and integrals. Similar expressions for currents also involve integrals and derivatives, and therefore it will often be necessary to take the Laplace transforms of derivatives and integrals if the theory is to be of any worth for our future electronic research.

The reader is urged to study these last two articles carefully, as several important ideas are presented which are important as background information. It will be found that these operations are much simpler to perform in the s -plane than in the time domain. Let us assume the following three conditions:

- (a) That $f(t) = 0$, for $t < 0$.
- (b) That $f(t)$ is transformable; that is,

$$\mathcal{L}[f(t)] = F(s)$$

- (c) That

$$\left. \frac{df(t)}{dt} \right|_{t=0} < \infty$$

We begin by looking at an elementary integral relation from calculus

$$\int u \, dv = uv - \int v \, du \quad (3.54)$$

Suppose we let

$$u = f(t) \quad (a) \quad (3.55)$$

then

$$du = \frac{df(t)}{dt} dt \quad (b) \quad (3.56)$$

Next, let

$$dv = \varepsilon^{-st} dt \quad (c) \quad (3.57)$$

then

$$v = \frac{-\varepsilon^{-st}}{s} \quad (d) \quad (3.58)$$

Now if we wish to take the Laplace transform of the derivative of $f(t)$, we have

$$\mathcal{L}[f'(t)] = F(s) = \int_0^{\infty} \left[\frac{df(t)}{dt} \right] \varepsilon^{-st} dt \quad (3.59)$$

by the usual definition. If we now write

$$F(s) = \int_0^{\infty} u \, dv = uv \Big|_0^{\infty} - \int_0^{\infty} v \, du \quad (3.60)$$

we may replace the u and dv by the equivalents from (a), (b), (c), and (d).

$$F(s) = \frac{-f(t)\varepsilon^{-st}}{s} \Big|_0^{\infty} - \int_0^{\infty} -\frac{\varepsilon^{-st}}{s} \frac{df(t)}{dt} dt \quad (3.61)$$

Evaluating the first right-hand part, and rearranging the second,

$$F(s) = \frac{f(0)}{s} + \frac{1}{s} \int_0^{\infty} \left[\frac{df(t)}{dt} \right] \varepsilon^{-st} dt \quad (3.62)$$

where it is noted that the factor s has been brought outside the integral sign. This is permissible because t is the variable of integration in this case. Thus we now can write

$$sF(s) - f(0) = \int_0^{\infty} \left[\frac{df(t)}{dt} \right] \varepsilon^{-st} dt \quad (3.63)$$

It is now easy to see that the right-hand side is the Laplace transform of the derivative.

$$\mathcal{L} \left[\frac{df(t)}{dt} \right] = sF(s) - f(0) \quad (3.64)$$

and this pair is listed as #16 in Table 3.1.

The second term on the right is merely the value of $f(t)$ at $t = 0$. We see, therefore, that if we have a function of time, and the Laplace transform is already known, it may be differentiated merely by multiplying by s , and then subtracting the initial value of $f(t)$. We will have much use for this form in later work.

This transform illustrates again how a complicated operation (differentiation) in the time domain goes over into a simpler operation (multiplication and subtraction) in the s -domain.

EXAMPLE 1. Given the function

$$f(t) = e^{-at} \quad (3.65)$$

find the Laplace transform of the derivative of $f(t)$. We could differentiate the function first, and place into the Laplace integral, but we choose to use pair #3 in Table 3.1 to write

$$F(s) = \frac{1}{s + a} \quad (3.66)$$

and perform our differentiation in the s -domain, which is much easier. To differentiate, we multiply $F(s)$ by s , and subtract the value of (3.65) for $t = 0$. This gives

$$\mathcal{L} \left[\frac{d e^{-at}}{dt} \right] = \frac{s}{s + a} - 1 \quad (3.67)$$

PROBLEM 1. Check the validity of (3.67) by differentiating (3.65) first, and then taking the transform by previous methods.

PROBLEM 2. Find the Laplace transform of the derivative of

$$f(t) = \sin \omega t \quad (3.68)$$

by differentiating in the s -domain.

3.11. The Laplace transform of an integral

As the last article in this chapter, we will now derive the Laplace transform of the integral of a function of time. We shall find that integration, like many other operations, is considerably simplified

when performed in the s -plane. Let us begin by writing the general transform

$$F(s) = \int_0^{\infty} f(t) \varepsilon^{-st} dt \quad (3.69)$$

which, to keep general, we now integrate by parts

$$F(s) = \int_0^{\infty} u dv = uv \Big|_0^{\infty} - \int_0^{\infty} v du \quad (3.70)$$

This time, however, let

$$u = \varepsilon^{-st} \quad (a) \quad (3.71)$$

from which

$$du = -s\varepsilon^{-st} dt \quad (b) \quad (3.72)$$

Then we let

$$dv = f(t) dt \quad (c) \quad (3.73)$$

so that by integration

$$v = \int f(t) dt = \int_0^t f(t) dt + \left[\int f(t) dt \right]_{t=0} \quad (3.74)$$

where the last term on the right is the value of the integral of $f(t)$ at $t = 0$. This could, for example, correspond to initial charge on a capacity. Using a fairly common terminology, we will denote this integration by a negative power, so that (3.74) may be written

$$v = \int_0^t f(t) dt + f^{-1}(0) \quad (d) \quad (3.75)$$

Note carefully that $f^{-1}(0)$ is the value of the integral at $t = 0$, and is not the same as $f(0)$ which we found in deriving the derivative transform in the last article.

If we now substitute the quantities (a), (b), (c) and (d) into (3.70) we have

$$F(s) = \left\{ \varepsilon^{-st} \left[\int_0^t f(t) dt + f^{-1}(0) \right] \right\}_0^{\infty} - \int_0^{\infty} \left[\int_0^t f(t) dt + f^{-1}(0) \right] (-s\varepsilon^{-st} dt) \quad (3.76)$$

When the limits are substituted in the first integral expression, we have

$$F(s) = -f^{-1}(0) + s \int_0^{\infty} \left[\int_0^t f(t) dt + f^{-1}(0) \right] \varepsilon^{-st} dt \quad (3.77)$$

where, in addition, the $-s$ in the second term has been brought outside the integral. This is permissible as the s is not the variable of integration. The last term in (3.77) is now rewritten as the sum of two integrals, as

$$F(s) = -f^{-1}(0) + s \int_0^{\infty} \left[\int_0^t f(t) dt \right] \varepsilon^{-st} dt + s \int_0^{\infty} f^{-1}(0) \varepsilon^{-st} dt \quad (3.78)$$

It will be noted that the last integral is merely the Laplace transform of a constant, which is the constant times $1/s$, and when multiplied by the factor s in the numerator, leaves the constant itself. Thus, canceling the first and last terms on the right, and dividing by s , gives

$$\frac{F(s)}{s} = \int_0^{\infty} \left[\int_0^t f(t) dt \right] \varepsilon^{-st} dt \quad (3.79)$$

Now we see that the term on the right is, by definition, the Laplace transform of the integral of $f(t)$, thus we may write

$$\mathcal{L} \left[\int_0^t f(t) dt \right] = \frac{F(s)}{s} \quad (3.80)$$

We note that the integral in (3.80) has limits, and thus is a definite integral. If we remove the limits, a constant of integration will appear when $f(t)$ is integrated. This constant may be Laplace transformed and added to the right-hand side of (3.80). Also, it will be noted that the value of the constant is the value of the integral at $t = 0$, thus

$$\mathcal{L} \left[\int f(t) dt \right] = \frac{F(s)}{s} + \frac{f^{-1}(0)}{s} \quad (3.81)$$

If the value of the integral is 0 at $t = 0$, i.e. if it is known that initial conditions are zero, the last term on the right will disappear. Equation (3.81) is listed as the last pair in Table 3.1.

EXAMPLE. Suppose we have a condenser which has an initial voltage a as shown in Fig. 3.1. This condenser is connected to a source of voltage $e(t)$ at time $t = 0$ as shown. We write the equation as

$$e(t) = \frac{1}{C} \int_0^t i dt + a$$

which is transformed term by term as

$$E(s) = \frac{I(s)}{Cs} + \frac{a}{s}$$

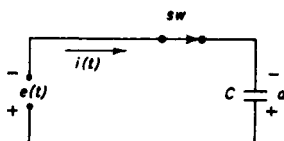


Fig. 3.1

NOTE. In this text we shall use the term current to be synonymous with electron flow. Although this differs from older terminology, the writer feels that the subject is too important to allow tradition or prejudice to interfere with the clearest possible presentation. The current, or electron flow, will in this text leave the negative terminal of the battery, will flow from cathode to plate in a tube, and from emitter to collector in an $N-P-N$ transistor.

CHAPTER IV
THE INVERSE LAPLACE TRANSFORMATION

4.1. Introduction

IN the last chapter we developed a number of Laplace transforms of the more common functions. It was found that the transform of an exponential could be used to obtain practically all of the other pairs. Later on in the text we will develop a number of theorems which will prove useful in practical cases, but now it is desirable that we spend some time in learning how to take the inverse transforms of functions which arise in problems.

Speaking in general, one usually has a problem involving an excitation function applied to some network. The network, upon being thus excited, develops some response. The response is often in the form of an output voltage. Symbolically, we may illustrate this general definition as in Fig. 4.1.

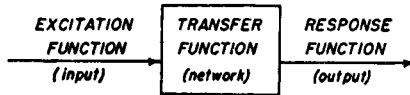


Fig. 4.1

In all future work, the transfer function will be defined as the ratio of output quantity to input quantity. If the input and output are voltages, we call the transfer function Z_t , and write the relation as

$$Z_t = \frac{e_o}{e_{IN}} \quad (4.1)$$

If the transfer function of a given network is known, the output for a given excitation is then merely

$$e_o = Z_t e_{IN} \quad (4.2)$$

The difficulty which arises in practice is that when complicated networks are involved, the expression for e_o usually involves combinations of derivatives, integrals, trigonometric terms, etc. By

the use of our Laplace transform theory, these quantities are all converted to algebraic forms, whereupon the output voltage is obtained as a function of s . The problem is then one of transforming the output as a function of s back into a function of time.

EXAMPLE 1. As an example of how the Laplace transform theory is applied, let us consider the case shown in Fig. 4.2. The switch is

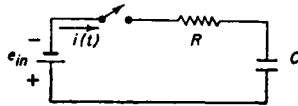


Fig. 4.2

closed at time $t = 0$, and it is required to find the resulting current as a function of time. By Kirchhoff's law, we can write the sum of the voltage drops as equal to the applied voltage, that is

$$e_{IN}(t) = Ri(t) + \frac{1}{C} \int i(t) dt \tag{4.3}$$

where we have specifically indicated that voltage and current are functions of time. There is no charge on the condenser prior to closing the switch.

We may transform (4.3) term by term as follows: $e_{IN}(t)$, being a battery, is constant, and by pair #2, Table 3.1, its transform is

$$e_{IN}(t) \rightarrow \frac{e_{IN}}{s} \tag{4.4}$$

where the arrow is read "transforms into". The second term is merely indicated by using a capital letter for the variable.

$$Ri(t) \rightarrow RI(s) \tag{4.5}$$

The last term requires the use of pair #17, which allows us to write

$$\frac{1}{C} \int i dt \rightarrow \frac{I(s)}{Cs} \tag{4.6}$$

The entire equation is now written as a function of s , and we have

$$\frac{e_{IN}}{s} = RI(s) + \frac{I(s)}{Cs} \tag{4.7}$$

Our problem called for $i(t)$ to be found. To do this we first solve (4.7) for current in the s domain, that is, I as a function of s .

$$\frac{e_{IN}}{s} = I(s) \left(R + \frac{1}{Cs} \right) \quad (4.8)$$

$$I(s) = \frac{e_{IN}}{s(R + 1/Cs)} \quad (4.9)$$

$$I(s) = \frac{e_{IN}}{Rs + 1/C} \quad (4.10)$$

and if we divide both numerator and denominator by R , we have

$$I(s) = \frac{e_{IN}}{R} \cdot \frac{1}{(s + 1/RC)} \quad (4.11)$$

The purpose of dividing by R was to get the part involving s into a familiar form. We see that the quantity multiplied by e_{IN}/R is, by pair #3, Table 3.1,

$$\frac{1}{(s + 1/RC)} \rightarrow \epsilon^{-t/RC} \quad (4.12)$$

where the α corresponds to $1/RC$. Equation (4.11) is thus re-converted into a function of time

$$i(t) = \frac{e_{IN}}{R} \epsilon^{-t/RC} \quad (4.13)$$

which the reader will recall from elementary work with circuit analysis as being correct.

In this example, the function of s to be transformed back into a function of time was very simple, and the transformation was accomplished by inspection. Such elementary forms are usually soon committed to memory. In most of the more advanced work, however, the function of s which results will be considerably more complex than this, and therefore we will spend the present chapter learning how to transform such functions back into the time domain.

EXAMPLE 2. After studying the above example, look at the problem in Fig. 4.3. This is the same problem as the previous example, except that the condenser now has a certain voltage v

prior to closing the switch. The Kirchoff's law equations are the same, namely

$$e_{IN}(t) = Ri(t) + \frac{1}{C} \int i(t) dt \tag{4.14}$$

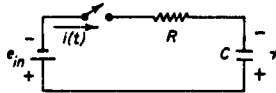


Fig. 4.3

but when we come to transform the integral term, note that the initial condition is not zero, and thus we must use the complete form as given in pair #17, Table 3.1.

$$\frac{e_{IN}}{s} = RI(s) + \frac{1}{Cs} [I(s) + i^{-1}(0)] \tag{4.15}$$

$$\frac{e_{IN}}{s} = RI(s) + \frac{I(s)}{Cs} + \frac{i^{-1}(0)}{Cs} \tag{4.16}$$

Now observe that the $i^{-1}(0)$ is the charge which was on the condenser prior to $t = 0$. Also note that this charge divided by capacity is the initial voltage v . Thus (4.16) becomes

$$\frac{e_{IN}}{s} = RI(s) + \frac{I(s)}{Cs} + \frac{v}{s} \tag{4.17}$$

This last term is brought to the left-hand side, and factored as

$$\frac{e_{IN} - v}{s} = I(s) \left(R + \frac{1}{Cs} \right) \tag{4.18}$$

Now in order to solve for $i(t)$, we first solve for $I(s)$, as

$$I(s) = \frac{(e_{IN} - v)}{s(R + 1/Cs)} \tag{4.19}$$

As before this is factored into the form

$$I(s) = \frac{(e_{IN} - v)}{R} \cdot \frac{1}{(s + 1/RC)} \tag{4.20}$$

We are now ready to take the inverse transform, which is the same as before, except that now the constant multiplier is $(e_{IN} - v)$ rather than e_{IN}

$$i(t) = \frac{(e_{IN} - v)}{R} e^{-\frac{t}{RC}} \quad (4.21)$$

As we progress further into the book, it will be realized that Laplace transform technique automatically handles the problems of initial conditions, whereas the classical differential equation methods usually give trouble in this respect.

PROBLEM. Solve Example 1 by straight integration, and compare the time required with the time using Laplace transforms.

4.2. Functions of s from electronic networks

Linear networks are composed of various combinations of R , L and C . The basic relations between voltage and current in each of these elements is:

for a resistance

$$e = Ri \quad (4.22)$$

for an inductance

$$e = L \frac{di}{dt} \quad (4.23)$$

and for a capacity

$$e = \frac{1}{C} \int i dt \quad (4.24)$$

We may use our Laplace transform theory to transform each of these quantities into functions of s

$$E(s) = RI(s) \quad (4.25)$$

$$E(s) = sLI(s) \quad (4.26)$$

and

$$E(s) = \frac{I(s)}{sC} \quad (4.27)$$

Impedance, in either the time domain or the s -domain, is the ratio of voltage to current, and therefore:

for a resistance

$$Z(s) = R \quad (4.28)$$

for an inductance

$$Z(s) = sL \quad (4.29)$$

and for a capacity

$$Z(s) = \frac{1}{sC} \quad (4.30)$$

Note the similarity between impedance as a function of s , and impedance in a.c. circuit theory, where s was replaced by $j\omega$. We have defined s as a complex variable

$$s = \sigma + j\omega \quad (4.31)$$

We can see now that replacing s by $j\omega$, as in classical a.c. circuit theory, places a severe restriction on our solutions.

In any network, it will be just as easy to write the equations directly as a function of s . We can label each impedance as a function of s , as well as currents and voltages.

EXAMPLE. Using the conventional fictitious current notation, the loop equations of Fig. 4.4 are written as

$$\left(R + \frac{2}{sC}\right) I_1(s) - \frac{I_2(s)}{sC} = E_{IN}(s) \quad (4.32)$$

$$-\frac{I_1(s)}{sC} + \left(R + \frac{1}{sC}\right) I_2(s) = 0 \quad (4.33)$$

We solve for $I_2(s)$ by determinants

$$I_2(s) = \frac{\frac{E_{IN}(s)}{sC}}{\begin{vmatrix} \left(R + \frac{2}{sC}\right) & -\frac{1}{sC} \\ -\frac{1}{sC} & \left(R + \frac{1}{sC}\right) \end{vmatrix}} \quad (4.34)$$

which can be expanded and simplified to

$$I_2(s) = \frac{E_{IN}(s)Cs}{s^2R^2C^2 + 3sRC + 1} \quad (4.35)$$

We note that the output voltage is

$$E_o(s) = RI_2(s) \quad (4.36)$$

therefore, using (4.35) and (4.36)

$$E_o(s) = \frac{E_{IN}(s)RCs}{s^2R^2C^2 + 3sRC + 1} \quad (4.37)$$

By the definition given in art. 4.1, the transfer function is the ratio of output to input.

$$Z_i(s) = \frac{RCs}{R^2C^2s^2 + 3RCs + 1} \quad (4.38)$$

In many places, the t subscript is omitted if it is clear that the Z refers to a transfer function. The transfer function of the network

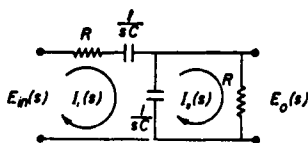


Fig. 4.4

shown in Fig. 4.4, and given by (4.38) can be factored by finding the roots of

$$R^2C^2s^2 + 3RCs + 1 = 0 \quad (4.39)$$

The roots are

$$s = \frac{-3 + \sqrt{5}}{RC} \quad (4.40)$$

and

$$s = \frac{-3 - \sqrt{5}}{RC} \quad (4.41)$$

The numbers are combined, and (4.38) is written in factored form as

$$Z_i(s) = \frac{RCs}{(s + 0.38/RC)(s + 2.62/RC)} \quad (4.42)$$

It will be observed that any transfer function can be written as the ratio of two polynomials, and can therefore be factored into a set of terms similar to (4.42). In some cases it will be necessary to solve cubic and higher order equations, but this can easily be done, graphically if necessary.

Recalling our complex variable theory from Chapter I, we note

that (4.42) has one zero, and two poles. These are shown in Fig. 4.5. Except for the constant multiplier, the pole-zero diagram completely describes the transfer function. It will be obvious that two identical networks will have exactly the same pole-zero diagram, while two identical pole-zero diagrams may or may not represent the same network. This last statement will be demonstrated later.

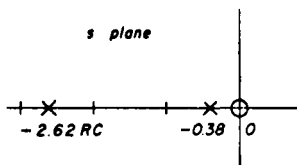


Fig. 4.5

If the transfer function $Z(s)$ is known, the response to any given stimulus can be written as

$$E_0(s) = Z(s)E_{IN}(s) \quad (4.43)$$

E_{IN} can be any signal; direct current, sine wave, pulses, etc. However, it can usually be written as a function of s . Observe that the pole-zero diagram of this product will have the same poles and zeros in the same locations as the transfer function alone, with various additional poles or zeros from $E_{IN}(s)$.

It should be apparent by now that one will often need to take inverse Laplace transforms of the form of (4.42) and (4.43). Thus it will be well if we concentrate for a while on taking the inverse of various abstract functions to become familiar with the technique.

After learning how to evaluate such terms with ease, we shall have a lot of interesting things to say about networks like Fig. 4.4, and others that are much more complex.

4.3. Functions of s involving simple poles

In many cases it will be found that the solution to a given problem in the s -domain results in an expression which is the product of several poles and zeros. In fact, this is the rule rather than the exception. The poles may be located at general points a and b , so that a general function of s having two poles is

$$F(s) = \frac{1}{(s + a)(s + b)} \quad (4.44)$$

Equation (4.42) had a zero of s in the numerator, as well as a constant multiplier. We will examine such cases shortly, but first we will begin with (4.44), which is made up of two factors only. The basic definition of the inverse Laplace transform is

$$f(t) = \frac{1}{2\pi j} \oint F(s) \varepsilon^{ts} ds \quad (4.45)$$

Placing (4.44), the function we wish to transform, into this definition gives

$$f(t) = \frac{1}{2\pi j} \oint \frac{\varepsilon^{ts} ds}{(s+a)(s+b)} \quad (4.46)$$

It is now necessary to recall (or review art. 1.15) that the integral of a function of s with respect to s is merely $2\pi j$ times the summation of the residues at the various poles of the function. It will be assumed from here on that we intend to integrate around all the poles. We note that the factor ε^{ts} in (4.46) is part of the function being integrated. We can call this entire quantity $G(s)$, to distinguish it from $F(s)$ alone. Thus we have

$$f(t) = \frac{1}{2\pi j} \oint G(s) ds \quad (4.47)$$

where

$$G(s) = F(s) \varepsilon^{ts} \quad (4.48)$$

In evaluating the residues of this integral, we find the residues at each of the two poles.

It will be recalled that within the confines of a very small circle about a pole, the function may be represented precisely by the product of the residue and the one factor which creates the pole. As an example, if K_a is the residue at the pole $s = -a$, then

$$G(s) = K_a \cdot \frac{1}{(s+a)} \quad (4.49)$$

or, as we wish to solve for the residue

$$K_a = (s+a)G(s) \quad (4.50)$$

Now note carefully that the $G(s)$ has a factor $(s+a)$, and that both terms cancel. This leads to the expression "removing a pole". We

may indicate the value of the residue then, by evaluating (4.50) at $s = -a$.

$$K_a = (s + a)G(s)|_{s=-a} \tag{4.51}$$

Since

$$G(s) = \frac{e^{ts}}{(s + a)(s + b)} \tag{4.52}$$

$$K_a = \frac{e^{ts}}{(s + b)} \Big|_{s=-a} \tag{4.53}$$

or finally,

$$K_a = \frac{e^{-at}}{b - a} \tag{4.54}$$

In (4.53) we observe the removal of the pole at $s = -a$.

The residue K_b at pole $s = -b$ is found in the same manner, by removing this pole and evaluating the remainder of the function at $s = -b$. Therefore

$$K_b = \frac{e^{ts}}{(s + a)} \Big|_{s=-b} \tag{4.55}$$

or

$$K_b = \frac{e^{-bt}}{a - b} \tag{4.56}$$

The total integral of $G(s)$ thus becomes

$$\oint G(s) ds = 2\pi j[K_a + K_b] \tag{4.57}$$

We recall, however, that there was a $1/2\pi j$ constant multiplier in the definition of the inverse Laplace transform, and therefore the $2\pi j$ terms cancel, so that

$$f(t) = K_a + K_b \tag{4.58}$$

Inserting the actual values of K_a and K_b , and simplifying, we have

$$f(t) = \frac{e^{-bt} - e^{-at}}{a - b} \tag{4.59}$$

This article may tend to be confusing, but several examples will serve to clarify the idea.

EXAMPLE 1. Given

$$F(s) = \frac{1}{s + 2} \tag{4.60}$$

find $f(t)$.

SOLUTION. There is only one pole, at $s = -2$, we therefore have only one residue. Set up $G(s)$, where

$$G(s) = \frac{e^{ts}}{s + 2} \quad (4.61)$$

Remove the factor causing the pole, and evaluate at the pole.

$$K = e^{ts} \Big|_{s=-2} \quad (4.62)$$

and finally,

$$f(t) = e^{-2t} \quad (4.63)$$

EXAMPLE 2. Given

$$F(s) = \frac{s}{s + 4} \quad (4.64)$$

find $f(t)$.

SOLUTION. Set up $G(s)$, where

$$G(s) = \frac{s e^{ts}}{s + 4} \quad (4.65)$$

Again, there is one pole and therefore one residue. We remove the pole and evaluate

$$K = s e^{ts} \Big|_{s=-4} \quad (4.66)$$

which gives

$$K = -4e^{-4t} \quad (4.67)$$

which is the function of time.

EXAMPLE 3. Given

$$F(s) = \frac{s + 6}{s - 3} \quad (4.68)$$

find $f(t)$.

SOLUTION. Set up the function $G(s)$, where

$$G(s) = \frac{(s + 6)e^{ts}}{(s - 3)} \quad (4.69)$$

Solve for the one residue by removing the factor that creates the pole, and evaluating the remainder at $s = 3$.

$$K = (s + 6)e^{ts} \Big|_{s=3} \quad (4.70)$$

which, when evaluated, becomes $f(t)$

$$f(t) = (3 + 6)e^{3t} = 9e^{3t} \quad (4.71)$$

Summary of article: To use the definition of the inverse transform:

- (a) Multiply the $F(s)$ by ε^{ts} . Call this product $G(s)$.
- (b) Integrate around all the poles of $G(s)$ by finding the residue at each pole, and adding.
- (c) The integral is the sum of residues times $2\pi j$.
- (d) The $1/2\pi j$ multiplier in the definition cancels the $2\pi j$ arising from the integration, so that:
- (e) The $f(t)$ is the summation of residues of $G(s)$.

The writer would mention at this point that he is departing radically from the methods used by most texts to evaluate inverse Laplace transforms. The usual approach is to break down functions that have several poles into a sum of partial fractions. Each fraction is then of a simple nature and the inverse is determined by inspection. Many books do not even mention the inverse Laplace integral.

The writer feels that the amount of work is about the same in either method, and feels also that once the reader grows accustomed to using the inverse integral, he will have no difficulty remembering the process. Chapter I provides a general discussion of line or circular integrals.

As a last comment, the writer wants each reader to become proficient in handling certain transcendental functions of s , rather than only algebraic functions. Such transcendental expressions arise often when other than direct current or sine wave input voltages are applied. Such transcendental functions cannot be expressed in partial fractions, yet the inverse Laplace integral is adequate for these types as well as the simple algebraic forms.

4.4. Functions of s involving both simple poles and zeros

In order to consolidate our understanding of the procedure in the previous article, let us examine a general algebraic function of s . General functions of s will arise when networks are analyzed, and will also be used to specify the properties of networks to be synthesized. At any rate, we usually find ourselves confronted with a ratio of polynomials in s , of the form

$$F(s) = \frac{a_0 s^n + a_1 s^{n-1} + a_2 s^{n-2} + \dots + a_n s^0}{b_0 s^{n+1} + b_1 s^n + b_2 s^{n-1} + \dots + b_{n+1} s^0} \quad (4.72)$$

It is necessary to point out that some of the a and b coefficients may be complex as well as real; however, this will not usually cause difficulties.

Now our work at this point will depend upon what we want to do with the function of s that is given. If $F(s)$ represents an impedance, or perhaps a transfer function, we probably will want to keep it in the given form, but if $F(s)$ as given represents the output voltage of a network as a function of s , it will be necessary to dissect the numerator and denominator into their individual factors. The roots of the numerator and denominator may be found by analytical techniques, or by graphical methods, and (4.72) may be rewritten in factored form as

$$F(s) = \frac{(s - \alpha_1)(s - \alpha_2)(s - \alpha_3) \cdots (s - \alpha_n)}{(s - \beta_1)(s - \beta_2)(s - \beta_3) \cdots (s - \beta_n)} \quad (4.73)$$

Once the function is in this factored form, the pole-zero diagram may be drawn by inspection.

Actually, since poles of the $F(s)$ are caused strictly by the factors in the denominator, it would not be necessary to factor the numerator. The only reason for doing so here is to bring out the point that if two factors, one in the numerator and one in the denominator, are equal, then they can be canceled at once and the function simplified.

We know that there will be one residue for every pole which remains, and for simple poles this residue can be found by removing the factor which causes the pole, and evaluating the remainder of the function at the value of s where the pole occurs. Regardless of the number of poles then, we can state that in general, the n th residue K_n is

$$K_n = [(s - \beta_n)F(s)]|_{s=\beta_n} \quad (4.74)$$

It is pointed out again that this residue is a constant, which, when multiplied by the one factor which caused the pole, gives a perfect representation of $F(s)$ within a very small circle centered on the residue point.

The kernel, e^{st} , which occurs in the defining inverse Laplace integral, will always appear in the numerator of functions for which we want to find residues, thus it will not affect our factoring of the usual algebraic denominators. Denominators which involve exponential functions of s will be considered in the next article.

EXAMPLE. Suppose we are given the function

$$F(s) = \frac{(s - 3)\epsilon^{4t}}{s^3 + 2s^2 + s + 2}$$

As a first step, it is necessary to solve the denominator to locate the poles of the function. The solution of the cubic can be had by formula or graphing the function. It will be found that the factors are

$$F(s) = \frac{(s - 3)\epsilon^{4t}}{(s + 2)(s - j)(s + j)}$$

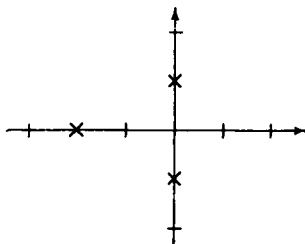


Fig. 4.6

The poles are shown in Fig. 4.6. At each pole there will be a residue. These are now found.

$$K_1 \Big|_{s=-2} = \frac{-5\epsilon^{-2t}}{(-2 - j)(-2 + j)} = -\epsilon^{-2t}$$

$$K_2 \Big|_{s=j} = \frac{(-3 + j)\epsilon^{jt}}{(2 + j)(2j)}$$

$$K_3 \Big|_{s=-j} = \frac{(-3 - j)\epsilon^{-jt}}{(2 - j)(-2j)}$$

The reader can show as an exercise that the sum of the three residues is

$$K_1 + K_2 + K_3 = \cos t - \sin t - \epsilon^{-2t}$$

This would be the time response corresponding to the original function of s .

4.5. Functions of s having higher order poles

It will often happen that we are required to find the function of time from a function of s of the form

$$F(s) = \frac{(s + a)}{s(s + b)^n} \quad (4.75)$$

where n is an integer greater than 1. Such multiple poles can be indicated on the pole-zero diagram as a six-arm cross, as in Fig. 4.7.

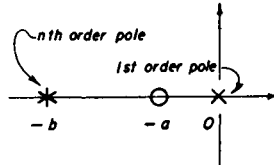


Fig. 4.7

In the chapters on “theorems” we will find easy ways of evaluating the time responses of such functions, but here it is desirable to develop a general formula for the residues. Equation (4.75) can be expanded in partial fractions as:

$$F(s) = \frac{B}{s} + \frac{A_1}{(s + b)} + \frac{A_2}{(s + b)^2} + \cdots + \frac{A_k}{(s + b)^k} + \cdots + \frac{A_n}{(s + b)^n} \quad (4.76)$$

Note that $k < n$. We can easily evaluate B as

$$B = sF(s) \Big|_{s=0} = \frac{s + a}{(s + b)^n} \Big|_{s=0} = \frac{a}{b^n} \quad (4.77)$$

Now let us multiply (4.76) by $(s + b)^n$,

$$(s + b)^n F(s) = \frac{B(s + b)^n}{s} + A_1(s + b)^{n-1} + A_2(s + b)^{n-2} + \cdots + A_k(s + b)^{n-k} + \cdots + A_n \quad (4.78)$$

We see that A_n can be determined by evaluating

$$(s + b)^n F(s) \Big|_{s=-b} = A_n \quad (4.79)$$

and that the general term A_k can be found by differentiating both sides of (4.78) successively $(n - k)$ times, until A_k stands alone.

$$\frac{d^{n-k}[(s + b)^n F(s)]}{ds^{n-k}} = \underline{n - k} A_k \quad (4.80)$$

From which we write a general formula

$$A_k = \frac{1}{(n-k)!} \cdot \left. \frac{d^{n-k}[(s+b)^n F(s)]}{ds^{n-k}} \right|_{s=-b} \quad (4.81)$$

where k is the number of the particular term, and n is the highest exponent in $F(s)$.

EXAMPLE 1. Suppose we are given

$$F(s) = \frac{1}{s(s+2)^2} \quad (4.82)$$

From (4.76) we write

$$F(s) = \frac{B}{s} + \frac{A_1}{s+2} + \frac{A_2}{(s+2)^2} \quad (4.83)$$

Here $n = 2$, and by (4.77)

$$B = sF(s)|_{s=0} = \frac{1}{4} \quad (4.84)$$

Now by (4.81), since $k = 1$,

$$A_1 = \frac{1}{(2-1)!} \left. \frac{d^{2-1} \left[\frac{1}{s} \right]}{ds^{2-1}} \right|_{s=-2} \quad (4.85)$$

$$A_1 = \left. \frac{d \frac{1}{s}}{ds} \right|_{s=-2} = \left[-\frac{1}{s^2} \right]_{-2} = -\frac{1}{4} \quad (4.86)$$

and for the $k = 2$ term

$$A_2 = \frac{1}{(2-2)!} \left. \frac{d^{2-2} \left[\frac{1}{s} \right]}{ds^{2-2}} \right|_{s=-2} = \left[\frac{1}{s} \right]_{-2} = -\frac{1}{2} \quad (4.87)$$

so that

$$F(s) = \frac{\frac{1}{4}}{s} - \frac{\frac{1}{4}}{(s-2)} - \frac{\frac{1}{2}}{(s-2)^2} \quad (4.88)$$

We will finish taking the inverse of $F(s)$ shortly, but first, let us look at another example.

EXAMPLE 2. We are given that

$$F(s) = \frac{s+1}{s(s+2)^2} \quad (4.89)$$

We write

$$F(s) = \frac{B}{s} + \frac{A_1}{s+2} + \frac{A_2}{(s+2)^2} + \frac{A_3}{(s+2)^3} \quad (4.90)$$

Here $n = 3$. First

$$B = sF(s)|_{s=0} = \frac{1}{2} \quad (4.91)$$

Then by using (4.81) with $k = 3$

$$A_3 = \frac{1}{\sqrt[3]{3-3}} \cdot \frac{d^{3-3}}{ds^{3-3}} \left[\frac{s+1}{s} \right] \Big|_{s=-2} = \frac{1}{2} \quad (4.92)$$

(It is easiest to do A_3 first, because this order, A_3, A_2, A_1 , requires differentiation in normal order.) Where $k = 2$, then

$$A_2 = \frac{1}{\sqrt[3]{3-2}} \cdot \frac{d^{3-2}}{ds^{3-2}} \left[\frac{s+1}{s} \right] \Big|_{s=-2} = -\frac{1}{4} \quad (4.93)$$

And finally, for $k = 1$,

$$A_1 = \frac{1}{\sqrt[3]{3-1}} \cdot \frac{d^{3-1}}{ds^{3-1}} \left[\frac{s+1}{s} \right] \Big|_{s=-2} = -\frac{1}{8} \quad (4.94)$$

So the sum of the partial fractions is,

$$F(s) = \frac{\frac{1}{2}}{s} - \frac{\frac{1}{8}}{(s+2)} - \frac{\frac{1}{4}}{(s+2)^2} + \frac{\frac{1}{2}}{(s+2)^3} \quad (4.95)$$

This may be double-checked by multiplying out to see that the original $F(s)$ is obtained. Again, we will find the $f(t)$ shortly. The main purpose here is to develop facility with higher order poles.

The foregoing discussion of the inverse Laplace transform is complete enough to allow you to determine the function of time for any $F(s)$ whose denominator is algebraic. For cases where the denominator is not algebraic, it is necessary to have additional methods available. Such additional methods usually involve the application of a number of theorems.

The "theorems" are of such importance in practical evaluation of functions of s that a rather long chapter will now follow on this subject. Rigorous proofs will not be given in all cases, but the proof offered will be adequate to allow the reader to accept the theorem for use.

After finishing the chapter on theorems, we will be ready to begin some actual circuit analysis studies.

CHAPTER V

LAPLACE TRANSFORM THEOREMS

5.1. Introduction

In this chapter we will study most of the important theorems of Laplace transforms. These theorems are rather simple, but it takes a fair amount of practice to use them in practical ways. A good working knowledge of the theorems is what takes the drudgery out of operations with Laplace transforms. Most of the theorems will relate operations in one plane to operations in the other plane.

In addition to their immediate value for taking inverse transforms, the theorems play a vital part in the development and extension of collected tables of Laplace transforms. The extensive tables in the back of this book have been developed from a few basic forms and repeated application of many theorems.

Each theorem has been given a definite name, and we will try to use the same names here as are common in the literature. Usually the names are descriptive of the operation involved, which makes them easy to remember.

5.2. Linear s -plane translation

We will begin our work with theorems by the study of shifting in the complex plane. This theorem, sometimes referred to as the "complex translation" theorem, tells us that if

$$F(s) = \mathcal{L}[f(t)] \quad (5.1)$$

then

$$F(s + a) = \mathcal{L}[e^{-at}f(t)] \quad (5.2)$$

This theorem says then, that if we have some function of time which has a transformed function of s , and if we should multiply the original $f(t)$ by an exponential decay factor e^{-at} , then the Laplace transform of the new time function could be found by merely shifting every point in the s -plane to the left by an amount a . A few examples will serve to clarify this concept.

EXAMPLE 1. Suppose we have a function of time

$$f(t) = \cos \omega t \quad (5.3)$$

which we know from previous work has a transform

$$F(s) = \frac{s}{s^2 + \omega^2} \quad (5.4)$$

Poles and zeros will be present at $\pm j\omega$, and 0, as shown in Fig. 5.1.

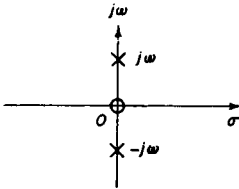


Fig. 5.1

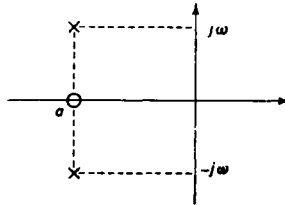


Fig. 5.2

If now we should multiply (5.3) by an exponential factor so that a new $f(t)$ is

$$f(t) = e^{-at} \cos \omega t \quad (5.5)$$

then the shifting theorem says that we would replace each s in (5.4) by the factor $(s + a)$, to have the transform of (5.5), or

$$F(s) = \frac{s + a}{(s + a)^2 + \omega^2} \quad (5.6)$$

The poles of this function, as well as the zero, will be shifted a units to the left, as shown in Fig. 5.2.

Since the location of the poles and zeros in the s -plane completely determines the function, we say in general that multiplying a function of time by e^{-at} goes over into the s -plane as a shift of all points in the s -plane a units to the left. If we should multiply the time function by e^{at} , we would then shift points in the s -plane in the opposite direction.

To prove the shifting theorem, let us use the definition of the Laplace transform to say that

$$\mathcal{L}[e^{-at}f(t)] = \int_0^{\infty} [f(t)e^{-at}]e^{-st} dt \quad (5.7)$$

$$= \int_0^{\infty} f(t)e^{-(s+a)t} dt \quad (5.8)$$

We can define

$$s + a = s_1 \quad (5.9)$$

so that

$$\mathcal{L}[\varepsilon^{-at}f(t)] = F(s_1) \quad (5.10)$$

or in other words

$$\mathcal{L}[\varepsilon^{-at}f(t)] = F(s + a) \quad (5.11)$$

EXAMPLE 2. Given

$$f(t) = \varepsilon^{-bt} \quad (5.12)$$

find the Laplace transform of $f(t)\varepsilon^{-at}$.

The Laplace transform of $f(t)$ alone is

$$\mathcal{L}[f(t)] = \frac{1}{s + b} \quad (5.13)$$

The shifting theorem says that we should merely shift all points in the s -plane a units to the left, or

$$\mathcal{L}[f(t)\varepsilon^{-at}] = \frac{1}{(s + a) + b} \quad (5.14)$$

This is easily shown to be true, because if we combine the two time functions before taking the Laplace transform, we have

$$\mathcal{L}[\varepsilon^{-(b+a)t}] = \frac{1}{s + (b + a)} \quad (5.15)$$

the same result as (5.14).

PROBLEMS

(a) Find the Laplace transforms of

$$(1) \quad f(t) = \varepsilon^{-at} \cos \omega t$$

$$(2) \quad f(t) = t\varepsilon^{-at}$$

$$\text{ANS. } \frac{1}{(s + a)^2}$$

$$(3) \quad f(t) = \int_0^t \varepsilon^t \cosh \omega t$$

$$(4) \quad f(t) = \int_0^t \varepsilon^{2t} U(t)$$

$$\text{ANS. } \frac{1}{s - 3}$$

(b) Find the inverse Laplace transforms of the following by applying the shifting theorem, and then recognizing the result.

$$(1) \quad F(s) = \frac{1}{s - 4}$$

Shift the points in the s -plane 4 units to the left, so that

$$F_1(s) = \frac{1}{s}$$

The function of time is therefore

$$f_1(t) = U(t)$$

and we can find the actual $f(t)$ by inserting the exponential factor

$$f(t) = e^{at}f_1(t) = e^{4t}$$

$$(2) \quad F(s) = \frac{1}{(s + \alpha)^2}$$

$$(3) \quad F(s) = \frac{s - 6}{(s - 6)^2 + 16}$$

$$(4) \quad F(s) = \frac{2}{(s - 1)^2 - 4}$$

ANS. $e^t \sinh 2t$.

This, and the following theorems to be developed in this chapter, will be numbered and collected into a table at the end of the book.

5.3. Final value theorem

In work with electronic circuits and networks (see Fig. 4.1), the transfer functions are often of such a nature that the output goes through certain variations, and finally approaches and settles down at some final, definite value. Final values of both current and voltage are often of interest, as in the example shown in Fig. 5.3. The transformed circuit diagram is (see art. 4.2) shown in Fig. 5.4. The equation for this simple one-loop network is seen by inspection to be

$$I(s) = \frac{E(s)}{sL + R} \quad (5.16)$$

Now under certain conditions $I(s)$ will have a final definite value, and under other conditions there will never be such a final value. For example, if the input voltage is a sine wave, then the current will never settle down to a steady value, but will continue indefinitely to oscillate between fixed limits as a sine wave of current. If $E(s)$ is a d.c. voltage, or step function, however, it is just as easy to see that the current does settle down to a definite final value (5.17).

$$i(t) = \frac{E}{R} \quad (5.17)$$

Having attempted to illustrate the meaning of the term "final value" as used in this article, we now proceed to state and prove the

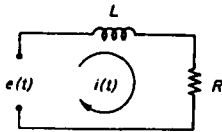


Fig. 5.3

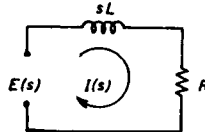


Fig. 5.4

theorem. The final value theorem is stated as an equality of limits, which is written as

$$\lim_{s \rightarrow 0} sF(s) = \lim_{t \rightarrow \infty} f(t) \quad (5.18)$$

There are two limitations to be recognized immediately. First, we saw earlier that when $F(s)$ is multiplied by s , this represents a differentiation. Therefore both $f(t)$ and its first derivative must be Laplace transformable. Secondly, as we saw intuitively in the example of Fig. 5.3, there must actually be a final value. This last limitation states that the expression $sF(s)$ does not have poles on the $j\omega$ axis, or in the right-hand plane.

To prove the theorem, let us write the expression for the Laplace transform of a derivative, which is

$$\int_0^{\infty} f'(t)e^{-st} dt = sF(s) - f(0) \quad (5.19)$$

Now observe that the parameter s is not a function of time, thus we can allow s to approach (0) before performing the integration if we wish. Thus considering only the left-hand side of (5.19) at first:

$$\lim_{s \rightarrow 0} \int_0^{\infty} f'(t)e^{-st} dt = \int_0^{\infty} f'(t) dt = \lim_{t \rightarrow \infty} \int_0^t f'(t) dt \quad (5.20)$$

and the last integral in (5.20) becomes

$$\lim_{t \rightarrow \infty} \int_0^t f'(t) dt = \lim_{t \rightarrow \infty} [f(t) - f(0)] \quad (5.21)$$

Since we have let $s \rightarrow 0$ for the left-hand side of (5.19), we must take the same limit on the right-hand side of (5.19), and combining this with the final result of (5.21),

$$\lim_{s \rightarrow 0} [sF(s) - f(0)] = \lim_{t \rightarrow \infty} [f(t) - f(0)] \quad (5.22)$$

As the $f(0)$ is neither a function of s nor of t , it may be canceled from both sides, leaving

$$\lim_{s \rightarrow 0} sF(s) = \lim_{t \rightarrow \infty} f(t) \quad (5.23)$$

and the theorem is proved.

Let us now apply this theorem to the function $I(s)$ of our example in (5.16). We choose $E(s)$ to be a step function of magnitude E , so that

$$I(s) = \frac{E}{s(L + R)} \quad (5.24)$$

The final value theorem requires that this function first be multiplied by s , to become

$$sI(s) = \frac{E}{sL + R} \quad (5.25)$$

whereupon the limit becomes

$$\lim_{s \rightarrow 0} sI(s) = \frac{E}{R} \quad (5.26)$$

which is simple enough to be apparent by inspection. Note that (5.24) has poles at $s = 0$, and $s = -R/L$. For other applied voltage functions, $I(s)$ could easily have poles on the $j\omega$ axis and thus make the theorem inapplicable.

Before going on to the next theorem, let us examine (5.24) in a slightly different way. Multiply out the denominator on the right-hand side, to get

$$I(s) = \frac{E}{s^2L + Rs} \quad (5.27)$$

Now if we let s become very small, the s^2 term will become insignificant compared with the first power s term, so that

$$I(s) = \frac{E}{R} \cdot \frac{1}{s} \quad (5.28)$$

and we recognize $1/s$ as being the transform of the unit step function $U(t)$, so that

$$i(t) = \frac{E}{R} \quad (5.29)$$

this result, as before, being obtained by letting s approach zero.

PROBLEMS

(1) Find the final value of the output voltage in Fig. 5.5. Assume that the input is a unit step function.

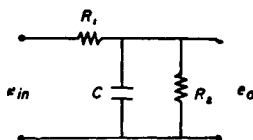


Fig. 5.5

(2) Assuming once more a unit step function, applied from a zero impedance source, state whether or not the final value theorem can be applied to find $e_o(t)$ in Fig. 5.6.

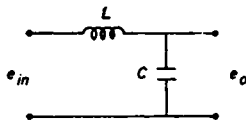


Fig. 5.6

5.4. Initial value theorem

Assume again as in the last article that both $f(t)$ and its derivative $f'(t)$ are Laplace transformable, and that the limit of the derivative of $F(s)$ exists as s approaches infinity. If these conditions hold, then the initial value theorem states that

$$\lim_{s \rightarrow \infty} sF(s) = \lim_{t \rightarrow 0} f(t) \quad (5.30)$$

Thus the theorem says that the rate of change of $F(s)$ near infinity in the s -plane corresponds to the behavior of $f(t)$ near $t = 0$ in the

time domain. The proof of the initial value theorem is straightforward, and proceeds as follows:

We have already derived the Laplace transform of a derivative which is

$$\int_0^{\infty} f'(t)\varepsilon^{-st} dt = sF(s) - f(0) \quad (5.31)$$

Now again, since s is a parametric variable and is not a function of time, we can allow s to approach infinity prior to the indicated integration.

$$\lim_{s \rightarrow \infty} \int_0^{\infty} f'(t)\varepsilon^{-st} dt = \lim_{s \rightarrow \infty} [sF(s) - f(0)] \quad (5.32)$$

Note that if $s \rightarrow \infty$, the exponential term becomes zero, making the entire left-hand side zero. Therefore

$$\lim_{s \rightarrow \infty} [sF(s) - f(0)] = 0 \quad (5.33)$$

As a final step, we note that

$$f(0) = \lim_{t \rightarrow 0} f(t) \quad (5.34)$$

and thus (5.33) becomes

$$\lim_{s \rightarrow \infty} sF(s) = \lim_{t \rightarrow 0} f(t) \quad (5.35)$$

whereupon the theorem is proved. Note carefully that this theorem is more general than the final value theorem as discussed in art. 5.3.

EXAMPLE. Consider Fig. 5.7.

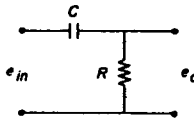


Fig. 5.7

If we let e_{IN} be $U(t)$, a unit step function, then the output as a function of s will be

$$E_0(s) = \frac{RC}{RCs + 1} \quad (5.36)$$

and it is required to find the initial value of $e_0(t)$ at the moment that

the step voltage is applied to the input. Equation (5.36) is multiplied by s as the theorem requires:

$$sE_0(s) = \frac{sRC}{RCs + 1} = \frac{RC}{RC + 1/s} \quad (5.37)$$

and taking the limit

$$e_0(0) = \lim_{s \rightarrow \infty} sE_0(s) = 1 \text{ volt} \quad (5.38)$$

which is the unit step voltage which was applied.

PROBLEM. It should have been discovered by now that the final value theorem did not apply in the case of problem 2 of the last article. Using the same Fig. 5.6, first find the output voltage as a function of s ; then, using the initial value theorem, find the initial value of $e_0(0)$ at the instant the step function is applied. Note that the $E_0(s)$ has conjugate poles on the $j\omega$ -axis. The final value theorem cannot be used in such cases, although the initial value theorem has no such limitations.

5.5. Real translation

In real translation, a curve which represents a function of time is shifted to a new position along the time axis, without otherwise

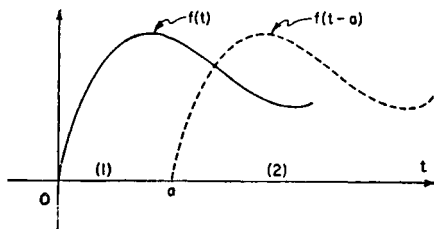


Fig. 5.8

changing the shape or characteristics of the function. For example, in Fig. 5.8. the function $f(t)$ which normally begins at $t = 0$ has been shifted intact by an amount a , whereupon it now becomes $f(t - a)$.

Now if the function $f(t)$ is not given as a curve, but is presented in tabular form, one could of course plot the curve from the given data. The position of such a curve would thus depend on the accuracy of the clock which was used to determine t .

Suppose for example that a function is measured by two independent observers, each having his own clock which he considers

correct. But suppose that in reality clock (1) is correct, and that clock (2) is a sec too fast. Observer (1) will tabulate the beginning of the function at $t = 0$ sec, and observer (2) will state that the function begins at $t = a$ sec. Let us now say that t represents the correct clock, while τ represents the clock which is a sec fast. That is,

$$\tau = t - a \quad (5.39)$$

from which

$$d\tau = dt \quad (5.40)$$

Equation (5.40) indicates that each clock is running at the same rate, but that the clock keeping τ time is merely offset a sec from the clock which is keeping t time. The curve on the right in Fig. 5.8 can thus be labelled as $f(\tau)$.

Observer (2) will write the Laplace transform of his function in τ rather than t time, and his expression would be

$$F(s) = \int_0^{\infty} f(\tau) e^{-s\tau} d\tau \quad (5.41)$$

However, because we know that his clock is in error by the amount a , we would correct his equation to read

$$F(s) = \int_a^{\infty} f(t - a) e^{-s(t-a)} dt \quad (5.42)$$

Note that we have changed his lower limit from 0 to a , since from (5.39) when $\tau = 0$, $t = a$. Also if $f(t - a)$ is 0 from $t = 0$ to $t = a$, as shown in Fig. 5.8, we are permitted to make the lower limit of (5.42) equal 0, thus

$$F(s) = \int_0^{\infty} f(t - a) e^{as} e^{-st} dt \quad (5.43)$$

Notice also that as the exponential e^{as} is not a function of time, it may be carried through the integral sign and to the other side as a negative exponent, the expression becoming

$$e^{-as} F(s) = \int_0^{\infty} f(t - a) e^{-st} dt \quad (5.44)$$

Having derived (5.44), we are now in a position to state the real translation theorem, which says that

$$\mathcal{L}[f(t - a)] = e^{-as} F(s) \quad (5.45)$$

The theorem thus states generally that translation in the time domain goes over into multiplication by an exponential in the

s -domain. Note that the a is considered to be a non-negative real number.

EXAMPLE 1. To illustrate, let us take as a simple example the case where $f(t) = U(t)$, the step function. We now translate this curve

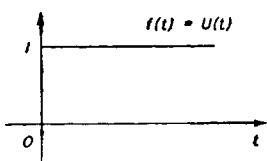


Fig. 5.9

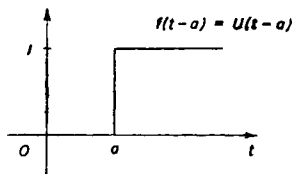


Fig. 5.10

a units to the right, to have Fig. 5.10. By the use of theorem (5.45) we write immediately

$$\mathcal{L}[f(t-a)] = \varepsilon^{-as}F(s) = \varepsilon^{-as} \cdot \frac{1}{s} \quad (5.46)$$

This can be checked by direct integration of $U(t-a)$.

$$\mathcal{L}[U(t-a)] = \int_0^{\infty} U(t-a)\varepsilon^{-st} dt \quad (5.47)$$

$$= \int_0^a (0)\varepsilon^{-st} dt + \int_a^{\infty} (1)\varepsilon^{-st} dt \quad (5.48)$$

or

$$\mathcal{L}[U(t-a)] = \frac{\varepsilon^{-as}}{s} \quad (5.49)$$

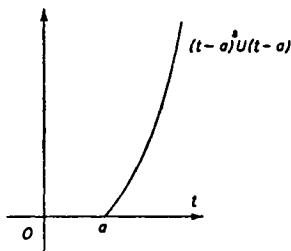


Fig. 5.11

EXAMPLE 2. Consider Fig. 5.11. By the real translation theorem,

$$F(s) = \varepsilon^{-as}\mathcal{L}[t^2U(t)] \quad (5.50)$$

or, from the tables

$$F(s) = \frac{6\varepsilon^{-as}}{s^4} \quad (5.51)$$

PROBLEM. Consider the time sampled step function shown in Fig. 5.12. Show that the transform is

$$F(s) = \frac{1}{s(1 + e^{-s})} \quad (5.52)$$

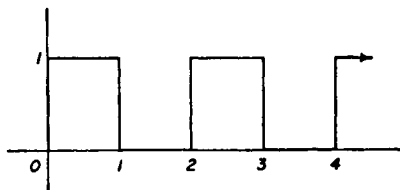


Fig. 5.12

HINT. Write the time function as a sum of displaced step functions, i.e.

$$f(t) = U(t) - U(t - 1) + U(t - 2) - U(t - 3) \cdots \quad (5.53)$$

and apply the theorem to each term, then simplify.

5.6. Complex differentiation

This theorem has limited usefulness in electronic circuit analysis, but is easy to prove and is quite valuable when used to extend a table of Laplace transforms. The mechanics of this theorem are compatible with those of the real differentiation, and also with real and complex integration theorems. The electronics engineer who eventually specializes in antennas, filter theory, network synthesis, and other branches of the art where s -plane operation is common will eventually find much use for this theorem.

In simple terms, the complex differentiation theorem states that if $F(s)$ is the Laplace transform of a function $f(t)$, then the derivative of $F(s)$ corresponds in the time world to multiplying the function of time by the variable t , as in (5.54)

$$\frac{dF(s)}{ds} = -\mathcal{L}[tf(t)] \quad (5.54)$$

Note that there is a sign change involved.

To prove this theorem, let us write the basic equation of the Laplace transform, which is:

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt \quad (5.55)$$

and differentiate with respect to s ,

$$\frac{dF(s)}{ds} = \frac{d}{ds} \int_0^{\infty} f(t) e^{-st} dt \quad (5.56)$$

Now we can rearrange the right-hand side of (5.56) somewhat, because s and t are not functions of each other.

$$\frac{dF(s)}{ds} = \int_0^{\infty} f(t) dt \frac{d e^{-ts}}{ds} \quad (5.57)$$

$$= \int_0^{\infty} f(t) dt (-t) e^{-ts} \quad (5.58)$$

$$= \int_0^{\infty} -t f(t) e^{-st} dt \quad (5.59)$$

and finally,

$$\frac{dF(s)}{ds} = -\mathcal{L}[t f(t)] \quad (5.60)$$

which proves the theorem.

EXAMPLES

(1) Consider the pair of functions

$$F(s) = \frac{1}{s}; \quad f(t) = U(t) = 1$$

Applying the complex differentiation theorem,

$$\frac{dF(s)}{ds} = -\frac{1}{s^2}; \quad -t f(t) = -t$$

we find that

$$\frac{1}{s^2} = \mathcal{L}(t) \quad (5.61)$$

The new function of s in (5.61) can be differentiated again,

$$\frac{d}{ds} \frac{1}{s^2} = -\frac{2}{s^3} \quad (5.62)$$

or

$$\frac{2}{s^3} = \mathcal{L}(t^2) \quad (5.63)$$

and we see that this process could go on indefinitely, leading us to a general form for powers of the original step function transform.

(2) Consider the pair

$$F(s) = \frac{s}{s^2 + a^2}; \quad f(t) = \cos at$$

Applying the theorem

$$\frac{dF(s)}{ds} = \frac{a^2 - s^2}{(s^2 + a^2)^2}; \quad -tf(t) = -t \cos at$$

we have the new pair

$$\mathcal{L}(-t \cos at) = \frac{a^2 - s^2}{(s^2 + a^2)^2} \quad (5.64)$$

Note in passing that the derived function of s has higher order poles on the imaginary axis.

PROBLEMS

(1) With $f(t) = \sin \omega t$, apply the theorem twice in succession to derive two new functions of s .

(2) With $f(t) = e^{-at}$, derive a new pair of transforms by using the theorem developed in this article.

(3) For an $F(s) = e^{-as}$, apply the complex differentiation theorem to derive a new function of time, and graph the first part of the resulting waveform.

5.7. Complex integration

This theorem, like the complex differentiation theorem developed in art. 5.6, is easy to prove, and serves among other things to extend and check tables of Laplace transforms, in addition to furthering our understanding of operations in the complex plane. Formally, the theorem states that

$$\int_s^\infty F(s) ds = \mathcal{L} \left[\frac{f(t)}{t} \right] \quad (5.65)$$

This is subject to the same conditions that apply throughout this chapter, namely that $f(t)$ is Laplace transformable, and obviously, from the way (5.65) is written, that $f(t)/t$ is also Laplace transformable, and that the left-hand integral exists.

To begin our development of this theorem, we write the original definition of the Laplace transform, which is, as always

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt \quad (5.66)$$

Both sides are now integrated with respect to s , from s to ∞ .

$$\int_s^{\infty} F(s) ds = \int_s^{\infty} \int_0^{\infty} f(t)e^{-st} dt ds \quad (5.67)$$

It is permissible to rearrange the double integral as follows:

$$\int_0^{\infty} f(t) \left[\int_s^{\infty} e^{-ts} ds \right] dt = \int_0^{\infty} \frac{f(t)e^{-ts}}{t} dt \quad (5.68)$$

wherein the integral within the brackets has been reduced to e^{-st}/t . Using this result, (5.67) becomes

$$\int_s^{\infty} F(s) ds = \int_0^{\infty} \frac{f(t) e^{-st}}{t} dt \quad (5.69)$$

or, by definition

$$\int_s^{\infty} F(s) ds = \mathcal{L} \left[\frac{f(t)}{t} \right] \quad (5.70)$$

and the proof is complete.

EXAMPLES

(1) Consider the pair of transforms

$$2s^{-3} \rightarrow t^2 \quad (5.71)$$

If the theorem is applied,

$$2 \int_s^{\infty} s^{-3} ds = \frac{2 \cdot s^{-2}}{-2} = \frac{1}{s^2}, \quad \text{and} \quad \frac{t^2}{t} = t \quad (5.72)$$

We have developed the new pair

$$\frac{1}{s^2} \rightarrow t \quad (5.73)$$

which may be checked by using the tables.

(2) Consider the pair

$$\frac{2as}{(s^2 + a^2)^2} \rightarrow t \sin at \quad (5.74)$$

Again applying the theorem

$$2a \int_s^\infty \frac{s ds}{(s^2 + a^2)^2} = \frac{a}{s^2 + a^2}, \quad \text{and} \quad \frac{t \sin at}{t} = \sin at \quad (5.75)$$

Thus we have the new pair

$$\frac{a}{s^2 + a^2} \rightarrow \sin at \quad (5.76)$$

which is a pair we remember from earlier work.

PROBLEMS

(1) Apply the complex integration theorem to (5.64) in the last article, to develop the original pair used in example (2) of that article.

(2) Using the function of time

$$f(t) = e^{j\omega_1 t} - e^{j\omega_2 t} \quad (5.77)$$

show that application of the theorem leads to the new function of s

$$F(s) = \ln \left(\frac{s - j\omega_1}{s - j\omega_2} \right) \quad (5.78)$$

What limitations must be imposed upon ω_1 and ω_2 ?

(3) Considering the basic definition of natural logarithms, (5.78) says that

$$e^{F(s)} = \frac{s - j\omega_1}{s - j\omega_2} \quad (5.79)$$

Is there any meaningful interpretation of this expression?

5.8. Sectioning a function of time

It often happens in electronic work that we wish to examine a function of time which has been "sampled". This sampling can occur in many ways, such as the electronic or mechanical switching in chopper-stabilized amplifiers, in telemetry, or in coded data transmission systems.

It is intended in this article to digress briefly for a short discussion of sectioning a function of time. The ideas presented will be simple, but will perhaps clarify one or two points that will arise in the next theorem which we shall develop.

The Faltung integral, or convolution theorem to be developed in the following article will involve one or two rather tricky limit changes, and it is best to prepare for them in advance, so as to avoid having to interrupt a development which will be somewhat tedious at best.

Let us consider some relatively simple function of time, such as the exponentially decaying wave in Fig. 5.13. Note that this

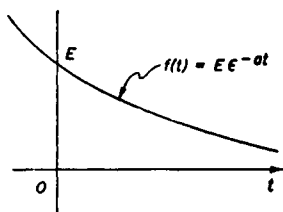


Fig. 5.13

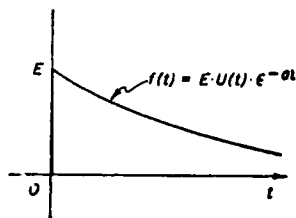


Fig. 5.14

function has values for both positive and negative values of t . If we multiply this function by a unit step function, we "slice off" the entire portion to the left of $t = 0$, to obtain the section shown in Fig. 5.14. Now let us take the original function, Fig. 5.13, and multiply it by a displaced step function, $U(t - b)$.

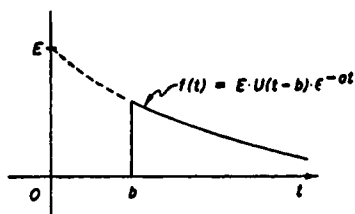


Fig. 5.15

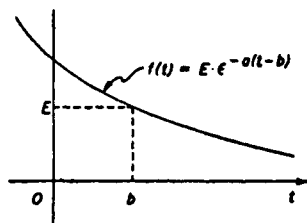


Fig. 5.16

The result is shown in Fig. 5.15. It is seen that part of the original function has been removed, but that the portion remaining has not been altered in any way.

Now let us start again with the function shown in Fig. 5.13. This time we shall first translate the curve to the right by an amount b , letting it become a function of $(t - b)$, as in Fig. 5.16.

After translating, the curve is now sectioned by multiplying by a displaced unit step function which begins at $t = b$. This is shown in Fig. 5.17. Notice the difference between Figs. 5.17 and 5.15.

Let us examine one or two more relations using step functions, and then we shall proceed to the next article. In most of our work in the time domain, we use t as the independent variable. If we choose some constant value of time (τ), we can call τ a parametric variable. We have spoken of parametric variables earlier. As

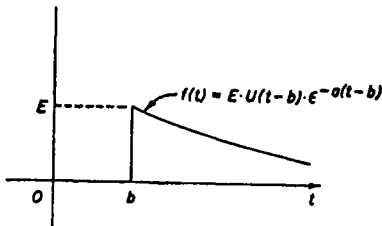


Fig. 5.17

another example, suppose we have current i flowing in an $R-L-C$ circuit. Normally we would consider L to be a constant, but we could find i , change L and find i again, change L and find i once more, etc. (this would result in a frequency response curve), here the L would be the parametric variable, or "selective" variable.

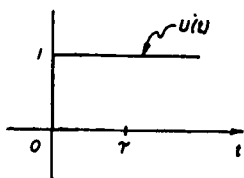


Fig. 5.18

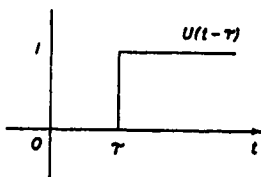


Fig. 5.19

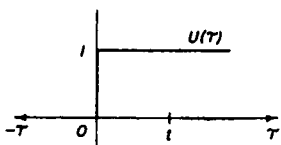


Fig. 5.20

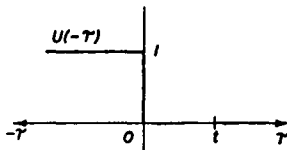


Fig. 5.21

Consider Fig. 5.18. Choose some value $t = \tau$ as a constant, and shift by an amount τ to have Fig. 5.19. Now, however, let us choose τ as the variable, and pick t as a fixed value of τ (see Fig. 5.20). Or, for $U(-\tau)$, we have in Fig. 5.21. We now shift by an amount t to have $U(t - \tau)$, as in Fig. 5.22.

In Fig. 5.22 τ has been replaced by $(t - \tau)$, which has folded the function around the vertical axis, and then translated by an amount t . This folding (Faltung) operation is used in the next section where we treat the Faltung integral.

These relations between t and τ will be used in the next article freely, without stopping then to show their graphical relations or

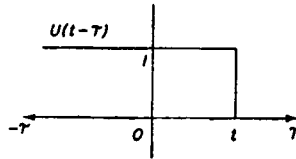


Fig. 5.22

directions. Thus, having prepared these curves for reference, we proceed now to the next theorem.

5.9. The convolution theorem

The theorem to be developed in this article deals with the complex multiplication of functions, and is also referred to as Borel's theorem, or the Faltung integral. This theorem will provide an additional way to take inverse Laplace transforms of functions of s when the $F(s)$ can be separated into factors whose inverse transforms are known. For ordinary algebraic functions of s , the previous methods usually require less work, but the convolution theorem can also be employed for transcendental functions of s , thus expanding our ability to deal with complex waveforms such as are found in modern electronic systems.

The development of this theorem is somewhat more involved than those undertaken previously, so in order not to become confused by excessive details, we shall define certain operations and refer back to art. 5.8. for ideas on sectioning.

To begin, if we multiply two functions of time, and then integrate the product between the limits of 0 and t , we perform a process which we define as convolution. That is

$$f(t) \triangleq \int_0^t f_1(t - \tau) \cdot f_2(\tau) d\tau \quad (5.80)$$

Here τ is the variable of integration, and t is constant while integrating. Do not attempt to see the reason for choosing this particular integral now. Let us merely work with it to see if we can arrive at

any worthwhile result. The Laplace transform of (5.80) can be written as

$$F(s) = \int_0^{\infty} \left[\int_0^t f_1(t - \tau) \cdot f_2(\tau) d\tau \right] \varepsilon^{-st} dt \quad (5.81)$$

The upper limit t can be changed to ∞ if we first multiply the product by $U(t - \tau)$. See Fig. 5.22, as this will make the over-all function zero from t to ∞ anyway. Equation (5.81) then becomes

$$F(s) = \int_0^{\infty} \int_0^{\infty} f_1(t - \tau) \cdot f_2(\tau) \cdot U(t - \tau) d\tau \varepsilon^{-st} dt \quad (5.82)$$

Now at this point, it is felt best to state that the order of integration can be changed, without giving a rigorous proof. Writing (5.82) in slightly different form gives

$$F(s) = \int_0^{\infty} f_2(\tau) \left[\int_0^{\infty} f_1(t - \tau) \cdot U(t - \tau) \cdot \varepsilon^{-st} dt \right] d\tau \quad (5.83)$$

Note that the integral in the bracketed term contains the product $f(t - \tau) U(t - \tau)$, which can be shown in Fig. 5.23.

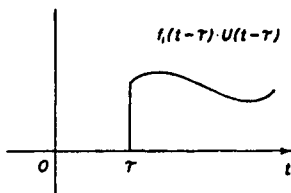


Fig. 5.23

In Fig. 5.23 it is evident that the function is zero from 0 to τ , and thus the lower limit in the bracketed term of (5.83) can be changed from 0 to τ , to give

$$F(s) = \int_0^{\infty} f_2(\tau) \left[\int_{\tau}^{\infty} f_1(t - \tau) \varepsilon^{-st} dt \right] d\tau \quad (5.84)$$

We have dropped the displaced step function term in (5.84), as it is of no importance after we change the lower limit.

If one now recalls the real translation theorem, (5.45) in art. 5.5, the entire bracketed term in (5.84) goes over into the s -plane as

$$\int_{\tau}^{\infty} f_1(t - \tau) \varepsilon^{-st} dt = \varepsilon^{-s\tau} F_1(s) \quad (5.85)$$

(the lower limit can be τ or 0, because we remember that the function is zero to the left of $t = \tau$ anyway).

Placing (5.85) back into (5.84), and bringing $F_1(s)$ outside the integral gives

$$F(s) = F_1(s) \cdot \int_0^{\infty} f_2(\tau) e^{-s\tau} d\tau \quad (5.86)$$

which, in view of our recent discussion of t -time and τ -time, we recognize as

$$F(s) = F_1(s) \cdot F_2(s) \quad (5.87)$$

Using (5.87) in combination with (5.81), it can be stated that

$$F_1(s) \cdot F_2(s) = \mathcal{L} \left[\int_0^t f_1(t - \tau) \cdot f_2(\tau) d\tau \right] \quad (5.88)$$

This equation (5.88) is the usual way of expressing the real convolution theorem. It is evident of course that

$$\mathcal{L}^{-1}[F(s)] = \mathcal{L}^{-1}[F_1(s) \cdot F_2(s)] = \int_0^t f_1(t - \tau) \cdot f_2(\tau) d\tau \quad (5.89)$$

It should be possible to use this theorem to find the inverse Laplace transform of any $F(s)$ which can be factored into two parts, if each part has an $f(t)$ which can be recognized. The procedure for using the theorem will be illustrated by examples.

EXAMPLES

(1) Using the real convolution theorem, find the inverse of

$$F(s) = \frac{1}{(s + \alpha)(s + \nu)} \quad (5.90)$$

Choose the two factors as

$$F_1(s) = \frac{1}{s + \alpha}; \quad \text{so that } f_1(t) = e^{-\alpha t}; \quad \text{or } f_1(t - \tau) = e^{-\alpha(t-\tau)}$$

$$F_2(s) = \frac{1}{s + \nu}; \quad \text{so that } f_2(t) = e^{-\nu t}; \quad \text{or } f_2(\tau) = e^{-\nu \tau}$$

Then

$$\mathcal{L}^{-1}[F(s)] = \int_0^t e^{-\alpha(t-\tau)} e^{-\nu \tau} d\tau \quad (5.91)$$

$$= e^{-\alpha t} \int_0^t e^{(\alpha - \nu)\tau} d\tau \quad (5.92)$$

$$= \frac{e^{-\alpha t}}{\alpha - \nu} [e^{(\alpha - \nu)\tau}]_0^t \quad (5.93)$$

or finally

$$\mathcal{L}^{-1}[F(s)] = \frac{\varepsilon^{-\nu t} - \varepsilon^{-\alpha t}}{\alpha - \nu} \quad (5.94)$$

which is known to be correct.

(2) Apply the theorem to find the inverse of

$$F(s) = \frac{1}{(s + \alpha)s^2} \quad (5.95)$$

Note that this function has a double pole at $s = 0$.

Choose the two factors as

$$F_1(s) = \frac{1}{s + \alpha}; \quad \text{or } f_1(t) = \varepsilon^{-\alpha t}, \quad \text{and } f_1(t - \tau) = \varepsilon^{-\alpha(t-\tau)}$$

$$F_2(s) = \frac{1}{s^2}; \quad \text{or } f_2(t) = t, \quad \text{and } f_2(\tau) = \tau$$

Then

$$\mathcal{L}^{-1}[F(s)] = \int_0^t \varepsilon^{-\alpha(t-\tau)} \tau \, d\tau \quad (5.96)$$

$$= \varepsilon^{-\alpha t} \int_0^t \tau e^{\alpha\tau} \, d\tau \quad (5.97)$$

Which may be completed by reference to a table of integrals, so that

$$\mathcal{L}^{-1}[F(s)] = \frac{\varepsilon^{-\alpha t} + \alpha t - 1}{\alpha^2} \quad (5.98)$$

Note that in both examples the functions which were integrated could have been drawn graphically, so that if it had not been possible to integrate analytically, at least we could have found the inverse by graphical means.

This makes it possible to set up mechanized computers to perform certain calculations related to Laplace transforms.

The convolution theorem developed in this article is quite general, and can be used to obtain some of the simpler theorems.

PROBLEM. Letting the s -plane function be $F(s)/s$, use the convolution theorem to prove that

$$\mathcal{L}^{-1} \left[\frac{F(s)}{s} \right] = \int_0^t f(t) \, dt$$

5.10. Scale change theorem

The time scale theorem to be developed in this article is useful for forming new transform pairs, for simplifying the arithmetical work when the transform contains unwieldy factors, and for work with partial differential equations.

We first state the scale change theorem in (5.99) as follows, assuming as usual that $f(t)$ is Laplace transformable:

$$\mathcal{L} \left[f \left(\frac{t}{a} \right) \right] = aF(as) \quad (5.99)$$

If the t -plane variable is divided by the constant a , then both the s -plane variable and the entire s -transform are multiplied by the constant.

The proof of the theorem is relatively straightforward and begins by writing the definition of the Laplace transform, which is

$$\mathcal{L}[f(t)] = \int_0^{\infty} f(t) \varepsilon^{-st} dt = F(s) \quad (5.100)$$

Let us next divide t by the constant a , so that

$$\mathcal{L} \left[f \left(\frac{t}{a} \right) \right] = \int_0^{\infty} f \left(\frac{t}{a} \right) \varepsilon^{-st} dt \quad (5.101)$$

The right-hand integral can be slightly altered as

$$\mathcal{L} \left[f \left(\frac{t}{a} \right) \right] = \int_0^{\infty} f \left(\frac{t}{a} \right) \varepsilon^{-\frac{sat}{a}} \frac{dat}{a} \quad (5.102)$$

$$= a \int_0^{\infty} f \left(\frac{t}{a} \right) \varepsilon^{-as \left(\frac{t}{a} \right)} d \left(\frac{t}{a} \right) \quad (5.103)$$

In the past, when variations in t have been necessary, the time as measured by a τ -clock has proved useful. Let us therefore make the substitution

$$\frac{t}{a} = \tau, \quad \text{and} \quad as = z \quad (5.104)$$

Using these new variables, (5.103) becomes

$$\mathcal{L} \left[f \left(\frac{t}{a} \right) \right] = a \int_0^{\infty} f(\tau) \varepsilon^{-z\tau} d\tau \quad (5.105)$$

As far as the integration is concerned, one can as well measure time with a τ -clock as with a t -clock, and therefore the only thing which appears unusual in (5.105) is that the transform variable is z rather than s . It seems then that

$$\mathcal{L} \left[f \left(\frac{t}{a} \right) \right] = aF(z) \quad (5.106)$$

but if z is replaced by its equivalent from (5.104),

$$\mathcal{L} \left[f \left(\frac{t}{a} \right) \right] = aF(as) \quad (5.107)$$

which is a proof of the scale change theorem.

The theorem is easy to use. If an original $f(t)$ has a transform $F(s)$, then one can change the t to t/a merely by replacing each s in the function of s by (as) , and multiplying the entire new s -plane function by a .

EXAMPLES

(1) If there exists the transform pair

$$\varepsilon^{-4t} \rightarrow \frac{1}{s+4} \quad (5.108)$$

then for $a = 2$,

$$\varepsilon^{-4\left(\frac{t}{2}\right)} \rightarrow \frac{2}{2s+4} = \frac{1}{s+2} \quad (5.109)$$

which is easy to see by inspection.

(2) If a more complicated transform pair is chosen, such as

$$\frac{t \sin \beta t}{2\beta} \rightarrow \frac{s}{(s^2 + \beta^2)^2} \quad (5.110)$$

it would not be quite so easy to determine the function of s if t were to be replaced by some new value, say, $t/5$. Using the scale change theorem, however, one writes by inspection

$$\frac{t/5 \sin (\beta t/5)}{2\beta} \rightarrow \frac{5(5s)}{[(5s)^2 + \beta^2]^2} \quad (5.111)$$

Because it is so easy to use, this theorem will find numerous applications in chapters to follow.

PROBLEMS

(1) Make free use of the table in Appendix III, and find the inverse Laplace transform of

$$F(s) = \frac{4}{(16s^2 + \beta^2)^2}$$

(2) Choose some function of s which has several symmetrical poles in the s -plane, and show that a radial contraction of the poles in the s -plane corresponds to a time expansion or stretching of the function in the t -domain in the same ratio. Discuss.

(3) Examine the pole-zero diagram, Fig. 5.24, which has two symmetrical poles on the $j\omega$ -axis.

The function of s is

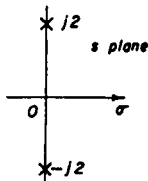


Fig. 5.24

$$F(s) = \frac{1}{(s + j2)(s - j2)} = \frac{1}{s^2 + 4}$$

from which

$$f(t) = \frac{\sin 2t}{2}$$

Suppose now that these two poles were moved uniformly toward the center of the s -plane, until they finally merged into a double pole at $s = 0$, whereupon the function would become

$$F(s) = \frac{1}{s^2}$$

Show that $f(t) = t$ by the use of the scale change theorem. Do not use the tables, or prior knowledge of what $f(t)$ would be.

5.11. Summary of Chapter V

The objective of this chapter has been not merely to derive transforms, but to develop and illustrate more subtle relations between the s - and the t -domains. These various relations have been collected and discussed as theorems, and form what are called "operational transform pairs." Once one has done a certain amount of practice work with the theorems, their use becomes more and more automatic, and it will be found that complicated forms can be simplified greatly through a good understanding of the theorems presented here. One will find additional theorems in more advanced

texts, but it is felt that the eight principle theorems here will suffice for all practical applications.

It is difficult, if not impossible, to assess any one of the theorems as being of more value, or more commonly used than any other. This depends entirely upon the problem at hand.

The linear s -plane translation theorem, dealing as it does with an exponential factor in the time domain, is certainly one of the more useful in electronics work, as we deal with decaying voltage waveforms, current discharges, attenuation, etc., almost every day.

The final and initial value theorems, although perhaps not quite so useful in an original analysis, nevertheless serve as guides for checking solutions, and in numerous cases allow a specific formula to be derived at a glance.

The real translation theorem begins an introduction into numerous problems concerning complex waveshapes. In fact this theorem, or concepts closely related to it, will be used in some way with almost every problem which involves other than sinusoidal voltages and currents.

The complex differentiation and integration theorems are of great value to extending and modifying tables of Laplace transforms, and also for increasing our general familiarity with operation in the time and complex frequency domains.

Although not in itself a theorem, the ideas on sectioning a function of time have been included as general subject matter, as these concepts are used throughout the structure of our electronics analyses.

The convolution theorem has been included to illustrate an entirely different way to take inverse Laplace transforms. This theorem may provide the only means of performing such inverse transformations if transcendental functions of s are included as factors. The convolution theorem also suggests a procedure for finding inverse transforms by graphical methods if the function of s cannot be handled analytically.

At this point, enough formal material has been covered to begin its application to network analysis. Many details and fine points will be brought out in the examination of the various circuits.

CHAPTER VI

NETWORK ANALYSIS BY MEANS OF THE LAPLACE TRANSFORMATION

6.1. Introduction

It is usually agreed that most theories are of little worth unless they can be applied to promote or serve some useful purpose. One of the most desirable features of the Laplace transform is its ability to promote more general and detailed understanding of the basic nature of network analysis problems. It also serves in most practical ways to let us furnish answers to network problems where transient or non-sinusoidal waveshapes are involved.

Most technicians and many engineers have, through long use, come to regard the concept of reactance, as expressed by $2\pi fL$ or $1/2\pi fC$, as all that it was necessary to know about network impedances, especially if the j -operator was used to indicate "direction" of the R - L - C terms.

The concept of "reactance" served for most analytical work in the early days of electronics and radio. Then one dealt usually with d.c., or sinewaves. Today, however, square waves, pulses, triangles, sawteeth and a host of other exotic waveshapes are every bit as common in our daily experiences as are sinewaves. Yet through habit and long association with the term "reactance", one is sometimes taken by surprise upon realizing that the concept of reactance breaks down entirely, indeed is meaningless, when other than sinusoidal waveforms are being considered.

In this chapter, we shall work with newer and more general concepts of impedance, which will not depend on waveshape. These new concepts will permit much deeper insight into the true working of network analysis, and will serve as background for the chapter on the fundamentals of network synthesis to follow. This chapter will be concerned entirely with specific networks. We shall attempt to choose for each article a network which is commonly used in a particular instrument, electronic system or situation.

6.2. Writing network equations for multiple loop circuits

Let us review briefly the procedure usually employed to write the equations of a multiple loop network. The reader is assumed to be familiar with Kirchhoff's laws, the theory of determinants, mutual impedances, etc. Rather than use n -meshes, we will choose a three loop circuit of general impedances, as in Fig. 6.1, and the reader can extend the ideas to more loops by inspection.

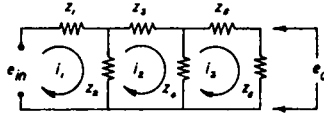


Fig. 6.1

From elementary work, using Maxwell's fictitious current notation, the reader will recall that the three loop equations are:

$$e_{IN} = z_{11}i_1 + z_{12}i_2 + z_{13}i_3 \tag{6.1}$$

$$0 = z_{21}i_1 + z_{22}i_2 + z_{23}i_3 \tag{6.2}$$

$$0 = z_{31}i_1 + z_{32}i_2 + z_{33}i_3 \tag{6.3}$$

Here it is noted that z_{11} represents the self-impedance of loop 1, z_{12} is the common, or mutual impedance between loop 1 and loop 2, etc., i.e.

$$z_{11} = z_1 + z_2 \tag{6.4}$$

$$z_{12} = -z_2 \tag{6.5}$$

$$z_{13} = 0 \tag{6.6}$$

$$z_{22} = z_2 + z_3 + z_4 \tag{6.7}$$

$$z_{21} = -z_2 \tag{6.8}$$

Note that since each element in Fig. 6.1 is labeled as a general impedance, it may actually be a resistor, inductor or condenser.

Having written the network equations in standard form, it is now possible to use them to solve for the various required quantities, such as input impedance, or output voltage. By way of further review,

if it is desired to solve for input impedance of the network in Fig. 6.1, we first solve for current i_1 , using determinants.

$$i_1 = \frac{\begin{vmatrix} e_{IN} & z_{12} & z_{13} \\ 0 & z_{22} & z_{23} \\ 0 & z_{32} & z_{33} \end{vmatrix}}{\begin{vmatrix} z_{11} & z_{12} & z_{13} \\ z_{21} & z_{22} & z_{23} \\ z_{31} & z_{32} & z_{33} \end{vmatrix}} \quad (6.9)$$

and expanding the numerator by minors

$$i_1 = \frac{e_{IN} \begin{vmatrix} z_{22} & z_{23} \\ z_{32} & z_{33} \end{vmatrix}}{\begin{vmatrix} z_{11} & z_{12} & z_{13} \\ z_{21} & z_{22} & z_{23} \\ z_{31} & z_{32} & z_{33} \end{vmatrix}} \quad (6.10)$$

At this point we can set up the ratio for the input impedance z_{IN} by inspection, as

$$z_{IN} = \frac{e_{IN}}{i_1} = \frac{\begin{vmatrix} z_{11} & z_{12} & z_{13} \\ z_{21} & z_{22} & z_{23} \\ z_{31} & z_{32} & z_{33} \end{vmatrix}}{\begin{vmatrix} z_{22} & z_{23} \\ z_{32} & z_{33} \end{vmatrix}} \quad (6.11)$$

and it is then only necessary to insert the algebraic or numerical values of the impedances into (6.11) to have the input impedance.

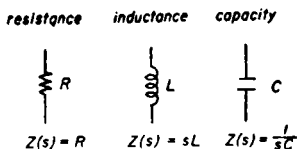


Fig. 6.2

It is necessary at this point to review art. 4.2, where the impedance of resistors, inductors and condensers was developed as a function of s . This information is shown in Fig. 6.2.

In equations (6.1), (6.2) and (6.3), i_1 goes at once into $I(s)$, and e_{1N} becomes $E_{1N}(s)$, thus these equations become

$$E_{1N}(s) = Z_{11}(s)I_1(s) + Z_{12}(s)I_2(s) + Z_{13}(s)I_3(s) \quad (6.12)$$

$$0 = Z_{21}(s)I_1(s) + Z_{22}(s)I_2(s) + Z_{23}(s)I_3(s) \quad (6.13)$$

$$0 = Z_{31}(s)I_1(s) + Z_{32}(s)I_2(s) + Z_{33}(s)I_3(s) \quad (6.14)$$

where the use of the lower case letters in the time world, and capital letters in the s -domain is consistent with our previous usage.

Note that the $Z(s)$ terms and $I(s)$ terms are usually written by inspection or direct conversion, but that the $E_{1N}(s)$ usually requires that a transformation from $e_{1N}(t)$ be effected.

Having defined our standard way of writing the network equations in terms of s or t , we now begin the study of typical network problems.

6.3. Relay damping problems

As a relatively simple problem to illustrate the use of the s -plane, and its pole-zero diagram, let us consider Fig. 6.3, where a relay L

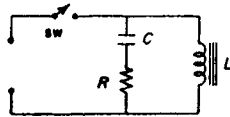


Fig. 6.3

is to be damped in such a manner that it will appear non-oscillatory to the contact points, thereby minimizing arcing. Someone has suggested that a series R - C circuit connected directly across the relay may do the job.

The problem to be analyzed then, is whether an R - C connection across L can make the entire combination appear to be non-oscillatory to the switch contacts.

Let us examine Fig. 6.4, where we show the impedance of each component as a function of s . By the usual rule of combining such a series-parallel impedance configuration, we have

$$Z_{1N}(s) = \frac{\left(R + \frac{1}{sC}\right) \cdot sL}{\left(R + \frac{1}{sC}\right) + sL} \quad (6.15)$$

or

$$Z_{\text{IN}}(s) = \frac{RLs + \frac{L}{C}}{R + \frac{1}{sC} + sL} \quad (6.16)$$

Clearing of fractions by multiplying both numerator and denominator by sC gives

$$Z_{\text{IN}}(s) = \frac{RLCs^2 + Ls}{LCs^2 + RCs + 1} \quad (6.17)$$

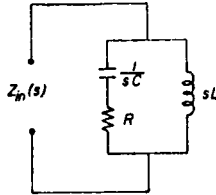


Fig. 6.4

Let us now draw the pole-zero diagram of this function of s . The zeros can be found by setting the numerator equal to 0.

$$s(RLCs + L) = 0 \quad (6.18)$$

from which the zeros are

$$\left. \begin{aligned} s &= 0 \\ s &= -\frac{1}{RC} \end{aligned} \right\} \quad (6.19)$$

The poles can be found by setting the denominator of (6.17) equal to 0.

$$LCs^2 + RCs + 1 = 0 \quad (6.20)$$

and by the use of the quadratic formula, the two poles are

$$\left. \begin{aligned} s &= \frac{-RC + \sqrt{(R^2C^2 - 4LC)}}{2LC} \\ s &= \frac{-RC - \sqrt{(R^2C^2 - 4LC)}}{2LC} \end{aligned} \right\} \quad (6.21)$$

Equation (6.21) can be manipulated slightly to give

$$\left. \begin{aligned} s &= -\frac{R}{2L} + \sqrt{\left(\frac{R^2}{4L^2} - \frac{1}{LC}\right)} \\ s &= -\frac{R}{2L} - \sqrt{\left(\frac{R^2}{4L^2} - \frac{1}{LC}\right)} \end{aligned} \right\} \quad (6.22)$$

A j may be removed from the radical if the signs are reversed inside, thus

$$s = -\frac{R}{2L} \pm j\sqrt{\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)} \quad (6.23)$$

The complete pole-zero diagram now appears as in Fig. 6.5.

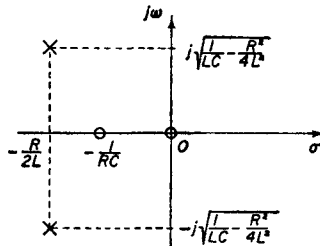


Fig. 6.5

We now come to the realization that the circuit of Fig. 6.3 (or 6.4) is completely described by the pole-zero diagram. That is, this pole-zero diagram gives all the information about the input impedance $Z_{IN}(s)$. In fact, having nothing more than the pole-zero diagram of Fig. 6.5, one could form the proper factors and recombine them to get (6.17). This is obvious, since the diagram was developed from (6.17) in the first place.

Now let us return to the problem at hand, that of making this total impedance appear non-oscillatory so that there will be minimum arcing at the contact points.

Examining the pole-zero diagram of $Z_{IN}(s)$, it is easily seen that the function $Z_{IN}(s)$ can be made non-oscillatory by reducing the $j\omega$ -component of the pole locations to 0, i.e. let us move both poles toward each other until they are both on the σ -axis.

All that we have to do to move the poles so, is to let their j -components become 0, that is,

$$\sqrt{\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)} = 0 \quad (6.24)$$

or

$$\frac{1}{LC} = \frac{R^2}{4L^2} \quad (6.25)$$

or

$$R = 2\sqrt{\left(\frac{L}{C}\right)} \quad (6.26)$$

Knowing the value L of the relay, and having derived (6.26) from the pole-zero diagram, we can now choose a suitable value of C and use the required value of R called for in (6.26). Since both poles now rest on the σ -axis, there are no j frequency components, and the circuit is thus completely non-oscillatory as required.

PROBLEM. Derive the relations between the parameters shown in Fig. 6.6, draw the pole-zero diagram, and show values of R and C which will make the circuit non-oscillatory.

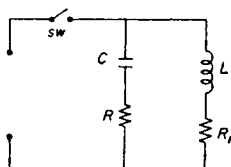


Fig. 6.6

6.4. The Wien-bridge oscillator

Oscillators of the Wien-bridge type are often used when it is necessary to generate frequencies of the order of from 1 c/s to 1 Mc/s. This wide range, some six orders of magnitude, together with the fact that this type of oscillator is by far the most commonly used in this range, regardless of cost, indicates that every electronics engineer should be thoroughly familiar with its operation.

Fig. 6.7 shows the essential features of the Wien-bridge oscillator. Actually, the series-parallel R - C arms shown represent only one-half the bridge circuit. The other half consists of a combination linear

and non-linear negative feedback circuit whose only function is to automatically adjust the amplifier gain to the precise value required.

In this article we shall be concerned with an analysis of the frequency determining network, and the gain and phase requirements of the amplifier. Let us examine the R - C network as shown in Fig. 6.8.

In this network, the voltage e_0 goes to the amplifier input, while the amplifier output feeds voltage back into the network input.

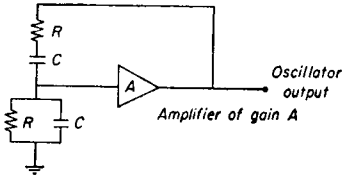


Fig. 6.7

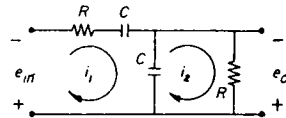


Fig. 6.8

Using the customary notation, we now write the Kirchhoff's law equations around both loops. We express all voltages, currents and impedances as functions of s .

$$E_{IN}(s) = \left(R + \frac{2}{sC} \right) I_1(s) - \frac{1}{sC} I_2(s) \tag{6.27}$$

$$0 = -\frac{1}{sC} I_1(s) + \left(R + \frac{1}{sC} \right) I_2(s) \tag{6.28}$$

The next step indicated is to solve this set of equations for $I_2(s)$, as follows:

$$I_2(s) = \frac{\begin{vmatrix} \left(R + \frac{2}{sC} \right) & E_{IN}(s) \\ -\frac{1}{sC} & 0 \end{vmatrix}}{\begin{vmatrix} \left(R + \frac{2}{sC} \right) & -\frac{1}{sC} \\ -\frac{1}{sC} & \left(R + \frac{1}{sC} \right) \end{vmatrix}} \tag{6.29}$$

The determinants are now expanded and like terms combined to give

$$I_2(s) = \frac{E_{IN}(s) \cdot \frac{1}{sC}}{R^2 + \frac{3R}{sC} + \frac{1}{s^2C^2}} \quad (6.30)$$

which is cleared of fractions by multiplying both numerator and denominator by s^2C^2

$$I_2(s) = \frac{E_{IN}(s)sC}{R^2C^2s^2 + 3RCs + 1} \quad (6.31)$$

This value for $I_2(s)$ can now be multiplied by R to obtain the output voltage $E_0(s)$, thus

$$E_0(s) = \frac{E_{IN}(s)RCs}{R^2C^2s^2 + 3RCs + 1} \quad (6.32)$$

We are now in a position to solve for the transfer function very easily (see art. 4.1).

$$Z_T(s) = \frac{E_0(s)}{E_{IN}(s)} = \frac{RCs}{R^2C^2s^2 + 3RCs + 1} \quad (6.33)$$

Equation (6.33) is the transfer function of the network shown in Fig. 6.8. It contains all the information that we need to know about both frequency and amplitude.

Both poles of (6.33) lie on the negative σ -axis in the s -plane, with no $j\omega$ -components present. If we were to take the inverse Laplace transform of this function we would get a pair of exponentially decreasing time functions. Thus the pole locations should indicate that this network alone can have no oscillatory properties. It is therefore incorrect to compare it in any way with similarly arranged L - C networks which actually can oscillate alone.

To make this R - C network oscillate, we can make up for all losses by means of the amplifier of gain A , setting the tandem combination for the network and amplifier equal to unity, i.e.

$$Z_T(s) \cdot A = 1 \quad (6.34)$$

or

$$RCsA = R^2C^2s^2 + 3RCs + 1 \quad (6.35)$$

or

$$R^2C^2s^2 + RCs(3 - A) + 1 = 0 \quad (6.36)$$

Now by inspection of (6.36) it is found that when the amplifier has zero phase shift, and when

$$A = 3 \tag{6.37}$$

then

$$R^2C^2s^2 = -1 \tag{6.38}$$

which makes

$$s^2 = -\frac{1}{R^2C^2} \tag{6.39}$$

or

$$s = \pm \frac{j}{RC} \tag{6.40}$$

But the general definition of s is

$$s = \sigma + j\omega = \frac{j}{RC} \tag{6.41}$$

and when we equate real terms to real terms and imaginary to imaginary, it is found that

$$\sigma = 0 \tag{6.42}$$

$$\omega = \frac{1}{RC} \tag{6.43}$$

or, since $\omega = 2\pi f$,

$$f = \frac{1}{2\pi RC} \tag{6.44}$$

Summarizing then, we observe that when the amplifier gain was set at 3 (6.37) and combined with the network of Fig. 6.8, the net result was to create a new function with new poles at $\pm 1/RC$ on the $j\omega$ -axis (6.40), as in Fig. 6.9.

These poles have no σ -component, and hence the inverse transform, or oscillator output is

$$e_o(t) \simeq \sin\left(\frac{t}{RC}\right) = \sin \omega t \tag{6.45}$$

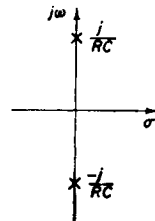


Fig. 6.9

Equation (6.45) indicates that the output waveshape is a pure sinuswave, with no distortion. Equations (6.37) and (6.44) give the results which should be retained for actual design use.

This particular method of working with the transfer function was used to give the reader more practice in reasoning in the s -plane alone. A practice problem will now bring out an alternate method.

PROBLEM

(1) Write the transfer function (6.33) upside down, as

$$\frac{E_{IN}(s)}{E_0(s)} = \frac{R^2C^2s^2 + 3RCs + 1}{RCs} \quad (6.46)$$

Substitute $j\omega$ for s throughout, and observe that to have zero phase shift between output and input, the j -term must be set to zero. Use this fact to solve for frequency of oscillation. Find the required oscillator gain from the remaining real part of (6.46).

(2) Using the previous results of this article, give the output voltage (magnitude), and state what the phase shift would be for the network shown in Fig. 6.10. Assume no loading on the output.

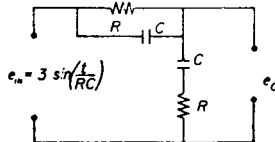


Fig. 6.10

6.5 A phase-shift oscillator

The Wien-bridge oscillator discussed in the previous article used an R - C network which had zero phase shift, together with an amplifier whose gain was 3 and whose phase shift was also zero. The zero phase shift requirement ordinarily would require two amplifying stages in cascade. The present objective is to discuss another

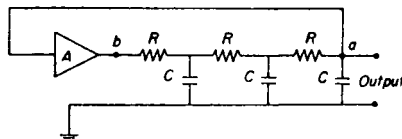


Fig. 6.11

network which will shift phase by 180° at the oscillating frequency, and which will therefore require only a single stage, that is, one which has an additional 180° of phase shift.

Let us examine Fig. 6.11, which shows a three-section R - C network, together with an amplifier stage of gain A . The oscillator

output is assumed to be unloaded, so that a cathode follower or some other type of buffer stage must be used.

The reason for taking the output from the point *a* rather than the point *b* will be apparent shortly. The three-section network to be

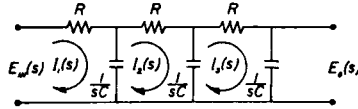


Fig. 6.12

analyzed is redrawn in Fig. 6.12, where each impedance is given as a function of *s*. The three network equations are

$$E_{IN}(s) = \left(R + \frac{1}{sC} \right) I_1(s) - \frac{1}{sC} I_2(s) + 0I_3(s) \quad (6.47)$$

$$0 = -\frac{1}{sC} I_1(s) + \left(R + \frac{2}{sC} \right) I_2(s) - \frac{1}{sC} I_3(s) \quad (6.48)$$

$$0 = 0I_1(s) - \frac{1}{sC} I_2(s) + \left(R + \frac{2}{sC} \right) I_3(s) \quad (6.49)$$

It is suggested at this point that the reader perform the algebra necessary to solve for $I_3(s)$, then multiply this by the final impedance in Fig. 6.12, which is $1/sC$, and simplify to obtain the transfer function, which is then shown to be

$$Z_T(s) = \frac{1}{R^3C^3s^3 + 5R^2C^2s^2 + 6RCs + 1} \quad (6.50)$$

Every electronics engineer should derive this result at least once, to satisfy himself that it is correct, straightforward, and that he can do it. After having once gone through the tedious job of obtaining $Z_T(s)$ for this network, he can thereafter look up the transfer function in Appendix I, which is a table of transfer functions of networks such as this one.

It is now most conventional and convenient to invert the transfer function, to obtain

$$\frac{E_{IN}}{E_0}(s) = 1 + 5R^2C^2s^2 + 6RCs + R^3C^3s^3 \quad (6.51)$$

The variable s can then be replaced by its imaginary component $j\omega$ (we assume for the moment that the input is a sine wave), this gives

$$\frac{e_{IN}}{e_0} = 1 - 5R^2C^2\omega^2 + j(6RC\omega - R^3C^3\omega^3) \quad (6.52)$$

Now for the input and output voltages to be displaced 180° in phase, the imaginary term must be exactly zero, thus

$$6RC\omega - R^3C^3\omega^3 = 0 \quad (6.53)$$

or, solving for ω

$$\omega = \frac{\sqrt{6}}{RC} \quad (6.54)$$

from which

$$f = \frac{\sqrt{6}}{2\pi RC} \quad (6.55)$$

Equation (6.55) thus gives the frequency of oscillation in terms of R and C . After letting the j -term in (6.52) become zero, there remains

$$\frac{e_{IN}}{e_0} = 1 - 5R^2C^2\omega^2 \quad (6.56)$$

If we square (6.54) we have

$$\omega^2 = \frac{6}{R^2C^2} \quad (6.57)$$

which can be substituted into (6.56) to give

$$\frac{e_{IN}}{e_0} = 1 - \frac{5R^2C^2 \cdot 6}{R^2C^2} \quad (6.58)$$

or

$$\frac{e_{IN}}{e_0} = -29 \quad (6.59)$$

Equation (6.59) thus shows that there is a 29 to 1 voltage reduction in the network, and that the amplifier A must have exactly this gain A for the oscillator to be successful. Equations (6.59) and (6.55) are the key results to be retained from this analysis. The minus sign in (6.59) shows that there is indeed a 180° phase shift between e_{IN} and e_0 .

One could interchange the R and C values in Fig. 6.12, and the circuit operation would be unchanged except that the formula for frequency would be

$$f = \frac{1}{2\pi\sqrt{6}RC} \quad (6.60)$$

The gain would still have to be 29.

To be successful as an oscillator, there must be some non-linearity in the amplifier which will standardize the gain at precisely 29. This non-linear quantity, however introduced, will create some distortion in the otherwise pure sinewave output. We will show in the next article that the network of Fig. 6.12 will act as a low-pass filter, greatly attenuating any harmonics which may occur as a result of the non-linearity. Interchanging R and C would allow proper oscillator action, but would accentuate any harmonic distortion. These same considerations make it desirable to take the output from the network, where distortion is small, rather than from the amplifier output, where the distortion is not only present, but amplified twenty-nine times.

This type of phase-shift oscillator can be made exceptionally stable with respect to B plus variations, temperature and tube parameter changes. With good attention to design it represents one of the most simple and satisfactory oscillators possible.

6.6. Harmonic Discrimination in a three-section phase shift oscillator

In the phase-shift oscillator described in the last article, probably the simplest form of non-linearity is clipping in the vacuum tube amplifier. Such clipping is usually symmetrical, and thus will create third harmonics (and higher odd harmonics) as distortion. Fortunately, however, the network itself (Fig. 6.12) acts as a low-pass filter to remove a large part of any such distortion. We should now determine the ratio of third harmonic reduction to fundamental signal reduction. Fifth and higher order harmonics will usually not be strong enough to prove troublesome.

Let us begin with the network input to output voltage ratio already given by (6.52)

$$\frac{e_{1N}}{e_0} = 1 - 5R^2C^2\omega^2 + j(6RC\omega - R^3C^3\omega^3) \quad (6.61)$$

At the fundamental frequency ω_0 , the j -term is equal to zero, from which

$$\omega_0 = \frac{\sqrt{6}}{RC} \quad (6.62)$$

Now the various harmonic frequencies ω are

$$\omega = n\omega_0 = \frac{n\sqrt{6}}{RC} \quad (6.63)$$

so that (6.61) becomes

$$\frac{e_{IN}}{e_0} = 1 - 5n^2 + j(6^{\frac{3}{2}}n - 6^{\frac{3}{2}}n^3) \quad (6.64)$$

or

$$\frac{e_{IN}}{e_0} = 1 - 30n^2 + j6^{\frac{3}{2}}(n - n^3) \quad (6.65)$$

As an absolute magnitude, (6.65) can be written as

$$\left| \frac{e_{IN}}{e_0} \right| = \sqrt{\{(1 - 30n^2)^2 + 6^3(n - n^3)^2\}} \quad (6.66)$$

or

$$\left| \frac{e_{IN}}{e_0} \right| = \sqrt{(216n^6 + 468n^4 + 156n^2 + 1)} \quad (6.67)$$

Considering (6.63) and (6.67), when $n = 1$, we have for the fundamental

$$\left| \frac{e_{IN}}{e_0} \right| = \sqrt{(216 + 468 + 156 + 1)} = 29 \quad (6.68)$$

A result which we recall from the last article.

Now for the third harmonic, $n = 3$, and (6.67) gives

$$\left| \frac{e_{IN}}{e_0} \right| = 444 \quad (6.69)$$

Assume the highly unlikely case where the fundamental and the third harmonic inputs are identical in magnitude. The actual reduction is

$$\frac{n_3}{n_1} = \frac{444}{29} = 15.3 \text{ to } 1 \quad (6.70)$$

which in itself would be relatively good discrimination against the third harmonic. Let us now assume that our worst possible case

could occur if the input to the network should become a square wave. If this should happen, the third harmonic would be one-third the amplitude of the fundamental, and the discrimination would be

$$\frac{444 \times 3}{29} \simeq 46 \text{ to } 1 \quad (6.71)$$

In practical oscillators, the non-linearity necessary to stabilize the gain at exactly 29 would be nowhere near enough to even approach square wave clipping, thus we can see that the third harmonic distortion for this oscillator can easily be only a very small fraction of 1%.

6.7. The $R-C$ cathode follower oscillator

The $R-C$ oscillator to be discussed in this article was patented some years ago by the writer,* and is somewhat unusual in that no voltage amplification is required. Most oscillators require a cathode follower or some other type of isolation between the actual oscillating network and the load. If a cathode follower is employed to achieve

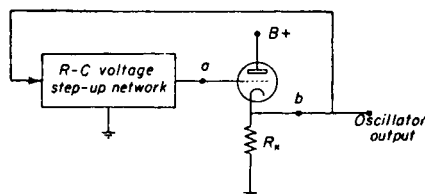


Fig. 6.13

a low output impedance for driving heavy loads, it seems only logical to use it to drive the $R-C$ network as well, thus eliminating one tube. The general arrangement is shown in Fig. 6.13, which the writer has named the " $R-C$ cathode follower oscillator".

It is required that no inductance be used in the frequency determining network, only resistance and capacity are allowed. One observes that if a voltage is applied to the grid of the cathode follower in Fig. 6.13, that the same voltage, with no change in phase, will appear at the cathode, slightly reduced in amplitude. Now if this cathode follower is to be made to oscillate, it will be necessary to take the output voltage from the cathode, feed it through some

* Amer. Pat. 2769088.

type of voltage step-up device, having no phase shift, and re-apply it to the grid.

An easy way to provide the required voltage step-up would be to use a transformer or a resonant tuned circuit, but since no inductance is permitted, it is necessary to choose a network which employs only resistance and capacity.

Now the writer has heard a great many engineers express the opinion that one cannot step up a voltage with a network which has only R and C elements. The reader can easily show that there is no basis for such thinking, by analyzing the network shown in Fig. 6.14.

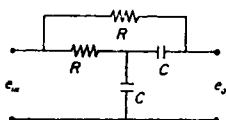


Fig. 6.14

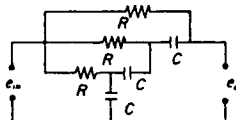


Fig. 6.15

It will be found upon analysis that the output voltage e_0 can exceed the input voltage considerably. Unfortunately, although the network in Fig. 6.14 has adequate voltage step-up, it is not suitable for use as the network required in Fig. 6.13 because the over-all phase shift cannot be made zero.

The slightly more involved network shown in Fig. 6.15 meets both the voltage step-up and the zero phase shift requirements, and is used in the circuit as the basis for the R - C cathode follower oscillator. If all R 's and all C 's are identical, it will be found that for a frequency

$$f = \frac{1}{2\pi\sqrt{(6)RC}} \quad (6.72)$$

the phase shift will be zero, and the voltage step-up will be adequate so that this network can be used in Fig. 6.13 to allow the cathode follower to oscillate. Since the output of the cathode follower is at a very low impedance, it is not ordinarily necessary to provide further isolation between oscillator and load. For additional practice in determining transfer functions, the reader is urged to work the following three problems.

PROBLEMS

(1) Show graphically that the network in Fig. 6.14 can have a voltage step-up greater than unity. Estimate the voltage gain, and phase shift for the condition $R = X_c$.

(2) Analyze the network of Fig. 6.15 and determine its transfer function.

ANS.
$$Z_T(s) = \frac{1 + 5RCs + 6R^2C^2s^2}{1 + 5RCs + 6R^2C^2s^2 + R^3C^3s^3}$$

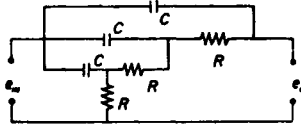


Fig. 6.16

(3) Consider the voltage step-up network of Fig. 6.16. Show that the transfer function is

$$Z_T(s) = \frac{6RCs + 5R^2C^2s^2 + R^3C^3s^3}{1 + 6RCs + 5R^2C^2s^2 + R^3C^3s^3}$$

Show further that when the complex frequency s is

$$s = \frac{j\sqrt{6}}{RC}$$

that the phase shift is zero. Find the exact voltage gain for this value of s . (*Note.* The gain for this circuit is only a few per cent.)

6.8. Odd and even functions of s

The several networks we have considered in the past few articles have required that the phase of $Z_T(s)$ be either 0° or 180° . With these examples fresh in mind, this is an ideal time to investigate the function $F(s)$ in a more general way, and to determine what is required for $F(s)$ to represent 0° or 180° phase shift. This brief introduction to the more analytical nature of transfer functions will serve as good background material for our later work with filters and network synthesis.

The function $F(s)$ will usually consist of a numerator and a denominator, each of which may themselves be functions of s . For example, $F(s)$ might be

$$F(s) = \frac{6s + 5s^2 + s^3}{1 + 6s + 5s^2 + s^3} \tag{6.73}$$

Now let us define any term where s is raised to an even power as being an even term, and any term where s is raised to an odd power as an odd term. In addition, sums of even terms will be even, and sums of odd terms will be odd, etc.

We thus define $m(s)$ as the sum of the *even* terms in a polynomial, and $n(s)$ as the sum of the *odd* terms in the same polynomial. We can use subscripts to distinguish the even and odd parts of the numerator and denominator. The general function of s is therefore

$$F(s) = \frac{m_1(s) + n_1(s)}{m_2(s) + n_2(s)} \quad (6.74)$$

For the specific function in (6.73) we see that

$$\left. \begin{aligned} m_1(s) &= 5s^2 \\ n_1(s) &= 6s + s^3 \\ m_2(s) &= 1 + 5s^2 \\ n_2(s) &= 6s + s^3 \end{aligned} \right\} \quad (6.75)$$

Now we see in (6.74) that the denominator contains odd powers of s . We can get rid of such odd powers in the denominator by rationalizing, that is by multiplying both numerator and denominator by the quantity $m_2(s) - n_2(s)$. Thus

$$F(s) = \frac{(m_1 + n_1)(m_2 - n_2)}{(m_2 + n_2)(m_2 - n_2)} \quad (6.76)$$

or

$$F(s) = \frac{m_1 m_2 - m_1 n_2 + m_2 n_1 - n_1 n_2}{m_2^2 - n_2^2} \quad (6.77)$$

and we see that the terms in the new denominator now have only even powers of s . In fact, we can now group the terms of the function into even and odd parts, thus

$$F(s) = \frac{m_1 m_2 - n_1 n_2}{m_2^2 - n_2^2} + \frac{m_2 n_1 - m_1 n_2}{m_2^2 - n_2^2} \quad (6.78)$$

or

$$F(s) = A(s) + B(s) \quad (6.79)$$

where

$$A(s) = \frac{m_1 m_2 - n_1 n_2}{m_2^2 - n_2^2} \quad (\text{even}) \quad (6.80)$$

$$B(s) = \frac{m_2 n_1 - m_1 n_2}{m_2^2 - n_2^2} \quad (\text{odd}) \quad (6.81)$$

Note that if we restrict s to the $j\omega$ axis, that $A(\omega)$ is always real, and $B(\omega)$ is always imaginary. A j will appear in each term in B and can be factored out as a multiplier.

The only requirement for the phase of $F(s)$ to be 0° or 180° is that the *odd* part, $B(s)$, be zero. Thus from (6.81), $F(s)$ has 0° phase when

$$m_2 n_1 = m_1 n_2 \quad (6.82)$$

For our sample $F(s)$ in (6.73), whose even and odd quantities are given in (6.75), (6.82) becomes

$$(1 + 5s^2)(6s + s^3) = 5s^2(6s + s^3) \quad (6.83)$$

Since the first terms on each side are not equal, the only solution is for both second terms to be zero, thus

$$6s + s^3 = 0 \quad (6.84)$$

$$s^2 = -6$$

or

$$s = j\sqrt{6} \quad (6.85)$$

If s is replaced by $j\omega$, (6.85) becomes

$$j\omega = j\sqrt{6}$$

$$\omega = \sqrt{6} \quad (6.86)$$

Most readers will have noticed by now that this function is the voltage step-up network shown in Fig. 6.16 but with $R = C = 1$.

Note finally that with the odd part, $B(s)$ being zero, $F(s)$ has left only the even part, $A(s)$, and from (6.79) and (6.80)

$$F(s) = \frac{m_1 m_2 - n_1 n_2}{m_2^2 - n_2^2} \quad (6.87)$$

and from (6.75)

$$F(s) = \frac{5s^2(1 + 5s^2) - (6s + s^3)(6s + s^3)}{(1 + 5s^2)^2 - (6s + s^3)^2} \quad (6.88)$$

and since

$$(6s - s^3) = 0$$

$$F(s) = \frac{5s^2(1 + 5s^2)}{(1 + 5s^2)^2} = \frac{5s^2}{1 + 5s^2} \quad (6.89)$$

substitution of (6.84) for s gives

$$F(s) = \frac{30}{29} \quad (6.90)$$

showing that the gain is about 3 per cent greater than unity. This gain, although small, is adequate for the Cathode Follower R - C Oscillator. The gain of this network could be increased to a theoretical value of $9/8$ by tapering each section so highly that the previous section is not appreciably loaded. However, let us examine a much more efficient R - C voltage step-up network in the following article.

6.9. R - C voltage step-up networks

In the R - C Cathode Follower Oscillator which we studied earlier, the network gave a voltage step-up which was only slightly greater than one. Let us now see what can be done to obtain a larger voltage step-up. We can suspect that it is not going to be feasible to get huge ratios, but it is instructive to examine the problem, and to be aware of what is practical to achieve.

Let us examine the network shown in Fig. 6.17, which, although it uses six elements as before, can be much more efficient.

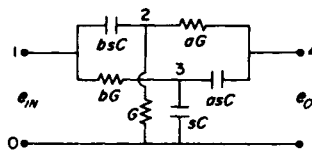


Fig. 6.17

The individual elements have been labeled as admittances here, merely from personal choice of the method used to work out the transfer function. The reader should verify the following result as a practice problem. One can use any method that achieves results. In the method used by the writer, it was easier to work with values in admittance, but it will be immaterial to our discussion here. The

transfer function for Fig. 6.17 is given in (6.91) where G and C have been normalized to one mho and one farad. We will discuss normalization in detail in Chapter eight. The values are not of great interest at the moment, the unity values merely make it easier to concentrate on the properties of the network rather than on the size of the components.

$$Z_T(s) = \frac{(1 + a + b)s}{s^2 + \left(a + b + \frac{a + 1}{b}\right)s + 1} \tag{6.91}$$

We could substitute $j\omega$ for s , and work this transfer function into standard form $A + jB$, however, let us make use of the *even* and *odd* properties which we have just discussed in art. 6.8. We saw from (6.81) that it was very easy to find the condition for phase shift to be zero merely by setting the numerator of the *odd* part of $Z_T(s)$ to 0. Thus

$$m_2(s)n_1(s) = m_1(s)n_2(s) \tag{6.92}$$

Now for this particular transfer function we have

$$\left. \begin{aligned} m_1(s) &= 0 \\ n_1(s) &= (1 + a + b)s \\ m_2(s) &= 1 + s^2 \\ n_2(s) &= \left(a + b + \frac{a + 1}{b}\right)s \end{aligned} \right\} \tag{6.93}$$

so that (6.92) becomes

$$(1 + s^2)(1 + a + b)s = 0 \tag{6.94}$$

from which the only non-trivial solution is

$$1 + s^2 = 0 \tag{6.95}$$

$$s = j \tag{6.96}$$

or if $s = j\omega$

$$\omega = 1 \tag{6.97}$$

At $\omega = 1$ we have 0° phase shift. The reader can verify this result by working the problem the long way, but the concept of *even* and *odd* parts of the transfer function simplifies the work enormously.

Since the odd part of the transfer function has been set to 0, only the even part remains. See (6.80).

$$Z_T(s) = \frac{-(1+a+b)s\left(a+b+\frac{a+1}{b}\right)s}{(1+s^2)^2 - \left(a+b+\frac{a+1}{b}\right)^2 s^2} \quad (6.98)$$

and taking note of (6.95), we can simplify (6.98) to

$$Z_T(s) = \frac{1+a+b}{a+b+\frac{a+1}{b}} \quad (6.99)$$

or

$$Z_T(s) = \frac{b+ab+b^2}{ab+b^2+a+1} \quad (6.100)$$

Next, suppose we keep the output section in Fig. 6.17 fixed by holding a constant, and find the rate of change of gain as we vary b .

$$(6.101)$$

$$\frac{dZ_T(s)}{db} = \frac{(ab+b^2+a+1)(1+a+2b) - (b+ab+b^2)(a+2b)}{(ab+b^2+a+1)^2}$$

As usual, we can find the maximum value of the function by setting the numerator of the derivative equal to 0. We merely outline a few steps. Multiply out, and simplify to the form

$$b^2 = a^2 + 2a + 2b + 2ab + 1 \quad (6.102)$$

$$b^2 - 2(1+a)b - (a^2 + 2a + 1) = 0 \quad (6.103)$$

$$b^2 - 2(1+a)b - (1+a)^2 = 0 \quad (6.104)$$

and by the quadratic formula

$$b = (1+a)(1+\sqrt{2}) \quad (6.105)$$

For this value of b , (6.100) becomes

$$\frac{e_o}{e_{IN}} = \frac{1+a}{a+2\sqrt{2}-2} \quad (6.106)$$

The maximum theoretical gain occurs as a approaches 0, in which case

$$\left. \frac{e_o}{e_{IN}} \right|_{\max} = \frac{1+\sqrt{2}}{2} = 1.21 \quad (6.107)$$

It may be helpful to illustrate the operation of this network in graphical or vector form. We can number the key points in Fig. 6.17 and draw the vectors as in Fig. 6.18.

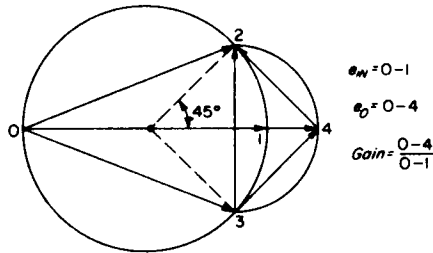


Fig. 6 18

Note that the output voltage vector e_{0-4} falls on a secondary circle, and that the phase of e_{0-4} can change by ± 10 degrees or so with almost no change in amplitude. For this example we have made the admittances asC and aG , represented by vectors e_{3-4} and e_{4-2} respectively, load the intermediate voltage vector e_{3-2} very lightly. This was done so that we could illustrate the maximum possible voltage gain.

6.10. R-C oscillator, single section variable capacity

The entire purpose of the Laplace transformation is to assist in the solution of problems, and the electronics engineer is regularly concerned with the problems of solving new and unusual networks. It is therefore felt necessary to include a discussion of at least one "non-standard" oscillator network problem for additional practice with transfer functions.

The oscillators covered earlier can be either fixed or variable frequency types. If the frequency is to be variable, one must resort to double or triple-section variable condensers for tuning. It would certainly be desirable if one could accomplish the same results with only a single-section variable condenser. That such is possible, at least in some cases, is brought out in the discussion of the oscillator network in Fig. 6.19. This network will be recognized as similar to that used in the Wien-bridge oscillator already considered. We

expect therefore, that an amplifier of zero phase shift, and of gain A , where

$$A = \frac{e_{IN}}{e_0}$$

will be required as the active element.

In the network of Fig. 6.19, the goal is to use only a single variable capacity C . The condenser C_1 is to remain fixed. Another obvious requirement is that the magnitude of the network gain (e_0/e_{IN})

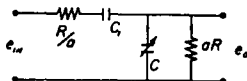


Fig. 6.19

remain relatively constant over the entire frequency range, otherwise the feedback amplifier gain will have to be continuously varied, which is neither practical nor desirable.

The amplifier employed can be either a vacuum tube or transistor device. If a transistor amplifier is used, the input impedance will be finite and can be included as a portion of aR . If the amplifier input value is $R_{IN} \Omega$ (ohms), then the increased gain A_1 will be

$$A_1 = \frac{aR}{R_{IN}} \cdot \frac{e_{IN}}{e_0} \quad (6.108)$$

Realizing that such is the case, let us ignore loading at this time, and proceed to analyze the network as shown.

The first step in this sort of analysis is, as usual, to write the network equations and then solve for the transfer function. The reader should do so at this point and show that (6.109) is correct.

$$Z_T(s) = \frac{saRC_1}{s^2R^2CC_1 + sR(Ca + C_1a + C_1/a) + 1} \quad (6.109)$$

As has been done before, the reader can now determine $z(\omega)$ by substituting $j\omega$ for each s in (6.109). The resulting equation takes the form

$$\frac{e_{IN}}{e_0} = \left(1 + \frac{1}{a^2} + \frac{C}{C_1}\right) + j \left(\frac{\omega CR}{a} - \frac{1}{\omega a RC_1}\right) \quad (6.110)$$

For zero phase shift, the imaginary term must be set to zero, which gives us information about the frequency, i.e.

$$\left(\frac{\omega CR}{a} - \frac{1}{\omega a RC_1} \right) = 0 \quad (6.111)$$

from which

$$f = \frac{1}{2\pi R\sqrt{CC_1}} \quad (6.112)$$

From (6.112) we note that if C_1 is a constant value, while C is the variable, we can lump all of the constants together as k and write

$$f = \frac{k}{R\sqrt{C}} \quad (6.113)$$

Provided that the network is otherwise satisfactory as a basis for the oscillator, this informs us that the frequency of oscillation is inversely proportional to the square root of the tuning capacity C . This recalls a similar formula for resonance in a parallel L - C circuit, which is

$$f = \frac{1}{2\pi\sqrt{LC}} \quad (6.114)$$

but the two circuits have nothing in common.

Assuming zero phase shift, the real part of (6.110) becomes

$$\frac{e_{IN}}{e_0} = 1 + \frac{1}{a^2} + \frac{C}{C_1} \quad (6.115)$$

Now let us choose C_1 , the fixed capacity, to be much larger than C . Then (6.115) becomes

$$\frac{e_{IN}}{e_0} = 1 + \frac{1}{a^2} \quad (6.116)$$

Such a choice of C_1 will allow the oscillator gain to remain essentially constant over the band. It is quite likely that we shall be using a transistor input stage, and the required total amplifier gain was given for that case by (6.108)

$$A_1 = \frac{aR}{R_{IN}} \cdot \frac{e_{IN}}{e_0} \quad (6.117)$$

where A_1 = over-all amplifier gain

R_{IN} = amplifier input resistance

$\left(\frac{e_{IN}}{e_0} \right)$ = network loss

Substituting (6.116) into (6.117) gives

$$A_1 = \frac{aR}{R_{IN}} \cdot \left(1 + \frac{1}{a^2}\right) \quad (6.118)$$

or

$$A_1 \propto a + \frac{1}{a} \quad (6.119)$$

Differentiating A_1 gives

$$\frac{dA_1}{da} = 1 - \frac{1}{a^2} \quad (6.120)$$

and setting to zero,

$$1 - \frac{1}{a^2} = 0 \quad (6.121)$$

which shows that when

$$a = 1 \quad (6.122)$$

the minimum amplifier gain is needed.

If there is no loading on the network, a suitable value for a can be chosen by inspection from (6.116). For the assumed transistor amplifier, we will require an optimum gain of 2, along with zero phase shift.

This sort of problem, with all its ramifications, is typical of an everyday network analysis which the engineer could be called upon to make at any time.

6.11. Active integrating and differentiating networks

We shall shortly become involved in filters, and an introduction to network synthesis. The two circuits to be discussed in this article are

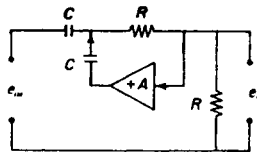


Fig. 6.20

special cases of such active networks. They have long been used where it is necessary to perform integration or to differentiate signals with greater flexibility and accuracy than can be done with simple R - C passive elements. (Consider the circuit shown in Fig. 6.20.)

For purposes of analysis, it is convenient to replace the amplifier of gain A by a voltage source Ae_0 , so that the new circuit will appear as in Fig. 6.21.

As usual, the first step is to write the network equations, which in this case are:

$$\frac{2}{sC} i_1 - \frac{1}{sC} i_2 = e_{IN} - Ae_0 \tag{6.123}$$

$$-\frac{1}{sC} i_1 + \left(2R + \frac{1}{sC}\right) i_2 = Ae_0 \tag{6.124}$$

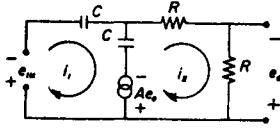


Fig. 6.21

Note that because of the feedback, a voltage source appears in loop 2, so that the equation about loop 2 is not zero, as has been the case in previous articles. The next step in the orderly process of deriving the transfer function is to solve for i_2 . (Note also that it does not matter in cases such as these whether we write the i and e as functions of s or t , since we plan to form a ratio. The ratio will be a function of s in either case.)

$$i_2 = \frac{\frac{e_{IN}}{sC} - \frac{Ae_0}{sC} + \frac{2Ae_0}{sC}}{\frac{4R}{sC} + \frac{2}{s^2C^2} - \frac{1}{s^2C^2}} \tag{6.125}$$

and the output voltage is this value multiplied by R .

$$e_0 = \frac{\frac{e_{IN}R}{sC} + \frac{Ae_0R}{sC}}{\frac{4R}{sC} + \frac{1}{s^2C^2}} \tag{6.126}$$

$$e_0 = \frac{e_{IN}R + AR e_0}{4R + \frac{1}{sC}} \tag{6.127}$$

or

$$4Re_0 + \frac{e_0}{sC} - ARe_0 = Re_{IN} \quad (6.128)$$

so that

$$\frac{e_0}{e_{IN}} = \frac{R}{4R + 1/sC - AR} \quad (6.129)$$

This may be put into the form

$$Z_T(s) = \frac{RCs}{1 + RCs(4 - A)} \quad (6.130)$$

Now let us set the gain of the feedback amplifier to exactly 4. The amplifier is to have zero phase shift so that gain will be plus rather than minus. Equation (6.130) then becomes

$$Z_T(s) = RCs \quad (6.131)$$

Let us further stipulate that the product $RC = 1$. We then have

$$Z_T(s) = s \quad (6.132)$$

Equation (6.132) thus indicates that for the imposed conditions, $RC = 1$; $A = +4$, that the transfer function of this network is the perfect derivative operator s . Or, as far as time functions are concerned,

$$e_0 = \frac{de_{IN}}{dt} \quad (6.133)$$

We see that within the frequency range and output limits of the amplifier, perfect differentiation can be performed. Also, the reader who is familiar with operational amplifiers connected as differentiators, will note that whereas the process discussed here requires a gain of exactly 4, the technique using operational amplifiers requires infinite, or, in practice, very large gains. The low gain of this circuit makes it possible to use enormous amounts of feedback to stabilize the gain at exactly the required value of 4.

PROBLEM. Using the same technique, step by step, as has been discussed here, analyze the circuit in Fig. 6.22.

Show that the transfer function of this circuit is

$$Z_T(s) = \frac{1}{s} \quad (6.134)$$

This result shows that within the frequency and amplitude limitations of the amplifier, that the circuit performs perfect integration such that

$$e_0 = \int_0^t e_{IN}(t) dt \tag{6.135}$$

These two useful circuits are merely special cases of general active ladder networks which will be covered in detail later in the text.

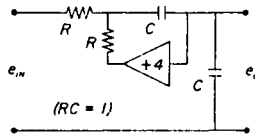


Fig. 6.22

6.12. Operational amplifiers

The last article discussed integration and differentiation through the process of using an amplifier of low gain, together with the appropriate network. Here we shall discuss briefly a more common method of doing the same job.

Consider the circuit shown in Fig. 6.23. If we assume that the amplifier presents no load to the voltage e_2 , then e_2 represents a

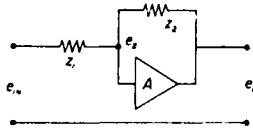


Fig. 6.23

single unknown voltage node, and we may write a single nodal equation to represent the circuit operation, which is

$$\frac{(e_2 - e_{IN})}{Z_1} + \frac{(e_2 - e_0)}{Z_2} = 0 \tag{6.136}$$

Now e_2 is seen by inspection to be

$$e_2 = \frac{e_0}{A} \tag{6.137}$$

and placing this into (6.136) gives

$$\frac{(e_0/A - e_{IN})}{Z_1} + \frac{(e_0/A - e_0)}{Z_2} = 0 \tag{6.138}$$

or

$$\frac{e_0}{AZ_1} - \frac{e_{IN}}{Z_1} + \frac{e_0}{AZ_2} - \frac{e_0}{Z_2} = 0 \quad (6.139)$$

from which

$$\frac{e_0}{e_{IN}} = \frac{1}{1/A + Z_1/AZ_2 - Z_1/Z_2} \quad (6.140)$$

Now observe that if the gain A is made very large, ideally approaching infinity, the first two denominator terms drop out, and if Z_1 and Z_2 are given as functions of s ; we can write the transfer function of Fig. 6.23 as

$$Z_T(s) = -\frac{Z_2(s)}{Z_1(s)} \quad (6.141)$$

If it is desired to perform integration with this network, one can choose

$$Z_1(s) = R; \quad Z_2(s) = \frac{1}{sC} \quad (6.142)$$

whereupon the transfer function becomes

$$Z_T(s) = -\frac{1}{RCs} \quad (6.143)$$

and we see that the transfer function is proportional to the integral operator $1/s$. Also, the proportionality constant $1/RC$ can easily be much greater than unity, thus giving amplification as well.

Should one choose to use the circuit as a differentiating network, the conditions

$$Z_1(s) = R; \quad Z_2(s) = sL \quad (6.144)$$

will provide an over-all transfer function

$$Z_T(s) = -\frac{Ls}{R} \quad (6.145)$$

It is to be noted, however, first that it will be difficult in practice to make the ratio L/R greater than unity, and second that since it is very difficult to construct high- Q inductances, the quality of the differentiation will suffer. Amplifier A must be of the inverting type.

PROBLEM. If the amplifier should be a transistor device, the input impedance would be finite, and we could not assume zero

loading at the point e_2 in Fig. 6.23. Showing a third impedance, Z_3 , from this point to ground, derive the transfer function.

$$\text{ANS.} \quad Z_T(s) = \frac{1}{1/A - Z_1/Z_2 + Z_1/AZ_2 + Z_1/AZ_3} \quad (6.146)$$

6.13. Charge amplifiers

There are a number of types of electrical transducers wherein the basic quantity of interest is electric *charge* rather than voltage. Some such common devices are the condenser microphone, the piezoelectric types of phonograph cartridges which use either Rochelle salt or other materials such as barium titanate, and some solid state nuclear particle detectors. In the last case the active detector volume is the depletion layer associated with a $p-n$ semiconductor junction. Unlike the transistor, such nuclear particle detectors are often made so that the depletion layer thickness is very large. The depletion layer in a Lithium drift particle detector is often as great as one centimeter. When such a $p-n$ junction is reverse biased, no current flows until a nuclear particle passes through the depletion volume. Such a particle, if stopped, gives up its kinetic energy in the creation of electron-hole pairs, and these charges, released within the active detector volume, are swept out by the applied field as impulses of current.

We use the nuclear particle detector as an example of a case where charge, rather than voltage, is the quantity of interest. Since the charge, or number of electron-hole pairs created, is directly proportional to the energy of the nuclear particle, it will be independent of the $p-n$ junction capacity. Thus the voltage given by the relation

$$E = \frac{Q}{C} \quad (6.147)$$

will be of no direct interest. Any attempt to measure the charge output by using a conventional voltage amplifier will fail because of the variable and unpredictable nature of the detector capacity.

To begin our analysis of the charge amplifier, it is best to consider the equivalent circuit of the transducer. This can be a Thevenin equivalent source as shown in Fig. 6.24, where the internal impedance is a capacity, rather than the more familiar resistance.

This same model can be used for such devices as piezoelectric

phonograph pickups and also for condenser microphones and

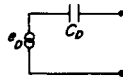


Fig. 6.24

hydrophones. If C_D is the detector capacity and e_D is the detector voltage, then the charge q_D on the detector is

$$q_D = e_D C_D \quad (6.148)$$

Now suppose we use an operational amplifier as discussed in the last Article. We can indicate a phase reversal and very high gain by $(-\infty)$ in Fig. 6.25.

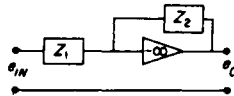


Fig. 6.25

As we learned earlier, the gain is

$$\frac{e_O}{e_{IN}} = -\frac{Z_2}{Z_1} \quad (6.149)$$

Specifically, if the impedances Z_1 and Z_2 are condensers with capacity C_1 and C_2 , we have

$$\frac{e_O}{e_{IN}} = -\frac{C_1}{C_2} \quad (6.150)$$

Let us combine Fig. 6.25 with the Thevenin equivalent circuit of the nuclear detector shown in Fig. 6.24. The result is seen in Fig. 6.26.

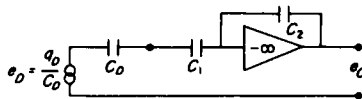


Fig. 6.26

Now a typical value of C_D will be about 10 picofarads, and we can make $C_1 = 0.1$ mfd. Then for all practical purposes, when

$C_1 \gg C_D$, the series combination is simply equal to C_D . The result is shown in Fig. 6.27

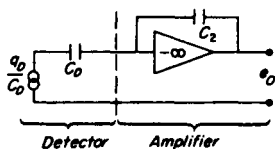


Fig. 6.27

We see that

$$e_0 = - \frac{C_D e_{IN}}{C_2} = - \frac{C_D q D}{C_2 C_D} \tag{6.151}$$

or

$$e_0 = - \frac{q D}{C_2} \tag{6.152}$$

(6.152) tells us that the output is directly proportional to detector charge, and that the capacity of the nuclear detector does not enter into the result. We see that the circuit gain, i.e. voltage output over charge input, can be adjusted by our choice of C_2 .

6.14. Analysis of the charge amplifier

Article 6.13 considered the ideal case where the operational amplifier had infinite input impedance and infinite gain. Let us now assume a practical case of an amplifier with finite gain and finite input impedance, as shown in Fig. 6.28.

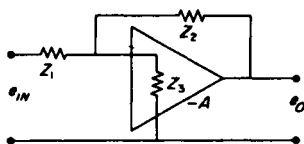


Fig. 6.28

We find that

$$\frac{e_0}{e_{IN}} = \frac{-Z_2}{\frac{Z_2}{A} + \frac{Z_1}{A} + Z_1 + \frac{Z_1 Z_2}{AZ_3}} \tag{6.153}$$

Now let Z_3 consist of the input shunt resistance and shunt capacity of the amplifier itself.

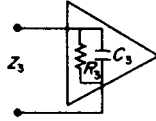


Fig. 6.29

so that

$$Z_3 = \frac{R_3}{sR_3C_3 + 1} \quad (6.154)$$

as before, let

$$Z_1 = \frac{1}{sC_D} \quad (6.155)$$

$$Z_2 = \frac{1}{sC_2} \quad (6.156)$$

then (6.153) becomes

$$\frac{e_0}{e_{IN}} = \frac{-\frac{1}{C_2}}{\frac{1}{C_2A} + \frac{1}{C_D} \left[\frac{1}{A} + 1 + \left(\frac{sR_3C_3 + 1}{sC_2R_3A} \right) \right]} \quad (6.157)$$

We now make various assumptions.

FIRST ASSUMPTION

$$\frac{1}{A} \ll 1.0 \quad (6.158)$$

(6.157) then becomes

$$\frac{e_0}{e_{IN}} = \frac{-1}{\frac{1}{A} + \frac{1}{C_D} \left[\frac{1 + sR_3(C_2A + C_3)}{sR_3A} \right]} \quad (6.159)$$

for $s = j\omega$

$$\frac{e_0}{e_{IN}} = \frac{-1}{\frac{1}{A} + \frac{1}{C_D} \left[\frac{\omega R_3(C_2A + C_3) - j}{\omega R_3A} \right]} \quad (6.160)$$

SECOND ASSUMPTION

$$AC_2 \gg C_3 \tag{6.161}$$

This assumption merely means that we must make the gain A large enough for it to be valid. Upon simplification,

$$\frac{e_0}{e_{IN}} = \frac{-A}{1 + \frac{1}{C_D} \left[\frac{\omega R_3 C_2 A - j}{\omega R_3} \right]} \tag{6.162}$$

Since $e = q_D/C_D$,

$$e_0 = \frac{-Aq_D}{C_D + \left[\frac{\omega R_3 C_2 A - j}{\omega R_3} \right]} \tag{6.163}$$

$$e_0 = \frac{-Aq_D}{C_D + C_2 A - \frac{j}{\omega R_3}} \tag{6.164}$$

THIRD ASSUMPTION

$$AC_2 \gg C_D \tag{6.165}$$

$$e_0 = \frac{-Aq_D}{AC_2 - \frac{j}{\omega R_3}} = \frac{-q_D}{C_2 - \frac{j}{\omega A R_3}} \tag{6.166}$$

and as a magnitude,

$$|e_0| = \frac{q_D}{\sqrt{C_2^2 + \frac{1}{\omega^2 A^2 R_3^2}}} \tag{6.167}$$

Now if we assume a cut-off frequency f_c , where

$$f_c = \frac{1}{2\pi A R_3 C_2} \tag{6.168}$$

when $\omega > \omega_c$, (6.167) will be

$$|e_0| = \frac{q_D}{C_2} \tag{6.169}$$

which is the same as for the result of (6.152) with an ideal amplifier.

Our four assumptions are summarized in (6.170)

$$\begin{aligned}
 A &\gg 1.0 \\
 AC_2 &\gg C_3 \\
 AC_2 &\gg C_D \\
 f_c &> \frac{1}{2\pi AR_3C_2}
 \end{aligned}
 \tag{6.170}$$

Since we can usually make all four assumptions valid by a suitable choice of the one parameter A , we see that a practical charge amplifier is not difficult to achieve.

6.15. Reactive feedback voltage amplifiers

The operational amplifier shown back in Fig. 6.25 is commonly used as a voltage amplifier. Z_1 and Z_2 are resistances, and the voltage gain is then

$$A = -\frac{R_2}{R_1} \tag{6.171}$$

which has the desirable property that the over-all gain is made independent of the active part of the network, assuming only that the active amplifier portion has great enough open-loop gain to make (6.171) valid.

We see at once that if the gain of the internal amplifier is truly very high, that the error signal at the junction of R_2 and R_1 approaches zero. Hence the input current is simply e_{IN} divided by the resistance R_1 and the amplifier input impedance is merely R_1 itself.

Now in many cases the size of the input impedance is not of great importance, but in many other cases we do want the input impedance to be very high, usually to avoid loading the source of the signal.

As an example, suppose we wish to have the input impedance of the amplifier network be 10-megohms, and that the over-all gain is to be 10. We assume that a suitable internal amplifier of adequate gain and frequency response is available. It then remains only make $R_1 = 10$ M and $R_2 = 100$ M.

Several problems now arise. First, we might question the long term stability of a 100 M resistor with age, temperature, humidity, etc. What if we wanted a gain of 100, or 1000? These gains are still

not excessive for many requirements, but in the latter case R_2 would have to be 10,000 M, and we would decide at once that such a resistor would be too erratic for normal use.

A second problem is that of the thermal noise voltage developed within R_1 itself. For any simple resistance, we have noise voltage developed by thermal agitation within the resistor itself. The noise voltage is of a strictly random nature and is independent of the material of which the resistor is made, but we can give the simple formula for the *effective* or *rms* value of the noise voltage as

$$e_{\text{RMS}} = \sqrt{4RkT \Delta f} \quad (6.172)$$

where

e_{RMS} = volts.

R = resistance in ohms.

k = Boltzmann's constant, 1.38×10^{-23} joules per degree Kelvin.

T = absolute temperature, in degrees Kelvin (room temperature is approximately 300° K).

Δf = the bandwidth of interest, in cycles per second.

Suppose now that we are interested in an audio amplifier with Δf equal to about 10 kcs. We can then use (6.172) to find the *rms* noise that will be developed spontaneously across the 10-megohm resistor R_1 . We find that the Boltzmann noise in this case is

$$e_{\text{NOISE}} = \sqrt{4 \cdot 10^7 \cdot 1.38 \cdot 10^{-23} \cdot 3 \cdot 10^2 \cdot 10^4}$$

$$e = \sqrt{16.56 \cdot 10^{-10}}$$

or

$$e_{\text{NOISE}} = 4 \cdot 10^{-5} = 40 \mu\text{V} \quad (6.173)$$

This value might seem small, but it is added directly to the input voltage e_{IN} and appears at the input to the internal amplifier. If our over-all operational system is to have a reasonable gain of say 100, we will probably set the open-loop gain of the internal amplifier at about 1000, to give 20-db negative feedback. Since the feedback will not affect the noise, our 40 microvolts will appear at the output as 40,000 microvolts or 0.04 volts. In a great many cases such noisy performance would make the system worthless.

As if these problems were not enough, suppose further that the feedback resistor R_2 has a stray shunt capacity of say 1.0 picofarad. The reactance at the 10 kc upper frequency is

$$X_c = 16 \text{ Megohms} \quad (6.174)$$

and the ratio of this to our 10-megohm value of R_1 will reduce the gain almost to unity at the upper frequencies. One tries to get around this problem by adding a compensating capacity across R_1 , but this value must be quite large in comparison, and thus the problem becomes more and more complex.

The writer has gone "all out" to stress a number of difficulties associated with a quite reasonable amplifier requirement, say a gain of 10 and an input impedance of 10-megohms. Being aware of some of the problems, it is hoped that the reader will consider the following *unorthodox* solution.

It would seem that the solution to all of the problems above would be to abandon the resistive feedback elements R_1 and R_2 completely and to use condensers instead for both Z_1 and Z_2 . If

$$Z_1 = \frac{1}{sC_1}$$

and

$$Z_2 = \frac{1}{sC_2}$$

then gain is

$$A = -\frac{C_1}{C_2} \quad (6.175)$$

We see that the frequency variable s drops out, making gain independent of frequency. Shunt capacity across both C_1 and C_2 , is absorbed simply as part of C_1 and C_2 , and the input impedance of the entire amplifier is just the capacity of C_1 across the input terminal to ground.

The first and most obvious question to arise is: What is the smallest value of C_1 for a practical amplifier, say an audio type amplifier with a bandwidth of from 20 cps to 20,000 cps?

This question is best answered by illustration with the amplifier circuit shown in Fig. 6.30, taken from the writer's engineering notebook.

The dashed lines are direct wire connections, and are shown this way only to emphasize the three distinct stages of the amplifier. The first stage uses a common field-effect transistor as a "source"

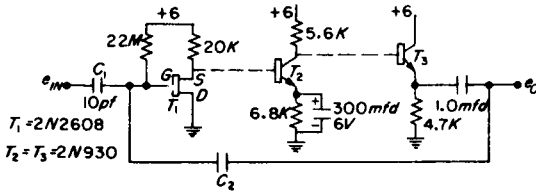


Fig. 6.30

follower. No measurable bias current flows in the 22 M bias resistor, so the gate is held at +6 volts. The d.c. voltage at point A will thus be $B +$ minus the pinch-off voltage of the FET, which is very stable. With the type used here, the pinch-off voltage is guaranteed to be not over 2.0 volts, and will never be much smaller than this, hence the d.c. voltage at A will be very close to about +3.5 volts. This value also sets the bias on T_2 and thus indirectly on T_3 .

Note that the 22 M bias resistor is *not* across the input, but is across the junction of $C_1 - C_2$, where the signal approaches zero. Hence no sensible signal current flows in this resistor, and it has no effect on input impedance.

The input impedance is a pure capacity, 10 pf. This is as small or smaller than the shunt capacity of most high-quality oscilloscope probes. With a good mica condenser the resistive component can be many thousands of megohms.

T_2 is the only straight amplifier stage. Here we use a large emitter resistance for high bias stability, and by-pass it for high signal gain.

T_3 provides an initial low output impedance and removes the output load from T_2 , thus making it possible to realize the highest gain with T_2 . The actual low output impedance is of course from the over-all feedback.

C_2 can be chosen as 1.0 pf for a total of 20-db gain. If C_2 is made 10 pf, gain is 1.0 and the unit makes an excellent impedance converter. Data on this mode is as follows:

$$C_2 = 10 \text{ pf}$$

$$\text{Open loop gain} = 60$$

Closed loop gain = 1.0

$Z_{IN} = 10$ pf (1600 M at 10 cps)

$Z_0 = 4$ ohms @ 1 kc, 50 mv p-p, 47 ohm load

e_0^{\max} p-p = 2 v @ 1 kc, no load

$BW = 10$ cps to 3 mc.

The circuit is ideal for driving a very long terminated 50 ohm transmission line at up to 50mv levels. With C_2 set for a gain of 10, BW will be cut to about 500 kc. Z_{IN} will be unchanged.

The writer is trying to promote this type of reactive feedback amplifier. There is nothing new about the idea, but in practice everyone uses resistors for Z_1 and Z_2 . Condensers seem a much more logical choice. All the good features are present and all the bad features, such as thermal noise, are absent.

Since C_1 in Fig. 6.30 can also be considered as the amplifier's input coupling capacity, the uninitiated observer will usually comment "a 10 pf coupling capacity at 10 cps, impossible!" Everyone wants to "correct" it to be 10 mfd. The reader should have no difficulty matching or improving on the circuit of Fig. 6.30.

6.16. Analysis of 3-stage reactive feedback amplifier

As the writer has proposed that reactive feedback be used in linear voltage amplifiers instead of resistive feedback, it is well to consider stability requirements and maximum permissible open loop amplifier gains.

Let us consider Fig. 6.31

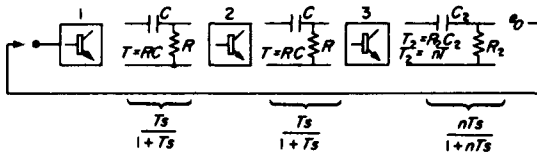


Fig. 6.31

Note that C_2 in Fig. 6.31 corresponds to the feedback C_2 of the last article, and the R_2 is the input resistance of the first *conventional* transistor stage. We are only concerned here with internal stability.

The over-all transfer function is the product of the three active

gains ($-G$) and the transfer functions of the three coupling and feedback networks.

$$\frac{e_0}{e_{IN}} = \frac{-GnT^2s^3}{(T^2s^2 + 2Ts + 1)(nTs + 1)} \tag{6.176}$$

$$\frac{e_0}{e_{IN}} = \frac{-GnT^3s^3}{nT^3s^3 + (2n + 1)T^2s^2 + (n + 2)Ts + 1} \tag{6.177}$$

For $s = j\omega$

$$\frac{e_0}{e_{IN}} = \frac{GnT^3\omega^3}{[(n + 2)\omega T - nT^3\omega^3] + j[(2n + 1)T^2\omega^2 - 1]} \tag{6.178}$$

We are most interested in the case where the phase of this gain reaches 180° . When phase reaches 180° we can find the lower frequency ω_L by setting the j -term to zero, from which

$$\omega_L^2 = \frac{1}{(2n + 1)T^2} \tag{6.179}$$

or

$$\omega_L = \frac{1}{(2n + 1)^{1/2}T} \tag{6.180}$$

and

$$\omega_L^3 = \frac{1}{(2n + 1)^{3/2}T^3} \tag{6.181}$$

Thus at ω_L the total phase shift in the coupling and feedback networks is 180° , and with the total of 180° in the three active stages, is of the correct phase for oscillation if the gain G is large enough. We insert (6.180) and (6.181) into the remaining real part of (6.178) to find the gain at ω_L as

$$\frac{e_0}{e_{IN}} = \frac{\frac{GnT^3}{(2n + 1)^{3/2}T^3}}{\frac{(n + 1)T^3(2n + 1)}{(2n + 1)^{1/2}T^3(2n + 1)} - \frac{nT^3}{(2n + 1)^{3/2}T^3}} \tag{6.182}$$

$$\frac{e_0}{e_{IN}} = \frac{Gn}{(n + 2)(2n + 1) - n} \tag{6.183}$$

$$\frac{e_0}{e_{IN}} = \frac{Gn}{2n^2 + 4n + 2} \tag{6.184}$$

or

$$\frac{e_0}{e_{IN}} = \frac{Gn}{2(n+1)^2} \quad (6.185)$$

To avoid oscillation, e_0/e_{IN} must be no greater than unity, or

$$\frac{Gn}{2(n+1)^2} = 1 \quad (6.186)$$

from which

$$G^{\max} = \frac{2(n+1)^2}{n} \quad (6.187)$$

If R_2C_2 should be the same as RC , so that $n = 1$, we see from (6.187) that the combined gain of all three stages must be less than 8 to avoid oscillation. Let us take a more practical example however.

EXAMPLE:

We choose $R = 5000 \Omega$

$C = 2 \text{ mfd}$

so that $T = 10^{-2}$. A convenient value for coupling. From sizes discussed in the previous article, we choose $C_2 = 2 \text{ pf}$, and if the first stage is an ordinary transistor rather than an FET, we can use $R_2 = 5000 \Omega$ as a typical input impedance. Thus

$$T_2 = 10^{-7} = n10^{-2}$$

or

$$n = 10^{-5}$$

Now placing this into (6.187) gives

$$G^{\max} = \frac{2(1.00001)^2}{10^{-5}} = 2(1.00002)10^5 = 2 \cdot 10^5$$

Our three stages can have a gain of 200,000 before instability sets in.

Assuming three equal gain stages, each transistor should have a gain of

$$G = \sqrt[3]{0.2 \cdot 10^6} = 60$$

Thus, with the loads and interstage coupling impedances we have, it is not likely that we would have enough gain to be troubled by oscillations when using reactive feedback in practical linear voltage amplifiers.

6.17. Single section low-pass $R-C$ filter

In this article we shall discuss the fundamental properties of a single section low-pass $R-C$ filter. This is almost the simplest type of electrical filter which can be built, yet several characteristics of the single, double, and triple section $R-C$ filters are not widely known.

Let us examine the simple network in Fig. 6.32. The transfer function of this network can easily be shown to be

$$Z_T(s) = \frac{1}{1 + RCs} \tag{6.188}$$

or, if we replace s by $j\omega$,

$$Z_T(s) = \frac{1}{1 + jRC\omega} \tag{6.189}$$

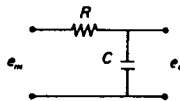


Fig. 6.32

Assume that the input to the network is unity, then the absolute magnitude of the transfer function, or the gain, becomes:

$$|A| = \frac{1}{\sqrt{1 + R^2C^2\omega^2}} \tag{6.190}$$

It is customary to refer to the upper cut-off frequency as the “half power point”, the “3 dB down point”, or the frequency where the gain is down to $1/\sqrt{2}$ times the low frequency gain. Therefore, if the cut-off frequency is denoted by ω_0 , (6.190) gives

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + R^2C^2\omega_0^2}} \tag{6.191}$$

and this can be solved to give

$$\omega_0 = \frac{1}{RC} \tag{6.192}$$

We note also that this result placed into (6.189) shows the output voltage lags the input voltage by 45° . This phase shift is called ϕ_0 .

$$\phi_0 = -45^\circ \quad (6.193)$$

Now in order to graph the magnitude as a function of frequency, we can say that any general frequency may be written as

$$\omega = n\omega_0 \quad (6.194)$$

where ω is in radians. This can be placed into the general expression for gain, (6.190), to give

$$|A| = \frac{1}{\sqrt{1+n^2}} \quad (6.195)$$

For graphing phase, we may use the same information and (6.189) to state that the phase gain is

$$\phi = -\tan^{-1} n \quad (6.196)$$

It is instructive to determine the rate of cut-off at the frequency ω_0 , or at the point on the gain-frequency curve where $n = 1$. Equation (6.195) can be differentiated to give

$$\frac{d|A|}{dn} = -\frac{1}{2}(1+n^2)^{-3/2}n \quad (6.197)$$

and the slope at $n = 1$ is

$$\left. \frac{d|A|}{dn} \right|_{n=1} = -\frac{1}{2}(2)^{-3/2} \cdot 2 = -0.3535 \text{ V/rad} \quad (6.198)$$

This value for the slope at the cut-off frequency will be compared with that obtained for the two- and three-section low-pass filters to be discussed next. Thus we shall determine whether or not there is any particular advantage in breaking a given filter up into more sections.

6.18. Two-section non-tapered R - C low-pass filter

A tapered network is one in which the input impedance of each added section is high enough that it does not appreciably load the preceding network. Thus, if we have a network which consists of two cascaded sections, each the same as the section just analyzed in art. 6.17, the resulting network is non-tapered. Such a two-section network is shown in Fig. 6.33.

At this point the reader should write and solve the equations of this network, to ascertain that the transfer function is

$$Z_T(s) = \frac{1}{R^2C^2s^2 + 3RCs + 1} \quad (6.199)$$

The reader may wonder why the transfer function is always solved first as a function of s . It is mentioned again that one does not always work with sine waves, and it is best to learn the most general

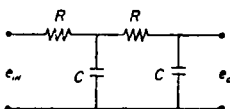


Fig. 6.33

method, which will work for any type of input waveshape. Thus, if we wish to catalog a set of transfer functions, it is most appropriate to show them as functions of s . Special cases where the exclusive use of sinewaves permit s to be replaced by $j\omega$ are easily handled if one has the general form to begin with. If in (6.199) we insert $j\omega$ for s , we have

$$A = \frac{1}{1 - R^2C^2\omega^2 + j3RC\omega} \quad (6.200)$$

The magnitude of this expression is

$$|A| = \frac{1}{\sqrt{(1 + 7R^2C^2\omega^2 + R^4C^4\omega^4)}} \quad (6.201)$$

As in the previous article, the radical is set equal to $\sqrt{2}$ to find ω_0 , the cut-off frequency.

$$\omega_0 = \frac{\sqrt{(-7 + \sqrt{53})}}{\sqrt{(2)RC}} \quad (6.202)$$

This simplifies numerically to

$$\omega_0 = \frac{0.374}{RC} \quad (6.203)$$

We can now let the general frequency $\omega = n\omega_0$, as in the previous article, thus

$$\omega = \frac{0.374n}{RC} \quad (6.204)$$

which can now be substituted back into (6.201) to obtain

$$|A| = \frac{1}{\sqrt{(1 + 0.98n^2 + 0.0196n^4)}} \quad (6.205)$$

Comparing this result with (6.195) in the last article, we see clearly that for values of n from 0 to 1.0, which is the normal pass-band, the gain curve is practically identical for both networks. We see from this analysis that there is no practical advantage in using a two-section network rather than a single-section network for low-pass filters. As far as phase shift is concerned, we note from (6.200) that

$$\phi = -\tan^{-1} \left(\frac{3RC\omega}{1 - R^2C^2\omega^2} \right) \quad (6.206)$$

or, at cut-off, where $\omega = \omega_0$

$$\phi_0 = -52.5^\circ \quad (6.207)$$

which is slightly greater than the -45° for the single section.

We shall now examine the three-section non-tapered case. This last will allow us to draw conclusions on the worth of using many sections rather than a single section for R - C low-pass filter networks.

6.19. Three-section non-tapered R - C low-pass filter

Following the trend of the two previous sections, we shall now derive the cut-off frequency and phase shift for a three-section low-pass R - C filter network. The network under consideration is shown in Fig. 6.34.

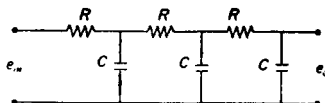


Fig. 6.34

If the reader has not done so already, it is suggested at this point that he write the network equations and determine that the transfer function is

$$Z_T(s) = \frac{1}{R^3C^3s^3 + 5R^2C^2s^2 + 6RCs + 1} \quad (6.208)$$

The next step is to substitute $j\omega$ for s , to give

$$A = \frac{1}{1 - 5R^2C^2\omega^2 + j(6RC\omega - R^3C^3\omega^3)} \quad (6.209)$$

Following the same pattern which has been established in the last two articles, we now write the magnitude of A as

$$|A| = \frac{1}{\sqrt{(R^6C^6\omega^6 + 13R^4C^4\omega^4 + 26R^2C^2\omega^2 + 1)}} \quad (6.210)$$

As before, the quantity inside the radical is set equal to 2.0. This gives

$$R^6C^6\omega^6 + 13R^4C^4\omega^4 + 26R^2C^2\omega^2 - 1 = 0 \quad (6.211)$$

Now physical reasoning (and the trend established by (6.203) and (6.192) earlier), shows us that the term $RC\omega_0$ will be much less than unity. This makes it easy to solve (6.211) by using only the last two terms. Thus

$$\omega_0 = \frac{1}{\sqrt{(26)RC}} \quad (6.212)$$

or

$$\omega_0 = \frac{0.2}{RC} \quad (6.213)$$

Next, we let

$$\omega = n\omega_0 = \frac{0.2n}{RC} \quad (6.214)$$

and insert this term into (6. 211) to have

$$|A| = \frac{1}{\sqrt{(1 + 1.04n^2 + 0.021n^4 + 0.000068n^6)}} \quad (6.215)$$

It will be observed that over the normal pass-band, i.e. where n is between 0 and 1.0, that (6.215) is essentially the same value as the gain function for both the single and double section networks. In fact, if one differentiates (6.215) and determines the slope of the curve at $n = 1$, the increase over a single section will be negligible. The phase shift is given by

$$\phi = -\tan^{-1} \left(\frac{6RC\omega - R^3C^3\omega^3}{1 - 5R^2C^2\omega^2} \right) \quad (6.216)$$

or at $\omega = \omega_0$,

$$\phi_0 = -56^\circ \quad (6.217)$$

The results of the last three sections can be summarized in Table 6.1.

TABLE 6.1. R - C non-tapered low-pass filter data

<i>Number of sections</i>	ω_0	ϕ_0	<i>Amplitude curve (practical, approximate)</i>
1	$\frac{1}{RC}$	-45°	$\frac{1}{\sqrt{(1+n^2)}}$
2	$\frac{0.374}{RC}$	-52°	$\frac{1}{\sqrt{(1+0.98n^2)}}$
3	$\frac{0.2}{RC}$	-56°	$\frac{1}{\sqrt{(1+1.04n^2)}}$

It would appear that the reader who requires a low-pass filter with a sharp cut-off at ω_0 should use some other type than the cascaded R - C sections. We shall develop filters with sharper cut-off characteristics shortly.

The non-tapered n -section R - C network, although of doubtful value as a quality filter, serves admirably for many phase shift problems and purposes. The next article will develop a general method of finding the transfer function of such non-tapered n -section networks.

6.20. Iterative networks

We will consider the detailed investigation of iterative networks in Chapter IX. As a brief introduction however, let us examine here the case where many identical L-sections are cascaded to form involved networks.

Consider the general network shown in Fig. 6.35. Let $Z(s)$ be the series impedance of the network (one section), and let $Y(s)$ be the shunt admittance arms. These may individually be any combination of impedances. (Note only that the sections must be L-shaped, as shown in Fig. 6.35.)

Write a general model for the transfer function as shown in (6.218) below.

$$Z_T(s) = \frac{1}{a + bZY + cZ^2Y^2 + dZ^3Y^3 + \dots + nZ^nY^n} \quad (6.218)$$

To make the problem easy, the coefficients a, b, c, \dots , may be taken from Pascal's triangle, as shown in Fig. 6.36. Pascal's triangle of binomial coefficients is constructed as follows. Draw the two

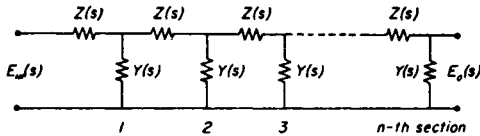


Fig. 6.35

boundary lines of ones, and then note that any number inside the boundary is formed by adding together the number x immediately above it, and x 's neighbor on the right, i.e.

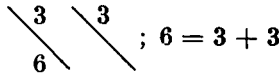


Fig. 6.36 illustrates the preferred construction.

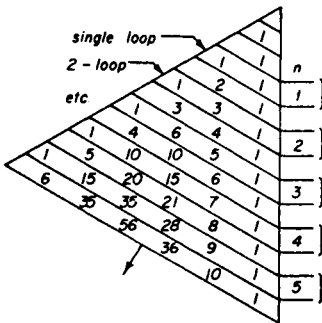


Fig. 6.36

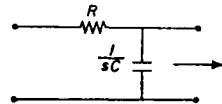


Fig. 6.37

As an example, if one has a five-section, cascaded $R-C$ network, all sections identical, merely choose the downward sloping row of coefficients that corresponds to the number of loops in the network, where each section is as shown in Fig. 6.37. That is

$$Z = R; Y = sC; ZY = RCs \quad (6.219)$$

Looking at Fig. 6.36, we note that there are six coefficients

$$\left. \begin{array}{cccccc} a & b & c & d & e & f \\ 1 & 15 & 35 & 28 & 9 & 1 \end{array} \right\} \quad (6.220)$$

and placing these into the general form

$$Z_T(s) = \frac{1}{1 + 15RCs + 35R^2C^2s^2 + 28R^3C^3s^3 + 9R^4C^4s^4 + R^5C^5s^5} \quad (6.221)$$

The obvious ease of using this method should make it the number one approach whenever identical n -section cascaded networks are encountered. It is noted that $Z(s)$ and $Y(s)$ can both be more involved than shown, without affecting the generality of the method.

PROBLEMS.

(1) Find the transfer function for Fig. 6.34 (in the previous article) by this method. Compare the times required for solution.

(2) Using the Pascal triangle method, find the transfer function of the network shown in Fig. 6.38.

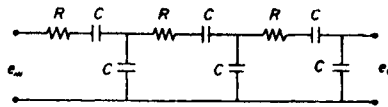


Fig. 6.38

Ans.

$$Z_T(s) = \frac{1}{13 + 19RCs + 8R^2C^2s^2 + R^3C^3s^3} \quad (6.222)$$

(3) Consider the network in Fig. 6.39. Assuming sine wave input, will there be any phase shift in this network? Justify your answer

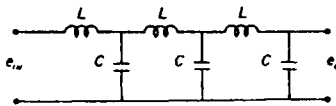


Fig. 6.39

by showing the presence or absence of j -terms in the transfer function.

6.21. Initial conditions in network parameters

When using the Laplace transform as a means of circuit analysis, we consider the action to begin at time $t = 0$. This follows from the basic defining integral. Excitation functions are tacitly assumed to begin at $t = 0$ even though we do not always say so in specific terms. Of course this situation is good, as the Laplace transform method of analysis will give us transient responses as well as the steady state response.

There are several situations which occur that we have not discussed formally up to this time. We refer here to the problems of initial conditions, and to the subject of mutual inductance.

It has been considered better to omit these topics during the formal development of the abstract material, and to present them at this point, since we are now working with actual networks in this chapter, and initial conditions usually are of importance only in practice.

The subject of mutual inductance and how to handle it mathematically is very hazy to many electronic engineers. One of the difficulties probably lies in the numerous definitions, special handbook formulas, and available methods of working problems where mutual inductance is involved. We shall attempt in the next few articles to present the most simple method of dealing with mutual inductance problems in networks.

First, however, let us examine some cases where initial conditions occur. Since this book is written for electronics people, we shall attempt to cover initial conditions by means of practical electronic examples, rather than to develop an isolated abstract theory.

6.22. Initial charge or voltage on condenser

Earlier in the text we discussed the relation between capacity, voltage and current. Suppose, however, that we now have the condenser charged to some fixed voltage α at the time we begin our analysis. This is shown in Fig. 6.40. Now by the most basic definition, we have the relation

$$i(t) = C \frac{de(t)}{dt} \quad (6.223)$$

We now take the Laplace transform of this equation, making certain that we use the complete form for the transform of the

derivative, as given in (3.64). This general form is

$$\mathcal{L} \left[\frac{df(t)}{dt} \right] = sF(s) - f(0) \quad (6.224)$$

where we recall that the $f(0)$ was the value of $f(t)$ at time $t = 0$, when approached from the right. Using this form, (6.223) transforms into

$$I(s) = C[sE(s) - \alpha] \quad (6.225)$$

where we see that α is $e(t)$ at $t = 0$, i.e. the initial voltage on the condenser. (One could deal with initial charge just as easily by

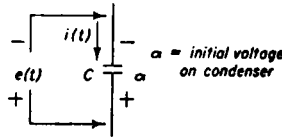


Fig. 6.40

noting that charge is voltage times capacity.) Let us multiply out (6.225) to obtain

$$I(s) = sC \cdot E(s) - \alpha C \quad (6.226)$$

Each item in (6.226) should be labeled as follows:

$I(s)$ = transformed current

sC = transformed admittance (Y)

$E(s)$ = transformed voltage

αC = current.

The only term which might be questioned is the last, αC . Note, however, that αC must have the dimension of current to be consistent with the other two terms in (6.226). We know, of course, that in the time domain the term αC (voltage times capacity) always equals charge. Thus we must remember that charge in the time-world goes over into current in the s -world.

Equation (6.226) can best be illustrated circuit-wise by the single node diagram shown in Fig. 6.41.

Somehow or other, many electronics engineers seem to prefer to deal with mesh equations rather than node equations. We should

therefore also examine the integral equivalent of (6.223) to develop a diagram suitable for mesh analysis. Observe that in general

$$e(t) = \frac{1}{C} \int_0^t i(t) dt + \alpha \tag{6.227}$$

and that this transforms into

$$E(s) = \frac{I(s)}{sC} + \frac{\alpha}{s} \tag{6.228}$$

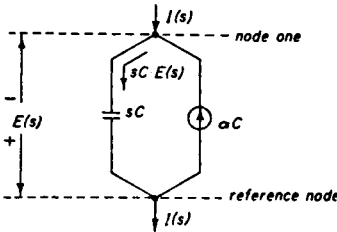


Fig. 6.41

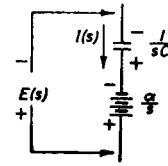


Fig. 6.42

Further, observe that since the left-hand side is a voltage, the right-hand side must be the sum of two voltages, i.e. two voltages connected in series. This leads us to the transformed diagram shown in Fig. 6.42. We shall use some examples to further illustrate these concepts after we consider initial current in an inductance.

6.23. Initial current in an inductance

Let us consider the inductance shown in Fig. 6.43, which carries a current ρ at time $t = 0$. The most basic way of relating the parameters is

$$e(t) = L \frac{di(t)}{dt} \tag{6.229}$$

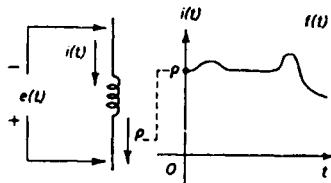


Fig. 6.43

Performing the transformation, and keeping the complete derivative we have

$$\mathcal{L}[e(t)] = L\mathcal{L}\left[\frac{di(t)}{dt}\right] \tag{6.230}$$

which becomes

$$E(s) = L[sI(s) - \rho] \quad (6.231)$$

This is next multiplied out to give

$$E(s) = sL \cdot I(s) - \rho L \quad (6.232)$$

It is to be noted that, dimension-wise

$E(s)$ = transformed voltage

sL = transformed impedance

$I(s)$ = transformed current

ρL = voltage.

The term ρL must be called a voltage to be consistent with the other two terms. We observe with interest that

$$e = L \frac{di}{dt} = N \frac{d\phi}{dt} \quad (6.233)$$

and for a linear inductance, that

$$L = N \cdot \frac{\phi}{i} \quad (6.234)$$

Now ρ was defined as a current, and if we multiply (6.234) by ρ we have

$$\rho L = \frac{\rho N \phi}{i} \quad (6.235)$$

which, dimension-wise, is

$$\rho L = \frac{\text{current} \cdot N\phi}{\text{current}} \quad (6.236)$$

Thus we can say, if someone should press us for details, that ρL represents the flux linkages in the coil at time $t = 0$.

Equation (6.232) can be illustrated circuit-wise as shown in Fig. 6.44, where ρL is shown in the transformed circuit as a "transformed" battery.

Whenever an initial current appears in an inductance which is part of a network to be analyzed, the new network in the s -plane can show a voltage source ρL in series with the inductance. The circuit

then can be treated as any other simple network that contains numerous voltage sources.

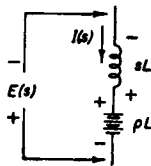


Fig. 6.44

EXAMPLE. Let us now consider a series $R-L-C$ circuit, to illustrate both cases of initial conditions. This is shown in Fig. 6.45. In this example, ρ represents an initial current flowing in the coil at $t = 0$, and α represents an initial voltage on the condenser at $t = 0$.

By the use of our "transformed battery" concept, it is easy to draw the s -plane equivalent circuit, shown in Fig. 6.46. It should

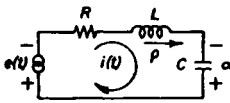


Fig. 6.45

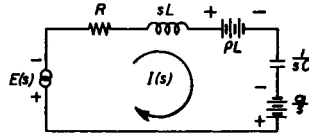


Fig. 6.46

now be easy to write the one Kirchoff's law equation around this loop, and this equation is

$$\left(E + sL + \frac{1}{sC} \right) I(s) = E(s) + \rho L - \frac{\alpha}{s} \quad (6.237)$$

The desired response, $I(s)$, is then

$$I(s) = \frac{E(s) + \rho L - \alpha/s}{R + sL + 1/sC} \quad (6.238)$$

Now observe that (6.238) can be written in the form

$$I(s) = \frac{E(s)}{R + sL + 1/sC} + \frac{(\rho L - \alpha/s)}{R + sL + 1/sC} \quad (6.239)$$

or

$$I(s) = I_1(s) + I_2(s) \quad (6.240)$$

Note that $I_1(s)$ is the component of I due to the driving function. This yields both steady-state and transient solutions. $I_2(s)$ is the current component due to the initial conditions, and can only yield a transient solution.

To continue our example, suppose we should choose a specific input voltage

$$e(t) = U(t) \quad (6.241)$$

so that

$$E(s) = \frac{1}{s} \quad (6.242)$$

Let us look first at $I_1(s)$, which becomes

$$I_1(s) = \frac{1}{Ls^2 + Rs + 1/C} \quad (6.243)$$

$I_1(s)$ will have no zeros, but will have poles at

$$s = \frac{-R \pm j\sqrt{(4L/C - R^2)}}{2L} \quad (6.244)$$

or in other words, $I_1(s)$ has the form

$$I_1(s) = \frac{1}{(s + \alpha + j\beta)(s + \alpha - j\beta)} \quad (6.245)$$

This has a pole-zero diagram shown in Fig. 6.47. Thus, by merely inspecting Fig. 6.47, we see that the application of $U(t)$ creates an exponentially decaying sinewave of current.

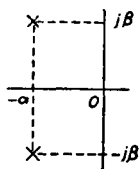


Fig. 6.47

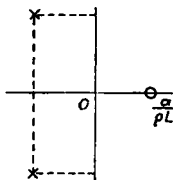


Fig. 6.48

We can now examine the $I_2(s)$ component. In this case

$$I_2(s) = \frac{\rho L - \alpha/s}{R + sL + 1/sC} \quad (6.246)$$

Multiplying both numerator and denominator by s gives

$$I_2(s) = \frac{(\rho Ls - \alpha)}{Ls^2 + Rs + 1/C} \quad (6.247)$$

The pole-zero diagram for $I_2(s)$ is now shown in Fig. 6.48.

We see here that in addition to the same two complex conjugate poles, we now have a zero on the positive σ -axis. Notice that the zero location does not determine the response, but only the magnitude and phase of the response. Since there are no poles on the vertical axis, or at the origin, there is no steady-state response.

It will be recalled again that a single pole at the origin represents

a steady d.c.; complex poles on the $j\omega$ -axis represent a steady a.c. sinewave; and complex conjugate poles in the left half-plane represent an exponentially decaying sinewave.

PROBLEM. Using the same symbols that we have employed in the last two articles, draw the transformed network of Fig. 6.49. Write the two loop equations as functions of s .

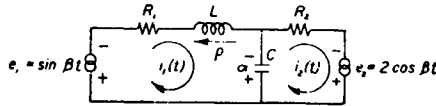


Fig. 6.49

6.24. Mutual inductance

It has been the writer's experience that many electronics engineers have a somewhat nebulous understanding of mutual inductance. In fact, some circuit design engineers have been observed to devise alternate, more elaborate networks just to avoid coupling two coils together. In a few such cases, the feeling seemed to be that mutual inductance was some uncertain, troublesome, unfriendly characteristic which should be avoided if at all possible.

It is unfortunate that such hesitancy should ever occur, but perhaps it is the result of lack of attention to the concept of mutual inductance in the engineer's early formulative courses in circuit theory. At any rate, to quote a more famous author, "circuit analysis is the engineer's bread and butter", so in this article we want to develop a logical, consistent and easily remembered way to handle mutual inductance in circuit analysis problems.

One more comment before we proceed: in view of the known facts about atoms and their behavior which were not available a century ago, the writer finds it most difficult to consider a "current" in a conductor which is something other than an electron flow. It is gratifying then, to observe that more and more authors are coming to accept "current" and "electron flow" to be one and the same thing. This in spite of much opposition from science teachers and engineering professors who should know better.

Having expressed the foregoing views, it is easy to see that if we label the inductance shown in Fig. 6.50 as an impedance sL , then application of a voltage e as shown will cause a current i to flow through the impedance as shown in Fig. 6.50.

The same signs and directions apply for any impedance. Many years ago, before much was understood about impedance, one had to invent devices such as "back e.m.f." to explain part of the relation between e and i . This "induced back voltage" was supposed to be opposite in sign from the applied voltage, and to this day causes no end of confusion.

The reader who has successfully studied the preceding portion of this text will assert that sL is a completely general impedance,

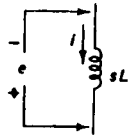


Fig. 6.50

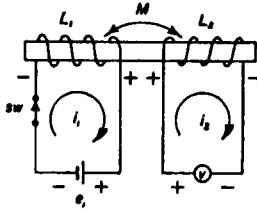


Fig. 6.51

expressing exactly and at all times the ratio e/i . This makes it unnecessary to consider such terms as "back e.m.f." further.

Suppose we redraw the coil pictorially, showing a mutually coupled coil and a switch to initiate a current in L_1 (see Fig. 6.51). The reader should now determine to his satisfaction that the meter



Fig. 6.52

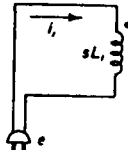


Fig. 6.53

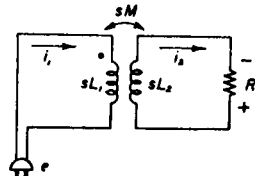


Fig. 6.54

will read up-scale immediately following closure of the switch, and that all polarities are correct as shown.

On a schematic, or network diagram, it is customary to employ small dots to indicate the ends of two or more coils which have the same instantaneous polarity. Thus Fig. 6.51 could be shown as in Fig. 6.52. L_1 might be the primary of a power transformer as shown in Fig. 6.53, with L_2 far removed and not loaded, that is, $i_2 = 0$.

If we should now place a load R across L_2 and move it close to L_1 , then M assumes a value, as in Fig. 6.54. We see that the induced

current in the secondary loop reduces the total impedance in the primary loop, because where in Fig. 6.53 we had

$$e = sL_1 i \tag{6.248}$$

or

$$Z_{IN} = sL_1 \tag{6.249}$$

in Fig. 6.54 we have

$$\left. \begin{aligned} e &= sL_1 i_1 - sM i_2 & (a) \\ 0 &= -sM i_1 + (sL_2 + R) i_2 & (b) \end{aligned} \right\} \tag{6.250}$$

Assume a turns-ratio of one to one, in which case $L_2 = L_1$ and $i_2 = i_1$, then (6.250(a)) becomes

$$e = s(L_1 - M) i_1 \tag{6.251}$$

This says that the input impedance e/i_1 is

$$Z_{IN} = s(L_1 - M) \tag{6.252}$$

M appears then to reduce the value of primary impedance, which we know to be a fact in actual reality. In writing the loop equations around loop one in Fig. 6.54 then, we consider the mutual current to be minus in the mathematical sense, as M does not, of course, represent a negative inductance.

RULE. We may formulate a general rule from the foregoing, as follows:

(a) If the current in loop j enters the dot end of an inductance in loop j , and a current in loop k leaves the dot end of an inductance in loop k , then i_{jk} is considered minus for combining with a mutual inductance M_{jk} .

(b) If the current in loop j enters the dot end of an inductance in loop j , and a current in loop k enters the dot end of an inductance in loop k , then the mutual current i_{jk} is considered plus for combining with a mutual inductance M_{jk} .

The rule is somewhat awkward when stated in words, but is easy to understand and memorize when illustrated with several examples.

EXAMPLE 1. Note that we sometimes write e and i as functions of time, while expressing impedances as functions of s . This is permissible if we recall that s is an operator, and provided we transform e and i into functions of s before doing anything else with such

“mixed” equations. The equations for the network shown in Fig. 6.55 are, using the above rules,

$$\left. \begin{aligned} e_1 &= sL_1 i_1 - sM i_2 \\ -e_2 &= -sM i_1 + sL_2 i_2 \end{aligned} \right\} \quad (6.253)$$

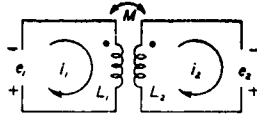


Fig. 6.55

EXAMPLE 2. Using the given rules, the equations for the circuit shown in Fig. 6.56 are:

$$e_1 = (sL_1 + R_1)i_1 - (R - sM)i_2 \quad (6.254)$$

$$0 = -(R - sM)i_1 + (R_1 + R_2 + sL_2)i_2 \quad (6.255)$$

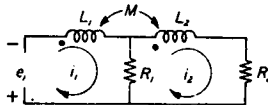


Fig. 6.56

EXAMPLE 3. (See Fig. 6.57.) The equations are:

$$e_1 = (sL_1 + R_1)i_1 - (R_1 + sM)i_2 \quad (6.256)$$

$$0 = -(R_1 + sM)i_1 + (R_1 + R_2 + sL_2)i_2 \quad (6.257)$$

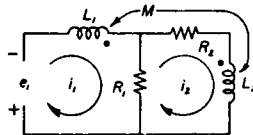


Fig. 6.57

Short digression on flux-linkages. Note carefully that an initial current in one loop will combine through any mutual inductance to form a transformed battery in the other loop (in addition to combining with inductance in its own loop).

We have shown that the transformed battery can be considered as a flux linkage. This fact can be used to determine which way to

show polarities. Let us examine Fig. 6.58. The physical shape of the coil determines the placement of the dots. The initial current ρ_1 in L_1 generates the transformed battery $\rho_1 L_1$ with polarity as shown. This direction is not obvious by inspection, but was determined from (6.232) and the use of Fig. 6.44 as a model.

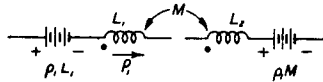


Fig. 6.58

If we now realize that flux linkages which are mutual to both coils will affect both coils in the same way, we observe that the current ρ_1 which causes flux linkages $\rho_1 L_1$ in coil L_1 must, by sharing flux linkage with L_2 , set up a transformed battery $\rho_1 M$ of the same polarity with respect to the dots. We are now in a position to consider example 4.

EXAMPLE 4. Fig. 6.59 shows a somewhat more involved situation where initial currents are present in the inductances. Writing the

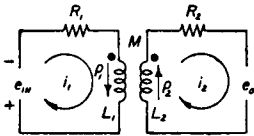


Fig. 6.59

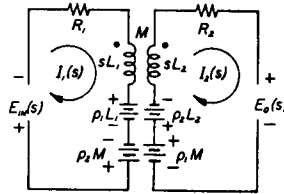


Fig. 6.60

equations as functions of s will be simple if we plan the approach carefully. First, let us draw the transformed circuit, using the “transformed battery” concept of art. 6.23. First, we note that the rule for mutual currents shows that

$$i_{12} = i_{21} = (\text{minus}) \tag{6.258}$$

Then we proceed to write the equations directly as functions of s . These are

$$(R_1 + sL_1)I_1(s) - sMI_2(s) = E_{IN}(s) + \rho_1 L_1 - \rho_2 M \tag{6.259}$$

$$-sMI_1(s) + (R_2 + sL_2)I_2(s) = E_0(s) + \rho_2 L_2 - \rho_1 M \tag{6.260}$$

EXAMPLE 5. Let us consider the network shown in Fig. 6.61. We will assume that the switch closes at $t = 0$.

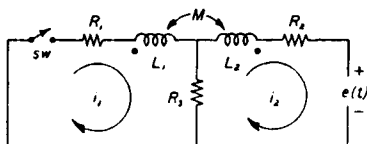


Fig. 6.61

As initial conditions, let us further assume that at time $t = 0$

$$\left. \begin{aligned} i_1(0) &= 0 \\ i_2(0) &= -\rho \end{aligned} \right\} \quad (6.261)$$

It will be noted that by the rule, the mutual current i_{12} and i_{21} will be minus for M (also the mutual current in R_3 will be minus by inspection). The transformed diagram is drawn in Fig. 6.62. Note

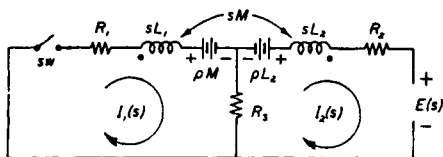


Fig. 6.62

that there is no transformed battery ρM in loop 2 as $i_1(0) = 0$, but the transformed ρM does appear in loop 1, due to M and the initial current ρ in loop 2. The equations are:

$$(R_1 + R_3 + sL_1)I_1(s) - (R_3 + sM)I_2(s) = \rho M \quad (6.262)$$

$$-(R_3 + sM)I_1(s) + (R_2 + R_3 + sL_2)I_2(s) = E(s) - \rho L_2 \quad (6.263)$$

Application of the concepts presented in this chapter should permit the reader to undertake rigorous analyses of almost any of the networks in general use, and allow him to begin work on special configurations for his own special requirements as time goes by.

CHAPTER VII
TRANSFORMS OF SPECIAL WAVESHAPES
AND PULSES

7.1. Introduction

Up to this point in the text we have been concerned primarily with developing the mathematical theory of the Laplace transformation, presenting the various theorems which make the theory useful in practice, and learning to work with transfer functions in the s -plane. Except for having taken the transforms of sine waves and the unit step function, there has been little discussion of the wide variety of possible excitation functions which are encountered in everyday work.

In this chapter we will develop the transforms for a number of such waveshapes and pulses. We will also develop a few new theoretical concepts as appropriate. It will obviously not be possible to give detailed examples of the application of each waveshape transform developed here to every transfer function that has been discussed, but several selected examples will illustrate typical applications to electronic engineering problems.

7.2. Laplace transform of a displaced step function

It was found in Chapter V that the transform of the unit step function $U(t)$ is

$$\mathcal{L}[U(t)] = \frac{1}{s} \tag{7.1}$$

It was also observed that such a function of s , having a pole at the origin, always inserts a d.c. component of voltage or current into the time function output. The displaced step function shown in Fig. 7.1 was also discussed briefly in Chapter V.

The corresponding function of s was written as

$$F(s) = \int_0^{\infty} U(t - a)\varepsilon^{-st} dt = \int_a^{\infty} \varepsilon^{-st} dt \tag{7.2}$$

which then became

$$\mathcal{L}[U(t - a)] = \frac{\varepsilon^{-as}}{s} \quad (7.3)$$

This result can now be employed to find the Laplace transform of the rectangular pulse shown in Fig. 7.2. This pulse can be expressed as

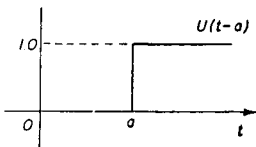


Fig. 7.1

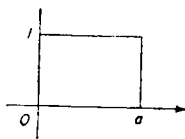


Fig. 7.2

a function of time by writing

$$f(t) = U(t) - U(t - a) \quad (7.4)$$

and by using (7.1) and (7.3) it is easily seen that

$$F(s) = \frac{1}{s} - \frac{\varepsilon^{-as}}{s} = \frac{1 - \varepsilon^{-as}}{s} \quad (7.5)$$

EXAMPLE. In the design of small mechanical and electronic devices for use in guided missiles, it is usually necessary to know whether or not the device will successfully withstand the high shock during acceleration when the missile is launched.

Actual shock patterns present during a launching are usually available for numerous points on the missile structure. Such patterns are obtained by recording the electrical output of accelerometers that have been placed at the selected points on the structure, and accumulating the data for the entire structure over a period involving many launchings.

An individual shock pattern, for a particular location of interest, is played back from a tape recording (with instantaneous voltage corresponding to instantaneous acceleration in g 's) into a shock spectrum computer. The shock spectrum computer then furnishes four separate functions of acceleration v. frequency, namely:

- (1) positive during the shock
- (2) negative during the shock
- (3) positive after the shock
- (4) negative after the shock

Now the electronics engineer may wish to mount a small wiring assembly, bracket, switch or vacuum tube device at this particular point on the missile. Suppose the item is a small, simple bracket. The engineer either knows the resonant frequency of the bracket assembly or he can find it by a simple test. Knowing the resonant frequency, the engineer merely looks at the shock spectrum chart and reads the acceleration which would occur on the part at the frequency involved, if the part should indeed be mounted at the location involved. He can thus decide prior to actually mounting the part and making a test whether the arrangement would be suitable, or whether it would shear off and fail in practice.

In this somewhat lengthy example, we will limit our interest to such a shock spectrum computer. The computer is, in essence, the electronic equivalent of a mechanical mass-spring oscillating system, which can be adjusted in steps to resonate over the entire frequency range of interest. It is thus the equivalent also of an entire set of vibrating reed type accelerometers, except that such reeds can give only very limited information from brief shock impulses.

An actual shock spectrum computer is synthesized from R - C networks and active feedback elements, but in principle, we can use

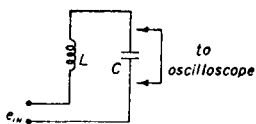


Fig. 7.3

a pure inductance and capacity to illustrate the problem, as shown in Fig. 7.3.

If the system is excited by the recorded shock pattern, the response will be presented on the oscilloscope screen, which is calibrated in g units. Now by using form 5, Appendix I(b), we see that the transfer function for the network of Fig. 7.3 is

$$Z_T(s) = \frac{1}{LCs^2 + 1} \quad (7.6)$$

It is necessary for the electronics engineer to have some standard test to determine whether or not the computer is working properly, and for use in calibration. Such a test often involves the application of a rectangular acceleration (voltage) input to the computer. Thus,

the task in this example is to find the computer response to the voltage pulse shown in Fig. 7.2. By definition, it is seen that

$$E_0(s) = Z_T(s)E_{IN}(s) \quad (7.7)$$

or

$$E_0(s) = \frac{1 - \varepsilon^{-as}}{LCs \left(s^2 + \frac{1}{LC} \right)} \quad (7.8)$$

The denominator can be factored to give

$$E_0(s) = \frac{1}{LC} \cdot \frac{(1 - \varepsilon^{-as})}{s \left(s + j \frac{1}{\sqrt{LC}} \right) \left(s - j \frac{1}{\sqrt{LC}} \right)} \quad (7.9)$$

or

$$E_0(s) = \frac{\omega^2(1 - \varepsilon^{-as})}{s(s + j\omega)(s - j\omega)} \quad (7.10)$$

where we let

$$\omega = \frac{1}{\sqrt{LC}} \quad (7.11)$$

We are now ready to determine $e_0(t)$, which may be found by using the line integral of the inverse transformation.

$$e_0(t) = \frac{\omega^2}{2\pi j} \oint \frac{(1 - \varepsilon^{-as})\varepsilon^{ts} ds}{s(s + j\omega)(s - j\omega)} \quad (7.12)$$

This is separated into two integrals as

$$e_0(t) = \underbrace{\frac{\omega^2}{2\pi j} \oint \frac{\varepsilon^{ts} ds}{s(s + j\omega)(s - j\omega)}}_{f(t)} - \underbrace{\frac{\omega^2}{2\pi j} \oint \frac{\varepsilon^{-as}\varepsilon^{ts} ds}{s(s + j\omega)(s - j\omega)}}_{f(t-a)U(t-a)} \quad (7.13)$$

Only single order poles are involved, and it is easily found that the two integrals give

$$e_0(t) = [1 - \cos \omega t] - [1 - \cos \omega(t - a)] \quad (7.14)$$

or

$$e_0(t) = \cos \omega(t - a) - \cos \omega t \quad (7.15)$$

This is the time response to a unit shock of duration a , where ω is the frequency to which the computer is tuned. Equation (7.15) can be manipulated into the form

$$e_0(t) = 2 \sin\left(\frac{\omega a}{2}\right) \cdot \sin\left(\omega t - \frac{\omega a}{2}\right) \tag{7.16}$$

Note that since the second integral in (7.13) gives a function multiplied by $U(t - a)$, equation (7.16) must be interpreted as the response of the computer after the shock. The response during the shock is given by the first bracketed term in (7.14).

Examining (7.16), we see that for shocks which are narrow compared with period T of the computer, the maximum acceleration after removal of the shock is

$$|e_0(t)|_{\max} = \frac{2\pi a}{T} \tag{7.17}$$

while for other applied shocks, the highest acceleration after the shock is finished is given by

$$|e_0(t)|_{\max} = 2 \sin\left(\frac{\pi a}{T}\right) \tag{7.18}$$

It is interesting to note that if the input pulse represents say, 100 g , up to 200 g may be applied to small parts mounted at the location in question. Equation (7.18) shows that the negative slope of the excitation at $t = a$ can remove all or part of the acceleration on the component, or leave it unchanged.

7.3. Transform of the dirac delta function

The delta function $\delta(t)$ is useful for many purposes. It may be defined by

$$\left. \begin{aligned} \delta(t) &= 0, \quad t \neq 0 \\ \int_{-\infty}^{\infty} \delta(t) dt &= 1 \end{aligned} \right\} \tag{7.19}$$

An equally valid definition is

$$\left. \begin{aligned} \delta(t) &= 0, \quad t < 0 \\ \delta(t) &= \lim_{\alpha \rightarrow \infty} \alpha e^{-\alpha t}, \quad t > 0 \end{aligned} \right\} \tag{7.20}$$

Still another definition, used often in connection with sampling electronic functions is

$$\delta(t) = \lim_{a \rightarrow 0} \frac{1}{a} [U(t) - U(t - a)] \tag{7.21}$$

This last definition is illustrated in Fig. 7.4.

It will be noted that (7.5), the transform of the rectangular pulse of unit height, can be multiplied by $1/a$ to give the transform of Fig. 7.4 directly thus

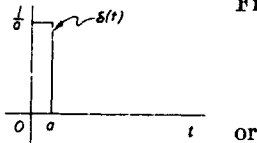


Fig. 7.4

$$\mathcal{L}[\delta(t)] = \lim_{a \rightarrow 0} \frac{1 - e^{-as}}{as} \tag{7.22}$$

$$\mathcal{L}[\delta(t)] = 1 \tag{7.23}$$

The delta function is also sometimes called the unit impulse.

PROBLEM. Find $\mathcal{L}[\delta(t - a)]$.

7.4. Derivatives of infinite slopes expressed as delta functions

Suppose we are given $f_a(t)$ as in Fig. 7.5. This is essentially the same function as $f(t)$ shown in Fig. 7.6 if τ is made very small. The

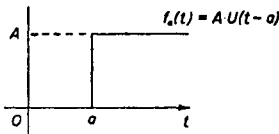


Fig. 7.5

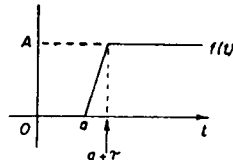


Fig. 7.6

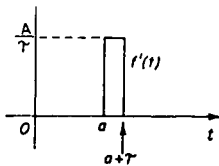


Fig. 7.7

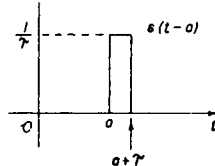


Fig. 7.8

derivative of $f(t)$ is illustrated in Fig. 7.7. Now let us examine the delta function $\delta(t - a)$ shown in Fig. 7.8. By comparing Fig. 7.8 with Fig. 7.7, it is noted that the height of $f'(t)$ is A times the height

of the δ -function, and since both are the same width τ , it follows that

$$f'(t) = A\delta(t - a) \tag{7.24}$$

and since A is the value of $f(a)$ from Fig. 7.5, (7.24) becomes

$$f'(t) = f(a)\delta(t - a) \tag{7.25}$$

Now $f(a)$ will be some constant, and thus we can differentiate any step function and express the result as a constant times a δ -function,

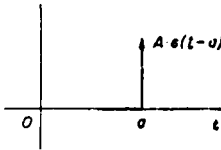


Fig. 7.9

as in (7.25). The derivative in Fig. 7.1 is usually drawn and labeled as in Fig. 7.9. For the unit δ -function, the A in Fig. 7.9 would be 1.0.

7.5. Sampling another function with a delta function

Suppose we have a function $f(t)$ as shown in Fig. 7.10, and sample it by the δ -function also shown. (This means that the functions are

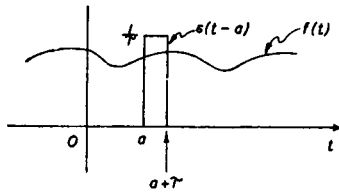


Fig. 7.10

multiplied point by point along the t -axis.) Having multiplied the two functions point by point, we observe that the integral of the result is

$$\int_{\phi_1}^{\phi_2} f(t)\delta(t - a) dt = \int_{\phi_1}^a 0 \cdot dt + \int_a^{a+\tau} f(a)\delta(t - a) dt + \int_{a+\tau}^{\phi_2} 0 \cdot dt \tag{7.26}$$

or, since the first and last terms on the right are zero, and since the $f(a)$ in the center term is a constant and can be brought outside the integral, then

$$\int_{\phi_1}^{\phi_2} f(t)\delta(t - a) dt = f(a) \int_a^{a+\tau} \delta(t - a) dt = f(a) \tag{7.27}$$

ϕ_1 and ϕ_2 can be any values, infinite or finite, as long as they are on opposite sides of $t = a$.

7.6. Fourier coefficients ascertained by means of delta functions

Let us assume that we have an even periodic waveshape, that is, one which is symmetrical about the j -axis. Such a function will be composed of harmonics which are cosine terms. We can express such even functions as

$$f(x) = \sum_{n=0}^{\infty} a_n \cos nx \quad (7.28)$$

Both sides can now be multiplied by $\cos mx$ to give

$$f(x) \cos mx = \cos mx \sum_{n=0}^{\infty} a_n \cos nx \quad (7.29)$$

If both sides are now integrated over one period of the waveform, that is, from $-\pi$ to π ,

$$\int_{-\pi}^{\pi} f(x) \cos mx \, dx = \int_{-\pi}^{\pi} \cos mx \sum_{n=0}^{\infty} a_n \cos nx \, dx \quad (7.30)$$

it is shown in texts on circuit analysis that the right-hand integral will be zero except where $n = m$, in which case the integral becomes equal to $a_n\pi$. Therefore

$$a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \cos nx \, dx \quad (7.31)$$

This formula allows us to find any Fourier coefficient a_n if the function $f(x)$ is known. It is also possible to solve for a_n in terms of derivatives of $f(x)$. Thus, starting with (7.28), we can differentiate to obtain

$$f'(x) = - \sum_{n=0}^{\infty} na_n \sin nx \quad (7.32)$$

which is next multiplied by $\sin mx$, and then integrated over a full period as before.

$$\int_{-\pi}^{\pi} f'(x) \sin mx \, dx = - \int_{-\pi}^{\pi} \sin mx \sum_{n=0}^{\infty} na_n \sin nx \, dx \quad (7.33)$$

The reader can easily show, as in the case before, that the right-hand integral is zero for every value of n except $n = m$, and that for this case the integral is $-na_n\pi$. Thus (7.33) becomes

$$a_n = -\frac{1}{n\pi} \int_{-\pi}^{\pi} f'(x) \sin nx \, dx \tag{7.34}$$

Starting again with (7.28), we can differentiate twice to obtain

$$f''(x) = -\sum_{n=0}^{\infty} n^2 a_n \cos nx \tag{7.35}$$

This can be multiplied by $\cos mx$ and integrated as before to solve for a_n , which is

$$a_n = -\frac{1}{n^2\pi} \int_{-\pi}^{\pi} f''(x) \cos nx \, dx \tag{7.36}$$

These formulas are now consolidated in Table 7.1.

TABLE 7.1

$$a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \cos nx \, dx$$

$$a_n = -\frac{1}{n\pi} \int_{-\pi}^{\pi} f'(x) \sin nx \, dx$$

$$a_n = -\frac{1}{n^2\pi} \int_{-\pi}^{\pi} f''(x) \cos nx \, dx$$

$$a_n = \frac{1}{n^3\pi} \int_{-\pi}^{\pi} f'''(x) \sin nx \, dx, \text{ etc.}$$

Now observe that if we can express $f(x)$ or any of its derivatives as a sum of δ -function, we can use (7.27) to write

$$\int_{-\pi}^{\pi} f^n(x) \delta(x - \tau) \, dx = \begin{cases} f(\tau) & \text{if } -\pi < \tau < \pi \\ 0 & \text{for } \tau \text{ otherwise} \end{cases} \tag{7.37}$$

Thus, for example, (7.36) can be written as

$$a_n = -\frac{1}{n^2\pi} [\cos n\tau_1 \cdot \delta(x - \tau_1) + \cos n\tau_2 \cdot \delta(x - \tau_2) + \dots] \tag{7.38}$$

where each cosine term is caused by one δ -function.

EXAMPLE. Let us apply the concepts presented in this article to find the Fourier coefficients of the waveform, one period of which is

shown in Fig. 7.11. In order to use one of the forms shown in Table 7.1, it will first be necessary to see if we can express some derivative of $f(x)$ as a set of δ -functions. Let us draw the first derivative of $f(x)$ as shown in Fig. 7.12.

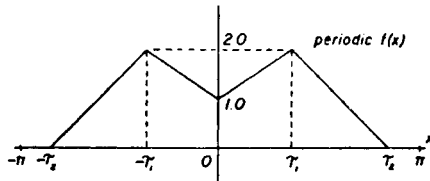


Fig. 7.11

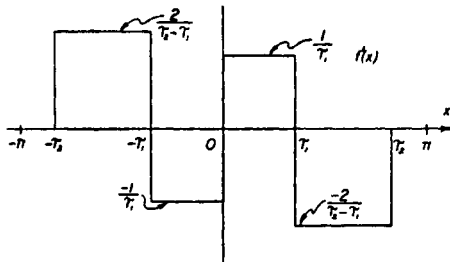


Fig. 7.12

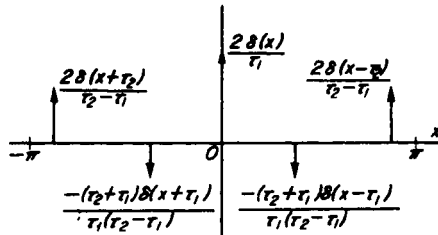


Fig. 7.13

Thus far no delta functions have appeared, but taking the second derivative will result in a set of δ -functions, as shown in Fig. 7.13. We may now choose the form given by (7.36) or (7.38) and write

$$a_n = -\frac{1}{n^2\pi} \left[\frac{2}{(\tau_2 - \tau_1)} \cos(-n\tau_2) - A \cos(-n\tau_1) + \frac{2}{\tau_1} \cos(0) - A \cos(n\tau_1) + \frac{2}{(\tau_2 - \tau_1)} \cos(n\tau_2) \right] \quad (7.39)$$

Where
$$A = \frac{\tau_2 + \tau_1}{\tau_2(\tau_2 - \tau_1)}$$

It will be recalled that the cosine of minus angles equals the cosine of the same positive angles, which allows several simplifications, therefore

$$a_n = \frac{2}{n^2\pi} \left[\frac{(\tau_2 + \tau_1)}{\tau_1(\tau_2 - \tau_1)} \cos n\tau_1 - \frac{2 \cos n\tau_2}{\tau_2 - \tau_1} - \frac{1}{\tau_1} \right] \quad (7.40)$$

This allows any coefficient to be found directly.

PROBLEM. The reader is now requested to analyze Fig. 7.11 by the usual Fourier transform method to determine the coefficients of the resulting series; reduce the results to (7.40), compare the time and labor required, and decide the merits of articles 7.5 and 7.6.

7.7. The Laplace transform of a series of pulses

Consider the periodic pulse train illustrated in Fig. 7.14, where the period is T , pulse width is a , and height is unity. The entire train

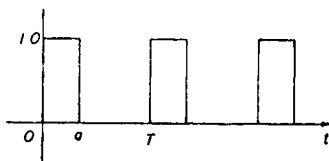


Fig. 7.14

of pulses, $f(t)$, can be expressed as a sum of displaced step functions, and is written as

$$\begin{aligned} f(t) = & U(t) - U(t - a) \\ & + U(t - T) - U(t - T - a) \\ & + U(t - 2T) - U(t - 2T - a) \\ & + \dots \end{aligned} \quad (7.41)$$

By the use of equation (7.3), we can transform term by term into $F(s)$, so that

$$F(s) = \frac{1}{s} - \frac{e^{-as}}{s} + \frac{e^{-Ts}}{s} - \frac{e^{-(T+a)s}}{s} + \frac{e^{-2Ts}}{s} - \frac{e^{-(2T+a)s}}{s} + \dots \quad (7.42)$$

By grouping alternate terms, this can be factored as follows:

$$F(s) = \frac{1}{s} [1 + \varepsilon^{-Ts} + \varepsilon^{-2Ts} + \varepsilon^{-3Ts} + \dots] \\ - \frac{\varepsilon^{-as}}{s} [1 + \varepsilon^{-Ts} + \varepsilon^{-2Ts} + \varepsilon^{-3Ts} + \dots] \quad (7.43)$$

It is observed that both bracketed terms are identical, so these may now be factored out to give

$$F(s) = \frac{1}{s} [1 - \varepsilon^{-as}] [1 + \varepsilon^{-Ts} + \varepsilon^{-2Ts} + \varepsilon^{-3Ts} + \dots] \quad (7.44)$$

It is further recognized that the infinite series on the right is an expansion of the form

$$\frac{1}{1-x} = 1 + x + x^2 + x^3 + x^4 + \dots \quad (7.45)$$

hence, (7.44) simplified, is

$$F(s) = \frac{1 - \varepsilon^{-as}}{s(1 - \varepsilon^{-Ts})} \quad (7.46)$$

which is the compact expression for the Laplace transform of the periodic train of pulses. Equation (7.46) is general, as pulses of any height A can be transformed simply by carrying the A through as a constant multiplier.

PROBLEM 1. Show that the square wave having amplitudes 0 and A , and period T , has for its transform

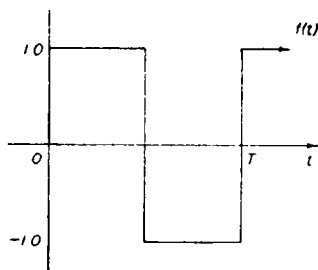


Fig. 7.15

$$F(s) = \frac{A}{s \left(1 + \varepsilon^{-\frac{T}{2}s}\right)} \quad (7.47)$$

PROBLEM 2. Show that the square wave pictured in Fig. 7.15 has the transform

$$F(s) = \frac{\tanh\left(\frac{T}{4}s\right)}{s} \quad (7.48)$$

Note: It would appear from (7.48) that we have a pole at $s = 0$, but notice that for small values of s , the tanh of the argument approaches the argument, thus

$$F(0) = \frac{T}{4} \tag{7.49}$$

and not ∞ , as would be required for a pole. Since no pole exists at zero, no d.c. term is present, as is obvious from looking at Fig. 7.15.

7.8. The Laplace transform of a general periodic wave

Suppose that a given waveform is periodic, with period T . We can then say with perfect generality that

$$f(t) = f(t + T) \tag{7.50}$$

and that the transform

$$F(s) = \int_0^\infty f(t)\epsilon^{-st} dt \tag{7.51}$$

If we wish, we may perform the integration in steps of one period, that is, from 0 to T , T to $2T$, $2T$ to $3T$, etc., to infinity. We can do this by using the shifting theorem to shift the entire function one period at a time, thus

$$\begin{aligned} \int_0^\infty f(t)\epsilon^{-st} dt &= \int_0^T f(t)\epsilon^{-st} dt + \int_T^{2T} f(t + T)\epsilon^{-s(t+T)} dt + \dots \\ &\quad + \int_{nT}^{(n+1)T} f(t + nT)\epsilon^{-s(t+nT)} dt \end{aligned} \tag{7.52}$$

However, because $f(t)$ is periodic, $f(t)$ will suffice for each term.

$$\int_0^\infty f(t)\epsilon^{-st} dt = \sum_{n=0}^\infty \int_{nT}^{(n+1)T} f(t)\epsilon^{-st}\epsilon^{-nTs} dt \tag{7.53}$$

The exponential term ϵ^{-nTs} is not a function of t , and can be brought through the integral sign, thus

$$\mathcal{L}[f(t)] = \sum_{n=0}^\infty \epsilon^{-nTs} \int_{nT}^{(n+1)T} f(t)\epsilon^{-st} dt \tag{7.54}$$

The integral is evaluated over one period, and since $f(t)$ is the same over any period we choose, we may just as well choose the first period from 0 to T . Therefore

$$F(s) = \sum_{n=0}^{\infty} \varepsilon^{-nTs} \int_0^T f(t) \varepsilon^{-st} dt \quad (7.55)$$

Finally, we observe that

$$\sum_{n=0}^{\infty} \varepsilon^{-nTs} = \frac{1}{1 - \varepsilon^{-Ts}} \quad (7.56)$$

which reduces (7.55) to the simple form

$$F(s) = \frac{1}{(1 - \varepsilon^{-Ts})} \int_0^T f(t) \varepsilon^{-st} dt \quad (7.57)$$

Equation (7.57) is thus a general result and can be applied to any type of periodic waveshape. Its use greatly simplifies the determination of the Laplace transform in many cases.

EXAMPLE 1. Let us find the Laplace transform of the pulse train shown in Fig. 7.14 by this technique.

Since the wave train is periodic, it is no longer necessary for us to integrate to infinity, but only from 0 to T . In fact, since we observe by inspection that the function is zero from a to T , it is really only necessary to integrate out to a . The simple result, using (7.57) as a guide, is

$$\mathcal{L}[f(t)] = \frac{1}{(1 - \varepsilon^{-Ts})} \int_0^a \varepsilon^{-st} dt \quad (7.58)$$

which simplifies almost by inspection to the answer

$$F(s) = \frac{1 - \varepsilon^{-as}}{s(1 - \varepsilon^{-Ts})} \quad (7.59)$$

As the reader can see, it is of little value for an engineer merely to know the definition of the Laplace transform. It is a good working knowledge of all the theorems, little tricks and manipulations which make the theory of real use.

EXAMPLE 2. It is not always expedient to use this periodicity theorem. As an example of a poor application, suppose that

$$f(t) = \sin \omega t$$

one of the first functions used in the text. Here the period is $T = 2\pi/\omega$, and the periodicity theorem shows that

$$F(s) = \frac{1}{\left(1 - e^{-\frac{2\pi s}{\omega}}\right)} \int_0^{\frac{2\pi}{\omega}} \sin \omega t e^{-st} dt \tag{7.60}$$

The reader should work this out as a separate test of the theorem. It will indeed reduce to the familiar form

$$F(s) = \frac{\omega}{s^2 + \omega^2} \tag{7.61}$$

but considerably more effort is required than merely to integrate from 0 to ∞ in the first place.

EXAMPLE 3. Let us find the Laplace transform of the sawtooth wave shown in Fig. 7.16

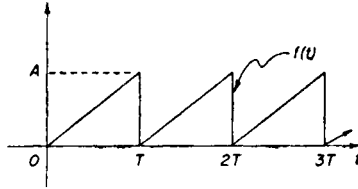


Fig. 7.16

Over the first period, the formula for $f(t)$ is

$$f(t) = \frac{At}{T} \tag{7.62}$$

The second and following periods will all have different constants added which would complicate things should we try to take the transform conventionally. However, we can use the periodicity theorem and state directly that

$$\mathcal{L}[f(t)] = \frac{A}{T(1 - e^{-Ts})} \int_0^T t e^{-st} dt \tag{7.63}$$

The integral is a standard form which is found in any set of integral tables. After inserting the limits and simplifying algebraically, one has

$$F(s) = A \left[\frac{1}{Ts^2} - \frac{e^{-Ts}}{s(1 - e^{-Ts})} \right] \tag{7.64}$$

EXAMPLE 4. We saw that for a sine wave, it was easier to take the transform directly, rather than trying to use the periodicity theorem.

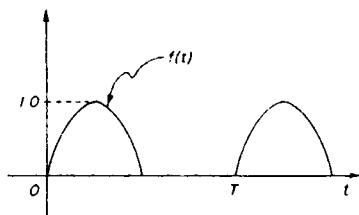


Fig. 7.17

Suppose, however, that one has a half-wave rectified sine wave as shown in Fig. 7.17. Using the periodicity theorem, we write

$$F(s) = \frac{1}{(1 - \varepsilon^{-Ts})} \int_0^{\frac{T}{2}} \sin \omega t \varepsilon^{-st} dt \tag{7.65}$$

$$F(s) = \frac{1}{(1 - \varepsilon^{-Ts})} \left[\frac{\varepsilon^{-st} s \sin \omega t - \omega \varepsilon^{-st} \cos \omega t}{s^2 + \omega^2} \right] \tag{7.66}$$

and since $T = 2\pi/\omega$, (7.66) reduces to

$$F(s) = \frac{\omega}{(s^2 + \omega^2) \left(1 - \varepsilon^{-\frac{2\pi s}{\omega}}\right)} \tag{7.67}$$

7.9. The Laplace transform of a single sawtooth pulse

Let us consider the case of a single sawtooth pulse, which occurs only once and does not repeat itself. This appears in Fig. 7.18.

Using the direct approach, we write

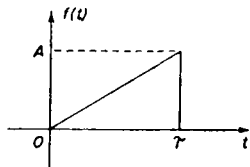


Fig. 7.18

$$f(t) = \frac{At}{\tau} \Big|_{t < \tau} \tag{7.68}$$

and

$$F(s) = \frac{A}{\tau} \int_0^{\tau} t \varepsilon^{-st} dt \tag{7.69}$$

After using a standard form for the integral, and inserting limits, we have

$$F(s) = \frac{A}{\tau s^2} \left[1 - (1 + \tau s) \varepsilon^{-\tau s} \right] \tag{7.70}$$

PROBLEM. Apply the single pulse shown in Fig. 7.18 to a network which has the transfer function

$$Z_T(s) = \frac{1}{LCs^2 + 1} \quad (7.71)$$

and solve for the output voltage as a function of time. What conclusions can be drawn (a) during the pulse? (b) after the pulse is finished?

7.10. Pulsed periodic functions

It often happens in electronics and radio work that one has short bursts or pulses of periodic functions. In radio telegraphy, for example, the $R-F$ carrier, which has its own particular frequency, is keyed on and off in accordance with the dot and dash sequence of the international code. In missile range timing systems, and in many types of data transmission systems, the signals are in the form of keyed sinewaves.

Inasmuch as these pulsed periodic functions play an important part in practical electronics, we should examine a typical waveform and determine its Laplace transform for addition to our list of reference transforms. Such a waveform is shown in Fig. 7.19.

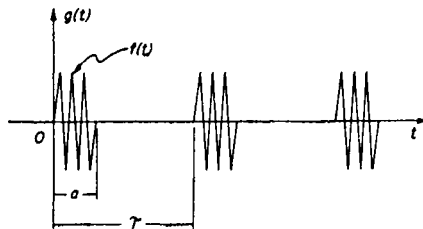


Fig. 7.19

Notice that $f(t)$ represents a continuous periodic function. This could be a sinewave, but we will keep it a general function until we finish the analysis; $g(t)$ represents the pulses of $f(t)$ after keying, and will involve the pulse length a and the keying period τ .

Let us first write an expression for $g(t)$ that is correct within the first period. The undesired portion of $f(t)$ can be blanked out by using two step functions, as

$$g(t) = f(t)[U(t) - U(t - a)] \quad (7.72)$$

Note again that this expression is only valid for the first period τ . However, the same format occurs for each succeeding period, and we learned in art. 7.8 that it was only necessary to integrate the Laplace transform over one period for such functions. We can therefore use (7.57) to write

$$G(s) = \frac{1}{(1 - e^{-\tau s})} \int_0^{\tau} g(t) e^{-st} dt \quad (7.73)$$

If we now replace $g(t)$ in the integral with its actual value taken from (7.72), we have

$$G(s) = \frac{1}{(1 - e^{-\tau s})} \int_0^a f(t) e^{-st} dt \quad (7.74)$$

The portion of the integral from a to τ is zero, and is omitted.

If the original function $f(t)$ had not been pulsed, we could have written its transform by using the periodicity theorem as

$$F(s) = \frac{1}{(1 - e^{-as})} \int_0^a f(t) e^{-st} dt \quad (7.75)$$

In integrating from 0 to a , we may cover several actual periods of $f(t)$, but the exponential in the multiplier involves the same a , and makes the actual number of periods of $f(t)$ immaterial. We can use (7.75) to write

$$\int_0^a f(t) e^{-st} dt = (1 - e^{-as}) F(s) \quad (7.76)$$

and finally, this result is placed into (7.74) to give

$$G(s) = \frac{(1 - e^{-as}) F(s)}{1 - e^{-\tau s}} \quad (7.77)$$

or

$$G(s) = \frac{(1 + e^{-as}) F(s)}{1 - e^{-\tau s}}; \quad \text{if } f(t + a) = -f(t) \quad (7.77a)$$

When using (7.77), make certain that $f(t + a) = f(t)$. If $f(t + a) = -f(t)$, reverse the sign on the exponential term in the numerator as shown in (7.77a). $F(s)$, of course, is the transform of $f(t)$, the original waveform before it was keyed. If the reader wishes to call the final transform $F(s)$ rather than $G(s)$, he can merely substitute some other letter for $f(t)$ and $F(s)$ above.

EXAMPLE. A telegraph key is used to modulate an R - F carrier with a series of dots. The key is down for 0.1 sec and up for 0.3 sec repeatedly. The carrier is 1 Mc. Write the transform of the voltage at the antenna (ignore amplitude)

$$f(t) = \sin \omega t; \quad \omega = 2\pi 10^6$$

from this,

$$F(s) = \frac{\omega}{s^2 + \omega^2}$$

The intervals of keying are

$$a = 0.1 \text{ sec}$$

$$\tau = a + 3a = 0.4 \text{ sec}$$

Using (7.77), we write

$$G(s) = \frac{\omega(1 - e^{-as})}{(s^2 + \omega^2)(1 - e^{-\tau s})}$$

or

$$G(s) = \frac{2\pi 10^6(1 - e^{-0.1s})}{(s^2 + 4\pi^2 10^{12})(1 - e^{-0.4s})}$$

PROBLEMS

(1) A sine wave $\sin \omega t$ is "keyed on" every other half-cycle by using a rectifier. This results in the same pattern shown in Fig. 7.17, i.e. half-wave rectification. Determine that the transform is

$$F(s) = \frac{\omega}{(s^2 + \omega^2) \left(1 - e^{-\frac{\pi s}{\omega}}\right)}$$

by using the theorem developed in this article. In other words, use (7.77) or (7.77a).

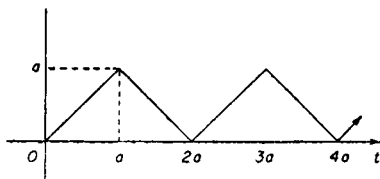


Fig. 7.20

(2) Consider Fig. 7.20. Show that the Laplace transform of the waveform shown in Fig. 7.20 is

$$F(s) = \frac{\tanh(as/2)}{s^2}$$

7.11. Transform of a displaced ramp function

Let us determine the transform of the function shown in Fig. 7.21. The function is 0 for values of t less than a , thus, by the direct definition

$$F(s) = \int_a^{\infty} (t - a)\varepsilon^{-st} dt \quad (7.78)$$

or

$$F(s) = \int_a^{\infty} t\varepsilon^{-st} dt - a \int_a^{\infty} \varepsilon^{-st} dt \quad (7.79)$$

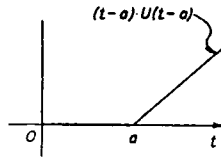


Fig. 7.21

The last term is recognized immediately as the transform of a step function of height a . The first integral is:

$$\int_a^{\infty} t\varepsilon^{-st} dt = \left[\frac{\varepsilon^{-st}}{s^2} (-st - 1) \right]_a^{\infty} \quad (7.80)$$

$$= \left[\frac{-t\varepsilon^{-st}}{s} \right]_a^{\infty} - \left[\frac{\varepsilon^{-st}}{s^2} \right]_a^{\infty} \quad (7.81)$$

The last bracketed term is ε^{-as}/s^2 , and the first bracketed term must be evaluated by l'Hospital's rule. The upper limit results in 0, and the lower limit gives ε^{-as}/s . Collecting the parts from (7.81) and (7.79), we have

$$F(s) = \frac{a\varepsilon^{-as}}{s} - \frac{a\varepsilon^{-as}}{s} + \frac{\varepsilon^{-as}}{s^2} \quad (7.82)$$

or going to the final result, we have

$$F(s) = \frac{\varepsilon^{-as}}{s^2} \quad (7.83)$$

CHAPTER VIII

ELECTRONIC FILTERS

8.1. Introduction

In this chapter, the writer would like to present several topics which most electronics engineers should find both informative and useful. It has been necessary to postpone some of the more interesting subjects until the reader has progressed through the complete sequence of operations with the Laplace transforms and associated theorems. Now, in accordance with the general intent of this text to enhance the reader's ability to work with modern concepts, we shall discuss several specialized applications of the complex frequency plane and its constellation of poles and zeros.

The Laplace transform has many uses not directly associated with network or waveform analysis. It can generally be used to solve differential equations, including those with an arbitrary number of independent variables, partial differential equations, integrals and finite difference equations. The Laplace transform can also be used to evaluate definite integrals, to sum series and to develop the theory of functions. Extended to distributed parameters, it plays an important role in recent theoretical developments in transmission lines, antenna theory and waveguides.

8.2. Normalization of transfer functions

The reader has now acquired considerable experience with transfer functions and their associated networks. We should at this time discuss two features which apply to all transfer functions, regardless of the ultimate purpose for the corresponding network.

The first feature of interest is the concept of impedance level. When one undertakes the analysis or synthesis of an involved network, it is certainly desirable to simplify the work as much as possible. For example, one way to simplify a network which contains many identical resistances is to label all of the resistances as 1 ohm (Ω). As an illustration, let us consider the transfer function given

as form 12, Appendix I(b). If we choose to let R assume the value 1Ω , we have the circuit shown in Fig. 8.1.

Although the choice of $R = 1 \Omega$ simplifies some such networks, it will probably be impossible to use such low impedances or impedance levels with practical vacuum tubes or transistors. Therefore,

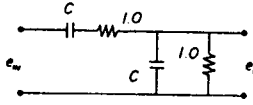


Fig. 8.1

we often have occasion to change the impedance levels of such networks.

The following general rule for changing the impedance level of a network is stated as:

- (I) If every individual impedance in a network is multiplied by a constant factor A , the transfer function of the network remains unchanged.

To apply this rule, observe that the three possible impedances in any network are

$$Z_R = R; \quad Z_C = \frac{1}{sC}; \quad Z_L = sL \quad (8.1)$$

If each impedance is increased by the factor A , then

$$Z_R^1 = AR; \quad Z_C^1 = \frac{A}{sC}; \quad Z_L^1 = sAL \quad (8.2)$$

Physically, this means that each resistor in the network is multiplied by A , each inductance is multiplied by A , but that each capacity in the network is divided by A . These operations have no effect on the transfer function.

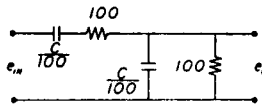


Fig. 8.2

If we should decide to raise the impedance level of Fig. 8.1 by 100 times, the application of the above rule gives the new circuit shown in Fig. 8.2, whose transfer function is the same as that of Fig. 8.1.

The second feature of interest is the concept of normalized frequency. In working with networks, more general results can often be obtained if we choose a critical frequency to be 1 rad/sec, rather than some special frequency which is of interest only in a specific problem. Such a critical frequency might be the upper cut-off frequency of a low-pass filter network, or the frequency of oscillation of the network shown in Fig. 8.2, when used as a Wien-bridge oscillator. To illustrate, we know from earlier work that the frequency of oscillation of a Wien-bridge oscillator, using the network of Fig. 8.2, is

$$f = \frac{1}{2\pi RC} \quad (8.3)$$

Upon examining the network shown in Fig. 8.3, it is seen that we have normalized the impedance level to 1 Ω , and the frequency has

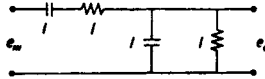


Fig. 8.3

been normalized also to 1 rad/sec. The transfer function for Fig. 8.3 has been simplified to

$$Z_T(s) = \frac{s}{s^2 + 3s + 1} \quad (8.4)$$

Should we be given a network where the frequency has been normalized to unity, we observe from (8.1) that if the frequency should be multiplied by a constant B , the resistors in the network remain as the same impedance. For the inductances in the network, however, we note that if the frequency is multiplied by B , the inductance must be divided by B to maintain the same impedance as before. Finally, all condensers in the network must also be divided by B if their impedances are to remain unchanged at the new frequency.

The general rule for removing a frequency normalization is therefore stated as follows:

- (II) To raise the frequency from $\omega = 1$ to $\omega = B$, leave all resistors in the network unchanged, and divide all L 's and all C 's in the network by B .

EXAMPLE. The low-pass filter shown in Fig. 8.4 has a cut-off frequency of $\omega_C = 1.0$ rad/sec. The output resistance is 1.0Ω .

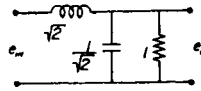


Fig. 8.4

First, let us remove the impedance normalization by using the rule (I). The impedance level is to be increased 10,000 times. From (8.2) we have

$$\left. \begin{aligned} R &= 10,000 \Omega \\ C &= \frac{10^{-4}}{\sqrt{2}} \text{ F} \\ L &= \sqrt{2} \cdot 10^4 \text{ H} \end{aligned} \right\} \quad (8.5)$$

Second, we wish to change the cut-off frequency from the normalized value of 1 rad/sec to a new value, 1,000 rad/sec. Using rule (II), equation (8.5) becomes

$$\left. \begin{aligned} R &= 10,000 \Omega \\ C &= 10^{-7}/\sqrt{2} \text{ F} \\ L &= 10\sqrt{2} \text{ H} \end{aligned} \right\} \quad (8.6)$$

The concepts of normalized impedance and normalized frequency are of considerable importance in network theory. For example, most data that is presented in handbooks is given for such normalized networks, which makes the data general, and useful for more applications. We shall use both concepts in our discussion of filter theory, which begins in the next article.

One can combine both rules, and remove both normalizations at once. Thus, to raise the impedance level by a factor A , and to raise the frequency by a factor B , one can:

$$\left. \begin{aligned} &\text{multiply each network resistor by } A \\ &\text{multiply each network inductor by } A/B \\ &\text{multiply each network condenser by } 1/AB \end{aligned} \right\} \quad (8.7)$$

This last is useful if a large number of elements are involved in a design, but the writer recommends the reader to work from the two

basic concepts instead. The two basic rules may easily be reasoned out if the engineer understands the principles, while special combinations or formulas such as (8.7) are soon forgotten or remembered in error.

8.3. Low-pass filters

One of the most useful low-pass filters that can be devised is the Butterworth filter. This type is based upon the properties of a "maximally flat function", and is named after the man who first used such a function for filter purposes. The primary feature of a Butterworth filter is its amplitude vs. frequency characteristic. The gain, or ratio of e_0/e_{IN} for a Butterworth low-pass filter is

$$A = \frac{e_0}{e_{IN}} = \frac{1}{\sqrt{1 + \omega^{2n}}} \quad (8.8)$$

We see by inspection of (8.8) that for values of ω slightly less than 1.0, the gain approximates unity, and the region from 0 to $\omega = 1.0$ is said to be a pass band. For values of ω slightly greater than unity, the gain approximates zero, and therefore little energy is passed at frequency values above $\omega = 1.0$. The approximation to a perfect filter which cuts off abruptly at $\omega = 1.0$ becomes better and better as n is increased. At $\omega = 1.0$, we see that the network gain is 0.707, and by definition this occurs at the upper cut-off frequency which is thus $\omega_0 = 1.0$.

The factor n in the expression is called the "order" of the filter. Thus, for a third-order Butterworth filter, the expression for gain is

$$A = \frac{1}{\sqrt{1 + \omega^6}} \quad (8.9)$$

We can see intuitively that the factor n determines the sharpness of cut-off of the filter at and beyond the point $\omega_0 = 1.0$.

Amplitude curves for the first-, third- and fifth-order Butterworth filters are shown in Fig. 8.5. For the fifth-order Butterworth filter, it is easy to see that the response is perfectly flat over the pass band, up to the point where drop-off begins. This accounts for the term "maximally flat function". If the filter has the true Butterworth shape, there will be no peaks or valleys within the pass band.

The curves of Fig. 8.5 and the function (8.8) have the frequency normalized to 1.0. We can discuss the entire subject of filters on this basis, knowing that when we finally become interested in a specific

result, the normalizations can easily be removed by the methods of art. 8.2.

The Butterworth amplitude function (8.8) allows us to determine the order n required for a given cut-off rate. For example, suppose we want to design a filter whose gain is 0.707 at the cut-off frequency

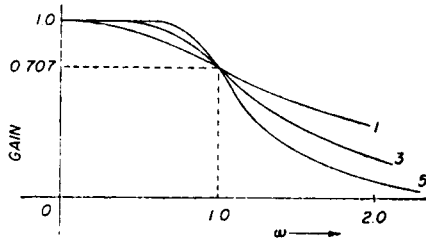


Fig. 8.5

$\omega_0 = 1.0$, and whose gain has dropped to 1.0% at $\omega = 2.0$, i.e. at the second harmonic of the cut-off frequency. For this case

$$\frac{1}{\sqrt{1 + 2^{2n}}} = \frac{1}{100} \quad (8.10)$$

or

$$1 + 2^{2n} = 10^4 \quad (8.11)$$

and for all practical purposes

$$2^{2n} = 10^4 \quad (8.12)$$

Taking the common logarithm of both sides, we have

$$\log 2^{2n} = 4 \quad (8.13)$$

or

$$2n \log 2 = 4 \quad (8.14)$$

$$n = \frac{2}{\log 2} \quad (8.15)$$

or finally,

$$n = 6.64 \quad (8.16)$$

Apparently we must use the next integral value, which means that we must build a seventh-order Butterworth filter to meet this specification.

It will be found shortly that the value of n is equal to the number of reactive elements in the final version of the filter. Thus, for

$n = 7.0$, to meet the amplitude specification above there must be seven separate reactive elements in the filter network.

8.4. Maximally flat functions

In the design of Butterworth filters, we will be interested in transfer functions which are maximally flat. Such functions of s will have the amplitude characteristic given by (8.8). The value n will correspond to the highest power of s in the transfer function.

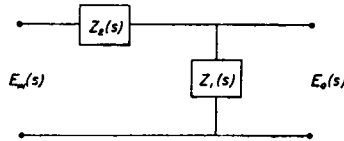


Fig. 8.6

To digress for a moment, suppose we consider Fig. 8.6. It does not require much effort to see that the transfer function of this network is

$$Z_T(s) = \frac{Z_1(s)}{Z_2(s) + Z_1(s)} \quad (8.17)$$

We observe that the entire numerator is contained in the denominator. Now if we can recognize such a correspondence between parts of the numerator and denominator of a given transfer function, it should be possible to draw the network which the function represents, merely by placing the component parameters into the two boxes shown in Fig. 8.6. This type of operation is called network synthesis, and is the opposite of analysis. In analyzing a given network, one proceeds to determine the transfer function. In synthesis, one is given a transfer function from which one must determine a corresponding network.

As an illustration of a very simple type of synthesis, suppose we are given the transfer function

$$Z_T(s) = \frac{1}{s + 1} \quad (8.18)$$

Comparing this with (8.17), we see that the numerator also occurs as part of the denominator. This is to say

$$\left. \begin{aligned} Z_1(s) &= 1.0 \\ Z_2(s) &= s \end{aligned} \right\} \quad (8.19)$$

$Z_2(s)$ evidently corresponds to a 1 H inductance, while $Z_1(s)$ appears to be a 1 Ω resistance. If these values are inserted into the boxes shown in Fig. 8.6, we have synthesized the network which appears in Fig. 8.7. Admittedly, this is a very simple network, but it serves in an elementary way to illustrate the principle.

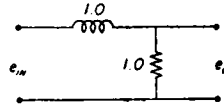


Fig. 8.7

As a further observation about (8.18), note that we can divide both the numerator and the denominator by s without algebraically changing the function, i.e.

$$Z_T(s) = \frac{1/s}{1 + 1/s} \quad (8.20)$$

so that

$$\left. \begin{aligned} Z_1(s) &= \frac{1}{s} \\ Z_2(s) &= 1.0 \end{aligned} \right\} \quad (8.21)$$

In this case $Z_1(s)$ would appear to be a 1 F condenser, while $Z_2(s)$ appears to be a 1 Ω resistor. Using Fig. 8.6 as a guide, the synthesized network is shown in Fig. 8.8. At this point, the reader

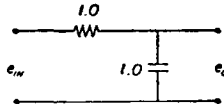


Fig. 8.8

should write the transfer functions for Fig. 8.7 and Fig. 8.8, and show that they are identical. Having digressed to discuss elementary synthesis, let us now examine the following second-order function of s .

$$F(s) = \frac{1}{s^2 + s\sqrt{2} + 1} \quad (8.22)$$

By inserting $j\omega$ for s in (8.22), the reader should ascertain that the magnitude of (8.22) is

$$|F(\omega)| = \frac{1}{\sqrt{1 + \omega^4}} \quad (8.23)$$

We observe that the highest power of s in (8.22) is 2.0, and that the amplitude function corresponds to the Butterworth function for $n = 2.0$. We can therefore conclude that (8.22) is the transfer function of a second-order Butterworth low-pass filter.

The numerator of (8.22) is contained in the denominator, but if we try to apply (8.17) immediately, we run into difficulty, as we have no impedance which equals s^2 . However, if we first divide both numerator and denominator by s , we have

$$Z_T(s) = \frac{1/s}{s + \sqrt{2} + 1/s} \quad (8.24)$$

If we now let

$$\left. \begin{aligned} Z_1(s) &= \frac{1}{s} \\ Z_2(s) &= \sqrt{2} + s \end{aligned} \right\} \quad (8.25)$$

we can again use Fig. 8.6 as a model, to synthesize the actual circuit which (8.24) represents. This network is shown in Fig. 8.9.

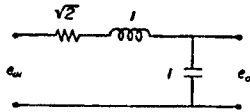


Fig. 8.9

The second-order Butterworth transfer function (8.22) could also be written as

$$Z_T(s) = \frac{1}{s(s + \sqrt{2}) + 1} \quad (8.26)$$

If we now divide both numerator and denominator by the factor $(s + \sqrt{2})$, we have

$$Z_T(s) = \frac{1/(s + \sqrt{2})}{s + 1/(s + \sqrt{2})} \quad (8.27)$$

We can now let

$$Z_1(s) = \frac{1}{s + \sqrt{2}}; \quad Z_2(s) = s$$

$Z_2(s)$ appears to represent a simple inductance of 1 H, but $Z_1(s)$ seems to be some combination. If we invert $Z_1(s)$ we obtain

$$Y_1(s) = s + \sqrt{2} \quad (8.28)$$

which, in this form, is recognized at once as the parallel combination of the susceptance sC and the conductance $\sqrt{2}$ mho. The parallel combination, with parts labeled as impedances, is shown in Fig. 8.10. Using Fig. 8.6 as a guide, we draw the complete second version of

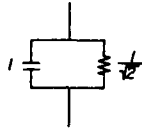


Fig. 8.10

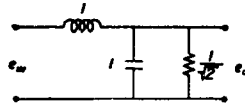


Fig. 8.11

this function as the circuit shown in Fig. 8.11. The reader should write the transfer functions of Fig. 8.11 and Fig. 8.9 separately, to show that they are indeed satisfied by (8.22).

We have demonstrated alternate network solutions for both the very simple first-order and the slightly more involved second-order Butterworth filters. It can be stated as a general rule that a given network can be analyzed and will have only one definite transfer function, but that if a transfer function is given instead, it is possible to synthesize an infinite number of networks which may represent it. Of course the transfer function must actually have a solution.

PROBLEMS

(1) Consider Fig. 8.12, where values are given in ohms (Ω), henrys (H) and farads (F). Show that the transfer function is

$$Z_T(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} \quad (8.29)$$

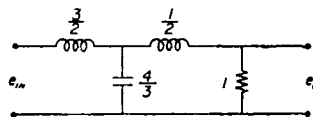


Fig. 8.12

(2) Show that the magnitude, for $s = j\omega$, is the third-order Butterworth filter

$$|Z(\omega)| = \frac{1}{\sqrt{1 + \omega^6}} \quad (8.30)$$

8.5. Pole location for Butterworth functions

The reader has probably begun to suspect that there is more order here than meets the eye thus far; and the orderliness does exist.

This will become evident when we locate the poles of the different order Butterworth functions in the s -plane. Once we point out the procedure for locating the poles in the s -plane, the formation of the functions will be obvious by inspection.

(a) We state first that an n th order Butterworth function has n poles in the s -plane, i.e. the function involves s to the n th power.

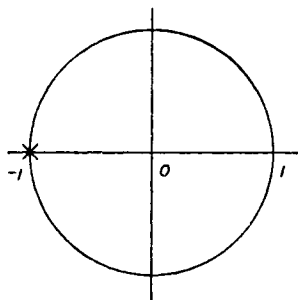


Fig. 8.13

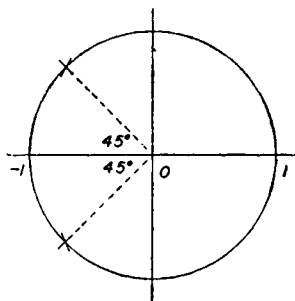


Fig. 8.14

(b) The poles are all located on a circle of unity radius, centered at the origin in the s -plane.

(c) The poles are all located in the left half-plane, and are symmetrical about the point $s = -1$.

Examples of pole locations for the first four orders will make the procedure more clear than trying to explain it by a rule. The first-order Butterworth function has one pole, located on the circle of unity radius at $s = -1$. This is shown in Fig. 8.13. The second-order Butterworth filter, represented by (8.22), has poles at

$$s = -\frac{1}{\sqrt{2}} \pm j \frac{1}{\sqrt{2}} \quad (8.31)$$

and these are also symmetrical on the unit circle, as shown in Fig. 8.14. The third-order Butterworth filter, represented by (8.29), has poles located at

$$\left. \begin{aligned} s &= -1 \\ s &= \epsilon^{\frac{j2\pi}{3}} \\ s &= \epsilon^{-\frac{j2\pi}{3}} \end{aligned} \right\} \quad (8.32)$$

and these are shown in Fig. 8.15. The fourth-order Butterworth filter has poles located as in Fig. 8.16. The fifth-order Butterworth filter would have poles at angles of 0° , $\pm 36^\circ$, $\pm 72^\circ$, measured from the negative real axis. Note that in all cases, the left half-circle is divided into n equal sectors, with one sector between each adjacent pair of poles, and one-half sector located between the top-most pole

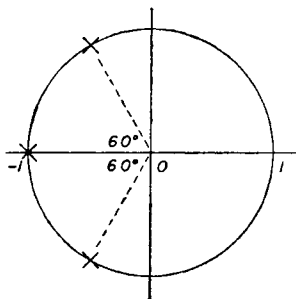


Fig. 8.15

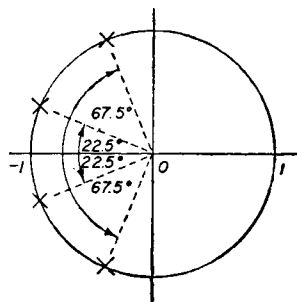


Fig. 8.16

and the upper j -axis, with the remaining half-sector between the bottom-most pole and the $-j$ -axis.

To derive the transfer function for a given order filter, it is easiest first to draw the pole diagram. One can then determine each factor in the denominator from the pole diagram.

For example, if there are three poles, one can use Fig. 8.15, and the pole locations given by (8.32) to write

$$Z_T(s) = \frac{1}{(s+1)\left(s - \epsilon \frac{j2\pi}{3}\right)\left(s - \epsilon^{-\frac{j2\pi}{3}}\right)} \quad (8.33)$$

which simplifies progressively as

$$Z_T(s) = \frac{1}{(s+1)\left(s^2 - s\epsilon \frac{j2\pi}{3} - s\epsilon^{-\frac{j2\pi}{3}} + 1\right)} \quad (8.34)$$

$$Z_T(s) = \frac{1}{(s+1)(s^2 - 2s \cos 2\pi/3 + 1)} \quad (8.35)$$

$$Z_T(s) = \frac{1}{(s+1)(s^2 + s + 1)} \quad (8.36)$$

and finally

$$Z_T(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} \quad (8.37)$$

with the usual property that

$$|Z_T| = \frac{1}{\sqrt{1 + \omega^6}} \quad (8.38)$$

If there are an even number of poles, one can take them in pairs. For example, in Fig. 8.16 one can combine both $\pi/8$ and $3\pi/8$ pairs to give

$$Z_T(s) = \frac{1}{(s^2 + 2s \cos \pi/8 + 1)(s^2 + 2s \cos 3\pi/8 + 1)} \quad (8.39)$$

which gives a fourth-order Butterworth function, and if $s = j\omega$, (8.39) becomes

$$|Z_T| = \frac{1}{\sqrt{(1 + \omega^2\sqrt{2} + \omega^4) \cdot \sqrt{(1 - \omega^2\sqrt{2} + \omega^4)}}} \quad (8.40)$$

or

$$|Z_T| = \frac{1}{\sqrt{1 + \omega^8}} \quad (8.41)$$

We can make a more formal statement about the location of the poles for the general Butterworth filter of order n . We let

n = number of poles (order of filter)

i = one particular pole in the group

then

$$i = 1, 2, 3, 4, \dots n.$$

One can determine by inspection that the general pole locations are

$$s_i = \cos \left[\left(\frac{2i-1}{n} - 1 \right) \frac{\pi}{2} \right] + j \sin \left[\left(\frac{2i-1}{n} - 1 \right) \frac{\pi}{2} \right]$$

Poles for the high pass Butterworth filter are merely reciprocals in magnitude (since the radius of the circle is unity, the reciprocal radius is also unity), and with signs of the angles changed. Since the low pass and high pass poles are merely exchanged in complex conjugate pairs, there is no net difference in the pole locations for the high pass and low pass maximally flat filters. Note of course that the *zeros* will be different.

8.6. Synthesis of the third-order maximally flat function

The third-order Butterworth filter has the function

$$Z_T(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} \quad (8.42)$$

As the order of the function increases, the circuit complexity must necessarily increase, and we may expect that the synthesis procedure will become more involved. It was possible to synthesize the first- and second-order functions by inspection, with a little algebraic manipulation of the function in advance. Such a simple procedure fails when we have a third-order function.

There are numerous formal ways of finding the actual circuit which has (8.42) as its transfer function, but the writer would prefer to choose a simplified approach which is certain to be understood by all readers. Let us first make a few observations about (8.42).

(a) We know from observation (or by proof if we should discuss the subject at greater length) that a third-order transfer function such as this will have three reactive elements.

(b) If we choose to have the final element in the filter be a shunt 1Ω resistance, as in the first two cases, this would make a total of four components, one of which is the 1.0Ω resistor.

(c) We feel that the input reactance will be a series element, since it would hardly affect the performance of the filter were it to be shunted directly across the input voltage.

(d) Finally, we suspect that in a low-pass filter, the series reactive elements will be inductances, while any shunt reactive elements will be condensers.

The above reasoning, which requires no great imagination, leads us to suspect that the actual circuit arrangement will be as in Fig.

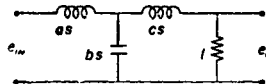


Fig. 8.17

8.17. The values of the three reactances are not yet known, of course, so we merely label them as a , b , c . Now if the reader will analyze this circuit, he will find that the transfer function is

$$Z_T(s) = \frac{1}{abc s^3 + abs^2 + (a + c)s + 1} \quad (8.43)$$

Since we want this to represent (8.42), we can set these two functions equal to each other, i.e.

$$\frac{1}{abc s^3 + abs^2 + (a + c)s + 1} = \frac{1}{s^3 + 2s^2 + 2s + 1} \quad (8.44)$$

The coefficients of like powers of s must be equal to each other, and thus we have

$$abc = 1 \quad (8.45)$$

$$ab = 2 \quad (8.46)$$

$$a + c = 2 \quad (8.47)$$

Inspection of this simple set of equations shows that

$$\left. \begin{aligned} a &= \frac{2}{3} \\ b &= \frac{3}{2} \\ c &= \frac{1}{2} \end{aligned} \right\} \quad (8.48)$$

When these values are inserted in Fig. 8.17, we have completed the problem, and the result appears as in Fig. 8.18. The reader will agree that this circuit has the transfer function given by (8.42), as he has already worked the same network as problem 1 in art. 8.4.

In Appendix I(b) he will find a set of networks for the first ten orders of Butterworth functions. These have all been normalized to 1.0 Ω impedance level and 1.0 rad/sec frequency.

The reader can thus build up to a tenth-order filter merely by using the appropriate network from Appendix I(b), removing the normalizations so as to meet his own particular design needs.

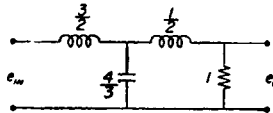


Fig. 8.18

8.7. High-pass maximally flat functions

Thus far we have discussed only low-pass filters. All of the theory thus far applies equally well to the design of high-pass filters.

We recall from Chapter I that startling results can often be obtained by making a change of variables. The low-pass normalized filters already developed can all be converted to normalized high-pass filters by making the very simple change of variables

$$S^* = \frac{1}{s} \quad (8.49)$$

The three possible impedance types in the filters were originally

$$Z_R = R; \quad Z_C = \frac{1}{sC}; \quad Z_L = sL \quad (8.50)$$

By the above transformation (8.49), each impedance becomes

$$Z_R^* = R; \quad Z_C^* = \frac{s^*}{C}; \quad Z_L^* = \frac{L}{s^*} \quad (8.51)$$

Thus all we have to do to convert the normalized low-pass filter into a corresponding normalized high-pass filter is to replace every capacity by an inductance of reciprocal numeric value, replace every inductor by a condenser of inverse numerical value, and leave all resistors unchanged. As a typical example, the normalized third-order Butterworth filter shown in Fig. 8.18 becomes the high-pass normalized filter shown in Fig. 8.19.

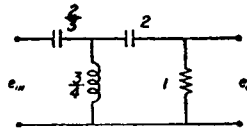


Fig. 8.19

8.8. Maximally flat band-pass filters

The low-pass Butterworth filters which we have discussed in some detail can also serve as a basis for designing band-pass filters. If we choose the following definitions for use with the band-pass filters:

$$\left. \begin{aligned} \omega_H &= \text{upper cut-off frequency} \\ \omega_L &= \text{lower cut-off frequency} \\ \Delta\omega &= \omega_H - \omega_L = \text{bandwidth} \\ \omega_C &= \text{center frequency} \end{aligned} \right\} \quad (8.52)$$

geometrical symmetry will dictate that

$$\omega_C^3 = \omega_L \omega_H \quad (8.53)$$

Suppose we take one of the normalized low-pass filters and change

its cut-off frequency to $\Delta\omega$. We can now make a change of variable whereby

$$s = s^* + \frac{\omega_c^2}{s^*} \quad (8.54)$$

Thus each s in the low-pass filter which has bandwidth $\Delta\omega$ is replaced by the new value in (8.54).

If we compare the old values with the required new values, we can arrive at the following simple conclusions:

(a) The normalized low-pass filter of desired order is first changed to have a cut-off frequency equal to $\Delta\omega$.

(b) Equation (8.54) requires that for every capacity in the network, we add an inductance in parallel whose value is given by

$$L = \frac{1}{\omega_c^2 C} \quad (8.55)$$

(c) Equation (8.54) requires also that for every inductance in the original network, we add a condenser in series whose value is

$$C = \frac{1}{\omega_c^2 L} \quad (8.56)$$

(d) All original resistors in the network are left unchanged.

After the above conversion has been made, one can then change the impedance level from 1.0Ω to whatever appropriate level is required. The steps (a), (b) and (c) are so simple that the reader is requested to work out several examples for practice by himself, using any of the low-pass networks already developed.

8.9. Design of a band-pass filter

This article will attempt to clarify the procedure just given. The writer feels that a suitable example will make the ideas very easy to follow, more so than any amount of formal discussion could do.

EXAMPLE. Since all of you know how to handle frequency and impedance transformations and normalizations (art. 8.2) the writer most strongly recommends that one design the bandpass filter with $\omega_c = 1.0$ radian per second. The transformations just given can do the job all in one step, but the reader with more patience can usually achieve much greater reliability by always choosing $\omega_c = 1.0$.

Our specifications call for a band-pass filter of *first-order* charac-

teristics, with $\omega_c = 1000$, and a bandwidth of 10 radians per second, however, we immediately change this to

$$\omega_c = 1.0 \quad (8.57)$$

$$\Delta\omega = 0.01 \quad (8.58)$$

We thus design our *first-order* low-pass model as a simple R - C filter which has a cutoff of 0.01 radians, as in Figs. 8.20 and 8.21.

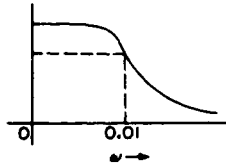


Fig. 8.20

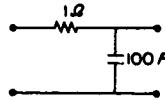


Fig. 8.21

The low-pass to band-pass transformation (8.54) now requires that we place an inductance whose value is

$$L = \frac{1}{\omega_c^2 C} = \frac{1}{C} = 10^{-2} \text{ hy} \quad (8.59)$$

in parallel with the condenser. This gives Fig. 8.22.

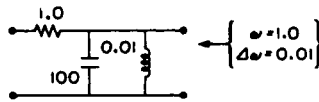


Fig. 8.22

Fig. 8.22 now has a center frequency of $\omega = 1$ and a bandwidth $\Delta\omega = 0.01$. When we renormalize to $\omega = 1000$, the new values are shown in Fig. 8.23.

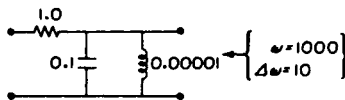


Fig. 8.23

We would then change the impedance level to something appropriate, and our design is finished. Starting with Fig. 8.21, let us go through the algebra once to illustrate how the equations work. The transfer function for Fig. 8.21 is

$$Z_T(s) = \frac{1}{100s + 1} \quad (8.60)$$

From (8.54) we replace s with $(s + 1/s)$, then

$$Z_T(s) = \frac{1}{100\left(s + \frac{1}{s}\right) + 1} \quad (8.61)$$

or

$$Z_T(s) = \frac{s}{100s^2 + s + 100} \quad (8.62)$$

replacing s by $j\omega$ gives

$$Z_T(j\omega) = \frac{1}{1 + j100\left(\omega - \frac{1}{\omega}\right)} \quad (8.63)$$

and the magnitude is

$$|Z_T(\omega)| = \frac{1}{\underbrace{\sqrt{10^4\left(\omega^2 + \frac{1}{\omega^2}\right) - 2 \cdot 10^4 + 1}}_x} \quad (8.64)$$

We will have the band edges where gain is $1/\sqrt{2}$, or where $x = 1$ in (8.64), i.e.

$$10^4\left(\omega^2 + \frac{1}{\omega^2}\right) - 2 \cdot 10^4 = 1 \quad (8.65)$$

or

$$\omega^4 - (2 + 10^{-4})\omega^2 + 1 = 0 \quad (8.66)$$

By the quadratic formula,

$$\omega^2 = \frac{2 + 10^{-4} \pm \sqrt{(2 + 10^{-4})^2 - 4}}{2} \quad (8.67)$$

$$\omega^2 = \frac{2 \pm \sqrt{4 \cdot 10^{-4}}}{2} \quad (8.68)$$

where we have dropped second order terms as being too small to affect results.

$$\omega^2 = 1 \pm 0.01 \quad (8.69)$$

$$\omega = 1.005 \text{ and } 0.995 \quad (8.70)$$

and finally,

$$\Delta\omega = 0.01 \quad (8.71)$$

8.10. The band rejection filter

It is sometimes necessary to design a filter network to pass all frequencies except those in a specific range. Such a band elimination or band rejection filter characteristic is shown in Fig. 8.24.

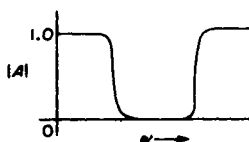


Fig. 8.24

We should merely point out here that the reader can readily design such networks using the material studied in art. 8.8. The only change is that in this case the change of variable calls for the transformation

$$s = \frac{1}{s^* + \frac{1}{s^*}} = \frac{s^*}{s^{*2} + 1} \quad (8.72)$$

where the center frequency of the eliminated band has already been chosen as 1 radian.

We do not have to insert this transformation into transfer functions, as we can do all of our theoretical work with the low-pass prototype as before. The transformation merely requires that we add an inductor of $1/C$ henrys in *series* with each original condenser

C , and that we add a condenser of capacity $1/L$ farads in *parallel* with each original inductor L . These statements are illustrated in Fig. 8.25 for emphasis.

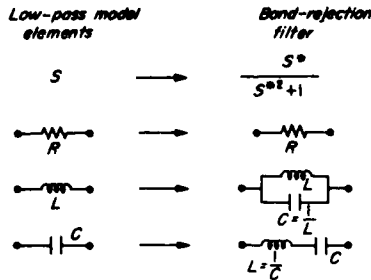


Fig. 8.25

8.11. Matched low-pass filters

In the theoretical discussion of the low-pass filter networks we usually assume that the source has zero impedance and that the load is infinite impedance. It is possible to have almost the opposite situation in some very practical cases. Thus a filter network that is fed directly from the collector of a transistor sees a very high impedance source. This same network could possibly feed into the emitter of a grounded base transistor amplifier where the network load impedance would thus be very low.

We can see that either or both cases will require modification of the network in some way if the characteristic response is to maintain its original shape.

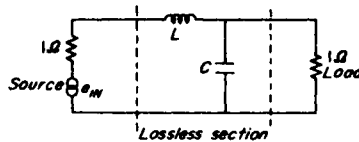


Fig. 8.26

Obviously we cannot discuss the infinity of possibilities here, but it will be well to consider at least one case to bring out the ideas involved. We can choose as an example the case where the load is one ohm and where the source impedance is also one ohm. If we

assume a second-order Butterworth filter, our total network including source and load will appear as in Fig. 8.26.

This is a case of a matched filter. We suspect that the best we can do is to get one-half the power into the load, or alternately, that at $s = 0$, or at d.c., we will have only one-half of e_{IN} across the load.

If we write the over-all transfer function of the network, with the source resistance included as the first series element, we have

$$Z_T(s) = \frac{1}{s^2 LC + (L + C)s + 2} \quad (8.73)$$

This may be put into the following form by multiplying through by $\frac{1}{2}$.

$$Z_T(s) = \frac{\frac{1}{2}}{s^2 \frac{LC}{2} + \left(\frac{L + C}{2}\right)s + 1} \quad (8.74)$$

Now we can arrange for this function to have the pole configuration of the Butterworth filter by choosing the coefficients in the denominator to match those in the second-order function

$$Z_T(s) = \frac{K}{s^2 + \sqrt{2}s + 1} \quad (8.75)$$

or, in other words

$$\left. \begin{aligned} \frac{LC}{2} &= 1 \\ \frac{L + C}{2} &= \sqrt{2} \end{aligned} \right\} \quad (8.76)$$

We solve these to find that

$$L = C = \sqrt{2} \quad (8.77)$$

and when these values are inserted into the circuit of Fig. 8.26, the response will be the second-order maximally flat filter and will have a cut-off at $\omega = 1$. We see that (8.74) shows a constant multiplier of $\frac{1}{2}$, as we would expect from observation of the network at zero frequency.

If desired, the reader can show that for the same 1-ohm source and load, the corresponding third-order Butterworth network has the values shown in Fig. 8.27.

For a different situation, suppose someone changes our load to two ohms, but the source remains one ohm. One easy solution would be for us to merely parallel the two-ohm load with another two ohms and insert the one-ohm combination as in Fig. 8.27. To do this

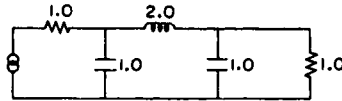


Fig. 8.27

would increase our losses needlessly however. In this case it is far better to redesign the network entirely, and come up with new values for the L 's and C 's. One of many possibilities is shown in Fig. 8.28, where we see that the output is $\frac{2}{3}$ of the input voltage at d.c., as opposed to $\frac{1}{2}$ if we had taken the easy solution of using a two-ohm dummy resistor in parallel with the load.

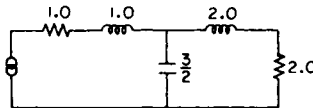


Fig. 8.28

8.12. Magnitude and phase functions of "s"

In the next two articles we are going to discuss the maximally flat *time delay* filter. In the development we shall make use of certain definitions and relations which are best derived as a separate exercise. We will hope to digress as little as possible when we reach that stage, and so we propose to develop several ideas and make some definitions here. We will then have the results available for use in the following articles.

Suppose we are given the voltage transfer function $Z_T(s)$, which has been defined as the ratio of output to input voltage. Since in general this will be a complex function, we can write $Z_T(s)$ in terms of a magnitude function $F(s)$ and a phase function $\phi_1(s)$ as

$$Z_T(s) = F(s)e^{j\phi_1(s)} \quad (8.78)$$

Note carefully that $\phi_1(s)$ is *not* the angle of $Z_T(s)$, but is a phase

function. It is an *odd* function of s which reduces to $j\phi(\omega)$ when $s = j\omega$.

Now for any given function $Z_T(s)$, we can form the conjugate function $Z_T(-s)$ by inspection. We now *define* a new function $A(s)$ as

$$A(s) = \frac{Z_T(s)}{Z_T(-s)} \quad (8.80)$$

or

$$A(s) = \varepsilon^{2\phi_1(s)} \quad (8.81)$$

Now we can see that

$$\varepsilon^{2\phi_1(s)} = \frac{\varepsilon^{\phi_1(s)}}{\varepsilon^{-\phi_1(s)}} = \frac{\cosh \phi_1(s) + \sinh \phi_1(s)}{\cosh \phi_1(s) - \sinh \phi_1(s)} \quad (8.82)$$

or

$$\frac{1 + \tanh \phi_1(s)}{1 - \tanh \phi_1(s)} = A(s) \quad (8.83)$$

If someone should give us $\phi_1(s)$, or $\tanh \phi_1(s)$, we can then immediately find $A(s)$ from (8.83).

The original transfer function $Z_T(s)$ will be composed of a numerator and a denominator, each of which is in general also a function of s . We can label the numerator and denominator as P_1 and P_2 , thus

$$Z_T(s) = \frac{P_1(s)}{P_2(s)} \quad (8.84)$$

Similarly, the function

$$Z_T(-s) = \frac{P_1(-s)}{P_2(-s)} \quad (8.85)$$

and if we know either $P_1(s)$ or $P_1(-s)$ we can get the other by inspection, the same with $P_2(s)$ and $P_2(-s)$.

Using the separate numerator and denominator parts from (8.84) and (8.85), we can write the intermediate function $A(s)$ in (8.80) as

$$A(s) = \frac{P_1(s)P_2(-s)}{P_2(s)P_1(-s)} \quad (8.86)$$

Suppose we are given a phase function $\phi_1(s)$ and we are to find the corresponding transfer function $Z_T(s)$ from which the phase function came. Using (8.38) we first find $A(s)$. Having $A(s)$, we

factor the numerator and denominator and assign the appropriate factors among the four P functions in (8.86). This will require some judgment, but will be relatively easy to do since we will assign any factors which represent right-half-plane poles to $P_1(-s)$. The other factors of the denominator must then belong to $P_2(s)$.

Having $P_2(s)$, we can find $P_2(-s)$ by inspection, merely replace each s in $P_2(s)$ by $-s$.

Once $P_2(-s)$ is found, we can see by inspection which of the remaining numerator factors belong to $P_1(s)$ in (8.86). Since we now have all four $P(s)$ functions listed separately, we merely lift out $P_1(s)$ and $P_2(s)$ and write

$$Z_T(s) = \frac{P_1(s)}{P_2(s)} \quad (8.87)$$

from the original definition back in (8.84).

The reader is now requested to rework the development up to this point for practice, using $s = j\omega$ in all steps, and to verify that

$$A(j\omega) = \frac{1 + j \tan \phi(\omega)}{1 - j \tan \phi(\omega)} \quad (8.88)$$

$$A(j\omega) = \frac{Z_T(j\omega)}{Z_T(-j\omega)} = e^{j2\phi(\omega)} \quad (8.89)$$

$$Z_T(j\omega) = |Z_T(\omega)|e^{j\phi(\omega)} \quad (8.90)$$

We note from (8.89) that the defined function $A(j\omega)$ has unity magnitude and an angle which is twice the angle of $Z_T(j\omega)$.

As an example of the application of these results, suppose we are given the phase function $\phi(\omega)$, or more specifically we are given $\tan \phi(\omega)$ as

$$\tan \phi(\omega) = \frac{\omega^3 - 2\omega}{1 - 2\omega^2} \quad (8.91)$$

and we are requested to find $Z_T(s)$. We use (8.88) to write

$$A(j\omega) = \frac{1 - 2\omega^2 + j\omega^3 - j2\omega}{1 - 2\omega^2 - j\omega^3 + j2\omega} \quad (8.92)$$

we now replace $j\omega$ by s , and write

$$A(s) = \frac{1 + 2s^2 - s^3 - 2s}{1 + 2s^3 + s^3 + 2s} \quad (8.93)$$

we now factor this expression and write $A(s)$ in the form shown by (8.86) to have

$$A(s) = \frac{(1-s)(s^2 - s + 1)}{(1+s)(s^2 + s + 1)} \quad (8.94)$$

Now since both factors in the denominator represent poles in the left-hand s -plane, they can both be assigned to $P_2(s)$, i.e.

$$P_2(s) = (1+s)(s^2 + s + 1) \quad (8.95)$$

and therefore

$$P_1(-s) = 1 \quad (8.96)$$

thus we also have

$$P_1(s) = 1 \quad (8.97)$$

and from (8.84) we have our final solution

$$Z_T(s) = \frac{1}{(1+s)(s^2 + s + 1)} \quad (8.98)$$

When this is multiplied out, we recognize the third-order Butterworth function

$$Z_T(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} \quad (8.99)$$

We have removed $P_2(-s)$ from the numerator because it shows zeros in the right-hand s -plane. It is fundamentally permissible to allow zeros in the right-half-plane, but not for the unbalanced ladder networks we discuss in this text. Networks with no zeros in the right-half s -plane are said to be *minimum phase-shift* networks.

Note that (8.99) is correct to within a constant multiplier, as we can multiply the numerator by any constant we wish without affecting phase of the network.

We shall refer to and use a number of these definitions and results in the following discussion of the maximally flat time-delay filters.

PROBLEM. Show that the phase function

$$\tan \phi(\omega) = \frac{\omega^3 - 4\omega}{2 - 3\omega^2} \quad (8.100)$$

comes from the transfer function

$$Z_T(s) = \frac{1}{s^3 + 3s^2 + 4s + 2} \quad (8.101)$$

8.13. Maximally flat time-delay filters

Thus far we have discussed the Butterworth, or maximally flat *amplitude* filter as if this was the only desirable characteristic. In actuality, the reader is probably aware that it is often more important to preserve the wave *shape* than to insist that the low-pass filter have an absolutely flat amplitude response. This is especially true for television waveforms, time-multiplex radio telemetry, high-fidelity music amplifiers, and other practical applications. A maximally flat time delay can be illustrated as in Fig. 8.29.

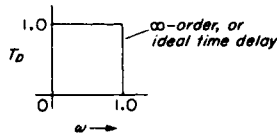


Fig. 8.29

A typical waveform such as a television video signal contains frequency components that range over a broad spectrum. If the *normalized* frequency spectrum falls within the range of 0 to 1, as in Fig. 8.29, we say that all frequency components should be delayed an equal amount, T_D seconds, and that the output waveform would be a faithful reproduction of the input. The ideal time delay has the same shape as the ideal Butterworth filter, except that we have labeled the abscissa as time delay T_D instead of amplitude A . Our objective in the next few articles will be to discuss how such filters can be described, and how good approximations to them can be built.

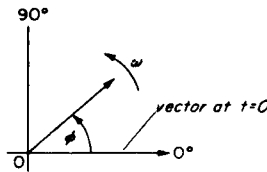


Fig. 8.30

Glancing at Fig. 8.30, we note that if we describe a sine wave as a vector that rotates about the origin with angular velocity ω , and if

the vector crosses the positive real axis at $t = 0$, then we can describe the phase at any time during the period by

$$\phi(\omega) = t\omega \quad (8.102)$$

We can differentiate (8.102) and write

$$T_D(\omega) = -\frac{d\phi(\omega)}{d\omega} \quad (8.103)$$

The sign of T_D is arbitrary, depending on whether we define time as forward from $t = 0$ at the origin to time at position ϕ , or measure the *delay* or time backward from the vector at phase ϕ to time at the origin. The point is trivial, and the sign in (8.103) is chosen to make T_D appear as a positive quantity with the phase functions which will appear.

The constant time delay shown in Fig. 8.29 for the ideal filter indicates that the filter must have a straight line, or *linear phase* characteristic, since only a straight line can have a derivative which is a constant, as required by (8.103). We expect of course that this linear phase relation will be true only for input signal frequency components that fall within the range of ω from 0 to 1.

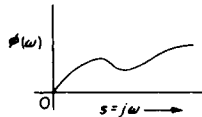


Fig. 8.31

Now $\phi(\omega)$ is an analytic function, and looking at Fig. 8.31, we may decide to no longer restrict $\phi(\omega)$ to the $j\omega$ axis of the s -plane. The analytic continuation of the phase function can be written as

$$T_D(s) = -\frac{d\phi_1(s)}{ds} \quad (8.104)$$

When s is restricted to $j\omega$, then $\phi_1(s)$ reduces to $\phi(\omega)$.

Now from (8.80) and (8.81) let us write

$$\epsilon^{2\phi_1(s)} = \frac{Z_T(s)}{Z_T(-s)} \quad (8.105)$$

We can take the logarithm and arrange as

$$\phi_1(s) = \frac{1}{2} \ln \left[\frac{Z_T(s)}{Z_T(-s)} \right] \quad (8.106)$$

Our low-pass functions have appeared as,

$$Z_T(s) = \frac{1}{1 + a_1s + a_2s^2 + a_3s^3 + \dots + a_ns^n} \quad (8.107)$$

and we have found it convenient to call the polynomial $P(s)$, thus

$$Z_T(s) = \frac{1}{P(s)} \quad (8.108)$$

so that (8.106) becomes

$$\phi_1(s) = \frac{1}{2} \ln \left[\frac{P(-s)}{P(s)} \right] \quad (8.109)$$

and using the derivative of this, (8.104) is found to be

$$T_D(s) = \frac{1}{2} \left[\frac{P'(s)}{P(s)} - \frac{P'(-s)}{P(-s)} \right] \quad (8.110)$$

Now at this point we could proceed to develop a *general* relation between the P terms in (8.110) and the a_k coefficients of (8.107). However, a specific example will be much less involved and will be entirely adequate to show the point we wish to bring out.

Let us consider a third order transfer function with general coefficients as the polynomial

$$Z_T(s) = \frac{1}{1 + a_1s + a_2s^2 + a_3s^3} \quad (8.111)$$

We can very easily convert this into the time delay function $T_D(s)$ by using (8.110). We first list the individual P functions as

$$\left. \begin{aligned} P(s) &= 1 + a_1s + a_2s^2 + a_3s^3 \\ P'(s) &= a_1 + 2a_2s + 3a_3s^2 \\ P(-s) &= 1 - a_1s + a_2s^2 - a_3s^3 \\ P'(-s) &= -a_1 + 2a_2s - 3a_3s^2 \end{aligned} \right\} \quad (8.112)$$

Placing these four parts into (8.110) gives

$$T_D(s) = \frac{a_1 + (3a_3 - a_1a_2)s^2 + a_2a_3s^4}{1 + (2a_2 - a_1^2)s^2 + (a_3^2 - 2a_1a_3)s^4 - a_3^2s^6} \quad (8.113)$$

We are now in a position to choose the coefficients so that (8.113) approximates $T_D(s)$ in a maximally flat manner. There are a number of ways of making (8.113) maximally flat, but the easiest way here is to require that the corresponding coefficients in the numerator and the denominator be equal up to the highest power in the numerator. This process is a general one, but I will avoid giving a proof of it here by saying that "it is outside the scope of this text". Setting the corresponding coefficients equal gives us

$$\left. \begin{aligned} a_1 &= 1 \\ 2a_2 - a_1^2 &= 3a_3 - a_1a_2 \\ a_2^2 - 2a_1a_3 &= a_2a_3 \end{aligned} \right\} \quad (8.114)$$

which we solve to obtain

$$\left. \begin{aligned} a_1 &= 1 \\ a_2 &= \frac{2}{5} \\ a_3 &= \frac{1}{15} \end{aligned} \right\} \quad (8.115)$$

The required transfer function (8.111) is therefore

$$Z_T(s) = \frac{1}{1 + s + \frac{2s}{5} + \frac{s^3}{15}} \quad (8.116)$$

which of course can also be written in the preferred form as

$$Z_T(s) = \frac{15}{s^3 + 6s^2 + 15s + 15} \quad (8.117)$$

Having obtained the required transfer function, we can design the physical network by using the technique developed in art. 8.6. In fact, if we use the model shown in Fig. 8.17, we can equate the *abc* coefficients of (8.43) to the corresponding coefficients in (8.116) here, solve for *a*, *b*, and *c*, and we have the new network finished. More formal procedures for solution will be treated in Chapter X.

8.14. The linear-phase approximation

In this article we will develop an alternate approach to the same maximally flat *time-delay* or *linear-phase* filter which we have just considered. We hope to find several points of theoretical interest

and practical design procedures. To begin, let us consider $Z_T(s)$ in the form

$$Z_T(s) = \frac{G(s)}{m(s) + n(s)} \quad (8.118)$$

where we see that $G(s)$ is the entire numerator polynomial and $m(s)$ and $n(s)$ are the even and odd parts of the denominator polynomial. In some cases $G(s)$ may simply be 1.0 of course.

We now want to form $Z_T(-s)$. Writing the denominator is easy, we merely change the sign on the odd part of $n(s)$. We must be very careful however, about the sign of $G(-s)$, for observe closely that the sign of $G(-s)$ is plus or minus, depending on whether $G(s)$ is even or odd. i.e.

$$\left. \begin{aligned} G(-s) &= G(s), G(s) \text{ even} \\ G(-s) &= -G(s), G(s) \text{ odd} \end{aligned} \right\} \quad (8.119)$$

Therefore, when we write the $A(s)$ function, we must choose its proper sign, depending on whether the numerator polynomial of $Z_T(s)$ is even or odd. As before,

$$A(s) = \frac{Z_T(s)}{Z_T(-s)} \quad (8.120)$$

Writing $Z_T(s)$ in terms of (8.118) and (8.119), we have

$$A(s) = \frac{m(s) - n(s)}{m(s) + n(s)}, G(s) \text{ even} \quad (8.121)$$

or

$$A(s) = \frac{n(s) - m(s)}{m(s) + n(s)}, G(s) \text{ odd} \quad (8.122)$$

Back in (8.88) we wrote

$$A(j\omega) = \frac{1 + j \tan \phi(\omega)}{1 - j \tan \phi(\omega)} \quad (8.123)$$

which may be solved for $\tan \phi(\omega)$ as

$$j \tan \phi(\omega) = \frac{A - 1}{A + 1} \quad (8.124)$$

and when (8.121) or (8.122) is used for A in this expression we have two cases:

$$j \tan \phi = -\frac{n}{m}, G(s) \text{ even} \quad (8.125)$$

and

$$j \tan \phi = -\frac{m}{n}, G(s) \text{ odd} \quad (8.126)$$

We will call attention to these last two equations later.

To return to the main theme of this article, let us consider a unit step-function of voltage, the Laplace transform of which is

$$U(t) \rightarrow \frac{1}{s} \quad (8.127)$$

Back in Chapter V, Fig. 5.10 and Eq. (5.46), we found that the *displaced*, or in our present case *delayed* step-function had the Laplace transform

$$U(t - T_D) \rightarrow \frac{\varepsilon^{-T_D s}}{s} \quad (8.128)$$

so that the transfer function of the ideal flat delay filter is simply the ratio of output to input as always, and is

$$Z_T(s) = \varepsilon^{-T_D s} \quad (8.129)$$

or

$$Z_T(s) = \frac{1}{\varepsilon^{T_D s}} \quad (8.130)$$

The first thought that occurs is to approximate the denominator of (8.130) by expanding into an infinite series and then using only the first few terms. We could normalize the time delay T_D to 1.0 second and write

$$Z_T(s) = \frac{1}{1 + s + \frac{s^2}{2} + \frac{s^3}{6} + \dots} \quad (8.131)$$

and omit all terms after perhaps the third-order. This would indeed provide an approximation, but not a very good one, as we can see

by comparing the coefficients here with those of (8.116) which were optimum.

Evidently the neglect of the remaining terms causes such a modification that this method is worthless as an approximation. By use of a test from formal network synthesis, we find that for the truncated series of order greater than 4, the polynomials are not even Hurwitz, and thus we cannot use them no matter how good the approximation.

For a different approach, let us normalize T_D to unity and use a basic identity to write

$$Z_T(s) = \frac{1}{\cosh s + \sinh s} \quad (8.132)$$

For the denominator, we can make the identification

$$\cosh s + \sinh s = m(s) + n(s) \quad (8.133)$$

However, we must be aware that this equation is approximate rather than exact, as we have always considered $m(s)$ and $n(s)$ to be polynomials of finite length rather than an infinite series. However, if we can find a suitable pair of finite polynomials for an accurate approximation, it will be permissible to consider (8.133) not as an *exact*, but as an *ideal* or *optimum* relation.

Because of the less than perfect correspondence between the algebraic $m(s)$ and the transcendental $\cosh s$, etc., we cannot use either (8.125) or (8.126) to solve directly for the phase function. We can set up some experimental relations between the parts of (8.133) however. We will examine the ratio

$$\coth s = \frac{m(s)}{n(s)} \quad (8.134)$$

We have no assurance at the outset that this will provide any useful results, but we know from previous work that the ratio of even to odd or odd to even parts of the transfer function is the phase function. Hence we say that if we can choose values for $m(s)$ and $n(s)$ so that (8.134) will accurately represent $\coth s$, then (8.134) will be optimally valid and we can write the transfer function as

$$Z_T(s) = \frac{1}{m(s) + n(s)} \quad (8.135)$$

The reader will be familiar with the process of expanding transcendental functions in infinite series, but it may not be so widely known that another procedure is the expansion as an infinite *product*. The *product* expansion of $\coth s$ will be of greater interest to us here, as we can see from this where the poles and zeros of the exact function are located.

The zeros of $\coth s$ are the zeros of $\cosh s$, since $\coth s$ is the ratio of $\cosh s$ to $\sinh s$. From the exponential equivalent of $\cosh s$, we can see that the zeros of $\cosh s$ are at

$$s = \pm j(k + \frac{1}{2})\pi; k = 0, 1, 2, 3 \dots \infty \quad (8.136)$$

Thus

$$\cosh s = \left(1 + \frac{s}{j\frac{\pi}{2}}\right) \left(1 - \frac{s}{j\frac{\pi}{2}}\right) \left(1 + \frac{s}{j\frac{3\pi}{2}}\right) \left(1 - \frac{s}{j\frac{3\pi}{2}}\right) \dots \quad (8.137)$$

The conjugate pairs are combined, and the result is the infinite product set indicated by

$$\cosh s = \prod_{k=0}^{\infty} \left[1 + \frac{s^2}{(k + \frac{1}{2})^2 \pi^2} \right] \quad (8.138)$$

Similarly, the poles of $\coth s$, which are the zeros of $\sinh s$, occur at $s = 0$, and at $s = \pm jk\pi$, so that

$$\sinh s = \prod_{k=1}^{\infty} \left[s \left(1 + \frac{s^2}{k^2 \pi^2} \right) \right] \quad (8.139)$$

so that the phase function $\coth s$ is expressed exactly in pole-zero form as

$$\coth s = \frac{\prod_{k=0}^{\infty} \left[1 + \frac{s^2}{(k + \frac{1}{2})^2 \pi^2} \right]}{\prod_{k=1}^{\infty} \left[s \left(1 + \frac{s^2}{k^2 \pi^2} \right) \right]} \quad (8.140)$$

The pole-zero scheme of the exact function $\coth s$ is shown in Fig. 8.32, and the poles and zeros alternate from $-\infty$ to $+\infty$. An alternating sequence of poles and zeros which lies only on the $j\omega$ axis is called a reactance function.

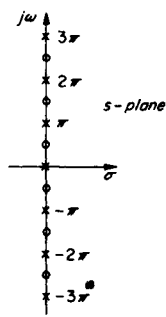


Fig. 8.32

We found earlier that we needed at least one reactive element for each pole or zero in a function. We see therefore that we cannot achieve this linear phase filter with a finite number of impedance elements.

It becomes clear however, that we can devise a most excellent approximation which will hold to any desired degree of accuracy within a limited region of the s -plane. For example, suppose we draw a circle of radius 3.2π , centered at the origin in Fig. 8.32. Within this region we will have seven poles and six zeros. Now if we have waveforms where the highest frequency components of interest lie within our circle, the poles and zeros well outside our circle can be omitted with little effect on performance.

We see clearly that we must make the poles and zeros of our approximating function $m(s)/n(s)$ coincide as exactly as possible with those of Fig. 8.32 near $s = 0$ and out as far along the $j\omega$ axis as we care to use factors for $m(s)$ and $n(s)$. We will be limited only by the number of coils and condensers we can afford to use, and by the patience of adjusting them to precise values.

The best treatment at this point is to recognize that since $\coth s$ is a reactance function, we can expand it as we would expand an L - C impedance network, by dividing and reciprocating to form a continued fraction. We can use the infinite series and long division,

or we can look up the result in a handbook, to write $\coth s$ as the continued fraction

$$\coth s = \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{1}{\frac{5}{s} + \frac{1}{\frac{7}{s} + \frac{1}{\frac{2n-1}{s}}}}} \quad (8.141)$$

Suppose we want to make a third-order filter, then with $n = 3$, we have

$$\coth s = \frac{1}{s} + \frac{1}{\frac{3}{s} + \frac{5}{s}} = \frac{m(s)}{n(s)} \quad (8.142)$$

This is rearranged to be

$$\frac{m(s)}{n(s)} = \frac{15 + 6s^2}{15s + s^3} \quad (8.143)$$

Since the sum of $m(s)$ and $n(s)$ is the denominator of $Z_T(s)$, we have

$$Z_T(s) = \frac{15}{s^3 + 6s^2 + 15s + 15} \quad (8.144)$$

where we have chosen the arbitrary multiplier to give unity gain at $s = 0$. Once the transfer function is available, we can find a suitable network by use of the same procedure that we used in the Butterworth case. A more formal procedure will also be developed in Chapter X.

8.15. Bessel polynomials, or linear-phase filter design made easy

The transfer function we have just derived (8.144) should now be compared with the result of our first procedure, which gave (8.117). We see that both transfer functions are identical! This should be encouraging, as both were attempts to optimize an approximation for a linear-phase filter.

By this time the reader will be wondering what we have accomplished by this detailed and lengthy effort, and whether the results are interesting and useful enough to have spent this amount of time. In this article we will attempt to show that the linear-phase transfer function is closely related to a large class of other problems.

This article will be very brief, because to be useful in practice, the relations we are about to present must be available in clear, simple format, and not obscured by a lengthy and abstract mathematical development. We have already examined the linear-phase problem in enough detail to have some feel for the complexity, now let us make some observations.

We begin by defining a new polynomial $P_n(x)$ as follows:

$$P_n(x) = \sum_{k=0}^n \frac{|n+k| x^k}{|n-k| k 2^k} \quad (8.145)$$

The values of this polynomial are shown for several orders n as

$$\left. \begin{aligned} P_1(x) &= 1 + x \\ P_2(x) &= 1 + 3x + 3x^2 \\ P_3(x) &= 1 + 6x + 15x^2 + 15x^3 \\ P_4(x) &= 1 + 10x + 45x^2 + 105x^3 + 105x^4 \end{aligned} \right\} \quad (8.146)$$

It will be found on examination that the polynomial $P_n(x)$ is an exact solution for the special Bessel equation

$$x^2 \frac{d^2 y}{dx^2} + 2(x+1) \frac{dy}{dx} - n(n+1)y = 0 \quad (8.147)$$

Through substitutions, change of variables, and other transformations, Bessel's equation can assume a number of modified forms. The one here is related to Bessel functions of half-integral order, since if we let $x = -j/w$,

$$P_n\left(\frac{1}{j\omega}\right) = \frac{\varepsilon^{j\omega}}{j^n} \sqrt{\frac{\pi\omega}{2}} \left[(-1)^n J_{-(n+1/2)}(\omega) - j J_{n+1/2}(\omega) \right] \quad (8.148)$$

We merely show the relation, details are covered in mathematics texts and are of no interest in our filter designs.

Let us change the variable in (8.145) so that we have a Bessel

polynomial in $1/s$ instead of x . This can be done by inspection, and we have

$$P_n\left(\frac{1}{s}\right) = \sum_{k=0}^n \frac{|n+k|}{|n-k|k} \frac{1}{2^k s^k} \tag{8.149}$$

We now form the denominator of the linear-phase transfer function $Z_T(s)$ by multiplying the Bessel polynomial in (8.149) by s^n . Thus our complete transfer function is

$$Z_T(s) = \frac{K}{s^n P_n\left(\frac{1}{s}\right)} \tag{8.150}$$

The constant K is chosen by inspection for each order so that $Z_T(s)$ is unity for $s = 0$. The denominators of (8.150) for the first five orders n are shown in Table 8.1 for convenience.

TABLE 8.1

n	$s^n P_n\left(\frac{1}{s}\right)$
1	$1 + s$
2	$3 + 3s + s^2$
3	$15 + 15s + 6s^2 + s^3$
4	$105 + 105s + 45s^2 + 10s^3 + s^4$
5	$945 + 945s + 420s^2 + 105s^3 + 15s^4 + s^5$

It will not be necessary to factor these polynomials when building passive filters, but if one is designing active filters it will be necessary to have the factors of the single and conjugate poles of $Z_T(s)$, and so we also give these in Table 8.2 for convenience.

TABLE 8.2

n	Factors of $s^n P_n\left(\frac{1}{s}\right)$
3	$(s + 2.3222)(s^2 + 3.6678s + 6.4595)$
4	$(s^2 + 5.7924s + 9.1401)(s^2 + 4.2076s + 11.488)$
5	$(s + 3.6467)(s^2 + 6.7039s + 14.272)(s^2 + 4.6493s + 18.156)$

The writer's philosophy is that usually one does not have to know the extreme details of a process in order to use it for practical benefit.

Few of us understand the fine points and details of automotive engineering, but this does not keep us from making good use of the product. Having gone through some fairly intricate discussion of both the Butterworth and Bessel polynomial filters, most readers can now use the tabulated results in future work without need to remember the fine details of the derivations. We even include some normalized Butterworth filters in the appendix so that in this case one does not even need the transfer functions.

8.16. Finding the transfer function from a given magnitude

In this article we will discuss the procedure for finding the complete transfer function $Z_T(s)$ when only the magnitude is given. We have seen for example that the Butterworth transfer functions gave rise to a magnitude which was maximally flat, and which was a function of ω^2 . In the process of finding the magnitude of a transfer function we have always had to take the square root of a sum of squares, hence any given amplitude function must have only ω^2 or ω^m terms, where m is even.

As a preliminary step, let us write

$$Z_T(j\omega) = |Z_T(j\omega)|e^{j\phi(\omega)} \quad (8.151)$$

and also the conjugate value

$$Z_T(-j\omega) = |Z_T(j\omega)|e^{-j\phi(\omega)} \quad (8.152)$$

Now as a temporary aid in organizing our work, let us define $B(j\omega)$ as the product of the conjugates. Thus

$$B(j\omega) = Z_T(j\omega)Z_T(-j\omega) = |Z_T(j\omega)|^2 \quad (8.153)$$

We note that the angle becomes zero when we multiply (8.151) and (8.152). It will be more convenient to work with the squared magnitude, and of course if we are given the magnitude we can always square it.

In connection with $B(j\omega)$, we do not have to restrict this to the $j\omega$ axis. We can write

$$B(s) = Z_T(s)Z_T(-s) \quad (8.154)$$

which is valid anywhere in the s -plane. We must be cautious to note however, that $B(s)$ is *not* equal to the square of the magnitude of $Z_T(s)$, except on the $s = j\omega$ axis.

Our procedure now becomes quite simple. Given the j -axis

squared magnitude, we first replace ω^2 by $-s^2$, this gives us $B(s)$. Then, knowing by (8.154) that $B(s)$ is the product of $Z_T(s)$ and $Z_T(-s)$, it remains only to factor $B(s)$. When this is done, any poles or zeros in the right-half-plane are obvious, and are assigned to $Z_T(-s)$. The remaining left-half-plane factors belong to $Z_T(s)$, which is the transfer function we seek.

The foregoing word description may be a bit obscure, hence it is best to illustrate this procedure with a familiar example. We are given the magnitude:

$$|Z_T(j\omega)| = \frac{1}{\sqrt{1 + \omega^{2n}}} \quad (8.155)$$

which we recognize as the Butterworth amplitude response. We square this to get

$$|Z_T(j\omega)|^2 = \frac{1}{1 + \omega^{2n}} \quad (8.156)$$

We next replace ω^2 by $-s^2$, and then (8.153) shows that

$$B(s) = \frac{1}{1 + (-s^2)^n} \quad (8.157)$$

In the general case, $B(s)$ would have a numerator polynomial and a denominator polynomial which would each have to be factored.

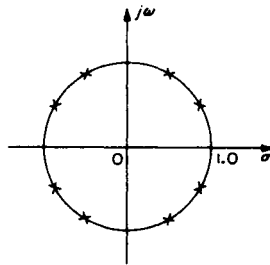


Fig. 8.33

In this simple case, we need only factor the simple denominator. We see that zeros of the denominator occur when

$$(-s^2)^n = -1 \quad (8.158)$$

or at

$$s^{2n} = 1; n \text{ odd}$$

$$s^{2n} = -1; n \text{ even}$$

For $n = 4$, as an example, we have eight roots given by

$$s = \sqrt[8]{-1} \quad (8.159)$$

all of which are equally spaced on the unit circle as shown in Fig. 8.33.

We discard the four right-half-plane poles as belonging to $Z_T(-s)$, and keep the four left-half-plane poles as the required $Z_T(s)$. The product of all four poles gives

$$Z_T(s) = \frac{1}{s^4 + 2.6131 s^3 + 3.4142 s^2 + 2.6131 s + 1} \quad (8.160)$$

The reader can see that it is very easy to get the general transfer function of practical filters if the magnitude is given. Having the transfer function, one can then synthesize the filter.

8.17. Tchebycheff and Legendre polynomial filters

Although we will not discuss them in great detail, we should at least mention several other types of filters which are commonly used. The reader's background in Laplace transform applications is by now broad enough to make good use of some additional data which we will provide in this article, even though the origin of most of it is outside the scope of this text.

It will be observed that our low-pass filters can always be described in the form

$$|Z_T(j\omega)| = \frac{K}{\sqrt{1 + f(\omega^2)}} \quad (8.161)$$

where K is usually chosen to make the gain equal to one at zero frequency, and $f(\omega^2)$ is some polynomial in ω^2 . In the Butterworth case

$$f(\omega^2) = \omega^{2n} \quad (8.162)$$

We have discussed the Butterworth and the Bessel Polynomial filters in terms of polynomials in s rather than as functions of ω^2 , but the reader can see that (8.161) applies to both cases.

One widely used polynomial that the reader will sooner or later

come to work with is the Tchebycheff polynomial $T_n(\omega)$ which is defined as

$$T_n(\omega) = \cos (n \cos^{-1} \omega); \quad -1 \leq \omega \leq 1 \quad (8.163)$$

and where the first six polynomials are shown in Table 8.3.

TABLE 8.3

n	$T_n(\omega) = \cos (n \cos^{-1} \omega)$
0	1
1	ω
2	$2\omega^2 - 1$
3	$4\omega^3 - 3\omega$
4	$8\omega^4 - 8\omega^2 + 1$
5	$16\omega^5 - 20\omega^3 + 5\omega$
6	$32\omega^6 - 48\omega^4 + 18\omega^2 - 1$

In the range of ω from -1 to $+1$ we see from (8.163) that $T_n(\omega)$ merely oscillates between -1 and $+1$. However, the polynomials as listed in Table 8.3 obviously have values for all values of ω . We note that as ω becomes greater than 1, the polynomial ceases to become oscillatory and begins to increase continuously with increasing ω . The rate is seen to increase rapidly with larger values of n .

We can reduce the peak-to-peak magnitude of the oscillatory function by multiplying the polynomial by the constant ϵ , and when we use this result for $f(\omega^2)$ in the general form (8.161), we have

$$|Z_T(\omega)|^2 = \frac{1}{1 + \epsilon^2 T_n^2(\omega^2)} \quad (8.164)$$

If ϵ is made quite small, the magnitude of $Z_T(\omega)$ will approximate unity in the range $-1 \leq \omega \leq 1$, and will rapidly approach zero for greater ω .

Suitable choice of ϵ can make the equal ripples within the pass-band lie between any desired levels, while choice of n determines how rapidly the response falls off beyond $\omega = 1$.

One can choose a value for ϵ , choose a suitable order polynomial, and find the corresponding $Z_T(s)$ as in previous work. Since there are an infinite number of choices for ϵ , we will not show completed filters. One often chooses ϵ to have a 1-db, 2-db, or perhaps $\frac{1}{2}$ -db ripple in the pass-band.

Regardless of the choice of ϵ or n , the poles of the Tchebycheff

filter will always be found to lie on an ellipse, with the major axis vertical and centered on the origin in the s -plane. Details are covered in most texts on network theory.

The chief advantages of the Tchebycheff filter over the Butterworth type is that although the Butterworth has a flatter response near the origin, the Tchebycheff filter has less *total* error, and the error is spread uniformly over the pass-band.

If the criterion is to have the maximum rate of attenuation past the band edge for a given variation within the pass-band, then the Tchebycheff is optimum from among all possible filters.

Still another criterion might be for the filter to have the greatest possible rate of attenuation past the edge of the band, but to have no ripple within the pass-band. By this definition, we could permit small, smooth, downward steps at intervals within the pass-band, but no upward steps, and with the regions between the small steps maximally flat. This would be called a monotonically decreasing response, and could be shown as in Fig. 8.34.

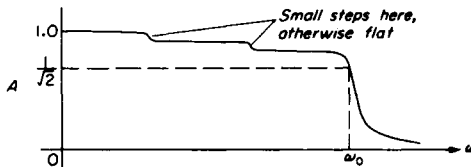


Fig. 8.34

It can be shown that this type of monotonically decreasing filter response can be achieved by the use of Legendre polynomials for $f(\omega^2)$ in (8.161).

Legendre polynomials appear in the study of the Legendre differential equation, similar to the case of Bessel's equation and the Bessel polynomials. We had no interest in the Bessel differential equation for filter work, but we did make good use of the Bessel polynomials in the easy design of linear-phase filters. In the same way, we can use the Legendre polynomials to achieve a purpose, even though we are not in a position to learn about their detailed mathematical origin and history. We never want to belittle the importance of the pure mathematical foundation for these functions, but that is for another time and another course.

We list the Legendre polynomials of order 3 through 6 in Table 8.4 in the format required for use in filter problems.

TABLE 8.4

n	$L_n(\omega^2)$
3	$3\omega^5 - 3\omega^4 + \omega^2$
4	$6\omega^5 - 8\omega^4 + 3\omega^4$
5	$20\omega^{10} - 40\omega^8 + 28\omega^6 - 8\omega^4 + \omega^2$
6	$50\omega^{12} - 120\omega^{10} + 105\omega^8 - 40\omega^6 + 6\omega^4$

It is noted in passing that there is no ω^2 term in the even-order polynomials.

If one makes use of the procedure given in art. 8.16, it will be relatively easy to find the corresponding normalized transfer functions of s . For order $n = 3$ for example,

$$Z_T(s) = \frac{0.577}{s^3 + 1.31s^2 + 1.359s + 0.577} \quad (8.165)$$

For $n = 4$

$$Z_T(s) = \frac{0.408}{s^4 + 1.563s^3 + 1.888s^2 + 1.242s + 0.408} \quad (8.166)$$

For $n = 5$

$$Z_T(s) = \frac{0.224}{s^5 + 1.551s^4 + 2.203s^3 + 1.693s^2 + 0.898s + 0.224} \quad (8.167)$$

and for $n = 6$

$$Z_T(s) = \frac{0.141}{s^6 + 1.726s^5 + 2.69s^4 + 2.434s^3 + 1.633s^2 + 0.689s + 0.141} \quad (8.168)$$

8.18. Active n th order low-pass filters

The n th order low-pass filter transfer function can be factored into a set of products, each term of which is generated by either a simple pole on the $-\sigma$ axis, or a complex conjugate pole-pair in the left-half s -plane. In this article we will discuss the Butterworth function, although the procedure is equally valid for all low-pass filters.

Now the reader may have observed that any passive network which consists only of resistors and condensers has poles which lie *only* on the $-\sigma$ axis. If no inductors are present, any physical *passive* network must have poles only on the $-\sigma$ axis. We should

be slightly more specific and say that if the poles of any *passive* network are to lie *off* the $-\sigma$ axis in the s -plane, then both L and C must be present in the network.

Since we have seen in our previous work that most useful transfer functions have poles which are distributed throughout the s -plane, it becomes clear that we cannot build the Butterworth filters for example, with only resistors and condensers (except for the first order, which is a trivial case).

It is often desirable however, to eliminate the inductances from electronic circuits, and to work only with R and C components. If we choose to design our filter networks without inductances, we must add active elements to be able to move the poles off the $-\sigma$ axis and out into the complex part of the plane.

The real problem then, is to devise electronic circuitry to generate the terms required for the complex conjugate pole-pairs of the transfer functions. Let us develop the procedure by means of an example.

Consider the second-order Butterworth filter, which has poles shown in Fig. 8.35

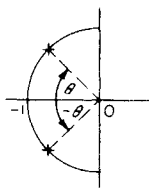


Fig. 8.35

where $\theta = \pm 45^\circ$ from the $-\sigma$ axis.

We see that this configuration creates a pole-pair which has the transfer function

$$Z_T(s) = \frac{1}{s^2 + 2s \cos \theta + 1} \quad (8.169)$$

Since any complex conjugate pole-pair can be normalized to have unity radius, and some angle θ as shown, (8.169) can also apply to any pole-pair whatever, and is not limited to Butterworth filters only. In the Butterworth example however, the form becomes

$$Z_T(s) = \frac{1}{s^2 + \sqrt{2}s + 1} \quad (8.170)$$

Now let us pause a moment and look at Fig. 8.36.

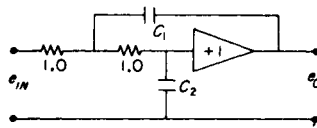


Fig. 8.36

The two resistors have been normalized to unity, and the amplifier has unity gain and zero phase shift. This amplifier is particularly simple, as we see that it will be a cathode follower or emitter follower. The only requirements are that the amplifier provide low output impedance and have high input impedance, so as to isolate the voltage across C_2 from the output terminals.

Further, we see that suitable d.c. bias is particularly easy to apply to an emitter follower with the network arrangement of Fig. 8.36. When we analyze the circuit, we find that the transfer function is

$$Z_T(s) = \frac{1}{s^2 C_1 C_2 + s 2C_2 + 1} \quad (8.171)$$

Comparing (8.171) with (8.169), it is easily seen that this active network will generate the required complex conjugate pole-pair if

$$C_1 C_2 = 1 \quad (8.172)$$

$$2C_2 = 2 \cos \theta \quad (8.173)$$

or, we require that

$$C_1 = \sec \theta \quad (8.174)$$

$$C_2 = \cos \theta \quad (8.175)$$

To make the second-order Butterworth filter then, we choose

$$\left. \begin{aligned} C_1 &= \sqrt{2} \\ C_2 &= 1/\sqrt{2} \end{aligned} \right\} \quad (8.176)$$

so that the network has the Butterworth transfer function (8.170).

We see that since the output is at low impedance, we can cascade these networks to generate any number of complex conjugate pole-pairs, without one pair reacting with another. If one *odd* pole

on the $-\sigma$ axis is required for an odd-order filter, it can be generated by adding on a single R - C passive section at the end of the active networks.

We see that the second-order transfer functions will require one transistor. The third orders will require one transistor and a separate R - C section at the output, the fourth-order filters will require only two transistors, etc., one transistor emitter follower being required for each conjugate pole-pair in the transfer function.

Quite often it will be easier and less expensive to use one or two transistors and a small amount of d.c. power rather than to make the filter strictly passive and use inductances.

For the reader's convenience, several orders of active Butterworth filters in normalized form are shown in Appendix I-c.

The only two cases I can think of where this active type of filter might not be too good are where the filter is working at extremely low signal levels, down in fractions of microvolts, in which case transistor noise could defeat the purpose, and in cases where the signal contains a d.c. level as well as the low-frequency signal spectrum. The transistor emitter follower will have a small d.c. offset voltage which, because of drift, might or might not prove troublesome, although this offset can be reduced almost to zero by proper design.

8.19. Optimum n -section R - C filters for high voltage power supplies

In many power supplies for cathode ray tubes, photo multipliers, etc., the currents are so low and the impedances so high that it is often impractical to use inductances in the filter networks. We then resort to R - C filters.

Circuit losses and available space will usually dictate the maximum amount of R and C that can be used. For example, maximum allowable R will usually be limited by the permissible d.c. voltage drop, while maximum C will be limited by voltage rating, cost, or physical space available.

At any rate, once a permissible value of *total* series resistance and *total* shunt capacity has been determined, it will be our purpose here to decide whether it is more desirable to lump all the R and C into one large single section, or to break up and distribute the given R and C into n smaller sections, and if the latter proves more suitable, how do we decide on the number of n -sections.

Let us examine the n -section filter shown in Fig. 8.37.

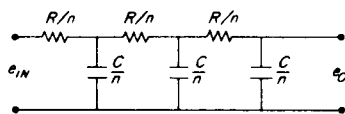


Fig. 8.37

The amplitude A of the transfer function of the network is

$$A = \frac{1}{\sqrt{1 + \dots + \left(\frac{\omega R C}{n}\right)^{2n}}} \quad (8.177)$$

We make the temporary substitution

$$\omega R C = x \quad (8.178)$$

and observe that in all practical cases, $\omega R C$ will be so large that only the last term will be of importance, hence we may omit the 1, and all lower order terms, and write

$$A = \frac{1}{\left(\frac{\omega R C}{n}\right)^n} = \frac{n^{2n}}{x^n} \quad (8.179)$$

or

$$A = \left(\frac{n^2}{x}\right)^n \quad (8.180)$$

We now take the natural logarithm,

$$\ln A = 2n \ln n - n \ln x \quad (8.181)$$

and differentiate with respect to n to have

$$\frac{d \ln A}{dn} = 2 + 2 \ln n - \ln x \quad (8.182)$$

To find the minimum point, we set the derivative to zero, giving

$$\ln n = \frac{\ln(x) - 2}{2} \quad (8.183)$$

or

$$\ln n = \frac{\ln(\omega R C) - 2}{2} \quad (8.184)$$

Suppose we consider a case where

$$\text{Total } R = 1.0 \text{ megohm}$$

$$\text{Total } C = 1.0 \text{ mfd}$$

$$f = 60 \text{ cycles}$$

then

$$\omega RC = 378 \tag{8.185}$$

and when this value is inserted in (8.184) the nearest integral value of $n = 7.0$. Evidently we will have the greatest reduction in ripple if we divide our total R and C into seven equal sections.

Let us test this conclusion by inserting $x = 378$ into (8.180) and solving directly for the gain for from 1 to 10 sections. We tabulate the values in Table 8.5.

TABLE 8.5

n	$\frac{e_0}{e_{IN}} = \left(\frac{n^2}{x}\right)^n$
1	$\frac{1}{378}$
2	$\frac{1}{8930}$
3	$\frac{1}{74000}$
4	$\frac{1}{310\ 000}$
5	$\frac{1}{780\ 000}$
6	$\frac{1}{1\ 360\ 000}$
7	$\frac{1}{1\ 630\ 000}$ ← Lowest gain
8	$\frac{1}{1\ 500\ 000}$
9	$\frac{1}{1\ 050\ 000}$
10	$\frac{1}{593\ 000}$

We see that the ripple is 4310 times lower in the optimum 7-section filter than for exactly the same amount of R and C lumped into a single section.

In every case of R - C filter design for power supplies, there is an optimum number of sections. One finds in many cases that use of the optimum value, found either by analysis or experimental trial and error, can often give dramatic improvement in ripple reduction. To take advantage of the extreme ripple reduction properties of the $n = 7$ section unit discussed here, it is usually necessary to shield some of the filter sections from each other.

CHAPTER IX

SPECIALIZED APPLICATIONS OF THE LAPLACE TRANSFORM

9.1. Functions of \sqrt{s}

It was mentioned early in the book that one of the reasons for using the Laplace transform was to simplify equations. In most cases where one had trigonometric, logarithmic, and exponential quantities for example, the transformed equations were of simple algebraic form. The solution then required only the ordinary manipulations of algebra.

Thus far we have encountered nothing that would suggest that functions of s might become as involved as some of the original functions we were trying to simplify. No attempt will be made to complicate things, but we should discuss one or two cases which involve functions of s to fractional powers. Most readers will have seen forms which involve the square root of s in tables of Laplace transforms. It is interesting to see what meaning if any we can give to such functions in our electronics work.

Most readers will have had some contact with transmission lines in theory or practice or both. We usually think of a transmission line as having distributed R , L , and C , as opposed to the lumped R , L , and C elements of our usual networks. We do not need to become involved here in a detailed discussion of transmission lines, but we can make use of a result or two of transmission line theory.

The concept of the characteristic impedance of transmission lines will be more or less familiar to most of you. The idea is that if we have a uniform line of perhaps 600 ohms characteristic impedance, when the far end of this line is terminated in a 600 ohm resistive load, the input will also be 600 ohms resistive regardless of the length of the line.

If we refer to standard texts on transmission lines, we usually find at the very beginning that the line is represented as being made up of elemental cascaded sections which have some series impedance,

and some shunt admittance. The series impedance can be perfectly general of course, as can the shunt admittance.

We should properly refer to either impedance per *unit length* when speaking of the differential section of a truly distributed line, or the impedance per *unit section* if the line is simulated by a large

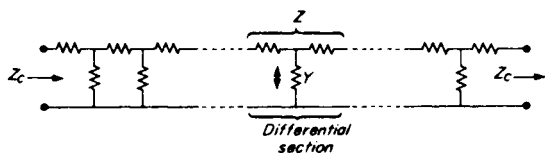


Fig. 9.1

number of small lumped sections. In Fig. 9.1 the Z is measured in the *forward* direction, while the Y is measured *across* the differential sections.

Transmission line theory gives us the result that the characteristic impedance of such a transmission line is given by

$$Z_c = \sqrt{\frac{Z}{Y}} \quad (9.1)$$

In the case of the lumped line, Z and Y are the values for each T-section. In a real distributed line, such as a radio frequency transmission line which carries power to an antenna, the series impedance will be mostly inductive, and the shunt admittance will be mostly capacitive so that

$$Z = sL/l \quad (9.2)$$

$$Y = sC/l \quad (9.3)$$

The characteristic impedance of such an *r-f* line will thus be

$$Z_c = \sqrt{\frac{sL/l}{sC/l}}$$

or

$$Z_c = \sqrt{\frac{L}{C}} \quad (9.4)$$

and since the s factor cancels, we see that the line is purely resistive. It must of course be terminated in a resistance equal to Z_c to obey the rules.

Now, suppose we consider a rather strange looking transmission line where the series elements are resistive and where the shunt admittance is capacitive, as in Fig. 9.2.

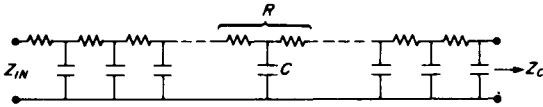


Fig. 9.2

For the characteristic impedance, which is also the input impedance of the terminated line, we have from (9.2) and (9.3)

$$Z = R \tag{9.5}$$

$$Y = sC \tag{9.6}$$

We have already become familiar with *normalized* networks, so to simplify appearance, let us normalize the R to 1Ω and the C to 1 F . (9.1) then gives us the input impedance as

$$Z_{IN} = \frac{1}{\sqrt{s}} \tag{9.7}$$

Now let us make this line of a number of sections and enclose it in a box with only the two terminals of the input brought to the outside. If we keep what is inside the box a secret, we need only label the box as a two-terminal impedance which has the unusual value $1/\sqrt{s}$ as in Fig. 9.3. We can place this beside the other three

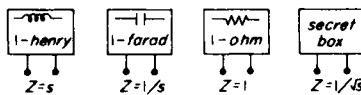


Fig. 9.3

components, a one-farad condenser, a one-ohm resistor, and a one-henry inductor, and consider that we now have four basic, passive, network elements.

Since the uninitiated will not know what is inside our secret box, we can merely call it Z^{sb} and use it as any other impedance in any network, perhaps as in Fig. 9.4.

If anyone should be concerned about having thousands of little $R-C$ sections inside the box, we can point out that since the indi-

vidual sections are extremely lossy, after the signal applied to the input terminals has traveled through four or five sections, it will be reduced essentially to zero. For this reason a very few sections will serve to make up our impedance $1/\sqrt{s}$ quite accurately. We do not even have to worry about properly terminating the network

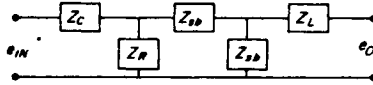


Fig. 9.4

for the same reason. If we wish to provide a d.c. path, we merely short the line. If we wish it insulated for d.c., we can leave it unshorted. The reader will be able to choose suitable values for good performance over an intended frequency range.

9.2. Application of the impedance $1/\sqrt{s}$ in oscillator design

Now that we have available this rather peculiar impedance $1/\sqrt{s}$, let us consider how it can be used in one very practical application. The reader will recall that in art. 6.4 we studied the Wien-bridge oscillator and the R - C network which is the frequency determining part of the system. We found (6.43) that the frequency of oscillation was

$$\omega = \frac{1}{RC} \quad (9.8)$$

or in other words, frequency is inversely proportional to C raised to the first power. We recall further that in the case of a resonant coil-condenser, the frequency is inversely proportional to C raised to the one-half power.

$$\omega = \frac{1}{\sqrt{LC}} \quad (9.9)$$

Let us now replace the resistors in the Wien-bridge network of

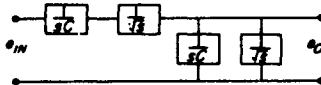


Fig. 9.5

Fig. 6.8 with our new impedance $1/\sqrt{s}$. We can normalize this part

to unity, but we will keep the capacity general, as we may want to vary it later on. The new network is now shown in Fig. 9.5.

We can find the transfer function by any one of the usual methods. In this simple case, we can combine the parts into one series element Z and one shunt element Y , where

$$Z = \frac{1 + C\sqrt{s}}{sC} \quad (9.10)$$

and

$$Y = sC + \sqrt{s} \quad (9.11)$$

as shown in Fig. 9.6.

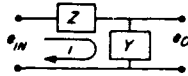


Fig. 9.6

We then may write

$$i = e_0 Y \quad (9.12)$$

$$e_{IN} = e_0 + iZ \quad (9.13)$$

or

$$e_{IN} = e_0 + e_0 YZ \quad (9.14)$$

$$\frac{e_{IN}}{e_0} = 1 + YZ \quad (9.15)$$

and using (9.10) and (9.11),

$$\frac{e_{IN}}{e_0} = 1 + (sC + \sqrt{s}) \left(1 + \frac{C\sqrt{s}}{sC} \right) \quad (9.16)$$

This is actually the reciprocal of the transfer function e_0/e_{IN} , but it does not matter for our purpose here.

$$\frac{e_{IN}}{e_0} = 1 + \frac{sC + \sqrt{s} + sC^2\sqrt{s} + sC}{sC} \quad (9.17)$$

$$\frac{e_{IN}}{e_0} = 1 + \frac{sC}{sC} + \frac{\sqrt{s}}{sC} + C\sqrt{s} + \frac{sC}{sC} \quad (9.18)$$

$$\frac{e_{IN}}{e_0} = 3 + \frac{1}{C\sqrt{s}} + C\sqrt{s} \quad (9.19)$$

which is a rather simple result.

It is now convenient to change to $j\omega$ notation.

$$s = j\omega \quad (9.20)$$

or

$$\sqrt{s} = \sqrt{j\omega} \quad (9.21)$$

$$\sqrt{s} = \sqrt{\frac{\omega}{2}} + j\sqrt{\frac{\omega}{2}} \quad (9.22)$$

With this substitution, (9.19) becomes

$$\frac{e_{IN}}{e_0} = 3 + \frac{1}{C\left(\sqrt{\frac{\omega}{2}} + j\sqrt{\frac{\omega}{2}}\right)} + C\left(\sqrt{\frac{\omega}{2}} + j\sqrt{\frac{\omega}{2}}\right) \quad (9.23)$$

The reader should carry out the simple algebra and get this into standard complex number form $A + jB$.

$$\frac{e_{IN}}{e_0} = \left[3 + \frac{1}{C\sqrt{2\omega}} + C\sqrt{\frac{\omega}{2}}\right] + j\left[C\sqrt{\frac{\omega}{2}} - \frac{1}{C\sqrt{2\omega}}\right] \quad (9.24)$$

Now in the Wien-bridge oscillator, we must always have the network phase shift be zero at the frequency of oscillation, and this is most easily done by setting the j -term in (9.24) to 0. So from (9.24) we have the information

$$C\sqrt{\frac{\omega}{2}} - \frac{1}{C\sqrt{2\omega}} = 0 \quad (9.25)$$

$$C^2\sqrt{\frac{\omega}{2}} = \frac{1}{\sqrt{2\omega}} \quad (9.26)$$

squaring gives

$$\frac{C^4\omega}{2} = \frac{1}{2\omega} \quad (9.27)$$

$$\omega^2 = \frac{1}{C^4} \quad (9.28)$$

and finally,

$$\omega = \frac{1}{C^2} \quad (9.29)$$

or if we wish

$$f = \frac{1}{2\pi C^2} \quad (9.30)$$

It is hoped that this result will be interesting and new to many readers. Here we have an oscillator where the frequency varies as the square of the capacity variation, as opposed to the square-root variation in the LC case and the first-power variation in the RC case. Here, a 10 to 1 capacity change will give us a 100 to 1 change in frequency, and we see the ease of building a very wide-range oscillator that covers the entire range without band switching.

As a final step, we see from (9.29) that

$$\sqrt{\omega} = \frac{1}{C} \quad (9.31)$$

and inserting this back into the real part of (9.24) gives

$$\frac{e_{IN}}{e_0} = 3 + \sqrt{2} \quad (9.32)$$

so that our amplifier requires a gain of 4.414 for operation of the oscillator.

9.3. Iterative networks

The reader who has faithfully worked all problems up to this point will have discovered that the classical solution of a third or higher mesh network as discussed in previous articles requires considerable work. The writer suspects that any suggestion on his part to work out transfer functions for five or six mesh networks would make the reader consider switching his interests to medicine or carpentry for a livelihood. To avoid this unpleasant state of events, let us now consider some easier ways to determine the transfer functions when the network consists of many L-shaped cascaded sections.

We are concerned in this text with the Laplace transform and practice with functions of s . For this reason we purposely try to cover a variety of material rather than to consider cases in extreme detail. I have tried to include a few novel and not too well known topics throughout the text. At risk of much severe criticism, I will say that I have never found "signal flow-graph theory" to be of much practical use. Since a large number of practical networks consist of cascaded L-sections however, it is quite useful to consider some simple methods which can be used in place of the Kirchhoff equations and high order determinants.

One method which has been in use for many years requires that

the series elements of the network be labeled as impedances and the shunt elements labeled as admittances, as in Fig. 9.7.

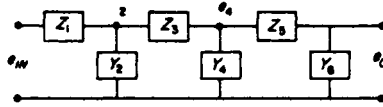


Fig. 9.7

The current in a particular element takes the subscript of that element. Thus the input current in Fig. 9.7 is i_1 , etc. The voltages across the admittances also use the subscripts from the Y 's as shown.

We can start at the output end of the network and work back. Thus we write

$$i_6 = e_0 Y_6 = i_5 \quad (9.33)$$

The next voltage node to the left is e_4 , which is

$$e_4 = e_0 + i_5 Z_5 \quad (9.34)$$

$$e_4 = e_0 + e_0 Y_6 Z_5 \quad (9.35)$$

We now have an internal node, e_4 , expressed in terms of the terminal voltage e_0 and the network parameters Y_6 and Z_5 . We now find i_4 as

$$i_4 = e_4 Y_4 \quad (9.36)$$

and using (9.35) for e_4 ,

$$i_4 = (e_0 + e_0 Y_6 Z_5) Y_4 \quad (9.37)$$

$$i_4 = e_0 Y_4 + e_0 Y_6 Z_5 Y_4 \quad (9.38)$$

The current i_3 is found by inspection as the sum of i_4 and i_5 , using (9.33) and (9.38)

$$i_3 = e_0 Y_4 + e_0 Y_6 Z_5 Y_4 + e_0 Y_6 \quad (9.39)$$

and the next voltage to the left, e_2 , is the sum of e_4 and the iZ voltage across Z_3 . Using (9.35) and (9.39)

$$e_2 = e_0 + e_0 Y_6 Z_5 + e_0 Y_4 Z_3 + e_0 Y_6 Z_5 Y_4 Z_3 + e_0 Y_6 Z_3 \quad (9.40)$$

The current i_2 is of course $e_2 Y_2$, and multiplying (9.40) by Y_2 gives

$$i_2 = e_0 Y_2 + e_0 Y_6 Z_5 Y_2 + e_0 Y_4 Z_3 Y_2 + e_0 Y_6 Z_5 Y_4 Z_3 Y_2 + e_0 Y_6 Z_3 Y_2 \quad (9.41)$$

and finally

$$i_1 = i_2 + i_3 \quad (9.42)$$

$$i_1 = e_0 Y_2 + e_0 Y_6 Z_5 Y_2 + e_0 Y_4 Z_3 Y_2 + e_0 Y_6 Z_5 Y_4 Z_3 Y_2 + e_0 Y_6 Z_3 Y_2 + e_0 Y_4 + e_0 Y_6 Z_5 Y_4 + e_0 Y_6 \quad (9.43)$$

or, if we wish to find e_{IN} ,

$$e_{IN} = e_2 + i_1 Z_1 \quad (9.44)$$

and from (9.40) and (9.43)

$$e_{IN} = e_0 + e_0 Y_6 Z_5 + e_0 Y_4 Z_3 + e_0 Y_6 Z_5 Y_4 Z_3 + e_0 Y_6 Z_3 + e_0 Y_2 Z_1 + e_0 Y_6 Z_5 Y_2 Z_1 + e_0 Y_4 Z_3 Y_2 Z_1 + e_0 Y_6 Z_5 Y_4 Z_3 Y_2 Z_1 + e_0 Y_6 Z_3 Y_2 Z_1 + e_0 Y_4 Z_1 + e_0 Y_6 Z_5 Y_4 Z_1 + e_0 Y_6 Z_1 \quad (9.45)$$

Of course we can factor out the e_0 from each term and bring it to the left-hand side under e_{IN} . The right-hand side of (9.45) then gives us the transfer function if we turn it upside down.

This procedure has been moderately involved, but we must remember that each impedance and admittance was kept perfectly general, so no terms could be combined as has often been the case in previous examples we have treated. Most of the work is merely recopying previous forms and requires little thought.

One distinct advantage of this procedure is that one can find any desired ratios to get other useful quantities. For example, the input impedance Z_{IN} is

$$Z_{IN} = \frac{e_{IN}}{i_1} = \frac{(9.45)}{(9.43)} \quad (9.46)$$

or, one might wish the transfer resistance of the network

$$Z_{21} = \frac{e_0}{i_1} = \frac{e_0}{(9.43)} \quad (9.47)$$

which we see is the same as the reciprocal of (9.43) after the e_0 has been factored out and canceled. Any other ratios can be formed at will. We will develop a system in the next article.

9.4. Transfer functions by tabular methods

Consider the general cascaded L-network shown in Fig. 9.8, with series elements Z and shunt elements Y . We use a slightly different numbering system here, but this is not important.

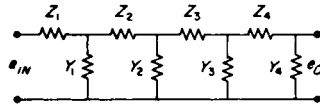


Fig. 9.8

This may be further generalized to include a load Y_5 by adding on another L-section as in Fig. 9.9,

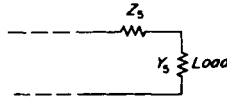


Fig. 9.9

and letting Z_5 approach 0 in the process to follow. We will use Fig. 9.8 alone, however, to illustrate the method. Certain facts about the transfer function are listed here for reference.

A. With the Z - Y notation used here, the numerator of the transfer function will be unity.

B. The denominator will be the sum of numerous terms, the first term of which is also unity.

C. The remaining terms of the denominator will each contain an even number of factors of the form

$$Z_1 Y_1; Z_1 Y_1 Z_2 Y_2; Z_3 Y_3, \text{ etc.}$$

D. There will be no terms of odd factors, such as

$$Z_1 Y_2 Z_4, \text{ etc.}$$

E. All terms will begin with Z , never with Y .

F. The highest order term in the denominator will be the product of all Z and all Y elements. Its coefficient will be unity.

G. The next highest order terms will be products of Z 's and Y 's having two less factors, since no term can have an odd number of factors, etc.

H. For the general network, there will be an unknown number of

terms having two factors, an unknown number having four factors, etc., up to the number of elements in the network.

The present task is to find the number and combination of factors which make up the denominator terms. To begin, we make a schedule as in Table 9.1, writing in a row all the elements of the network, in order, from left to right.

TABLE 9.1

Z_1	Y_1	Z_2	Y_2	Z_3	Y_3	Z_4	Y_4

to Y_n
(When network is longer than Fig. 9.8.)

We now determine all the two-factor terms in the denominator as follows:

Using Table 9.1, write across the rows all permutations of Z and Y in the *forward* direction only. Begin each term with a Z , and the second factor being any Y further to the right. Fig. 9.8 thus becomes

TABLE 9.2

	Z_1	Y_1	Z_2	Y_2	Z_3	Y_3	Z_4	Y_4
1	Z_1	Y_1						
2	Z_1			Y_2				
3	Z_1					Y_3		
4	Z_1							Y_4
5			Z_2	Y_2				
6			Z_2			Y_3		
7			Z_2					Y_4
8					Z_3	Y_3		
9					Z_3			Y_4
10							Z_4	Y_4

The two-factor terms of the transfer function are Z_1Y_1
 $+ Z_1Y_2$
 $+ Z_1Y_3$
 $+ Z_1Y_4$
 $+ Z_2Y_2$
 $+ Z_2Y_3$
 $+ Z_2Y_4$
 $+ Z_3Y_3$
 $+ Z_3Y_4$
 $+ Z_4Y_4$
 or, ten two-factor terms.

TABLE 9.3

	Z ₁	Y ₁	Z ₂	Y ₂	Z ₃	Y ₃	Z ₄	Y ₄
1	Z ₁	Y ₁	Z ₂	Y ₂				
2	Z ₁	Y ₁	Z ₂			Y ₃		
3	Z ₁	Y ₁	Z ₂					Y ₄
4	Z ₁	Y ₁			Z ₃	Y ₃		
5	Z ₁	Y ₁			Z ₃			Y ₄
6	Z ₁	Y ₁					Z ₄	Y ₄
7	Z ₁			Y ₂	Z ₃	Y ₃		
8	Z ₁			Y ₂	Z ₃			Y ₄
9	Z ₁			Y ₂			Z ₄	Y ₄
10	Z ₁					Y ₃	Z ₄	Y ₄
11			Z ₂	Y ₂	Z ₃	Y ₃		
12			Z ₂	Y ₂	Z ₃			Y ₄
13			Z ₂	Y ₂			Z ₄	Y ₄
14			Z ₂			Y ₃	Z ₄	Y ₄
15					Z ₃	Y ₃	Z ₄	Y ₄

The four-factor terms are also the product of each row
 $Z_1 Y_1 Z_2 Y_3$
 $+ Z_1 Y_1 Z_2 Y_3$
 $+ Z_1 Y_1 Z_3 Y_4$
 $+ Z_1 Y_1 Z_3 Y_3$
 $+ \dots$
 etc.

or fifteen terms in all.

Next, using the same procedure, we find the six-factor terms

TABLE 9.4

	Z ₁	Y ₁	Z ₂	Y ₂	Z ₃	Y ₃	Z ₄	Y ₄
1	Z ₁	Y ₁	Z ₂	Y ₂	Z ₃	Y ₃		
2	Z ₁	Y ₁	Z ₂	Y ₂	Z ₃			Y ₄
3	Z ₁	Y ₁	Z ₂	Y ₂			Z ₄	Y ₄
4	Z ₁	Y ₁	Z ₂			Y ₃	Z ₄	Y ₄
5	Z ₁	Y ₁			Z ₃	Y ₃	Z ₄	Y ₄
6	Z ₁			Y ₂	Z ₃	Y ₃	Z ₄	Y ₄
7			Z ₂	Y ₂	Z ₃	Y ₃	Z ₄	Y ₄

The seven 6-factor terms are
 $Z_1 Y_1 Z_2 Y_3 Z_3 Y_3$
 $+ Z_1 Y_1 Z_2 Y_3 Z_3 Y_4$
 $+ Z_1 Y_1 Z_2 Y_3 Z_4 Y_4$
 $+ \dots$
 etc.

The eight-factor terms will have only one permutation, according to the above procedure. It is

$$Z_1 Y_1 Z_2 Y_2 Z_3 Y_3 Z_4 Y_4$$

The final transfer function is

$$Z_T(s) = \frac{1}{1 + \left[\begin{array}{c} \text{sum of} \\ \text{2-factor} \\ \text{products} \end{array} \right] + \left[\begin{array}{c} \text{sum of} \\ \text{4-factor} \\ \text{products} \end{array} \right] + \left[\begin{array}{c} \text{sum of} \\ \text{6-factor} \\ \text{products} \end{array} \right] + \left[\begin{array}{c} \text{one} \\ \text{8-factor} \\ \text{term} \end{array} \right]} \tag{9.48}$$

Assuming that all elements in Fig. 9.8 are different, none of the terms above can be combined. Thus the denominator will consist of

$$1 + 10 + 15 + 7 + 1 = 34 \text{ terms}$$

which is a sizeable expression. The reader should be convinced that this method is advantageous in such cases.

9.5. Simplifications with the tabular method

If each successive section is identical, it would be simpler to use the Pascal Triangle method of article 9.6. However, it will be found that if only some of the Z 's and Y 's are identical, it will be possible to collect *some* terms and thus reduce the complexity of the final transfer function.

EXAMPLE 1. Suppose that all Z elements are identical, and all Y elements are identical. We have only to eliminate the subscripts on all Z and Y terms in Tables 9.2, 9.3, and 9.4 and add all the corresponding terms to get

$$Z_T(s) = \frac{1}{1 + 10ZY + 15Z^2Y^2 + 7Z^3Y^3 + Z^4Y^4} \tag{9.49}$$

which contains only five terms instead of the thirty-four terms for the completely general case.

EXAMPLE 2. Suppose the network originally contained only three meshes, consisting of $Z_1 Y_1 Z_2 Y_2 Z_3 Y_3$, but that we had added Y_4 as a load, with Z_4 inserted to maintain format. Suppose further that all Z 's and Y 's except Z_4 and Y_4 are identical.

In collecting terms from Tables 9.2, 9.3, and 9.4, let Z_4 and all factors containing it be zero.

From Table 9.2, Lines 1,2,3,5,6,8 do not contain Y_4 , hence these lines combine to give $6ZY$.
Line 10 drops out, since Z_4 is 0.
Lines 4,7,9 combine to give $3ZY_4$.
The 2-factor terms are thus:

$$[6ZY + 3ZY_4] \quad (9.50)$$

From Table 9.3, Lines 6,9,10,13,14,15 give products of, zero, since Z_4 is zero.
Lines 1,2,4,7,11 combine to give $5Z^2Y^2$.
Lines 3,5,8,12 combine to give $4Z^2Y_4^2$.
The 4-factor terms are thus:

$$[5Z^2Y^2 + 4Z^2Y_4^2] \quad (9.51)$$

From Table 9.4, Lines 3,4,5,6,7 drop out since Z_4 is 0.
Lines 1 and 2 yield

$$[Z^3Y^3 + Z^3Y_4^3] \quad (9.52)$$

The one 8-factor term is 0, since it contains Z_4 .

Thus, the denominator of the transfer function is 1.0 plus the sums of (9.50), (9.51), and (9.52).

$$Z_T(s) = \frac{1}{1 + 6ZY + 3ZY_4 + 5Z^2Y^2 + 4Z^2Y_4^2 + Z^3Y^3 + Z^3Y_4^3} \quad (9.53)$$

The network with external load Y_4 is shown in Fig. 9.10.

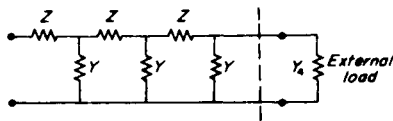


Fig. 9.10

The number of lines in Tables 9.2, 9.3, and 9.4 can be found independently from Pascal's triangle as a verification that no permutation has inadvertently been missed.

EXAMPLE 3. Networks such as we have been discussing are often tapered in such a way as to avoid having one section load a previous section. This may have both practical and theoretical advantages. Suppose we consider the four section network of Fig. 9.11, which we will give an upward taper of three. Each section will have three times the impedance level of the previous section.

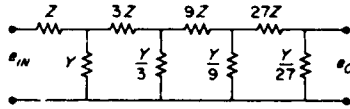


Fig. 9.11

With this taper value, we have the relations

$$Z_2 = 3Z_1; Z_3 = 3Z_2$$

$$Y_2 = \frac{Y_1}{3}; Y_3 = \frac{Y_2}{3} \text{ etc.}$$

This form of tapering can effect considerable simplification in the over-all transfer function.

Beginning with the numbered lines in Table 9.2, we have

- | | |
|---|--|
| 1. $Z_1 Y_1 = Z_1 Y_1$ | 6. $Z_2 Y_3 = \frac{3Z_1 Y_1}{9} = \frac{Z_1 Y_1}{3}$ |
| 2. $Z_1 Y_2 = \frac{Z_1 Y_1}{3}$ | 7. $Z_2 Y_4 = \frac{3Z_1 Y_1}{27} = \frac{Z_1 Y_1}{9}$ |
| 3. $Z_1 Y_3 = \frac{Z_1 Y_1}{9}$ | 8. $Z_3 Y_3 = \frac{9Z_1 Y_1}{9} = Z_1 Y_1$ |
| 4. $Z_1 Y_4 = \frac{Z_1 Y_1}{27}$ | 9. $Z_3 Y_4 = \frac{9Z_1 Y_1}{27} = \frac{Z_1 Y_1}{3}$ |
| 5. $Z_2 Y_2 = \frac{3Z_1 Y_1}{3} = Z_1 Y_1$ | 10. $Z_4 Y_4 = \frac{Z_1 27 Y_1}{27} = Z_1 Y_1$ |

Upon collection of terms, we have

$$4ZY + 3\left(\frac{ZY}{3}\right) + 2\left(\frac{ZY}{9}\right) + \frac{ZY}{27}$$

or, from Table 9.2 we have the result

$$\left[\frac{\text{sum of 2-term}}{\text{products}} \right] = \left[\frac{142ZY}{27} \right] \quad (9.54)$$

From Table 9.4 we have

$$\begin{array}{ll}
 1. \quad Z_1 Y_1 \frac{3Z_1 Y_1}{3} \frac{9Z_1 Y_1}{9} = Z_1^3 Y_1^3 & 5. \quad \frac{Z_1 Y_1}{3} \frac{9Z_1 Y_1}{9} \frac{27Z_1 Y_1}{27} = Z_1^3 Y_1^3 \\
 2. \quad Z_1 Y_1 \frac{3Z_1 Y_1}{3} \frac{9Z_1 Y_1}{27} = \frac{Z_1^3 Y_1^3}{3} & 6. \quad \frac{Z_1 Y_1}{3} \frac{9Z_1 Y_1}{9} \frac{27Z_1 Y_1}{27} = \frac{Z_1^3 Y_1^3}{3} \\
 3. \quad Z_1 Y_1 \frac{3Z_1 Y_1}{3} \frac{27Z_1 Y_1}{27} = Z_1^3 Y_1^3 & 7. \quad \frac{3Z_1 Y_1}{3} \frac{9Z_1 Y_1}{9} \frac{27Z_1 Y_1}{27} = Z_1^3 Y_1^3 \\
 4. \quad Z_1 Y_1 \frac{3Z_1 Y_1}{9} \frac{27Z_1 Y_1}{27} = \frac{Z_1^3 Y_1^3}{3} &
 \end{array}$$

These terms combine to give

$$4Z_1^3 Y_1^3 + 3\left(\frac{Z_1^3 Y_1^3}{3}\right)$$

or, finally

$$\left[\begin{array}{l} \text{sum of 6-term} \\ \text{products} \end{array} \right] = [5Z_1^3 Y_1^3] \quad (9.55)$$

From Table 9.3 we have the following terms

$$\begin{array}{ll}
 1. \quad \frac{Z_1 Y_1}{3} \frac{3Z_1 Y_1}{3} = Z_1^2 Y_1^2 & 9. \quad \frac{Z_1 Y_1}{3} \frac{27Z_1 Y_1}{27} = \frac{Z_1^2 Y_1^2}{3} \\
 2. \quad \frac{Z_1 Y_1}{9} \frac{3Z_1 Y_1}{9} = \frac{Z_1^2 Y_1^2}{3} & 10. \quad \frac{Z_1 Y_1}{9} \frac{27Z_1 Y_1}{27} = \frac{Z_1^2 Y_1^2}{9} \\
 3. \quad \frac{Z_1 Y_1}{27} \frac{3Z_1 Y_1}{27} = \frac{Z_1^2 Y_1^2}{9} & 11. \quad \frac{3Z_1 Y_1}{3} \frac{9Z_1 Y_1}{9} = Z_1^2 Y_1^2 \\
 4. \quad \frac{Z_1 Y_1}{9} \frac{9Z_1 Y_1}{9} = Z_1^2 Y_1^2 & 12. \quad \frac{3Z_1 Y_1}{3} \frac{9Z_1 Y_1}{27} = \frac{Z_1^2 Y_1^2}{3} \\
 5. \quad \frac{Z_1 Y_1}{27} \frac{9Z_1 Y_1}{27} = \frac{Z_1^2 Y_1^2}{3} & 13. \quad \frac{3Z_1 Y_1}{3} \frac{27Z_1 Y_1}{27} = Z_1^2 Y_1^2 \\
 6. \quad \frac{Z_1 Y_1}{27} \frac{27Z_1 Y_1}{27} = Z_1^2 Y_1^2 & 14. \quad \frac{3Z_1 Y_1}{9} \frac{27Z_1 Y_1}{27} = \frac{Z_1^2 Y_1^2}{3} \\
 7. \quad \frac{Z_1 Y_1}{3} \frac{9Z_1 Y_1}{9} = \frac{Z_1^2 Y_1^2}{3} & 15. \quad \frac{9Z_1 Y_1}{9} \frac{27Z_1 Y_1}{27} = Z_1^2 Y_1^2 \\
 8. \quad \frac{Z_1 Y_1}{3} \frac{9Z_1 Y_1}{27} = \frac{Z_1^2 Y_1^2}{9} &
 \end{array}$$

The above terms are combined and simplified to give

$$\left[\begin{array}{l} \text{sum of 8-term} \\ \text{products} \end{array} \right] = \left[\frac{25Z_1^2 Y_1^2}{3} \right] \quad (9.56)$$

The denominator of the final transform is 1.0 plus the sum of (9.54), (9.55), and (9.56), which is, with the last term

$$Z_T(s) = \frac{1}{1 + \frac{142ZY}{27} + \frac{25Z^2Y^2}{3} + 5Z^3Y^3 + Z^4Y^4} \quad (9.57)$$

9.6. Iterative networks, Pascal triangle method

Back in Chapter VI we had a brief introduction to Pascal's triangle as a means of obtaining the transfer function of iterated networks. In the present article we will examine this method in much more detail. The procedure is so easy and so useful that the writer has tried to promote it as an essential subject in all courses of network analysis and synthesis.

From our work in the last article, where successive products were tabulated and added to get terms of transfer functions, one might suspect that the procedure could be organized as a much more compact operation. This is especially easy if each section of a long chain network is identical. Let us begin our study with a brief digression on elementary matrices of networks.

Most readers will be familiar with the basic principles of a matrix. For example, if we write the simple equations for the network inside the box shown in Fig. 9.12, we have many possible ways of relating



Fig. 9.12

the four external variables. One most common way is to use the *ABCD* form, which in this case is

$$e_1 = Ae_2 + Bi_2 \quad (9.58)$$

$$i_1 = Ce_2 + Di_2 \quad (9.59)$$

The coefficients *A*, *B*, *C*, and *D* form the network matrix, and the two equations may be combined as

$$\begin{bmatrix} e_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} e_2 \\ i_2 \end{bmatrix} \quad (9.60)$$

We will not do more than touch on this matrix notation, as it is really not necessary to know anything about matrices to use the results of this article.

Now the $ABCD$ matrix in (9.60) completely describes the network of Fig. 9.12 as far as external measurements are concerned. For example, if the network is a filter, and if the output is not loaded, then i_2 is 0 and for (9.58) we see that

$$\frac{e_2}{e_1} = \frac{1}{A} \quad (9.61)$$

So our old familiar transfer function is seen to be just the reciprocal of the A element of the general network matrix. For the same filter, when $i_2 = 0$, the input impedance of the network is simply obtained by dividing (9.58) by (9.59)

$$Z_{\text{IN}} = \frac{e_1}{i_1} = \frac{A}{C} \quad (9.62)$$

If we short the output terminals to measure i_2 , we see that the current transfer conductance, or transconductance, is

$$\frac{i_2}{e_1} = \frac{1}{B} \quad (9.63)$$

Which of course is from (9.58), as e_2 is 0 when we shorted the output to measure i_2 . By (9.59) we also have

$$\frac{i_2}{i_1} = \frac{1}{D} \quad (9.64)$$

Let us now look inside the box and examine a specific network.

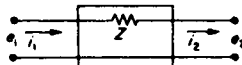


Fig. 9.13

As a most simple case, suppose the box has only one simple series impedance Z as in Fig. 9.13.

(9.58) and (9.59) then have the values

$$e_1 = 1e_2 + Zi_2 \quad (9.65)$$

$$i_1 = 0e_2 + 1i_2 \quad (9.66)$$

so that the network matrix for this elaborate network is

$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \quad (9.67)$$

We now examine a second box, shown in Fig. 9.14.

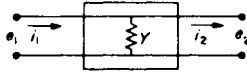


Fig. 9.14

and by the same procedure, the matrix of this single shunt element admittance is

$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \quad (9.68)$$

Now one of the nice features of using the $ABCD$ system is that if the networks are cascaded, we can get the $ABCD$ matrix of the new over-all network by merely multiplying the two individual matrices, i.e. if the two networks of Fig. 9.13 and Fig. 9.14 are cascaded, as shown in Fig. 9.15,

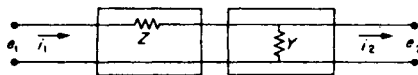


Fig. 9.15

and over-all matrix is

$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} = \begin{bmatrix} (1 + ZY) & Z \\ Y & 1 \end{bmatrix} \quad (9.69)$$

Note that the matrices must be multiplied in the same order as the networks are cascaded. Also note in Fig. 9.15 that the e_2 and i_2 are not the same as in the earlier Figures, but e_2 is the new output voltage of the combination.

The key idea thus far is that if we have a single network L-section, of series Z and shunt Y as in Fig. 9.16,

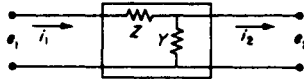


Fig. 9.16

the network matrix will be given by (9.69) as

$$\begin{bmatrix} (1 + ZY) & Z \\ Y & 1 \end{bmatrix} \quad (9.70)$$

Thus, the $ABCD$ notation is

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \quad (9.71)$$

where

$$\left. \begin{aligned} A &= 1 + ZY \\ B &= Z \\ C &= Y \\ D &= 1 \end{aligned} \right\} \quad (9.72)$$

We are now ready to begin the key work of this article. Suppose that we have a large number n of such cascaded L-sections. We can express the network matrix of the entire chain very simply as the n th power of (9.70) or (9.71), i.e.

$$\begin{bmatrix} (1 + ZY) & Z \\ Y & 1 \end{bmatrix}^n \quad (9.73)$$

or

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}^n \quad (9.74)$$

Our problem now is to raise the matrix to any desired power, and this is where Pascal's triangle will finally come to our aid.

Let us take the same Pascal triangle we have used in Chapter VI, and draw it in Table form, as in Table 9.5. In this arrangement, n is the number of internal sections, or the power to which our matrix (9.73) or (9.74) must be raised. Under each value n we have two sub-columns a and b . Where necessary we can identify a or b with

the corresponding n by using subscripts, as a_3 or b_7 to denote the a for the column where $n = 3$, and b from the $n = 7$ column, etc. It will not always be necessary to use such subscripts on a and b .

We can also use simple subscripts to distinguish the $ABCD$ values of the original single section from the corresponding $ABCD$ values of the n -section iterated network. The single L-section A element would thus be A_1 , while the A element of the final network of seven cascaded sections would be A_7 . We can thus write formally

$$\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix}^n = \begin{bmatrix} A_n & B_n \\ C_n & D_n \end{bmatrix} \tag{9.75}$$

Rather than state long, abstract rules to follow, let us illustrate the use of Table 9.5 with one general example and model. It is really a waste of time to try to memorize this procedure, and inasmuch as the book is available, one can always refer back to the following general model as such problems come up in the future.

TABLE 9.5

n 1		2		3		4		5		6		7		
a_1	b_1	a_2	b_2	a_3	b_3	a_4	b_4	a_5	b_5	a_6	b_6	a_7	b_7	
1	1	2	1	3	1	4	1	5	1	6	1	7	1	
	1		3		6		10		15		21		28	
		1	1	4	5	6	7	8	9	10	11	12	13	
				1	6		15		21		28		35	42
					1	1	1	1	1	1	1	1	1	1

For the example, let us choose $n = 4$.

We now proceed to write the four $ABCD$ values of the *entire* 4-mesh network as follows

$$A_4 = 1 + 10ZY + 15Z^2Y^2 + 7Z^3Y^3 + Z^4Y^4 \tag{9.76}$$

(we have taken all the numerical coefficients directly from Table 9.5 in the b_4 column).

Next, we write the B matrix element as

$$B_4 = Z(4 + 10ZY + 6Z^2Y^2 + Z^3Y^3) \quad (9.77)$$

(Note carefully that the numerical coefficients are all taken directly from column a_4 in Table 9.5. The B elements will always be multiplied by Z , as above.)

Next, we write the C_4 element of the total network.

$$C_4 = Y(4 + 10ZY + 6Z^2Y^2 + Z^3Y^3) \quad (9.78)$$

(Note that C will always be the same as B , except that the polynomial is always multiplied by Y rather than Z . The coefficients are taken from under column a_4 .)

Finally, we write the D element of the network as

$$D_4 = 1 + 6ZY + 5Z^2Y^2 + Z^3Y^3 \quad (9.79)$$

(Use caution here. Note carefully that the coefficients of D are always taken from the b group under $n - 1$, rather than n . Thus the coefficients in (9.79) are taken from the b_3 column.)

Since the $ABCD$ parameters completely describe the network, we can get the usual functions as follows. The transfer function Z_T is

$$Z_T = \frac{e_0}{e_{IN}} = \frac{1}{A} \quad (9.80)$$

The input impedance of the iterated network is

$$Z_{IN} = \frac{e_{IN}}{i_{IN}} = \frac{A}{C} \quad (9.81)$$

Eqs. (9.58) and (9.59) can easily be solved for any ratio desired, and the $ABCD$ elements used as in the foregoing model equations.

EXAMPLE. The short-circuit current gain i_0/i_{IN} is found from (9.59) to be

$$\frac{i_0}{i_{IN}} = \frac{1}{D} \quad (9.82)$$

and thus for the four-mesh network we used as a model

$$\left. \frac{i_0}{i_{IN}} \right|_{e_o=0} = \frac{1}{1 + 6ZY + 5Z^2Y^2 + Z^3Y^3} \quad (9.83)$$

EXAMPLE. The open-circuit transfer function of the network is

$$Z_T = \frac{1}{1 + 10ZY + 15Z^2Y^2 + 7Z^3Y^3 + Z^4Y^4} \quad (9.84)$$

The reader should be able to carry on from here. We might mention that to extend Table 9.5 it is only necessary to note that for any three elements of the following pattern

$$\begin{array}{|c|} \hline B \\ \hline A \quad C \\ \hline \end{array}$$

we always have

$$C = A + B \tag{9.85}$$

This relation extends over the entire Pascal triangle.

9.7. Formulas for iterative network coefficients

In the interest of completeness, and for the readers who are more analytically inclined, it will be pointed out briefly in this article that the coefficients of the *ABCD* parameters can also be expressed in closed form, as a ratio of factorials. Thus for the general iterative network in Fig. 9.17,

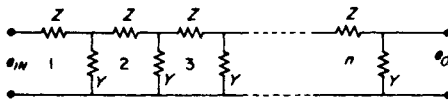


Fig. 9.17

we can write the model transfer function as

$$\frac{e_o}{e_{IN}} = \frac{1}{A} = \frac{1}{1 + a_1ZY + a_2Z^2Y^2 + \dots + a_mZ^mY^m + \dots + Z^nY^n} \tag{9.86}$$

n is the order of the network, and a_m is any coefficient in the n th order polynomial. Thus the m th coefficient of an n th order polynomial is the following ratio of factorials

$$a_{m,n} = \frac{|m+n|}{|2m| |n-m|} \tag{9.87}$$

The element C_n as in (9.78) can be written as

$$C_n = Y(n + c_1ZY + c_2Z^2Y^2 + \dots + c_mZ^mY^m + \dots + Z^{n-1}Y^{n-1}) \tag{9.88}$$

and we have the coefficients as

$$c_{m,n} = \frac{|m+n|}{|n-m-1| |2m+1|} \quad (9.89)$$

As before, the input impedance Z_{IN} is thus

$$Z_{IN} = \frac{A_n}{C_n} \quad (9.90)$$

Enterprising instructors will no doubt have their students in the class work out the simple factorial ratios for the $b_{m,n}$ and $d_{m,n}$ coefficients as a short assignment to be done over the Christmas holidays. By this time most students would wish they had never heard of the $d_{m,n}$ coefficients.

9.8. Alternate approach to the Laplace integral

As an additional topic, the writer would like to present an alternate development of the Laplace integral, which is based upon the power expansion of a function. A power series is often used to represent some function of time. If the time function is called $f(t)$, then

$$f(t) = a_0 + a_1 t + a_2 t^2 + a_3 t^3 + \cdots + a_n t^n \quad (9.91)$$

We note here that any particular a is a function of n , and therefore,

$$f(t) = \sum_{n=0}^{\infty} a(n) t^n \quad (9.92)$$

Now since a is a function of n , which will in all probability not have integral values for most practical functions, suppose we allow a to become some general variable which can assume any appropriate value. To do this, let us choose two variables u and v , along with a new function G , and write by comparison with (9.91)

$$G(v) = u_0 + u_1 v + u_2 v^2 + u_3 v^3 + \cdots + u_n v^n \quad (9.93)$$

or

$$G(v) = \sum_{n=0}^{\infty} u(n) v^n \quad (9.94)$$

If we should factor out a quantity Δn from every term in the series u still remains a function of n , and therefore

$$G(v) = \sum_{n=0}^{\infty} u(n) v^n \Delta n \quad (9.95)$$

In (9.95), n represents only integral values from 0 to ∞ , but to make things more general, suppose we allow n to become another variable w , which can assume any value, then

$$G(v) = \sum_{w=0}^{\infty} u(w)v^w \Delta w \quad (9.96)$$

Now regardless of the value of v , there is always some variable s such that

$$v = \varepsilon^{-s} \quad (9.97)$$

from which we can state that

$$G(v) = F(s) \quad (9.98)$$

Re-writing (9.96), we have

$$F(s) = \int_0^{\infty} u(w)\varepsilon^{-sw} dw \quad (9.99)$$

Now if the general variable w should be chosen specifically as time t , then $u(w)$ will be some specific function which we can call $f(t)$, so that (9.99) becomes

$$F(s) = \int_0^{\infty} f(t)\varepsilon^{-st} dt \quad (9.100)$$

a result which should appear familiar by this time.

The writer hopes that he will be forgiven by the pure mathematicians (or at least by the engineering reader) for the somewhat unorthodox manipulations which led to (9.100). At any rate, this book is intended for practical electronics engineers who are often accused of similar unconventional approaches to design. The chief reason for this derivation is to permit the reader to relate intuitively the now familiar Laplace transform very closely with operations involving an infinite series.

The reader who pursues the subject of Laplace transforms well beyond the scope of this book will uncover many areas of usefulness not necessarily related to electronics or radio. Since this article has shown the close relation between an infinite series and the Laplace transform integral, we shall now discuss ways of using the Laplace transform to sum an infinite number of terms of a series, to obtain a result in closed form. Closed form being specific values for a series, as in (9.101)

$$\sum_{n=1}^{\infty} \frac{1}{2^n} = 1 \quad (9.101)$$

9.9. The Laplace integral used to sum infinite series into closed form

Every electronics engineer finds it necessary at times to work with infinite series. There are numerous functions that can only be expressed as some form of infinite series. Many of the large computers will derive values for a function by summing a large number of terms of its corresponding series, this being more practical than to store tabulated values in the computer. We can say that, in general, any detailed engineering analysis is quite likely to encounter an infinite series at some point.

It is unfortunate that most of the series having practical engineering applications converge quite slowly. When evaluating such a series manually this means that considerable work must be expended. When such a series in this form is programmed for evaluation by a digital computer, storage for a large number of terms must be provided. In any event, it is usually desirable, when possible, to express such an infinite series in closed form.

By closed form, one refers to a simple, complete function which represents the infinite series. For example, if

$$f(x) = x - \frac{x^3}{\sqrt{3}} + \frac{x^5}{\sqrt{5}} - \frac{x^7}{\sqrt{7}} + \cdots \quad (9.102)$$

we say that

$$f(x) = \sin x \quad (9.103)$$

and therefore the expression $\sin x$ is the closed form of the infinite series given by (9.102).

The reader will recall from his earlier work with series that he can apply various tests to determine whether or not the series converges. Such tests usually involve specific operations with the n th term of the given series.

To be completely known, the n th term of a series must be given, because some series which seem to progress in a fixed manner term by term will suddenly appear to become erratic after a certain number of terms.

If the n th term of a series is known, it would be well to have some procedure available to determine what the closed form of the series would be, if such a closed form exists. The Laplace transform serves as a basis for such a procedure.

Suppose we are given the general, or n th term of some series which we do not recognize. The n th term is then a function of n , or

$$F(n) = n\text{th term} \quad (9.104)$$

(n) is called the dummy index of summation, and would take on successive values from some lower limit to infinity.

Now suppose we associate n , the index of summation, with the complex variable s , and define a function of s as

$$F(s) = \int_0^{\infty} f(t)\varepsilon^{-st} dt \quad (9.105)$$

where (9.105) is the definition of the Laplace transform also, as used throughout the text. If we simulate the n th term of the series as a function of s , it will then be necessary to sum each side of (9.104) in the same way that it was necessary to sum the n th term from the lower limit to infinity. Accordingly, (9.105) can be written as

$$\sum F(s) = \sum \int_0^{\infty} f(t)\varepsilon^{-st} dt \quad (9.106)$$

The summation and integration process can be interchanged for operation on s , because s is not a function of t , and therefore (9.106) can become

$$\sum F(s) = \int_0^{\infty} f(t) dt \sum (\varepsilon^{-t})^s \quad (9.107)$$

Equation (9.107) is now in proper form and ready for use in summing series. First, however, we will list two auxiliary relations with which every electronics engineer is familiar. We write them here merely for reference. These are:

$$(A) \quad \sum_{s=0}^{\infty} a^s = \frac{1}{1-a}, \quad |s| < 1.0 \quad (9.108)$$

and

$$(B) \quad \sum_{s=0}^{\infty} \frac{a^s}{s} = \varepsilon^a, \quad |a| \text{ finite} \quad (9.109)$$

Slight variations can be applied if the summation is to begin at some other value such as $s = 1$, $s = 2$, $s = 3$, etc. For example (A) becomes

$$\sum_{s=1}^{\infty} a^s = \frac{a}{1-a} \quad (9.110)$$

$$\sum_{s=2}^{\infty} a^s = \frac{a^2}{1-a} \quad (9.111)$$

and

$$\sum_{s=3}^{\infty} a^s = \frac{a^3}{1-a}, \text{ etc.} \quad (9.112)$$

Having developed (9.107) as the general form for summation, and having listed the obvious relations (9.108) through (9.112), let us apply this technique to evaluate the closed form of several infinite series. It is expected that the reader will see the procedure more clearly by following several examples than by reading a more abstract word description.

EXAMPLE 1. Suppose we choose the series

$$F(n) = \frac{1}{2} + \frac{1}{6} + \frac{1}{12} + \frac{1}{20} + \cdots + \frac{1}{n(n+1)} \quad (9.113)$$

We now replace n by the Laplace variable s , and write the n th term as

$$F(s) = \frac{1}{s(s+1)} \quad (9.114)$$

This notation places us upon familiar territory in the s -plane, and we can see from Appendix III that $F(s)$ corresponds to a time function $f(t)$, so that

$$\frac{1}{s(s+1)} \leftrightarrow (1 - \varepsilon^{-t}) \quad (9.115)$$

In other words

$$\frac{1}{s(s+1)} = \int_0^{\infty} (1 - \varepsilon^{-t}) \varepsilon^{-st} dt \quad (9.116)$$

To sum this simulated n th term, say from 1.0 to ∞ , we use the general form (9.107) to write

$$\sum_{s=1}^{\infty} \frac{1}{s(s+1)} = \int_0^{\infty} (1 - \varepsilon^{-t}) dt \sum_{s=1}^{\infty} (\varepsilon^{-t})^s \quad (9.117)$$

or, breaking the right-hand side down into two integrals

$$\sum_{s=1}^{\infty} \frac{1}{s(s+1)} = \int_0^{\infty} \sum_{s=1}^{\infty} (\varepsilon^{-t})^s dt - \int_0^{\infty} \varepsilon^{-t} \sum_{s=1}^{\infty} (\varepsilon^{-t})^s dt \quad (9.118)$$

For simplification, we can let

$$\left. \begin{aligned} \varepsilon^{-t} &= a \\ t &= -\ln a \\ dt &= -\frac{da}{a} \end{aligned} \right\} \quad (9.119)$$

and for the new limits,

$$\left. \begin{aligned} t &= 0, \quad a = 1 \\ t &= \infty, \quad a = 0 \end{aligned} \right\} \quad (9.120)$$

When these substitutions are made, (9.118) becomes

$$\sum_{s=-1}^{\infty} \frac{1}{s(s+1)} = -\int_1^0 \sum_{s=-1}^{\infty} a^s \frac{da}{a} + \int_1^0 a \sum_{s=-1}^{\infty} a^s \frac{da}{a} \quad (9.121)$$

We now observe from (9.110) that

$$\sum_{s=-1}^{\infty} a^s = \frac{a}{1-a} \quad (9.122)$$

and by using this information, (9.121) becomes

$$\sum_{s=-1}^{\infty} \frac{1}{s(s+1)} = \int_0^1 \frac{da}{1-a} - \int_0^1 \frac{a da}{1-a} \quad (9.123)$$

where the signs have been changed merely by interchanging upper and lower limits. This is of minor importance.

The two parts of (9.123) can now be combined into a single integral as follows:

$$\sum_{s=-1}^{\infty} \frac{1}{s(s+1)} = \int_0^1 \frac{(1-a) da}{(1-a)} \quad (9.124)$$

or

$$\sum_{s=-1}^{\infty} \frac{1}{s(s+1)} = \int_0^1 da = 1.0 \quad (9.125)$$

If we now return to the n th term of the series given in (9.113), we can see that the infinite sequence of terms adds up to unity and that the closed form is

$$\sum_{n=-1}^{\infty} \frac{1}{n(n+1)} = 1.0 \quad (9.126)$$

a result which the writer does not feel is obvious from a casual inspection of (9.113).

EXAMPLE 2. Let us examine the sequence

$$\frac{1}{3} + \frac{1}{8} + \frac{1}{15} + \frac{1}{24} + \cdots + \frac{1}{n^2 - 1} \quad (9.127)$$

For variation, let us attempt to sum this series from $n = 2$ to $n = \infty$. If we allow n to be replaced by s , so that our work can be done in the familiar s -plane, we observe from the tables of transforms that

$$\frac{1}{s^2 - 1} = \int_0^{\infty} \sinh t \varepsilon^{-st} dt \quad (9.128)$$

We note in passing that the function of s has two real conjugate poles, symmetrical about zero on the σ axis. The hyperbolic sine of t can be expressed exponentially as

$$\sinh t = \frac{\varepsilon^t}{2} - \frac{\varepsilon^{-t}}{2} \quad (9.129)$$

from which (9.128) can be written as

$$\frac{1}{s^2 - 1} = \frac{1}{2} \int_0^{\infty} \varepsilon^t \varepsilon^{-st} dt - \frac{1}{2} \int_0^{\infty} \varepsilon^{-t} \varepsilon^{-st} dt \quad (9.130)$$

Using the general summation form (9.107), this becomes

$$\sum_{s=2}^{\infty} \frac{1}{s^2 - 1} = \frac{1}{2} \int_0^{\infty} \varepsilon^t dt \sum_{s=2}^{\infty} (\varepsilon^{-t})^s - \frac{1}{2} \int_0^{\infty} \varepsilon^{-t} dt \sum_{s=2}^{\infty} (\varepsilon^{-t})^s \quad (9.131)$$

Let us now make the substitution of variables

$$\left. \begin{aligned} \varepsilon^{-t} &= a \\ t &= -\ln a \\ dt &= -\frac{da}{a} \end{aligned} \right\} \quad (9.132)$$

and let us also make use of (9.111) to write

$$\sum_{s=2}^{\infty} a^s = \frac{a^2}{1 - a} \quad (9.133)$$

Then we note that the new limits will be:

$$\left. \begin{aligned} t = 0, \quad a = 1 \\ t = \infty, \quad a = 0 \end{aligned} \right\} \quad (9.134)$$

Placing these substitutions into (9.131) results in

$$\sum_{s=2}^{\infty} \frac{1}{s^2 - 1} = \frac{1}{2} \int_1^0 \frac{1}{a} \frac{a^2(-da)}{(1-a)a} - \frac{1}{2} \int_1^0 \frac{aa^2(-da)}{(1-a)a} \quad (9.135)$$

This simplifies to

$$\sum_{s=2}^{\infty} \frac{1}{s^2 - 1} = \frac{1}{2} \int_0^1 \frac{(1-a^2) da}{1-a} \quad (9.136)$$

or

$$\sum_{s=2}^{\infty} \frac{1}{s^2 - 1} = \frac{1}{2} \int_0^1 (1+a) da \quad (9.137)$$

and finally

$$\sum_{s=2}^{\infty} \frac{1}{s^2 - 1} = \frac{1}{2} \left[\frac{(1+a)^2}{2} \right]_0^1 \quad (9.138)$$

Substituting the limits, and replacing s by the original quantity (n) , gives the final sum of the series, which is

$$\sum_{n=2}^{\infty} \frac{1}{n^2 - 1} = \frac{3}{4} \quad (9.139)$$

EXAMPLE 3. As a variation, let us choose a general term whose analog function of s has double order poles. A typical function of this type might be

$$F(n) = \frac{4n}{(n^2 - 1)^2} \quad (9.140)$$

It is desired to evaluate this series from $n = 2$ to $n = \infty$.

We begin by looking up the analog $F(s)$ in Appendix III. Note that minor sign changes in such functions can usually be handled by inspection. We would use form number 86, replacing α by j , to write

$$\frac{4s}{(s^2 - 1)^2} = 2 \int_0^{\infty} t \sinh t \varepsilon^{-st} dt \quad (9.141)$$

The integral can be written in exponential form as

$$\frac{4s}{(s^2 - 1)^2} = \int_0^\infty t \varepsilon^t \varepsilon^{-st} dt - \int_0^\infty t \varepsilon^{-t} \varepsilon^{-st} dt \quad (9.142)$$

At this point we can make the substitutions

$$\left. \begin{aligned} \varepsilon^{-t} &= a \\ t &= -\ln a \\ dt &= -\frac{da}{a} \end{aligned} \right\} \quad (9.143)$$

from which the new limits are

$$\left. \begin{aligned} t = 0, & \quad a = 1 \\ t = \infty, & \quad a = 0 \end{aligned} \right\} \quad (9.144)$$

With these new quantities inserted, (9.142) becomes

$$\frac{4s}{(s^2 - 1)^2} = \int_1^0 \frac{a^s \ln a da}{a^2} - \int_1^0 a^s \ln a da \quad (9.145)$$

The standard summation from (9.107) results in

$$\sum_{s=-2}^{\infty} \frac{4s}{(s^2 - 1)^2} = \int_1^0 \sum_{s=-2}^{\infty} \frac{a^s \ln a da}{a^2} - \int_1^0 \sum_{s=-2}^{\infty} a^s \ln a da \quad (9.146)$$

We see from (9.111) that

$$\sum_{s=-2}^{\infty} a^s = \frac{a^2}{1 - a} \quad (9.147)$$

so that (9.146) will become

$$\sum_{s=-2}^{\infty} \frac{4s}{(s^2 - 1)^2} = \int_1^0 \frac{\ln a da}{1 - a} - \int_1^0 \frac{a^2 \ln a da}{1 - a} \quad (9.148)$$

Both integrals are combined to give

$$\sum_{s=-2}^{\infty} \frac{4s}{(s^2 - 1)^2} = \int_1^0 \frac{(1 - a^2) \ln a da}{1 - a} \quad (9.149)$$

$$= \int_1^0 (1 + a) \ln a da \quad (9.150)$$

$$= \int_1^0 \ln a da + \int_1^0 a \ln a da \quad (9.151)$$

Both of these are standard forms

$$\sum_{s=2}^{\infty} \frac{4s}{(s^2 - 1)^2} = \left[\left(1 + \frac{a^2}{2} \right) \ln a - a - \frac{a^2}{4} \right]_1^0 \quad (9.152)$$

When the limits are inserted, and with n replacing s , we have the final result

$$\sum_{n=2}^{\infty} \frac{4n}{(n^2 - 1)^2} = \frac{5}{4} \quad (9.153)$$

EXAMPLE 4. As another example, let us examine the series

$$F(n) = 1 + \frac{1}{4} + \frac{1}{9} + \frac{1}{16} + \cdots + \frac{1}{n^2} \quad (9.154)$$

and see if this series can be summed from $n = 1$ to $n = \infty$. As usual we find an analog function of s corresponding to the n th term. From Appendix III, one finds

$$\frac{1}{s^2} = \int_0^{\infty} t \varepsilon^{-st} dt \quad (9.155)$$

Now by the same procedure that went into the derivation of (9.107) we sum both sides as follows:

$$\sum_{s=1}^{\infty} \frac{1}{s^2} = \int_0^{\infty} t dt \sum_{s=1}^{\infty} (\varepsilon^{-t})^s \quad (9.156)$$

If we now make the substitutions

$$\left. \begin{aligned} \varepsilon^{-t} &= a \\ t &= -\ln a \\ dt &= -\frac{da}{a} \end{aligned} \right\} \quad (9.157)$$

and insert new limits

$$\left. \begin{aligned} t = 0, \quad a &= 1 \\ t = \infty, \quad a &= 0 \end{aligned} \right\} \quad (9.158)$$

then (9.156) becomes

$$\sum_{s=1}^{\infty} \frac{1}{s^2} = \int_1^0 \frac{\ln a da}{1-a} \quad (9.159)$$

This is a standard definite integral. We replace s by n , and consult a table of definite integrals to find that

$$\sum_{n=1}^{\infty} \frac{1}{n^2} = \frac{\pi^2}{6} \quad (9.160)$$

EXAMPLE 5. As a final example to illustrate one or two new points, let us find the closed form of the series

$$F(n) = \sum_{n=1}^{\infty} \frac{1}{2^n} \quad (9.161)$$

First, we note that the n th term can be written as

$$\frac{1}{2^n} = \frac{1}{e^{an}} \quad (9.162)$$

where

$$e^a = 2 \quad (9.163)$$

We now move into the s -plane by the simple process of replacing n by s , and locating a function of s to match, i.e.

$$\frac{1}{e^{as}} = \int_0^{\infty} \delta(t - a) e^{-st} dt \quad (9.164)$$

It appears that the analog of the n th term is a delta function. If the summation is performed as before, we have

$$\sum_{n=1}^{\infty} \frac{1}{e^{as}} = \int_0^{\infty} \delta(t - a) \sum_{n=1}^{\infty} (\varepsilon^{-t})^n dt \quad (9.165)$$

Observing (9.110), we see that

$$\sum_{n=1}^{\infty} \varepsilon^{-tn} = \frac{\varepsilon^{-t}}{1 - \varepsilon^{-t}} = \frac{1}{\varepsilon^t - 1} \quad (9.166)$$

This is inserted into (9.165) so that

$$\sum_{n=1}^{\infty} \frac{1}{e^{as}} = \int_0^{\infty} \frac{\delta(t - a) dt}{\varepsilon^t - 1} \quad (9.167)$$

We now recall from art. 7.5 in Chapter VII that the integral of a δ -function and some second function is merely the value of the

second function evaluated at the point where it is sampled by the δ -function (see (7.27)). Thus the integral in (9.167) reduces very easily to

$$\sum_{s=1}^{\infty} \frac{1}{e^{as}} = \frac{1}{e^a - 1} \quad (9.168)$$

and as a last step, if we replace s by n , and make use of (9.163), we have the answer

$$\sum_{n=1}^{\infty} \frac{1}{2^n} = 1 \quad (9.169)$$

The processes illustrated here assume, of course, that the series, as represented by the n th term, is convergent; that we can find a function of s which is the analog of the n th term, and that we can evaluate the integral which results when (9.107) is applied.

SYNTHESIS OF TRANSFER FUNCTIONS BY MODELS

10.1. Introduction

IN Chapters VI and VIII we worked with transfer functions of oscillators and filter networks, and found that it was possible to determine element values in some cases by a process of reverse analysis. In this last chapter, we will examine a few concepts taken from more formal network synthesis procedures. We should state here that formal synthesis theory would fill many volumes, and we only wish to touch on a few topics which will illustrate the use of the Laplace transforms which we have been studying. The writer feels, however, that careful examples can give a good introduction to a topic, even if one does not go deeply into the subject. Accordingly, it is hoped that the few ideas presented here may prove useful, and complete enough that the reader can gain a good understanding of the first principles of formal network synthesis.

10.2. Lossless network models

In this development we will define the particular transfer function as the ratio of output voltage e_0 to input voltage e_{IN} , and assume that the problem is to discover a network whose transfer function $Z_T(s)$ is given.

$$Z_T(s) = \frac{e_0}{e_{IN}}(s) \tag{10.1}$$

There are many networks which could be used, but let us consider

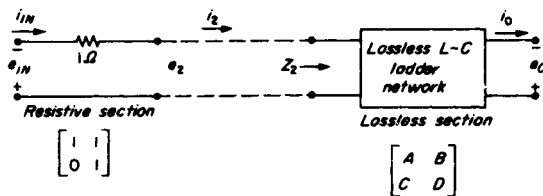


Fig. 10.1

the development of $Z_T(s)$ as the cascade connection of a simple

resistive section, and a simple *lossless* ladder network, with the two sections shown partly separated in Fig. 10.1.

We use the $ABCD$ parameters so that the over-all matrix can be found easily and directly by multiplying the matrices of the two sections of the network. Thus the total network matrix is

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} (A + C) & (B + D) \\ C & D \end{bmatrix} \quad (10.2)$$

The input and output quantities are thus related as shown in (10.3) and (10.4)

$$e_{\text{IN}} = (A + C)e_0 + (B + D)i_0 \quad (10.3)$$

$$i_{\text{IN}} = Ce_0 + Di_0 \quad (10.4)$$

Now we will specify that no load is to be applied to the network, i.e. we go directly into a very high impedance amplifier, and under this condition, i_0 will always be zero. Thus from (10.3) we have

$$e_{\text{IN}} = (A + C)e_0$$

or, using (10.1),

$$Z_T(s) = \frac{e_0}{e_{\text{IN}}} = \frac{1}{A + C} \quad (10.5)$$

Both A and C are of course functions of s .

Now let us examine the lossless ladder section by itself. Its input and output, shown in Fig. 10.1, is as follows:

$$e_2 = Ae_0 + Bi_0 \quad (10.6)$$

$$i_2 = Ce_0 + Di_0 \quad (10.7)$$

Again, since i_0 is always zero, we have

$$e_2 = Ae_0 \quad (10.8)$$

$$i_2 = Ce_0 \quad (10.9)$$

and the ratio is

$$Z_2 = \frac{e_2}{i_2} = \frac{A}{C} \quad (10.10)$$

where Z_2 is the two-terminal input impedance looking into the second (lossless) section.

The only results of interest thus far are Eqs. (10.5) and (10.10). These two equations are all that we need to retain to use the model of Fig. 10.1.

EXAMPLE. At this point an example of the procedure is in order, and should make clear the application of (10.5) and (10.10).

We are required to synthesize a network for a low-pass filter, and we are told that the transfer function is

$$Z_T(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} \quad (10.11)$$

which we recognize as the third-order Butterworth filter, with the magnitude of the gain being

$$\left| \frac{e_0}{e_{IN}} \right| = \frac{1}{\sqrt{1 + \omega^6}} \quad (10.12)$$

We begin by equating (10.11) to (10.5), which gives

$$s^3 + 2s^2 + 2s + 1 = A(s) + C(s) \quad (10.13)$$

And now it only remains to satisfy (10.10). For this example we see that (10.10) is satisfied if we choose to assign the even terms to A and all the odd terms to C . (10.10) then becomes

$$Z_2 = \frac{A}{C} = \frac{2s^2 + 1}{s^3 + 2s} \quad (10.14)$$

or

$$Y_2 = \frac{s^3 + 2s}{2s^2 + 1} \quad (10.15)$$

The reason for inverting is merely to assure ourselves that the

first element in the lossless network is a shunt condenser. We expand (10.15) as a continued fraction.

$$\begin{array}{r}
 \frac{s}{2} \xrightarrow{\hspace{10em}} \text{First Element} \\
 \text{(shunt admittance)} \\
 2s^2 + 1 \overline{) s^3 + 2s} \\
 \hline
 s^3 + \frac{s}{2} \xrightarrow{\hspace{10em}} \text{Second Element} \\
 \text{(series impedance)} \\
 \frac{4s}{3} \\
 \frac{3s}{2} \overline{) 2s^2 + 1} \\
 \hline
 2s^2 \xrightarrow{\hspace{10em}} \text{Last Element} \\
 \text{(shunt admittance)} \\
 \frac{3s}{2} \\
 1 \overline{) \frac{3s}{2}} \\
 \hline
 \frac{3s}{2} \\
 0
 \end{array}
 \tag{10.16}$$

In case the reader does not recognize what we have done in (10.16), we merely started to divide our (10.15) by long division, and the first thing removed was an element $s/2$. This is a $1/2$ farad condenser. We now invert the remainder to form an *impedance* again, and this time we divide again and take out an *impedance* element $4s/3$, which we recognize as a $4/3$ henry inductor. We next

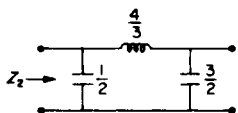


Fig. 10.2

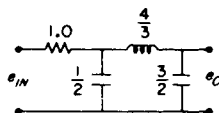


Fig. 10.3

invert the remainder once more, and make one last division to take out the $3s/2$ *admittance* which we should recognize as a condenser of $3/2$ farad capacity.

The impedance Z_2 thus corresponds to the *lossless* network shown in Fig. 10.2.

Putting both sections back together, we finally complete the model for the third-order Butterworth filter as in Fig. 10.3.

10.3. Odd and even parts of the transfer function

$Z_T(s)$ may be considerably more involved than in this simple example, and therefore it is well to develop a general procedure for assigning parts of $Z_T(s)$ between A and C . We can write as

$$Z_T = \frac{m_1 + n_1}{m_2 + n_2} \quad (10.17)$$

where m_1 is the *even* part of the numerator, n_1 is the odd part of the numerator, etc. If we divide through by the numerator, and use (10.5)

$$\frac{m_2}{m_1 + n_1} + \frac{n_2}{m_1 + n_1} = A + C \quad (10.18)$$

We can rationalize by multiplying by $m_1 - n_1$,

$$\frac{m_2(m_1 - n_1)}{m_1^2 - n_1^2} + \frac{n_2(m_1 - n_1)}{m_1^2 - n_1^2} = A + C \quad (10.19)$$

which is easily arranged as

$$\frac{m_1 m_2 - n_1 n_2}{m_1^2 - n_1^2} + \frac{m_1 n_2 - n_1 m_2}{m_1^2 - n_1^2} = A + C \quad (10.20)$$

We see that the first term is always even, and the second term is always odd.

We now make the formal assignments

$$A = \frac{m_1 m_2 - n_1 n_2}{m_1^2 - n_1^2} \quad (10.21)$$

$$C = \frac{m_1 n_2 - n_1 m_2}{m_1^2 - n_1^2} \quad (10.22)$$

and (10.10) becomes

$$Z_2(s) = \frac{m_1 m_2 - n_1 n_2}{m_1 n_2 - n_1 m_2} \quad (10.23)$$

EXAMPLE. Let us illustrate by using the same example as before, the third-order Butterworth function. Thus we are given that

$$Z_T(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} \tag{10.24}$$

and we assign the even and odd parts as

$$\left. \begin{aligned} m_1 &= 1 \\ n_1 &= 0 \\ m_2 &= 1 + 2s^2 \\ n_2 &= 2s + s^3 \end{aligned} \right\} \tag{10.25}$$

so that

$$Z_2 = \frac{m_2}{n_2} = \frac{2s^2 + 1}{s^3 + 2s} \tag{10.26}$$

and

$$Y_2 = \frac{s^3 + 2s}{2s^2 + 1} \tag{10.27}$$

Using the continued fraction development as before,

$$\begin{array}{l} \frac{s}{2} \xrightarrow{\hspace{1.5cm}} \text{Admittance} \\ \frac{2s^2 + 1}{s^3 + 2s} \\ \frac{s^3 + \frac{s}{2}}{\frac{4s}{3}} \xrightarrow{\hspace{1.5cm}} \text{Impedance} \\ \frac{\frac{3s}{2} \sqrt{2s^2 + 1}}{2s^2} \\ \frac{\frac{3s}{2}}{1 / \frac{3s}{2}} \xrightarrow{\hspace{1.5cm}} \text{Admittance} \end{array} \tag{10.28}$$

which results in the same network as found in the last article.

10.4. Synthesis of transfer impedances

Suppose that we are given the transfer impedance

$$Z_{12} = \frac{e_0}{i_{IN}} \tag{10.29}$$

to synthesize. We could proceed along the same lines as in art. 10.2 and derive independent results. However, we can make use of Thevenin's theorem and replace the first *series* resistor in Fig. 10.1 with a *shunt* resistance of 1.0 ohm. If we now speak of the input as a current i_{IN} and the output as the voltage e_0 , the transfer impedance is the same function of s as the voltage transfer functions we have normally considered.

It would be good practice to develop this procedure formally as an exercise, and so we merely indicate the network as shown in Fig. 10.4, along with the formula for the input impedance of the lossless $L-C$ section, which is the same Z_2 as before, Z_2 is thus

$$Z_2 = \frac{m_1 m_2 - n_1 n_2}{m_1 n_2 - n_1 m_2} \tag{10.30}$$

where the even and odd terms have the same meaning as before.

The third-order Butterworth transfer impedance is thus as shown in Fig. 10.5.

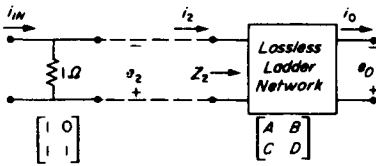


Fig. 10.4

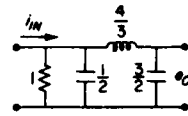


Fig. 10.5

10.5. Alternate method of transfer function synthesis

Let us now consider an independent method similar to the one discussed in art. 10.2, but this time we will have the resistive termination at the output end rather than at the input. As usual, the $ABCD$ parameters for the network shown in Fig. 10.6 are related as

$$e_1 = Ae_2 + Bi_2 \tag{10.31}$$

$$i_1 = Ce_2 + Di_2 \tag{10.32}$$

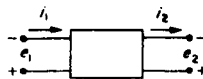


Fig. 10.6

and in particular, for the network shown in Fig. 10.7, the matrix is

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \tag{10.33}$$



Fig. 10.7

Next, let us consider the cascade connection of a general *lossless L-C* network and the 1-ohm load, as shown in Fig. 10.8.

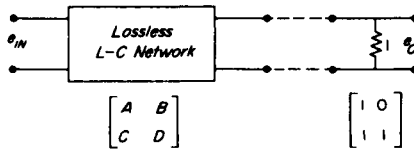


Fig. 10.8

The *ABCD* matrix for the combination of the 1-ohm termination and the lossless section is therefore

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} = \begin{bmatrix} (A + B) & B \\ (C + D) & D \end{bmatrix} \tag{10.34}$$

and with no further loading on the output, we see from (10.31) that since $i_2 = 0$,

$$\frac{e_0}{e_{IN}} = \frac{1}{A + B} \tag{10.35}$$

Also, for the over-all network, e_0/e_{IN} is the transfer function $Z_T(s)$, thus

$$Z_T(s) = \frac{1}{A(s) + B(s)} \tag{10.36}$$

where we note that *A* and *B* are still parameters of the *lossless* network only.

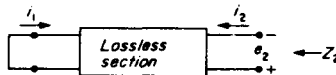


Fig. 10.9

Now let us consider the lossless section by itself. Suppose we short the input, as in Fig. 10.9.

If we apply (10.31) to the shorted, lossless network of Fig. 10.9, with e_1 being 0, we have

$$Ae_2 - Bi_2 = 0 \quad (10.37)$$

Notice that the direction of i_2 has been reversed from the definition of Fig. 10.6. This accounts for the minus sign in (10.37). (10.37) therefore becomes

$$\frac{e_2}{i_2} = \frac{B}{A} \quad (10.38)$$

But we now see that e_2/i_2 is the input impedance of the shorted lossless section in Fig. 10.9 as seen from the *right-hand side looking back to the left*. Thus

$$Z_2 = \frac{B}{A} \quad (10.39)$$

Now let us choose a specific transfer function such as the third-order Butterworth function.

$$Z_T(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} \quad (10.40)$$

From (10.36),

$$\frac{1}{s^3 + 2s^2 + 2s + 1} = \frac{1}{A(s) + B(s)} \quad (10.41)$$

Looking at (10.41), several groupings suggest themselves for $A(s)$ and $B(s)$. However, (10.39) requires that the ratio B/A be an impedance. Furthermore, since the network is lossless, the ratio B/A must be purely reactive.

Suppose we group all the even terms in the polynomial and assign these to $A(s)$, and assign the remaining odd terms to $B(s)$. Thus in the example,

$$B(s) = s^3 + 2s \quad (10.42)$$

$$A(s) = 2s^2 + 1 \quad (10.43)$$

Note in passing that $A(s)$ can never be reactive, since it contains only even powers of s , i.e.

$$s^2 = (j\omega)^2 = -\omega^2$$

$$s^4 = (j\omega)^4 = +\omega^2 \text{ etc.}$$

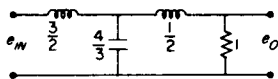


Fig. 10.11

Another example: Let

$$Z_T(s) = \frac{1}{s^2 + \sqrt{2}s + 1} = \frac{1}{A + B} \tag{10.47}$$

$$Z_2 = \frac{B}{A} = \frac{\sqrt{2}s}{s^2 + 1} \tag{10.48}$$

This cannot be expanded directly as before, but we invert to get

$$Y_2 = \frac{s^2 + 1}{\sqrt{2}s} = \frac{s}{\sqrt{2}} + \frac{1}{\sqrt{2}s} \tag{10.49}$$

which we can recognize as the elements in Fig. 10.12.

When we remove the temporary short, reconnect the terminating one-ohm resistor, we have the synthesized second-order Butterworth filter shown in Fig. 10.13.

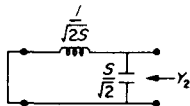


Fig. 10.12

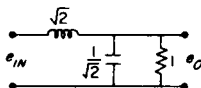


Fig. 10.13



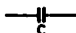
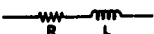
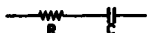
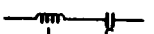
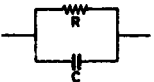
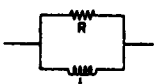

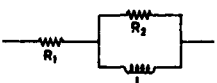
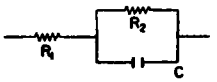
We have chosen all the examples here from the class of low-pass filters. The writer feels justified in spending most of the available theoretical time on the low-pass functions, as one can use these as prototypes from which the high-pass, band-pass, and band-rejection filters can be derived by simple transformations already discussed. Although our treatment has been brief, more on the order of an introduction rather than a detailed study, the reader who has followed all of the material thus far will be able to design low-pass, band-pass, high-pass, and band-rejection filters of any order. This is really quite a practical accomplishment. Especially when one recalls that many people go through a full semester of classes in formal network synthesis and still cannot accomplish these very same designs. The writer feels that this type of material should be a bare minimum in all college synthesis courses.

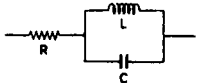
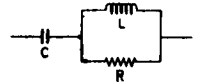
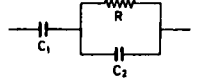
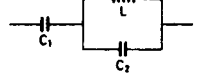
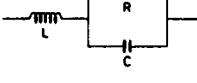
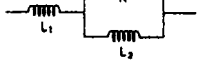
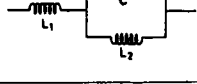
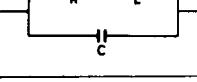
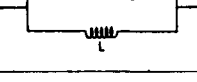

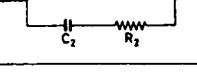
10.6. Conclusion

And now it is time for me to say goodbye to the reader. I should especially like to express my thanks to those hardy individuals who withstood the rigors of the book to the very end. I hope you will continue your interest in Laplace transform studies. You will find applications to electrical network problems fascinating, and use of the theory we have developed in other areas of science can prove rewarding as well. One area where Laplace transforms should prove invaluable is in Physical Oceanography, where the transforms could be used to study the differential equations of ocean waves and seismic disturbance propagation. Applications to many other areas have scarcely been touched upon, and most likely some of my readers will make original contributions of their own. For these and other reasons it has been a pleasant task to have written the book for you, and the best of luck to you in your future studies and in your personal life.







APPENDIX I







(a) Driving point transforms







1	$Z = R$	
2	$Z = Ls$	
3	$Z = \frac{1}{Cs}$	
4	$Z = R + Ls$	
5	$Z = \frac{RCs + 1}{Cs}$	
6	$Z = \frac{LCs^2 + 1}{Cs}$	
7	$Z = \frac{R}{RCs + 1}$	
8	$Z = \frac{RLs}{Ls + R}$	
9	$Z = \frac{Ls}{LCs^2 + 1}$	
10	$Z = \frac{(R_1 + R_2)Ls + R_1R_2}{Ls + R_2}$	
11	$Z = \frac{(R_1 + R_2) + R_1R_2Cs}{R_2Cs + 1}$	







12	$Z = \frac{RLCs^2 + Ls + R}{LCs^2 + 1}$	
13	$Z = \frac{RLs^2 + Ls + R}{s(Ls + R)}$	
14	$Z = \frac{R(C_1 + C_2)s + 1}{s(RC_1C_2s + C_1)}$	
15	$Z = \frac{L(C_1 + C_2)s^2 + 1}{s(LC_1C_2s^2 + C_1)}$	
16	$Z = \frac{LRCs^2 + Ls + R}{RCs + 1}$	
17	$Z = \frac{s(L_1L_2s + R[L_1 + L_2])}{L_2s + R}$	
18	$Z = \frac{s[L_1L_2Cs^2 + (L_1 + L_2)]}{L_2Cs^2 + 1}$	
19	$Z = \frac{Ls + R}{LCs^2 + RCs + 1}$	
20	$Z = \frac{s(RLCs + L)}{LCs^2 + RCs + 1}$	
21	$Z = \frac{R_1R_2C_1C_2s^2 + (R_1C_1 + R_2C_1 + R_2C_2)s + 1}{s(R_2C_1C_2s + C_1)}$	
22	$Z = \frac{R_1R_2C_1C_2s^2 + (R_1C_1 + R_2C_2)s + 1}{s[(R_1 + R_2)C_1C_2s + (C_1 + C_2)]}$	

(t) Transfer functions

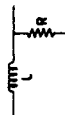
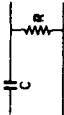
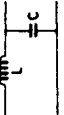
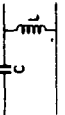
	Network	$Z_T(s) = \frac{E_0(s)}{E_{in}(s)}$; $T = RC$; $T_1 = R_1C_1$; etc.
1		$Z_T(s) = \frac{1}{RCs + 1}$
2		$Z_T(s) = \frac{Ls}{Ls + R}$
3		$Z_T(s) = \frac{R}{Ls + R}$
4		$Z_T(s) = \frac{RCs}{RCs + 1}$
5		$Z_T(s) = \frac{1}{LCs^2 + 1}$
6		$Z_T(s) = \frac{LCs^2}{LCs^2 + 1}$

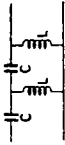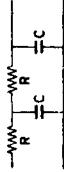
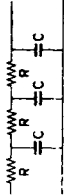
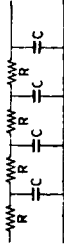
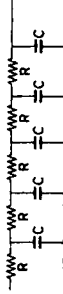
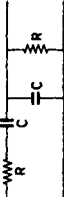
	Network	$Z_T(s) = \frac{E_0(s)}{E_{TR}(s)}$; $T = RC$; $T_1 = R_1C_1$; etc.
7		$Z_T(s) = \frac{L^2C^2s^4 + LCs^2}{L^2C^2s^4 + 3LCs^2 + 1}$
8		$Z_T(s) = \frac{1}{R^2C^2s^2 + 3RCs + 1}$
9		$Z_T(s) = \frac{1}{T^2s^3 + 5T^2s^2 + 6Ts + 1}$
10		$Z_T(s) = \frac{1}{T^2s^4 + 7T^2s^3 + 15T^2s^2 + 10Ts + 1}$
11		$Z_T(s) = \frac{1}{T^2s^5 + 9T^2s^4 + 28T^2s^3 + 36T^2s^2 + 15Ts + 1}$
12		$Z_T(s) = \frac{T_s}{T^2s^2 + 3Ts + 1}$

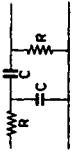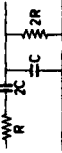
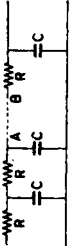
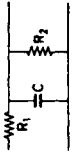
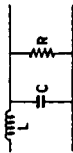
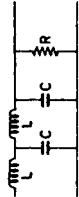
13		$Z_T(s) = \frac{T_s}{T^2s^2 + 3Ts + 1}$ <p>(same transfer function as form #12)</p>
14		$Z_T(s) = \frac{4RCs}{4R^2C^2s^2 + 8RCs + 1}$
15	<p>One section isolated (either one)</p>  <p>Cathode follower between A and B</p>	$Z_T(s) = \frac{1}{(Ts + 1)(T^2s^2 + 3Ts + 1)}$
16		$Z_T(s) = \frac{R_2}{R_1R_2Ts + R_1 + R_2}$
17		$Z_T(s) = \frac{1}{LC} \left(\frac{1}{s^2 + \frac{1}{RC} + LC} \right)$
18		$Z_T(s) = \frac{1}{L^2C^2s^4 + \frac{LC^2s^3}{R} + 3LCs^2 + \frac{2Ls}{R} + 1}$

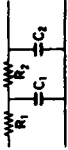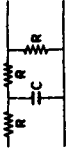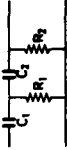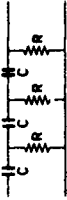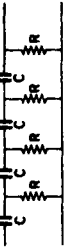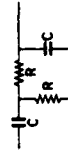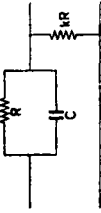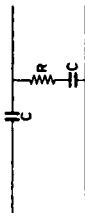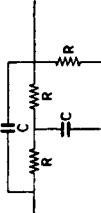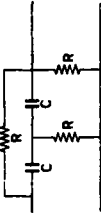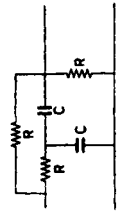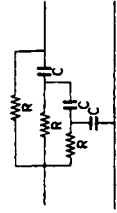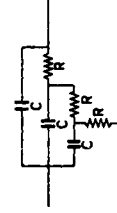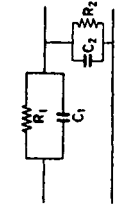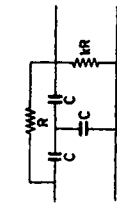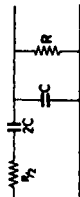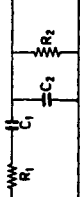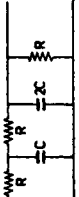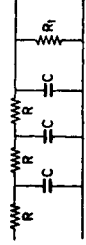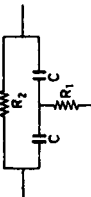
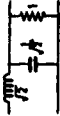



	Network	$Z_T(s) = \frac{E_o(s)}{E_{in}(s)}$; $T = RC$; $T_1 = R_1C_1$; etc.
19		$Z_T(s) = \frac{1}{T_1 T_2 s^2 + (T_1 + T_2 + R_1 C_1) s + 1}$
20		$Z_T(s) = \frac{1}{2T_2 s + 3}$
21		$Z_T(s) = \frac{T_1 T_2 s^2}{T_1 T_2 s^2 + (T_1 + T_2 + R_1 C_1) s + 1}$
22		$Z_T(s) = \frac{T^2 s^2}{T^2 s^2 + 6T^2 s^2 + 5T s + 1}$
23		$Z_T(s) = \frac{T^4 s^4}{T^4 s^4 + 10T^2 s^2 + 15T^2 s^2 + 7T s + 1}$
24		$Z_T(s) = \frac{T s}{T^2 s^2 + 3T s + 1}$ <p>(same as forms 12 and 13)</p>

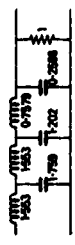
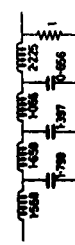

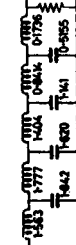
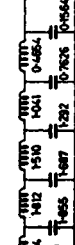
25		$Z_p(s) = \frac{T\theta}{3T\theta + 1}$
26		$Z_p(s) = \frac{T\theta + 1}{2T\theta + 1}$
27		$Z_p(s) = \frac{T\theta + 1}{2T\theta + 1}$ (same as form 26)
28		$Z_p(s) = \frac{(T\theta + 1)^2}{T\theta^2 + 3T\theta + 1}$
29		$Z_p(s) = \frac{T\theta + 1}{T\theta + 2}$

	Network	
		$Z_T(s) = \frac{E_0(s)}{E_T(s)}$; $T = RC$; $T_1 = R_1C_1$; etc.
30		$Z_T(s) = \frac{k(Ts + 1)}{kTs + (1 + k)}$
31		$Z_T(s) = \frac{Ts + 1}{Ts + 2}$ (same as form 29)
32		$Z_T(s) = \frac{Ts + 1}{Ts + 3}$
33		$Z_T(s) = \frac{(Ts + 1)^2}{Ts^2 + 5Ts + 2}$


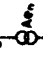
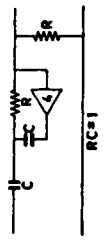
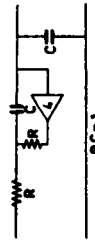
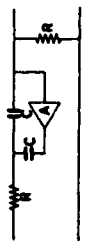
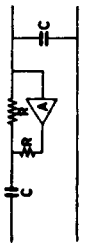
<p>34</p> 	$Z_x(s) = \frac{3Ts + 1}{T^2s^2 + 5Ts + 2}$
<p>35</p> 	$Z_x(s) = \frac{6T^2s^2 + 5Ts + 1}{T^2s^2 + 6T^2s^2 + 5Ts + 1}$
<p>37</p> 	$Z_x(s) = \frac{T^2s^2 + 5T^2s^2 + 6Ts}{T^2s^2 + 5T^2s^2 + 6Ts + 1}$
<p>38</p> 	$Z_x(s) = \frac{R_2(Ts + 1)}{(R_1T_s + R_2T_1)s + (R_1 + R_2)}$
<p>39</p> 	$Z_x(s) = \frac{k(Ts + 3)}{2kTs + 3(1 + k)}$

	Network	
		$Z_T(\theta) = \frac{E_0(\theta)}{E_{IN}(\theta)}; T = RC; T_1 = R_1C_1; \text{ etc.}$
40		$Z_T(\theta) = \frac{2T\theta}{T^2\theta^2 + 4T\theta + 1}$
41		$Z_T(\theta) = \frac{R_2C_1\theta}{R_1R_2C_1C_2\theta^2 + (R_1C_1 + R_2C_2 + R_2C_1)\theta + 1}$
42		$Z_T(\theta) = \frac{1}{2T^2\theta^2 + 6T\theta + 3}$
43		$Z_T(\theta) = \frac{1}{R^2C^2\theta^4 + \frac{R^2C^2\theta^3}{R_1} + 5R^2C^2\theta^2 + \frac{4R^2C\theta}{R_1} + 6RC\theta + \frac{3R}{R_1} + 1}$
44		$Z_T(\theta) = \frac{R_1R_2C^2\theta^2 + 2R_1C\theta + 1}{R_1R_2C^2\theta^2 + (2R_1 + R_2)C\theta + 1}$






45	<p>(Normalized series)</p> 	$Z_T(s) = \frac{1}{s + 1}$
46		$Z_T(s) = \frac{1}{s^2 + (\sqrt{2})s + 1}$
47		$Z_T(s) = \frac{1}{s^2 + 2s^2 + 2s + 1}$
48		$Z_T(s) = \frac{1}{s^4 + 2.6131s^3 + 3.4142s^2 + 2.6131s + 1}$
49		$Z_T(s) = \frac{1}{s^5 + 3.236s^4 + 5.236s^3 + 5.236s^2 + 3.236s + 1}$


	Network	$Z_p(s) = \frac{E_d(s)}{E_{IN}(s)}$; $T = RC$; $T_1 = R_1C_1$; etc.
50		$Z_p(s) = \frac{1}{s^6 + 3.8637s^5 + 7.4641s^4 + 9.1416s^3 + 7.4641s^2 + 3.8637s + 1}$
51		$Z_p(s) = \frac{1}{s^7 + 4.4939s^6 + 10.0978s^5 + 14.5918s^4 + 14.5918s^3 + 10.0978s^2 + 4.4939s + 1}$
52		$Z_p(s) = \frac{1}{s^8 + 5.126s^7 + 13.14s^6 + 21.85s^5 + 25.69s^4 + 21.85s^3 + 13.14s^2 + 5.126s + 1}$
53		$Z_p(s) = \frac{1}{s^9 + 5.759s^8 + 16.58s^7 + 31.16s^6 + 41.99s^5 + 41.99s^4 + 31.16s^3 + 16.58s^2 + 5.759s + 1}$
54		$Z_p(s) = \frac{1}{s^{10} + 6.392s^9 + 20.43s^8 + 42.80s^7 + 64.88s^6 + 74.23s^5 + 64.88s^4 + 42.80s^3 + 20.43s^2 + 6.392s + 1}$

(c) Active transfer functions

	<p>Amplifiers are shown as either  or  where e_1 is input voltage to the amplifier</p>	
<p>1</p> 	$Z_T(e) = e$	
<p>2</p> 	$Z_T(e) = \frac{1}{e}$	
<p>3</p> 	$Z_T(e) = \frac{RCe}{(1-A)R^2C^2e^2 + 3RCe + 1}$	
<p>4</p> 	$Z_T(e) = \frac{RCe}{R^2C^2e^2 + 3RCe + 1 - A}$	

5		$Z_T(s) = \frac{(RCs + 1)^2}{R^2C^2s^2 + (3 - A)RCs + 1}$
6		$Z_T(s) = \frac{1}{R^2C^2s^2 + (3 - A)RCs + 1}$
7		$Z_T(s) = \frac{1}{(RCs + 1)^2}$
8		$Z_T(s) = \frac{1}{1 - RCs}$
9		$Z_T(s) = \frac{2}{R^2C^2s^2 + 1}$

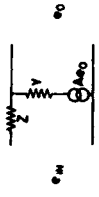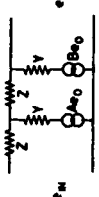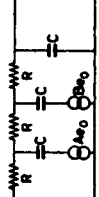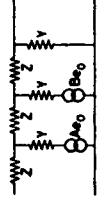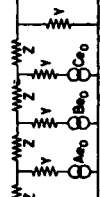10		$ZY = Z(e)Y(e)$ $Z_r(e) = \frac{1}{(1-A)ZY + 1}$
11		$Z_r(e) = \frac{1}{(1-B)ZY^2 + (3-4B-A)ZY + 1 - 2B}$
12		$Z_r(e) = \frac{1}{R^2C^2s^2 + (5-B)R^2Cs + (6-2B-A)RCs + 1}$
13		$Z_r(e) = \frac{1}{Z^2Ys + (5-B)Z^2Y^2 + (6-2B-A)ZY + 1}$
14		$Z_r(e) = \frac{1}{Z^2Y^2 + (7-C)Z^2Y^2 + (12-B)Z^2Y^2 + (10-2C-2B-A)ZY + 1}$

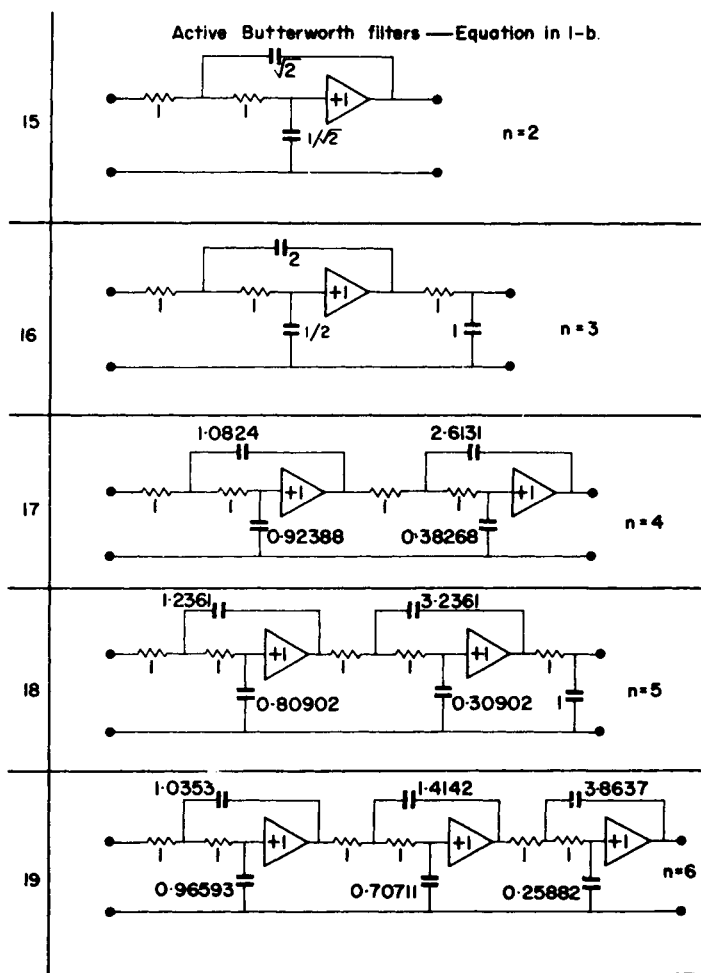

APPENDIX II

OPERATIONAL LAPLACE TRANSFORM PAIRS

No.	$f(t)$	$F(s)$
1	$af(t)$	$aF(s)$
2	$\varepsilon^{at}f(t)$	$F(s - a)$
3	$-tf(t)$	$\frac{dF(s)}{ds}$
4	$f\left(\frac{t}{a}\right)$	$aF(as)$
5	$\int_0^t f(t)dt$	$\frac{F(s)}{s}$
6	$f^n(t)$	$s^n F(s) - s^{n-1}f(0) - s^{n-2}f'(0) - \dots - f^{n-1}(0)$
7	$(t - a)U(t - a)$	$\varepsilon^{-as}F(s)$
8	$f(t) = f(t - a)$	$\frac{1}{1 - \varepsilon^{-as}} \int_0^a f(t)\varepsilon^{-st} dt$
9	$\lim_{t \rightarrow 0} f(t)$	$\lim_{s \rightarrow \infty} sF(s)$
10	$\lim_{t \rightarrow \infty} f(t)$	$\lim_{s \rightarrow 0} sF(s)$
11	$\int_0^t f_1(t - \tau)f_2(\tau)d\tau$	$F_1(s) \cdot F_2(s)$
12	$f'(t)$	$sF(s) - f(0)$

APPENDIX III

TABLE OF LAPLACE TRANSFORM PAIRS

No.	$F(s)$	$f(t)$
1	1	$U_1(t) = \lim_{a \rightarrow 0} \frac{U(t) - U(t-a)}{a}$, unit impulse
2	s	$U_2(t) = \lim_{a \rightarrow 0} \frac{U(t) - 2U(t-a) + U(t-2a)}{a^2}$, unit doublet impulse
3	$\frac{1}{s}$	$U(t)$, unit step function
4	$\frac{1}{s^2}$	t
5	$\frac{1}{s^n} (n = 1, 2, 3, \dots)$	$\frac{t^{n-1}}{(n-1)!}$
6	$\frac{1}{s^n} (n > 0)$	$\frac{t^{n-1}}{\Gamma(n)}$
7	$\frac{1}{s^{1/2}}$	$\frac{1}{\sqrt{\pi t}}$
8	$\frac{1}{s^{3/2}}$	$\sqrt{\frac{4t}{\pi}}$

9	$\frac{1}{s + \alpha}$	$e^{-\alpha t}$
10	$\frac{1}{(s + \alpha)^n}$	$\frac{t^{n-1} e^{-\alpha t}}{(n-1)!}$
11	$\frac{1}{(s + \alpha)(s + \beta)}$	$\frac{e^{-\alpha t} - e^{-\beta t}}{\beta - \alpha}$
12	$\frac{1}{s(s + \alpha)(s + \beta)}$	$\frac{1}{\alpha\beta} + \frac{\beta e^{-\alpha t} - \alpha e^{-\beta t}}{\alpha\beta(\alpha - \beta)}$
13	$\frac{1}{(s + \alpha)(s + \beta)(s + \nu)}$	$\frac{e^{-\alpha t}}{(\beta - \alpha)(\nu - \alpha)} + \frac{e^{-\beta t}}{(\alpha - \beta)(\nu - \beta)} + \frac{e^{-\nu t}}{(\alpha - \nu)(\beta - \nu)}$
14	$\frac{1}{s(s + \alpha)(s + \beta)(s + \nu)}$	$\frac{1}{\alpha\beta\nu} - \frac{e^{-\nu t}}{\nu(\alpha - \nu)(\beta - \nu)} - \frac{e^{-\beta t}}{\beta(\alpha - \beta)(\nu - \beta)} - \frac{e^{-\alpha t}}{\alpha(\beta - \alpha)(\nu - \alpha)}$
15	$\frac{1}{s^2(s + \alpha)}$	$\frac{1}{\alpha^2} (e^{-\alpha t} + \alpha t - 1)$
16	$\frac{1}{s^2(s + \alpha)(s + \beta)}$	$\frac{1}{\alpha^2\beta^2} \left[\frac{1}{(\alpha - \beta)} (\alpha^2 e^{-\beta t} - \beta^2 e^{-\alpha t}) + \alpha\beta t - \alpha - \beta \right]$
17	$\frac{1}{s^2(s + \alpha)(s + \beta)(s + \nu)}$	$\frac{\alpha\beta(\nu t - 1) - \alpha\nu - \beta\nu}{(\alpha\beta\nu)^3} + \frac{e^{-\alpha t}}{\alpha^2(\nu - \alpha)(\beta - \alpha)} + \frac{e^{-\beta t}}{\beta^2(\nu - \beta)(\alpha - \beta)} + \frac{e^{-\nu t}}{\nu^2(\beta - \nu)(\alpha - \nu)}$
18	$\frac{1}{s^3 + \alpha^3}$	$\frac{\sin \alpha t}{\alpha}$
19	$\frac{1}{s^3 - \alpha^3}$	$\frac{\sinh \alpha t}{\alpha}$

No.	$F(s)$	$f(t)$
20	$\frac{1}{s(s^2 + \alpha^2)}$	$\frac{1 - \cos \alpha t}{\alpha^2}$
21	$\frac{1}{s^2(s^2 + \alpha^2)}$	$\frac{t}{\alpha^2} - \frac{\sin \alpha t}{\alpha^3}$
22	$\frac{1}{(s + \alpha)(s^2 + \beta^2)}$	$\frac{1}{\alpha^2 + \beta^2} \left(e^{-\alpha t} + \frac{\alpha}{\beta} \sin \beta t - \cos \beta t \right)$
23	$\frac{1}{s(s + \alpha)(s^2 + \beta^2)}$	$\frac{1}{\alpha\beta^2} - \frac{1}{\alpha^2 + \beta^2} \left(\frac{\sin \beta t}{\beta} + \frac{\alpha \cos \beta t}{\beta^2} + \frac{e^{-\alpha t}}{\alpha} \right)$
24	$\frac{1}{s^2(s + \alpha)(s^2 + \beta^2)}$	$\frac{t}{\alpha\beta^2} - \frac{1}{\alpha^2\beta^2} + \frac{e^{-\alpha t}}{\alpha^2(\alpha^2 + \beta^2)} + \frac{\cos(\beta t + \phi)}{\beta^2\sqrt{(\alpha^2 + \beta^2)^2}}, \quad \phi = \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
25	$\frac{1}{(s + \alpha)(s + \beta)(s^2 + \gamma^2)}$	$\frac{e^{-\alpha t}}{(\beta - \alpha)(\alpha^2 + \gamma^2)} + \frac{e^{-\beta t}}{(\alpha - \beta)(\beta^2 + \gamma^2)} + \frac{\sin(\gamma t - \phi)}{\gamma\sqrt{\{\gamma^2(\alpha + \beta)^2 + (\alpha\beta - \gamma^2)^2\}}}, \quad \phi = \tan^{-1} \left(\frac{\gamma}{\alpha} \right) + \tan^{-1} \left(\frac{\gamma}{\beta} \right)$
26	$\frac{1}{s(s + \alpha)(s + \beta)(s^2 + \gamma^2)}$	$\frac{1}{\alpha\beta\gamma^2} + \frac{e^{-\alpha t}}{\alpha(\alpha - \beta)(\alpha^2 + \gamma^2)} + \frac{e^{-\beta t}}{\beta(\beta - \alpha)(\beta^2 + \gamma^2)} + \frac{\cos(\gamma t + \phi)}{\gamma^2\sqrt{\{(\alpha\beta - \gamma^2)^2 + \gamma^2(\alpha + \beta)^2\}}}, \quad \phi = \tan^{-1} \left(\frac{\beta}{\gamma} \right) + \tan^{-1} \left(\frac{\alpha}{\gamma} \right)$
27	$\frac{1}{s^2(s + \alpha)(s + \beta)(s^2 + \gamma^2)}$	$\frac{1}{\alpha\beta\gamma^2} \left(t - \frac{1}{\alpha} - \frac{1}{\beta} \right) + \frac{e^{-\alpha t}}{\alpha^2(\beta - \alpha)(\alpha^2 + \gamma^2)} + \frac{e^{-\beta t}}{\beta^2(\alpha - \beta)(\beta^2 + \gamma^2)} + \frac{\cos(\gamma t + \phi)}{\gamma^2\sqrt{\{(\alpha\beta - \gamma^2)^2 + (\alpha + \beta)^2\gamma^2\}}}, \quad \phi = \tan^{-1} \left(\frac{\beta}{\gamma} \right) - \tan^{-1} \left(\frac{\alpha}{\gamma} \right)$

28	$\frac{1}{(\sigma^2 + \alpha^2)(\sigma^2 + \beta^2)}$	$\frac{1}{\beta^2 - \alpha^2} \left(\frac{\sin \alpha t}{\alpha} - \frac{\sin \beta t}{\beta} \right)$
29	$\frac{1}{(\sigma + \alpha)^2 + \beta^2}$	$\frac{e^{-\alpha t} \sin \beta t}{\beta}$
30	$\frac{1}{\sigma^2[(\sigma + \alpha)^2 + \beta^2]}$	$\frac{1}{\alpha^2 + \beta^2} \left(t - \frac{2\alpha}{\alpha^2 + \beta^2} \right) + \frac{e^{-\alpha t} \sin(\beta t + \phi)}{\beta(\alpha^2 + \beta^2)}$, $\phi = 2 \tan^{-1} \left(\frac{\beta}{\alpha} \right)$
31	$\frac{1}{(\sigma + \nu)[(\sigma + \alpha)^2 + \beta^2]}$	$\frac{e^{-\nu t}}{\beta^2 + (\nu - \alpha)^2} + \frac{e^{-\alpha t} \sin(\beta t - \phi)}{\beta \sqrt{(\nu - \alpha)^2 + \beta^2}}$, $\phi = \tan^{-1} \left(\frac{\beta}{\nu - \alpha} \right)$
32	$\frac{1}{\sigma(\sigma + \nu)[(\sigma + \alpha)^2 + \beta^2]}$	$\frac{1}{\nu(\alpha^2 + \beta^2)} - \frac{e^{-\nu t}}{\nu[(\alpha - \nu)^2 + \beta^2]} + \frac{e^{-\alpha t} \sin(\beta t + \phi)}{\beta \sqrt{(\alpha^2 + \beta^2)[(\alpha - \nu)^2 + \beta^2]}}$, $\phi = \tan^{-1} \left(\frac{\beta}{\alpha} \right) + \tan^{-1} \left(\frac{\beta}{\alpha - \nu} \right)$
33	$\frac{1}{\sigma^2(\sigma + \nu)[(\sigma + \alpha)^2 + \beta^2]}$	$\frac{1}{\nu(\alpha^2 + \beta^2)} \left(t - \frac{1}{\nu} - \frac{2\alpha}{\alpha^2 + \beta^2} \right) + \frac{e^{-\nu t}}{\nu^2[(\nu - \alpha)^2 + \beta^2]} + \frac{e^{-\alpha t} \sin(\beta t + \phi)}{\beta(\alpha^2 + \beta^2) \sqrt{(\nu - \alpha)^2 + \beta^2}}$, $\phi = 2 \tan^{-1} \left(\frac{\beta}{\alpha} \right) - \tan^{-1} \left(\frac{\beta}{\nu - \alpha} \right)$
34	$\frac{1}{(\sigma + \nu)(\sigma + \delta)[(\sigma + \alpha)^2 + \beta^2]}$	$\frac{e^{-\nu t}}{(\delta - \nu)[(\alpha - \nu)^2 + \beta^2]} + \frac{e^{-\delta t}}{(\nu - \delta)[(\alpha - \delta)^2 + \beta^2]} + \frac{e^{-\alpha t} \cos(\beta t + \phi)}{\beta \sqrt{[(\alpha - \delta)^2 + \beta^2][(\alpha - \nu)^2 + \beta^2]}}$, $\phi = \tan^{-1} \left(\frac{\beta}{\alpha - \delta} \right) - \tan^{-1} \left(\frac{\alpha - \nu}{\beta} \right)$
35	$\frac{1}{(\sigma^2 + \nu^2)[(\sigma + \alpha)^2 + \beta^2]}$	$\frac{\beta \sin(\nu t + \phi_1) + \nu e^{-\alpha t} \sin(\beta t + \phi_2)}{\beta \nu \sqrt{4\alpha^2 \nu^2 + (\alpha^2 + \beta^2 - \nu^2)^2}}$, $\phi_1 = \tan^{-1} \left(\frac{2\alpha \nu}{\nu^2 - \alpha^2 - \beta^2} \right)$, $\phi_2 = \tan^{-1} \left[\frac{2\alpha \beta}{\alpha^2 - \beta^2 + \nu^2} \right]$

No.	$F(s)$	$f(t)$
36	$\frac{1}{s(s^2 + \nu^2)(s + \alpha)^2 + \beta^2}$	$\frac{1}{\nu^2(\alpha^2 + \beta^2)} + \frac{\sin(\nu t - \phi_1)}{\beta\sqrt{(\alpha^2 + \beta^2)[4\alpha^2\nu^2 + (\alpha^2 + \beta^2 - \nu^2)^2]}} - \frac{\sin(\nu t + \phi_2)}{\nu^2\sqrt{4\alpha^2\nu^2 + (\alpha^2 + \beta^2 - \nu^2)^2}}$ $\phi_1 = \tan^{-1}\left(\frac{\alpha}{\beta}\right) + \tan^{-1}\left(\frac{\alpha^2 - \beta^2 + \nu^2}{2\alpha\beta}\right), \quad \phi_2 = \tan^{-1}\left(\frac{\alpha^2 + \beta^2 - \nu^2}{2\alpha\beta}\right)$
37	$\frac{1}{(s + \nu)(s^2 + \delta^2)(s + \alpha)^2 + \beta^2}$	$\frac{e^{-\nu t}}{(\nu^2 + \delta^2)(\alpha - \nu)^2 + \beta^2} + \frac{e^{-\alpha t} \sin(\beta t + \phi_1)}{\beta\sqrt{[\nu - \alpha]^2 + \beta^2}[4\alpha^2\delta^2 + (\alpha^2 + \beta^2 - \delta^2)^2]}}$ $- \frac{\sin(\delta t + \phi_2)}{\delta\sqrt{(\nu^2 + \delta^2)[4\alpha^2\delta^2 + (\alpha^2 + \beta^2 - \delta^2)^2]}}$ $\phi_1 = \tan^{-1}\left(\frac{\nu - \alpha}{\beta}\right) - \tan^{-1}\left(\frac{\alpha^2 - \beta^2 + \delta^2}{2\alpha\beta}\right), \quad \phi_2 = \tan^{-1}\left(\frac{\nu}{\delta}\right) + \tan^{-1}\left(\frac{\alpha^2 + \beta^2 - \delta^2}{2\alpha\delta}\right)$
38	$\frac{1}{s(s + \alpha)^2}$	$\frac{1 - e^{-\alpha t} - \alpha t e^{-\alpha t}}{\alpha^3}$
39	$\frac{1}{s^2(s + \alpha)^2}$	$\frac{t}{\alpha^2} - \frac{2}{\alpha^3} + \frac{t e^{-\alpha t}}{\alpha^2} + \frac{2e^{-\alpha t}}{\alpha^3}$
40	$\frac{1}{(s + \alpha)(s + \beta)^2}$	$\frac{e^{-\alpha t}}{(\alpha - \beta)^2} + \frac{[(\alpha - \beta)t - 1]e^{-\beta t}}{(\alpha - \beta)^2}$
41	$\frac{1}{s(s + \alpha)(s + \beta)^2}$	$\frac{1}{\alpha\beta^2} - \frac{e^{-\alpha t}}{\alpha(\alpha - \beta)^2} - \left[\frac{t}{\beta(\alpha - \beta)} + \frac{\alpha - 2\beta}{\beta^2(\alpha - \beta)^2} \right] e^{-\beta t}$
42	$\frac{1}{s^2(s + \alpha)(s + \beta)^2}$	$\frac{e^{-\alpha t}}{\alpha^2(\beta - \alpha)^2} + \frac{1}{\alpha\beta^2} \left(t - \frac{1}{\alpha} - \frac{2}{\beta} \right) + \left[\frac{t}{\beta^2(\alpha - \beta)} + \frac{2(\alpha - \beta) - \beta}{\beta^2(\beta - \alpha)^2} \right] e^{-\beta t}$

43	$\frac{1}{(\sigma + \beta)(\sigma + \nu)(\sigma + \alpha)^2}$	$\left[\frac{t}{(\alpha - \beta)(\alpha - \nu)} + \frac{2\alpha - \beta - \nu}{(\alpha - \beta)^2(\alpha - \nu)^2} \right] \varepsilon^{-\alpha t} + \frac{\varepsilon^{-\beta t}}{(\nu - \beta)(\alpha - \beta)^2} + \frac{\varepsilon^{-\nu t}}{(\beta - \nu)(\alpha - \nu)^2}$
44	$\frac{1}{\sigma(\sigma + \beta)(\sigma + \nu)(\sigma + \alpha)^2}$	$\frac{1}{\beta \nu \alpha^2} + \frac{\varepsilon^{-\beta t}}{\beta(\beta - \nu)(\alpha - \beta)^2} + \frac{\varepsilon^{-\nu t}}{\nu(\nu - \beta)(\alpha - \nu)^2} + \left[\frac{t}{\alpha(\alpha - \nu)(\beta - \alpha)} - \frac{(\alpha - \nu)(\alpha - \beta) + \alpha(2\alpha - \nu - \beta)}{\alpha^2(\alpha - \nu)^2(\alpha - \beta)^2} \right] \varepsilon^{-\alpha t}$
45	$\frac{1}{\sigma^2(\sigma + \beta)(\sigma + \nu)(\sigma + \alpha)^2}$	$\left[\frac{t}{\alpha^2(\alpha - \nu)(\alpha - \beta)} + \frac{2(\alpha - \nu)(\alpha - \beta) + \alpha(2\alpha - \nu - \beta)}{\alpha^2(\alpha - \nu)^2(\alpha - \beta)^2} \right] \varepsilon^{-\alpha t} + \frac{\varepsilon^{-\beta t}}{\beta^2(\nu - \beta)(\alpha - \beta)^2} + \frac{\varepsilon^{-\nu t}}{\beta \nu \alpha^2} \left(t - \frac{2}{\alpha} - \frac{1}{\beta} - \frac{1}{\nu} \right) + \frac{\varepsilon^{-\nu t}}{\nu^2(\beta - \nu)(\alpha - \nu)^2}$
46	$\frac{1}{(\sigma^2 + \alpha^2)(\sigma + \beta)^2}$	$\frac{\sin(\alpha t + \phi)}{\alpha(\alpha^2 + \beta^2)} + \left[\frac{t}{\alpha^2 + \beta^2} + \frac{2\beta}{(\alpha^2 + \beta^2)^2} \right] \varepsilon^{-\beta t}, \quad \phi = 2 \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
47	$\frac{1}{\sigma(\sigma^2 + \alpha^2)(\sigma + \beta)^2}$	$\frac{1}{\alpha^2 \beta^2} - \frac{\sin(\alpha t + \phi)}{\alpha^2(\alpha^2 + \beta^2)} - \left[\frac{t}{\beta(\alpha^2 + \beta^2)} + \frac{3\beta^2 + \alpha^2}{\beta^2(\alpha^2 + \beta^2)^2} \right] \varepsilon^{-\beta t}, \quad \phi = \tan^{-1} \left(\frac{\beta}{\alpha} \right) - \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
48	$\frac{1}{\sigma^2(\sigma^2 + \alpha^2)(\sigma + \beta)^2}$	$\frac{\sin(\alpha t + \phi)}{\alpha^2(\alpha^2 + \beta^2)} + \frac{t\varepsilon^{-\beta t}}{\beta^2(\alpha^2 + \beta^2)} + \frac{2(\alpha^2 + 2\beta^2)\varepsilon^{-\beta t}}{\beta^2(\alpha^2 + \beta^2)^2} + \frac{t}{\alpha^2\beta^2} - \frac{2}{\alpha^2\beta^2}, \quad \phi = 2 \tan^{-1} \left(\frac{\beta}{\alpha} \right)$
49	$\frac{1}{(\sigma + \nu)(\sigma^2 + \alpha^2)(\sigma + \beta)^2}$	$\frac{\sin(\alpha t - \phi)}{\alpha(\alpha^2 + \beta^2)\sqrt{(\alpha^2 + \nu^2)}} + \frac{t\varepsilon^{-\beta t}}{(\nu - \beta)(\alpha^2 + \beta^2)} + \left[\frac{2(\nu - \beta)\beta - (\alpha^2 + \beta^2)}{(\nu - \beta)^2(\alpha^2 + \beta^2)^2} \right] \varepsilon^{-\beta t} + \frac{\varepsilon^{-\nu t}}{(\alpha^2 + \nu^2)(\beta - \nu)^2}, \quad \phi = 2 \tan^{-1} \left(\frac{\alpha}{\beta} \right) + \tan^{-1} \left(\frac{\alpha}{\nu} \right)$
50	$\frac{1}{(\sigma + \nu)^2(\sigma + \beta)^2 + \alpha^2}$	$\frac{\varepsilon^{-\beta t} \sin(\alpha t - \phi)}{\alpha[\alpha^2 + (\beta - \nu)^2]} + \frac{2(\nu - \beta)\varepsilon^{-\nu t}}{[(\beta - \nu)^2 + \alpha^2]^2} + \frac{t\varepsilon^{-\nu t}}{\alpha^2 + (\beta - \nu)^2}, \quad \phi = 2 \tan^{-1} \left(\frac{\alpha}{\nu - \beta} \right)$

No.	$F(s)$	$f(t)$
51	$\frac{1}{s(s+v)^2(s+\beta)^2+\alpha^2}$	$\frac{e^{-\beta t} \sin(\alpha t + \phi)}{\alpha(\alpha^2 + (\beta - v)^2)\sqrt{(\alpha^2 + \beta^2)}} - \left(\frac{(\alpha^2 + (\beta - v)^2) - 2v(\beta - v)}{v^2(\alpha^2 + (\beta - v)^2)^2} \right) e^{-vt} - \frac{te^{-vt}}{v(\alpha^2 + (\beta - v)^2)}$ $+ \frac{1}{v^2(\alpha^2 + \beta^2)}, \quad \phi = 2 \tan^{-1} \left(\frac{v - \beta}{\alpha} \right) + \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
52	$\frac{1}{(s + \alpha)^2(s + \beta)^2}$	$\frac{te^{-\alpha t}}{(\beta - \alpha)^2} - \frac{2e^{-\alpha t}}{(\beta - \alpha)^2} + \frac{te^{-\beta t}}{(\alpha - \beta)^2} - \frac{2e^{-\beta t}}{(\alpha - \beta)^2}$
53	$\frac{1}{s(s + \alpha)^2(s + \beta)^2}$	$\frac{(3\alpha - 2\beta)e^{-\alpha t}}{\alpha^2(\beta - \alpha)^2} - \frac{te^{-\alpha t}}{\alpha(\beta - \alpha)^2} + \frac{(3\beta - \alpha)e^{-\beta t}}{\beta^2(\alpha - \beta)^2} - \frac{te^{-\beta t}}{\beta(\alpha - \beta)^2} + \frac{1}{\alpha^2\beta^2}$
54	$\frac{1}{s^2(s + \alpha)^2(s + \beta)^2}$	$\frac{2(\beta - 2\alpha)e^{-\alpha t}}{\alpha^2(\beta - \alpha)^2} + \frac{te^{-\alpha t}}{\alpha^2(\beta - \alpha)^2} + \frac{2(\alpha - 2\beta)e^{-\beta t}}{\beta^2(\alpha - \beta)^2} + \frac{te^{-\beta t}}{\beta^2(\alpha - \beta)^2} + \frac{t}{\alpha^2\beta^2} - \frac{2(\alpha + \beta)}{\alpha^2\beta^2}$
55	$\frac{1}{(s + v)(s + \alpha)^2(s + \beta)^2}$	$\frac{e^{-vt}}{(\alpha - v)^2(\beta - v)^2} + \frac{[3\beta - (\alpha + 2v)]e^{-\beta t}}{(\alpha - \beta)^2(v - \beta)^2} + \frac{te^{-\beta t}}{(v - \beta)(\alpha - \beta)^2} + \frac{[3\alpha - (\beta - 2v)]e^{-\alpha t}}{(\alpha - \beta)^2(\beta - \alpha)^2} + \frac{te^{-\alpha t}}{(v - \alpha)(\beta - \alpha)^2} + \frac{e^{-vt}}{(\alpha - v)^2(\beta - v)^2}$
56	$\frac{1}{(s^2 + v^2)(s + \alpha)^2(s + \beta)^2}$	$\frac{\sin(vt + \phi)}{v(\alpha^2 + v^2)(\beta^2 + v^2)} - 2 \left[\frac{(\alpha^2 + v^2) - \alpha(\beta - \alpha)}{(\alpha^2 + v^2)(\beta - \alpha)^2} \right] e^{-\alpha t} + \frac{te^{-\alpha t}}{(\alpha^2 + v^2)(\beta - \alpha)^2}$ $- 2 \left[\frac{\beta^2 + v^2 - \beta(\alpha - \beta)}{(\beta^2 + v^2)(\alpha - \beta)^2} \right] e^{-\beta t} + \frac{te^{-\beta t}}{(\beta^2 + v^2)(\alpha - \beta)^2}, \quad \phi = 2 \tan^{-1} \left(\frac{\beta}{v} \right) + 2 \tan^{-1} \left(\frac{\alpha}{v} \right)$
57	$\frac{1}{[\alpha^2 + (s + \beta)^2]^2}$	$\frac{e^{-\beta t} (\sin \alpha t - \alpha t \cos \alpha t)}{2\alpha^3}$

58	$\frac{1}{(e^2 + \alpha^2)^2}$	$\frac{\sin \alpha t - \alpha t \cos \alpha t}{2\alpha^2}$
59	$\frac{1}{e(e^2 + \alpha^2)^2}$	$\frac{(1 - \cos \alpha t)}{\alpha^4} - \frac{t \sin \alpha t}{2\alpha^2}$
60	$\frac{1}{e^2(e^2 + \alpha^2)^2}$	$\frac{3 \sin \alpha t}{2\alpha^4} + \frac{t \cos \alpha t}{2\alpha^4} + \frac{t}{\alpha^4}$
61	$\frac{1}{(e + \beta)(e^2 + \alpha^2)^2}$	$\frac{e^{-\beta t}}{(\alpha^2 + \beta^2)^2} - \frac{t \sin(\alpha t + \phi_1)}{2\alpha^2 \sqrt{(\alpha^2 + \beta^2)}} - \frac{(\sqrt{\beta^2 + 4\alpha^2}) \cos(\alpha t + \phi_2)}{2\alpha^2(\alpha^2 + \beta^2)}$ $\phi_1 = \tan^{-1} \left(\frac{\beta}{\alpha} \right), \quad \phi_2 = \tan^{-1} \left[\frac{\beta(3\alpha^2 + \beta^2)}{2\alpha^4} \right]$
62	$\frac{1}{e(e + \beta)(e^2 + \alpha^2)^2}$	$\frac{t \cos(\alpha t + \phi_1)}{2\alpha^2 \sqrt{(\alpha^2 + \beta^2)}} - \frac{(\sqrt{9\alpha^2 + 4\beta^2}) \cos(\alpha t + \phi_2)}{2\alpha^2(\alpha^2 + \beta^2)} - \frac{e^{-\beta t}}{\beta(\alpha^2 + \beta^2)^2} + \frac{1}{\alpha^2 \beta}$ $\phi_1 = \tan^{-1} \left(\frac{\beta}{\alpha} \right), \quad \phi_2 = \tan^{-1} \left(\frac{3\alpha}{2\beta} \right) + 2 \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
63	$\frac{1}{e^2(e + \beta)(e^2 + \alpha^2)^2}$	$\frac{t \sin(\alpha t + \phi_1)}{2\alpha^2 \sqrt{(\alpha^2 + \beta^2)}} - \frac{(16\alpha^2 + 9\beta^2)^{1/2} \sin(\alpha t + \phi_2)}{4\alpha^2(\alpha^2 + \beta^2)} + \frac{e^{-\beta t}}{\beta^2(\alpha^2 + \beta^2)^2} + \frac{t}{\alpha^2 \beta} - \frac{1}{\alpha^4 \beta^2}$ $\phi_1 = \tan^{-1} \left(\frac{\beta}{\alpha} \right), \quad \phi_2 = \tan^{-1} \left(\frac{4\alpha}{3\beta} \right) - 2 \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
64	$\frac{1}{e(e + \alpha)^2}$	$\frac{1}{\alpha^2} - \left(\frac{t}{2\alpha} + \frac{t}{\alpha^2} + \frac{1}{\alpha^2} \right) e^{-\alpha t}$
65	$\frac{1}{e^2(e^2 + \alpha^2)}$	$\frac{t^2}{2\alpha^2} + \frac{(\cos \alpha t - 1)}{\alpha^4}$

No.	$F(s)$	$f(t)$
66	$\frac{1}{s^2(s^2 - \alpha^2)}$	$\frac{\sinh \alpha t}{\alpha^3} - \frac{t}{\alpha^2}$
67	$\frac{1}{s^2(s^2 + \alpha^2)}$	$\frac{(\cosh \alpha t - 1)}{\alpha^4} - \frac{t^2}{2\alpha^2}$
68	$\frac{1}{s^4 - \alpha^4}$	$\frac{\sinh \alpha t - \sin \alpha t}{2\alpha^3}$
69	$\frac{1}{s\sqrt{(s+1)}}$	$\text{erf}(\sqrt{t})$
70	$\frac{1}{\sqrt{s^2 + \alpha^2}(s + \sqrt{s^2 + \alpha^2})}$	$\frac{J_1(\alpha t)}{\alpha}$
71	$\frac{1}{(s + \sqrt{(s^2 + \alpha^2)})^n}$	$\frac{n J_n(\alpha t)}{\alpha^n t}$
72	$\frac{1}{s(s + \sqrt{(s^2 + \alpha^2)})^n}$	$\frac{n}{\alpha^n} \int_0^t \frac{J_n(\alpha t)}{t} dt$
73	$\frac{1}{\sqrt{s(s-1)}}$	$e^t \text{erf}(\sqrt{t})$
74	$\frac{1}{1 + \sqrt{s}}$	$\frac{1}{\sqrt{(\pi t)}} - e^t - e^t \text{erf}(\sqrt{t})$
75	$\frac{1}{\sqrt{(s^2 + \alpha^2)}}$	$J_0(\alpha t)$

76	$\frac{1}{\sqrt{(\rho^2 - \alpha^2)}}$	$J_0(\rho \alpha t)$
77	$\frac{1}{\rho + \sqrt{(\rho^2 + \alpha^2)}}$	$\frac{J_1(\alpha t)}{\alpha t}$
78	$\frac{1}{\sqrt{\rho^2 + \alpha^2}(\rho + \sqrt{\rho^2 + \alpha^2})^n}$	$\frac{J_n(\alpha t)}{\alpha^n}$
79	$\frac{1}{\rho e^{\rho t}}$	$J_0(2\sqrt{\alpha t})$
80	$\frac{1}{\sqrt{\rho e^{\rho t}}}$	$\frac{\cos 2\sqrt{\alpha t}}{\sqrt{(\pi t)}}$
81	$\frac{e^{-\rho t}}{\rho}$	$U(t - a)$
82	$\frac{\rho}{\rho^2 + \alpha^2}$	$\cos \alpha t$
83	$\frac{\rho}{\rho^2 - \alpha^2}$	$\cosh \alpha t$
84	$\frac{\rho}{(\rho^2 + \alpha^2)(\rho^2 + \beta^2)}$	$\frac{\cos \alpha t - \cos \beta t}{\beta^2 - \alpha^2}, \quad \alpha^2 \neq \beta^2$
85	$\frac{\rho}{[\rho^2 + (\alpha + \beta)^2][\rho^2 + (\alpha - \beta)^2]}$	$\frac{\sin \beta t \cdot \sin \alpha t}{2\alpha\beta}$
86	$\frac{\rho}{(\rho^2 + \alpha^2)^2}$	$t \frac{\sin \alpha t}{2\alpha}$

No.	$F(s)$	$f(t)$
87	$\frac{s^2}{(s^2 + \alpha^2)^2}$	$\frac{\sin \alpha t + \alpha t \cos \alpha t}{2\alpha}$
88	$\frac{s}{(s + \alpha)^2}$	$e^{-\alpha t}(1 - \alpha t)$
89	$\frac{s}{s^4 - \alpha^4}$	$\frac{\cosh \alpha t - \cos \alpha t}{2\alpha^3}$
90	$\frac{s^2}{s^4 - \alpha^4}$	$\frac{\sinh \alpha t + \sin \alpha t}{2\alpha}$
91	$\frac{s^3}{s^4 - \alpha^4}$	$\frac{\cosh \alpha t + \cos \alpha t}{2}$
92	$\frac{s}{s^4 + 4\alpha^4}$	$\frac{\sinh \alpha t \cdot \sin \alpha t}{2\alpha^3}$
93	$\frac{s}{(s - \alpha)(s - \beta)}$	$\frac{\alpha s - \alpha^2 - \beta s + \beta^2}{\alpha - \beta}, \quad \alpha \neq \beta$
94	$\frac{8\alpha^2 s^3}{(s^2 + \alpha^2)^3}$	$(1 + \alpha^2 t^2) \sin \alpha t - \alpha t \cos \alpha t$
95	$\frac{s}{(s - \alpha)^{3/2}}$	$\frac{e^{\alpha t}(1 + 2\alpha t)}{\sqrt{(\pi t)}}$
96	$\frac{\sqrt{s}}{s - \alpha^2}$	$\frac{1}{\sqrt{(\pi t)}} + \alpha e^{\alpha^2 t} \operatorname{erf}(\alpha\sqrt{t})$

97	$\frac{s + a_0}{s(s + \alpha)}$	$\frac{a_0 - (a_0 - \alpha)e^{-\alpha t}}{\alpha}$
98	$\frac{s + a_0}{(s + \alpha)(s + \beta)}$	$\frac{(a_0 - \alpha)e^{-\alpha t} + (\beta - a_0)e^{-\beta t}}{\beta - \alpha}$
99	$\frac{s + a_0}{s(s + \alpha)(s + \beta)}$	$\frac{a_0}{\alpha\beta} + \frac{(\alpha - a_0)e^{-\alpha t}}{\alpha(\beta - \alpha)} + \frac{(\beta - a_0)e^{-\beta t}}{\beta(\alpha - \beta)}$
100	$\frac{s + a_0}{s^2(s + \alpha)(s + \beta)}$	$\frac{(1 + \frac{a_0 t}{\alpha\beta}) - \frac{(\alpha + \beta)a_0}{\alpha^2\beta^2} + \frac{1}{\beta - \alpha} \left[\frac{(a_0 - \alpha)e^{-\alpha t}}{\alpha^2} - \frac{(a_0 - \beta)e^{-\beta t}}{\beta^2} \right]}$
101	$\frac{s + a_0}{(s + \alpha)(s + \beta)(s + \gamma)}$	$\frac{(a_0 - \alpha)e^{-\alpha t}}{(\gamma - \alpha)(\beta - \alpha)} + \frac{(a_0 - \beta)e^{-\beta t}}{(\alpha - \beta)(\gamma - \beta)} + \frac{(a_0 - \gamma)e^{-\gamma t}}{(\alpha - \gamma)(\beta - \gamma)}$
102	$\frac{s + a_0}{s(s + \alpha)(s + \beta)(s + \gamma)}$	$\frac{a_0}{\alpha\beta\gamma} + \frac{(\alpha - a_0)e^{-\alpha t}}{\alpha(\beta - \alpha)(\gamma - \alpha)} + \frac{(\beta - a_0)e^{-\beta t}}{\beta(\alpha - \beta)(\gamma - \beta)} + \frac{(\gamma - a_0)e^{-\gamma t}}{\gamma(\alpha - \gamma)(\beta - \gamma)}$
103	$\frac{s + a_0}{s^2(s + \alpha)(s + \beta)(s + \gamma)}$	$\frac{1 + \frac{a_0 t}{\alpha\beta\gamma} - \frac{a_0(\alpha\beta + \beta\gamma + \alpha\gamma)}{\alpha^2\beta^2\gamma^2} + \frac{(a_0 - \alpha)e^{-\alpha t}}{\alpha^2(\beta - \alpha)(\gamma - \alpha)} + \frac{(a_0 - \beta)e^{-\beta t}}{\beta^2(\alpha - \beta)(\gamma - \beta)} + \frac{(a_0 - \gamma)e^{-\gamma t}}{\gamma^2(\alpha - \gamma)(\beta - \gamma)}$
104	$\frac{s + a_0}{s^2 + \alpha^2}$	$\frac{\sqrt{(a_0^2 + \alpha^2)} \sin(\alpha t + \phi)}{\alpha}, \quad \phi = \tan^{-1} \left(\frac{\alpha}{a_0} \right)$
105	$\frac{s + a_0}{s(s^2 + \alpha^2)}$	$\frac{a_0}{\alpha^2} + \sqrt{\frac{1}{\alpha^2} + \frac{a_0^2}{\alpha^4}} \sin(\alpha t - \phi), \quad \phi = \tan^{-1} \left(\frac{a_0}{\alpha} \right)$
106	$\frac{s + a_0}{s^2(s^2 + \alpha^2)}$	$\left[\frac{1}{\alpha^2} + \frac{a_0 t}{\alpha^2} - \sqrt{\frac{1}{\alpha^2} + \frac{a_0^2}{\alpha^4}} \cdot \sin(\alpha t + \phi) \right], \quad \phi = \tan^{-1} \left(\frac{\alpha}{a_0} \right)$
107	$\frac{s + a_0}{(s + \alpha)(s^2 + \beta^2)}$	$\frac{(a_0 - \alpha)e^{-\alpha t}}{\alpha^2 + \beta^2} + \sqrt{\frac{a_0^2 + \beta^2}{\alpha^2\beta^2 + \beta^4}} \cdot \sin(\beta t + \phi), \quad \phi = \tan^{-1} \left(\frac{\alpha}{\beta} \right) - \tan^{-1} \left(\frac{a_0}{\beta} \right)$

No.	$F(s)$	$f(t)$
108	$\frac{s + a_0}{s^2(s + \alpha)(s^2 + \beta^2)}$	$\frac{a_0}{\alpha\beta^2} - \frac{(a_0 - \alpha)e^{-\alpha t}}{\alpha(\alpha^2 + \beta^2)} - \sqrt{\frac{a_0^2 + \beta^2}{\alpha^2\beta^2 + \beta^4}} \cdot \cos(\beta t + \phi), \quad \phi = \tan^{-1}\left(\frac{\alpha}{\beta}\right) - \tan^{-1}\left(\frac{a_0}{\beta}\right)$
109	$\frac{s + a_0}{s^2(s + \alpha)(s^2 + \beta^2)}$	$\frac{1}{\alpha\beta^2} - \frac{a_0}{\alpha\beta^2}\left(\frac{1}{\alpha} - t\right) + \frac{a_0\alpha e^{-\alpha t}}{\alpha^2(\alpha^2 + \beta^2)} + \frac{1}{\beta^2}\sqrt{\frac{a_0^2 + \beta^2}{\alpha^2 + \beta^2}} \cdot \cos(\beta t + \phi)$ $\phi = \tan^{-1}\left(\frac{\alpha}{\beta}\right) + \tan^{-1}\left(\frac{\beta}{a_0}\right)$
110	$\frac{s + a_0}{(s + \alpha)(s + \beta)(s^2 + \gamma^2)}$	$\frac{(a_0 - \alpha)e^{-\alpha t}}{(\beta - \alpha)(\alpha^2 + \gamma^2)} + \frac{(a_0 - \beta)e^{-\beta t}}{(\alpha - \beta)(\gamma^2 + \beta^2)} + \sqrt{\frac{a_0^2 + \gamma^2}{\gamma^2(\alpha^2 + \gamma^2) + \beta^2}} \cdot \sin(\gamma t + \phi)$ $\phi = \tan^{-1}\left(\frac{\beta}{\gamma}\right) - \tan^{-1}\left(\frac{a_0}{\gamma}\right) - \tan^{-1}\left(\frac{\gamma}{\alpha}\right)$
111	$\frac{s + a_0}{s^2(s + \alpha)(s + \beta)(s^2 + \gamma^2)}$	$\frac{a_0}{\alpha\beta\gamma^2} + \frac{(\alpha - a_0)e^{-\alpha t}}{\alpha(\beta - \alpha)(\alpha^2 + \gamma^2)} + \frac{(\beta - a_0)e^{-\beta t}}{\beta(\alpha - \beta)(\alpha^2 + \gamma^2)} + \frac{1}{\gamma^2}\sqrt{\frac{\gamma^2 + a_0^2}{\gamma^2(\alpha + \beta)^2 + (\alpha\beta - \gamma^2)}} \cdot \sin(\gamma t + \phi)$ $\phi = \tan^{-1}\frac{\gamma}{\alpha} + \tan^{-1}\frac{\gamma}{\beta} + \tan^{-1}\frac{a_0}{\gamma}$
112	$\frac{s + a_0}{s^2(s + \alpha)(s + \beta)(s^2 + \gamma^2)}$	$\frac{1}{\alpha\beta\gamma^2} + \frac{a_0\left(t - \frac{1}{\beta} - \frac{1}{\alpha}\right)}{\alpha\beta\gamma^2} + \frac{(a_0 - \alpha)e^{-\alpha t}}{\alpha^2(\beta - \alpha)(\alpha^2 + \gamma^2)} + \frac{(a_0 - \beta)e^{-\beta t}}{\beta^2(\alpha - \beta)(\alpha^2 + \gamma^2)} + \frac{1}{\gamma^2}\sqrt{\frac{a_0^2 + \gamma^2}{\gamma^2(\alpha + \beta)^2 + (\alpha\beta - \gamma^2)^2}} \cdot \cos(\gamma t + \phi), \quad \phi = \tan^{-1}\frac{\beta}{\gamma} - \tan^{-1}\frac{\gamma}{\alpha} + \tan^{-1}\frac{\gamma}{a_0}$
113	$\frac{s + a_0}{(s^2 + \alpha^2)(s^2 + \beta^2)}$	$\frac{1}{\alpha^2 - \beta^2}\left[\sqrt{\left(1 + \frac{a_0^2}{\beta^2}\right)} \cdot \cos(\beta t - \phi_1) - \sqrt{\left(1 + \frac{a_0^2}{\alpha^2}\right)} \cdot \cos(\alpha t - \phi_2)\right]$ $\phi_1 = \tan^{-1}\frac{a_0}{\beta}, \quad \phi_2 = \tan^{-1}\frac{a_0}{\alpha}$

114	$\frac{s + a_0}{(s + \alpha)^2 + \beta^2}$	$\sqrt{\left(1 + \frac{(a_0 - \alpha)^2}{\beta^2}\right)} \cdot \varepsilon^{-\alpha t} \cdot \sin(\beta t + \phi), \quad \phi = \tan^{-1}\left(\frac{\beta}{a_0 - \alpha}\right)$
115	$\frac{s + a_0}{s[(s + \alpha)^2 + \beta^2]}$	$\frac{a_0}{\alpha^2 + \beta^2} - \sqrt{\left(\frac{\beta^2 + (a_0 - \alpha)^2}{\beta^2(\alpha^2 + \beta^2)}\right)} \cdot \varepsilon^{-\alpha t} \cdot \sin(\beta t + \phi), \quad \phi = \tan^{-1}\frac{\beta}{\alpha} + \tan^{-1}\frac{\beta}{a_0 - \alpha}$
116	$\frac{s + a_0}{s^2[(s + \alpha)^2 + \beta^2]}$	$\frac{1 + a_0 t}{\alpha^2 + \beta^2} - \frac{2\alpha a_0}{(\alpha^2 + \beta^2)^2} + \frac{\sqrt{\{\beta^2 + (a_0 - \alpha)^2\}}}{\beta(\alpha^2 + \beta^2)} \cdot \varepsilon^{-\alpha t} \cdot \sin(\beta t + \phi), \quad \phi = \tan^{-1}\frac{\beta}{a_0 - \alpha} + 2 \tan^{-1}\frac{\beta}{\alpha}$
117	$\frac{s + a_0}{(s + \nu)[(s + \alpha)^2 + \beta^2]}$	$\frac{(a_0 - \nu)\varepsilon^{-\nu t}}{(\nu - \alpha)^2 + \beta^2} + \frac{1}{\beta} \sqrt{\left(\frac{\beta^2 + (a_0 - \alpha)^2}{\beta^2 + (\nu - \alpha)^2}\right)} \cdot \varepsilon^{-\alpha t} \cdot \sin(\beta t + \phi), \quad \phi = \tan^{-1}\left(\frac{\beta}{a_0 - \alpha}\right) - \tan^{-1}\left(\frac{\beta}{\nu - \alpha}\right)$
118	$\frac{s + a_0}{s(s + \nu)[(s + \alpha)^2 + \beta^2]}$	$\frac{a_0}{\nu(\alpha^2 + \beta^2)} + \frac{(\nu - a_0)\varepsilon^{-\nu t}}{\nu[\beta^2 + (\alpha - \nu)^2]} + \frac{1}{\beta} \sqrt{\left(\frac{\beta^2 + (a_0 - \alpha)^2}{\beta^2 + (\alpha - \nu)^2}\right)} \cdot \varepsilon^{-\alpha t} \cdot \sin(\beta t + \phi)$ $\phi = \tan^{-1}\frac{\beta}{\alpha} + \tan^{-1}\frac{\beta}{a_0 - \alpha} + \tan^{-1}\frac{\nu}{\alpha - \nu}$
119	$\frac{s + a_0}{s^2(s + \nu)[(s + \alpha)^2 + \beta^2]}$	$\frac{a_0}{\nu(\alpha^2 + \beta^2)} \left[t + \frac{1}{a_0} - \frac{1}{\nu} - \frac{2\alpha}{(\alpha^2 + \beta^2)} \right] + \frac{(a_0 - \nu)\varepsilon^{-\nu t}}{\nu^2[\beta^2 + (\nu - \alpha)^2]}$ $+ \frac{\varepsilon^{-\alpha t}}{\beta(\alpha^2 + \beta^2)} \sqrt{\left(\frac{\beta^2 + (a_0 - \alpha)^2}{\beta^2 + (\nu - \alpha)^2}\right)} \cdot \sin(\beta t + \phi),$ $\phi = \tan^{-1}\frac{\beta}{a_0 - \alpha} - \tan^{-1}\frac{\beta}{\nu - \alpha} + 2 \tan^{-1}\frac{\beta}{\alpha}$
120	$\frac{s + a_0}{(s + \delta)(s + \nu)[(s + \alpha)^2 + \beta^2]}$	$\frac{(\nu - a_0)\varepsilon^{-\nu t}}{(\nu - \delta)[(\alpha - \nu)^2 + \beta^2]} + \frac{(\delta - a_0)\varepsilon^{-\delta t}}{(\delta - \nu)[(\alpha - \nu)^2 + \beta^2]}$ $+ \sqrt{\left(\frac{\beta^2 + (a_0 - \alpha)^2}{(\alpha - \nu)^2[\beta^2 + (\alpha - \delta)^2]}\right)} \cdot \varepsilon^{-\alpha t} \cdot \cos(\beta t + \phi),$ $\phi = \tan^{-1}\frac{\beta}{a_0 - \alpha} - \tan^{-1}\frac{\alpha - \nu}{\beta} + \tan^{-1}\frac{\beta}{\alpha - \delta}$

No.	$F(e)$	$f(t)$
121	$\frac{e + \alpha_0}{(e + \alpha)^2}$	$[1 + (\alpha_0 - \alpha)]e^{-\alpha t}$
122	$\frac{e + \alpha_0}{e^2(e + \alpha)^2}$	$\frac{\alpha_0}{\alpha} + \left[\left(1 - \frac{\alpha_0}{\alpha}\right)t - \frac{\alpha_0}{\alpha^2} \right] e^{-\alpha t}$
123	$\frac{e + \alpha_0}{e^2(e + \alpha)^2}$	$\frac{1}{\alpha^2} \left(1 + \alpha e^t - \frac{2\alpha_0}{\alpha} \right) - \frac{1}{\alpha^2} \left(1 - \frac{2\alpha_0}{\alpha} + [\alpha - \alpha_0]t \right) e^{-\alpha t}$
125	$\frac{e + \alpha_0}{(e + \beta)(e + \alpha)^2}$	$\frac{(\alpha_0 - \beta)e^{-\beta t}}{(\beta - \alpha)^2} + \left[\frac{\alpha_0 - \alpha}{\beta - \alpha} + \frac{\beta - \alpha_0}{(\beta - \alpha)^2} \right] e^{-\alpha t}$
126	$\frac{e + \alpha_0}{e(e + \beta)(e + \alpha)^2}$	$\frac{\alpha_0}{\alpha^2\beta} + \frac{\beta - \alpha_0}{\beta(\alpha - \beta)^2} + \left[\frac{(\alpha_0 - \alpha)t}{\alpha(\alpha - \beta)} - \frac{\alpha^2 - \alpha_0(2\alpha - \beta)}{\alpha^2(\alpha - \beta)^2} \right] e^{-\alpha t}$
127	$\frac{e + \alpha_0}{e^2(e + \beta)(e + \alpha)^2}$	$\frac{\alpha_0}{\alpha^2\beta} \left(\frac{1}{\alpha} - \frac{1}{\beta} - \frac{2}{\alpha} + t \right) - \frac{(\beta - \alpha_0)e^{-\beta t}}{\beta^2(\alpha - \beta)^2} - \left[\frac{\alpha - \alpha_0}{\alpha^2(\beta - \alpha)} + \frac{2\alpha_0 - \alpha(2\alpha - \beta) - \alpha\alpha_0}{\alpha^2(\alpha - \beta)^2} \right] e^{-\alpha t}$
128	$\frac{e + \alpha_0}{(e + \beta)(e + \gamma)(e + \alpha)^2}$	$\frac{(\alpha_0 - \beta)e^{-\beta t}}{(\gamma - \beta)(\alpha - \beta)^2} + \frac{(\alpha_0 - \gamma)e^{-\gamma t}}{(\beta - \gamma)(\alpha - \gamma)^2} + \left[\frac{\alpha_0 - \alpha}{(\alpha - \gamma)(\alpha - \beta)^2} + \frac{\alpha_0(2\alpha - \beta - \gamma) - \alpha^2 + \beta\gamma}{(\alpha - \beta)^2(\alpha - \gamma)^2} \right] e^{-\alpha t}$
130	$\frac{e + \alpha_0}{e(e + \beta)(e + \gamma)(e + \alpha)^2}$	$\frac{\alpha_0}{\alpha^2\beta\gamma} - \frac{(\alpha_0 - \gamma)e^{-\gamma t}}{\gamma(\beta - \gamma)(\alpha - \gamma)^2} - \frac{(\alpha_0 - \beta)e^{-\beta t}}{\beta(\gamma - \beta)(\alpha - \beta)^2} + \left[\frac{(\alpha - \alpha_0)t}{\alpha^2(\alpha - \gamma)(\alpha - \beta)} - \frac{\alpha_0(\alpha - \gamma)(\alpha - \beta) + \alpha(\alpha_0 - \alpha)(2\alpha - \beta - \gamma)}{\alpha^2(\alpha - \gamma)^2(\alpha - \beta)^2} \right] e^{-\alpha t}$
131	$\frac{e + \alpha_0}{(e^2 + \beta^2)(e + \alpha)^2}$	$\left[\frac{2\alpha_0\alpha - \alpha^3 + \beta^2}{(\alpha^2 + \beta^2)^2} - \frac{(\alpha - \alpha_0)}{\alpha^2 + \beta^2} \right] e^{-\alpha t} + \frac{\sqrt{(\beta^2 + \alpha_0^2)}}{\beta(\alpha^2 + \beta^2)} \cdot \sin(\beta t + \phi), \quad \phi = \tan^{-1} \frac{\beta}{\alpha_0} - \tan^{-1} \frac{\beta}{\alpha}$

132	$\frac{e + \alpha_0}{e^2(e^2 + \beta^2)(e + \alpha)^2}$	$\frac{\alpha_0}{\alpha^2 \beta^2} + \left[\frac{2\alpha^2(\alpha - \alpha_0) - \alpha_0(\alpha^2 + \beta^2)}{\alpha^2(\alpha^2 + \beta^2)^2} + \frac{(\alpha - \alpha_0)^2}{\alpha(\alpha^2 + \beta^2)^2} \right] e^{-\alpha t} - \frac{\cos(\beta t + \phi)}{\beta^2(\alpha^2 + \beta^2)} \cdot \sqrt{(\alpha_0^2 + \beta^2)},$ $\phi = \tan^{-1} \frac{\beta}{\alpha_0} - 2 \tan^{-1} \frac{\beta}{\alpha}$
133	$\frac{e + \alpha_0}{e^2(e^2 + \beta^2)(e + \alpha)^2}$	$\frac{1 + \frac{\alpha_0 e}{\alpha^2 \beta^2} - \frac{2\alpha_0}{\alpha^2 \beta^2}}{\alpha^2 \beta^2} + \left[\frac{(\alpha^2 + \beta^2)(2\alpha_0 - \alpha) + 2\alpha^2(\alpha_0 - \alpha)}{\alpha^2(\alpha^2 + \beta^2)^2} + \frac{(\alpha_0 - \alpha)^2}{\alpha^2(\alpha^2 + \beta^2)} \right] e^{-\alpha t}$ $+ \frac{\sqrt{(\alpha_0^2 + \beta^2)} \sin(\beta t + \phi)}{\beta^2(\alpha^2 + \beta^2)}, \quad \phi = \tan^{-1} \frac{\beta}{\alpha_0} + 2 \tan^{-1} \frac{\alpha}{\beta}$
134	$\frac{e + \alpha_0}{(e + \nu)(e^2 + \beta^2)(e + \alpha)^2}$	$\frac{(\alpha_0 - \nu)e^{-\nu t}}{(\beta^2 + \nu^2)(\alpha - \nu)^2} + \left[\frac{\alpha^2(\alpha - \alpha_0) + \beta^2(\nu - \alpha_0) + \alpha(\nu - \alpha)(2\alpha_0 - \alpha)}{(\alpha^2 + \beta^2)^2(\nu - \alpha)^2} + \frac{(\alpha_0 - \alpha)^2}{(\nu - \alpha)(\alpha^2 + \beta^2)} \right] e^{-\alpha t}$ $+ \sqrt{\frac{(\alpha_0^2 + \beta^2)}{\beta^2 + \nu^2}} \cdot \frac{\sin(\beta t + \phi)}{\beta(\alpha^2 + \beta^2)}, \quad \phi = \tan^{-1} \frac{\nu}{\beta} - \tan^{-1} \frac{\alpha_0}{\beta} - 2 \tan^{-1} \frac{\beta}{\alpha}$
135	$\frac{e + \alpha_0}{(e + \nu)^2(e + \alpha)^2 + \beta^2}$	$\frac{(\alpha_0 - \nu)^2}{\beta^2 + (\alpha - \nu)^2} + \frac{[\alpha^2 + \beta^2 + 2\alpha_0(\nu - \alpha) - \nu^2]e^{-\nu t}}{[\beta^2 + (\alpha - \nu)^2]} + \frac{\sqrt{\beta^2 + (\alpha_0 - \alpha)^2}}{\beta[\beta^2 + (\alpha - \nu)^2]} \cdot e^{-\alpha t} \cdot \sin(\beta t + \phi),$ $\phi = \tan^{-1} \left(\frac{\beta}{\alpha_0 - \alpha} \right) - 2 \tan^{-1} \left(\frac{\beta}{\nu - \alpha} \right)$
136	$\frac{e + \alpha_0}{e(e + \nu)^2(e + \alpha)^2 + \beta^2}$	$\frac{\alpha_0}{\nu^2(\alpha^2 + \beta^2)} + \frac{e^{-\alpha t}}{\beta[(\nu - \alpha)^2 + \beta^2]} \sqrt{\frac{(\alpha - \alpha_0)^2 + \beta^2}{\alpha^2 + \beta^2}} \cdot \sin(\beta t + \phi) + \dots$ $+ \dots + \left[\frac{2\nu(\alpha_0 - \nu)(\alpha - \nu) - \alpha_0^2(\nu - \alpha)^2 + \beta^2}{\nu^2[(\nu - \alpha)^2 + \beta^2]} + \frac{(\nu - \alpha_0)^2}{\nu[(\nu - \alpha)^2 + \beta^2]} \right] e^{-\nu t}$ $\phi = \tan^{-1} \frac{\beta}{\alpha} - 2 \tan^{-1} \frac{\beta}{\nu - \alpha} - \tan^{-1} \frac{\beta}{\alpha - \alpha_0}$

No.	$F(s)$	$f(t)$
137	$\frac{s + a_0}{s^2(s + v)^2(s + \alpha)^2 + \beta^2}$	$\frac{a_0 t}{v^2(\alpha^2 + \beta^2)} + \frac{(v - 2a_0)(\alpha^2 + \beta^2) - 2a_0\alpha v}{v^2(\alpha^2 + \beta^2)^2} + \frac{\sqrt{[(\alpha - a_0)^2 + \beta^2]}e^{-\alpha t}}{\beta(\alpha^2 + \beta^2)[(\alpha - v)^2 + \beta^2]} \sin(\beta t + \phi) + \dots$ $\dots + \left[\frac{(2a_0 - v)[(v - \alpha)^2 + \beta^2] + 2v(a_0 - v)(\alpha - v)}{v^2[(v - \alpha)^2 + \beta^2]} + \frac{(a_0 - v)t}{v^2[(v - \alpha)^2 + \beta^2]} \right] e^{-vt}$ $\phi = \tan^{-1} \frac{\beta}{\alpha} - \tan^{-1} \frac{\alpha}{\beta} + \tan^{-1} \left(\frac{v - \alpha}{\beta} - \tan^{-1} \left(\frac{\beta}{v - \alpha} \right) + \tan^{-1} \left(\frac{\beta}{a_0 - \alpha} \right) \right)$
138	$\frac{s + a_0}{(s + \delta)(s + v)^2(s + \alpha)^2 + \beta^2}$	$\frac{(a_0 - \delta)e^{-\delta t}}{(\delta - v)^2[(\delta - \alpha)^2 + \beta^2]} + \frac{e^{-\alpha t} \sin(\beta t + \phi)}{\beta[(\alpha - v)^2 + \beta^2]} \sqrt{\frac{(\alpha - a_0)^2 + \beta^2}{(\alpha - \delta)^2 + \beta^2}} + \dots$ $\dots + \left[\frac{(\delta - a_0)[(v - \alpha)^2 + \beta^2] - 2(\alpha - v)(\delta - v)(a_0 - v)}{(v - \delta)^2[\beta^2 + (v - \alpha)^2]} + \frac{(a_0 - v)t}{(\delta - v)[(v - \alpha)^2 + \beta^2]} \right] e^{-vt}$ $\phi = \tan^{-1} \left(\frac{\beta}{a_0 - \alpha} \right) - 2 \tan^{-1} \left(\frac{\beta}{v - \alpha} \right) - \tan^{-1} \left(\frac{\beta}{\delta - \alpha} \right)$
139	$\frac{s + a_0}{(s + \alpha)^2(s + \beta)^2}$	$\left[\frac{a_0 - \beta}{(\alpha - \beta)^2} + \frac{\alpha + \beta - 2a_0}{(\alpha - \beta)^2} \right] e^{-\beta t} + \left[\frac{a_0 - \alpha}{(\beta - \alpha)^2} + \frac{\alpha + \beta - 2a_0}{(\beta - \alpha)^2} \right] e^{-\alpha t}$
140	$\frac{s + a_0}{s(s + \alpha)^2(s + \beta)^2}$	$\frac{a_0}{\alpha^2\beta^2} + \left[\frac{(\beta - a_0)t}{\beta(\alpha - \beta)^2} + \frac{3a_0\beta - a_0\alpha - 2\beta^2}{\beta^2(\alpha - \beta)^2} \right] e^{-\beta t} + \left[\frac{(\alpha - a_0)t}{\alpha(\beta - \alpha)^2} + \frac{3a_0\alpha - a_0\beta - 2\alpha^2}{\alpha^2(\beta - \alpha)^2} \right] e^{-\alpha t}$
141	$\frac{s + a_0}{s^2(s + \alpha)^2(s + \beta)^2}$	$\left[\frac{1 + a_0 t}{\alpha^2\beta^2} - \frac{2a_0(\alpha + \beta)}{\alpha^2\beta^2} \right] + \left[\frac{(a_0 - \alpha)t}{\alpha^2(\beta - \alpha)^2} + \frac{2a_0(\beta - 2\alpha) + \alpha(3\alpha - \beta)}{\alpha^2(\beta - \alpha)^2} \right] e^{-\alpha t}$ $+ \left[\frac{(a_0 - \beta)t}{\beta^2(\alpha - \beta)^2} + \frac{2a_0(\alpha - 2\beta) + \beta(3\beta - \alpha)}{\beta^2(\alpha - \beta)^2} \right] e^{-\beta t}$

142	$\frac{s + \alpha_0}{(s + \nu)(s + \alpha)^2(s + \beta)^2}$	$\frac{(\alpha_0 - \nu)e^{-\nu t}}{(\nu - \alpha)^2(\nu - \beta)^2} + \left[\frac{(\alpha - 2\alpha_0)(\nu - \alpha) + (\nu\beta - \alpha^2) - \alpha_0(\beta - \alpha)}{(\alpha - \nu)^2(\alpha - \beta)^2} + \frac{(\alpha_0 - \alpha)t}{(\nu - \alpha)(\alpha - \beta)^2} \right] e^{-\alpha t} + \dots$ $+ \left[\frac{(\beta - 2\alpha_0)(\nu - \beta) + (\nu\alpha - \beta^2) - \alpha_0(\alpha - \beta)}{(\beta - \nu)^2(\alpha - \beta)^2} + \frac{(\alpha_0 - \beta)t}{(\nu - \beta)(\alpha - \beta)^2} \right] e^{-\beta t}$
143	$\frac{s + \alpha_0}{(s^2 + \nu^2)(s + \alpha)^2(s + \beta)^2}$	$\left[\frac{(\alpha_0 - \alpha)t}{(\alpha - \beta)^2(\alpha^2 + \nu^2)} + \frac{2\alpha(\alpha_0 - \alpha)}{(\beta - \alpha)^2(\alpha^2 + \nu^2)} + \frac{\alpha + \beta - 2\alpha_0}{(\beta - \alpha)^2(\alpha^2 + \nu^2)} \right] e^{-\alpha t} + \frac{\sqrt{(\alpha_0^2 + \nu^2)} \sin(\nu t + \phi)}{\nu(\beta^2 + \nu^2)(\alpha^2 + \nu^2)}$ $+ \dots + \left[\frac{(\alpha_0 - \beta)t}{(\alpha - \beta)^2(\beta^2 + \nu^2)} + \frac{2\beta(\alpha_0 - \beta)}{(\alpha - \beta)^2(\beta^2 + \nu^2)} + \frac{\alpha + \beta - 2\alpha_0}{(\alpha - \beta)^2(\beta^2 + \nu^2)} \right] e^{-\beta t}$ $\phi = 2 \tan^{-1} \frac{\alpha}{\nu} + 2 \tan^{-1} \frac{\beta}{\nu} + \tan^{-1} \frac{\nu}{\alpha_0}$
144	$\frac{s + \alpha_0}{[(s + \alpha)^2 + \beta^2]^2}$	$\left[(\alpha_0 - \alpha + \beta^2 t) \sin \beta t + (\alpha - \alpha_0) \beta t \cos \beta t \right] \frac{e^{-\alpha t}}{2\beta^2}$
145	$\frac{s + \alpha_0}{(s^2 + \alpha^2)^2}$	$\frac{(\alpha_0 + \alpha^2 t) \sin \alpha t - \alpha_0 \alpha t \cos \alpha t}{2\alpha^3}$
146	$\frac{s + \alpha_0}{s(\alpha^2 + \alpha^2)^2}$	$\frac{\alpha_0}{\alpha^2} + \frac{(1 - \alpha_0 t) \sin \alpha t}{2\alpha^2} - \frac{(2\alpha_0 + \alpha^2 t) \cos \alpha t}{2\alpha^4}$
147	$\frac{s + \alpha_0}{s^2(s^2 + \alpha^2)^2}$	$\frac{1 + \alpha_0 t}{\alpha^4} - \frac{\sqrt{(4\alpha^2 + 9\alpha_0^2)} \sin(\alpha t + \phi_1)}{2\alpha^5} + \frac{(\sqrt{\alpha_0^2 + \alpha^2})^2 \cos(\alpha t + \phi_2)}{2\alpha^4}$ $\phi_1 = \tan^{-1} \frac{2\alpha}{3\alpha_0}, \quad \phi_2 = \tan^{-1} \frac{\alpha^2}{\alpha_0}$
148	$\frac{s + \alpha_0}{(s + \beta)(s^2 + \alpha^2)^2}$	$\frac{(\alpha_0 - \beta)e^{-\beta t}}{(\alpha^2 + \beta^2)^2} - \frac{t}{2\alpha^2} \sqrt{\frac{(\alpha_0^2 + \alpha^2)}{(\alpha^2 + \beta^2)}} \sin(\alpha t + \phi_1) + \frac{\sqrt{[(\alpha^2 - \beta\alpha_0)^2 + 4\beta^2\alpha_0^2]} \cos(\alpha t + \phi_1)}{2\alpha^2(\alpha^2 + \beta^2)}$ $\phi_1 = \tan^{-1} \frac{\alpha}{\alpha_0} + \tan^{-1} \frac{\beta}{\alpha}, \quad \phi_2 = \tan^{-1} \left(\frac{\alpha^2 - \beta\alpha_0}{2\alpha\alpha_0} \right) - 2 \tan^{-1} \frac{\alpha}{\beta}$

No.	$F(s)$	$f(t)$
149	$\frac{s + a_0}{s(s + \beta)(s^2 + \alpha^2)^2}$	$\frac{a_0}{\beta\alpha^4} + \frac{(\beta - a_0)e^{-\beta t}}{\beta(\alpha^2 + \beta^2)^2} + \frac{t}{2\alpha^2} \sqrt{\frac{\alpha^2 + a_0^2}{\alpha^2 + \beta^2}} \cos(\alpha t + \phi_1)$ $- \frac{\sqrt{(\alpha^2(3a_0 + \beta)^2 + 4(\beta a_0 - \alpha^2)^2)} \cos(\alpha t + \phi_2)}{2\alpha^4(\alpha^2 + \beta^2)}$ $\phi_1 = \tan^{-1} \frac{\alpha}{a_0} + \tan^{-1} \frac{\beta}{\alpha}, \quad \phi_2 = \tan^{-1} \frac{\alpha(3a_0 + \beta)}{2(\beta a_0 - \alpha^2)} - 2 \tan^{-1} \frac{\alpha}{\beta}$
150	$\frac{s + a_0}{s^2(s + \beta)(s^2 + \alpha^2)^2}$	$\frac{1 - a_0/\beta + a_0 t}{\alpha^4 \beta} + \frac{(a_0 - \beta)e^{-\beta t}}{\beta^2(\alpha^2 + \beta^2)^2} + \frac{t}{2\alpha^4} \sqrt{\frac{\alpha^2 + a_0^2}{\alpha^2 + \beta^2}} \sin(\alpha t + \phi_1) + \dots$ $\dots + \frac{\sqrt{4\alpha^2(2a_0 + \beta) + 9(a_0\beta - \alpha^2)^2}}{4\alpha^4(\alpha^2 + \beta^2)} \sin(\alpha t + \phi_2),$ $\phi_1 = \tan^{-1} \frac{\alpha}{a_0} + \tan^{-1} \frac{\beta}{\alpha}, \quad \phi_2 = \tan^{-1} \left[\frac{2\alpha(2a_0 + \beta)}{3(a_0\beta - \alpha^2)} \right] - 2 \tan^{-1} \frac{\alpha}{\beta}$
151	$\frac{s + a_0}{(s + \alpha)^2}$	$\left[1 + \left(\frac{a_0 - \alpha}{2} \right) t \right] e^{-\alpha t}$
152	$\frac{s + a_0}{s(s + \alpha)^2}$	$\frac{a_0}{\alpha^2} + \left[\frac{(\alpha - a_0)t^2}{2} - \frac{2a_0}{\alpha^2} - \frac{a_0 t}{\alpha} \right] e^{-\alpha t}$
153	$\frac{s + a_0}{s^2(s + \alpha)^2}$	$\frac{1 + a_0 t}{\alpha^2} - \frac{3a_0}{\alpha^4} + \left[\frac{1}{\alpha^2} + \frac{(a_0 - \alpha)t^2}{2\alpha^2} + \frac{(2a_0 - \alpha)t}{\alpha^3} \right] e^{-\alpha t}$
154	$\frac{s + a_0}{(s + \beta)(s + \alpha)^2}$	$\frac{(a_0 - \beta)e^{-\beta t}}{(\alpha - \beta)^2} + \left[\frac{a_0 - \beta}{(\beta - \alpha)^2} + \frac{(\beta - a_0)t}{(\alpha - \beta)^2} + \frac{(a_0 - \alpha)t^2}{2(\beta - \alpha)} \right] e^{-\alpha t}$
155	$\frac{s^2 + a_1 s + a_0}{s^2(s + \alpha)}$	$\frac{a_1 \alpha - a_0 + a_0 \alpha t}{\alpha^2} + \frac{(a^2 - \alpha a_1 + a_0)e^{-\alpha t}}{\alpha^2}$

156	$\frac{s^2 + a_1 s + a_0}{s(s + \alpha)(s + \beta)}$	$\frac{a_0}{\alpha\beta} + \frac{(a_1\alpha - a_0 - \alpha^2)e^{-\alpha t}}{\alpha(\beta - \alpha)} + \frac{(\beta^2 - a_1\beta + a_0)e^{-\beta t}}{\beta(\beta - \alpha)}$
157	$\frac{s^2 + a_1 s + a_0}{s^2(s + \alpha)(s + \beta)}$	$\frac{a_1 + a_0\beta}{\alpha\beta} - \frac{a_0(\alpha + \beta)}{\alpha^2\beta^2} + \frac{1}{\beta - \alpha} \left[\left(1 + \frac{a_0}{\alpha^2} - \frac{a_1}{\alpha} \right) e^{-\alpha t} - \left(1 + \frac{a_0}{\beta^2} - \frac{a_1}{\beta} \right) e^{-\beta t} \right]$
158	$\frac{s^2 + a_1 s + a_0}{(s + \alpha)(s + \beta)(s + \gamma)}$	$\frac{(\alpha^2 - a_1\alpha + a_0)e^{-\alpha t}}{(\gamma - \alpha)(\beta - \alpha)} + \frac{(\gamma^2 - a_1\gamma + a_0)e^{-\gamma t}}{(\alpha - \gamma)(\beta - \gamma)} + \frac{(\beta^2 - a_1\beta + a_0)e^{-\beta t}}{(\alpha - \beta)(\gamma - \beta)}$
159	$\frac{s^2 + a_1 s + a_0}{s(s + \alpha)(s + \beta)(s + \gamma)}$	$\frac{a_0}{\alpha\beta\gamma} + \frac{(\alpha^2 - a_1\alpha + a_0)e^{-\alpha t}}{\alpha(\alpha - \beta)(\gamma - \alpha)} + \frac{(\beta^2 - a_1\beta + a_0)e^{-\beta t}}{\beta(\alpha - \beta)(\beta - \gamma)} + \frac{(\gamma^2 - a_1\gamma + a_0)e^{-\gamma t}}{\gamma(\alpha - \gamma)(\gamma - \beta)}$
160	$\frac{s^2 + a_1 s + a_0}{s^2(s + \alpha)(s + \beta)(s + \gamma)}$	$\frac{a_1 + a_0\beta}{\alpha\beta\gamma} - \frac{a_0(\alpha\beta + \beta\gamma + \alpha\gamma)}{\alpha^2\beta^2\gamma^2} + \frac{(\alpha^2 - a_1\alpha + a_0)e^{-\alpha t}}{\alpha^2(\alpha - \beta)(\alpha - \gamma)} + \frac{(\beta^2 - a_1\beta + a_0)e^{-\beta t}}{\beta^2(\beta - \alpha)(\beta - \gamma)} + \frac{(\gamma^2 - a_1\gamma + a_0)e^{-\gamma t}}{\gamma^2(\gamma - \alpha)(\gamma - \beta)}$
161	$\frac{s^2 + a_1 s + a_0}{s(s^2 + \alpha^2)}$	$\frac{a_0}{\alpha^2} + \sqrt{\left(\frac{a_1}{\alpha}\right)^2 + \left(\frac{a_0}{\alpha^2} - 1\right)^2} \cos(\alpha t + \phi), \quad \phi = -\tan^{-1} \left(\frac{a_1\alpha}{\alpha^2 - a_0} \right)$
162	$\frac{s^2 + a_1 s + a_0}{s^2(s^2 + \alpha^2)}$	$\frac{a_1 + a_0\beta}{\alpha^2} - \frac{\sin(\alpha t + \phi)}{\alpha^2} \sqrt{\alpha^2 + \left(\alpha - \frac{a_0}{\alpha}\right)^2}, \quad \phi = \tan^{-1} \left(\frac{a_1\alpha}{a_0 - \alpha^2} \right)$
163	$\frac{s^2 + a_1 s + a_0}{(s + \beta)(s^2 + \alpha^2)}$	$\frac{(\beta^2 - a_1\beta + a_0)e^{-\beta t}}{\alpha^2 + \beta^2} + \frac{\sin(\alpha t + \phi)}{\alpha} \sqrt{\left(\frac{\alpha^2 - a_0}{\alpha}\right)^2 + \alpha^2}, \quad \phi = \tan^{-1} \left(\frac{\beta}{\alpha} \right) - \tan^{-1} \left(\frac{a_0 - \alpha^2}{a_1\alpha} \right)$
164	$\frac{s^2 + a_1 s + a_0}{s(s + \beta)(s^2 + \alpha^2)}$	$\frac{a_0}{\alpha^2\beta} - \frac{(\beta^2 - a_1\beta + a_0)e^{-\beta t}}{\beta(\alpha^2 + \beta^2)} - \frac{\alpha^2}{\cos(\alpha t + \phi)} \sqrt{\left(\frac{\alpha^2 - a_0}{\alpha}\right)^2 + \alpha^2}, \quad \phi = \tan^{-1} \left(\frac{\beta}{\alpha} \right) - \tan^{-1} \left(\frac{a_0 - \alpha^2}{a_1\alpha} \right)$

No.	$F(\theta)$	$f(t)$
165	$\frac{\theta^2 + \alpha_1\theta + \alpha_0}{\theta^2(\theta + \beta)(\theta^2 + \alpha^2)}$	$\frac{1}{\alpha^2\beta} \left[\alpha_1 - \frac{\alpha_0}{\beta} + \alpha_0\theta \right] + \frac{(\beta^2 - \alpha_1\beta + \alpha_0)e^{-\beta t}}{\beta^2(\alpha^2 + \beta^2)} + \frac{\cos(\alpha t + \phi)}{\alpha^2} \sqrt{\left(\frac{(\alpha^2 - \alpha_0)^2 + \alpha_1^2\alpha^2}{\alpha^2 + \beta^2} \right)}$ $\phi = \tan^{-1} \left(\frac{\beta}{\alpha} \right) + \tan^{-1} \left(\frac{\alpha_1\alpha}{\alpha_0 - \alpha^2} \right)$
166	$\frac{\theta^2 + \alpha_1\theta + \alpha_0}{(\theta + \beta)(\theta + \nu)(\theta^2 + \alpha^2)}$	$\frac{(\beta^2 - \alpha_1\beta + \alpha_0)e^{-\beta t}}{(\nu - \beta)(\alpha^2 + \beta^2)} + \frac{(\nu^2 - \alpha_1\nu + \alpha_0)e^{-\nu t}}{(\beta - \nu)(\alpha^2 + \nu^2)} + \frac{\sin(\alpha t + \phi)}{\alpha} \sqrt{\left(\frac{(\alpha^2 - \alpha_0)^2 + \alpha_1^2\alpha^2}{(\alpha^2 + \beta^2)(\alpha^2 + \nu^2)} \right)}$ $\phi = \tan^{-1} \left(\frac{\alpha_1\alpha}{\alpha_0 - \alpha^2} \right) - \tan^{-1} \left(\frac{\alpha}{\nu} \right) - \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
167	$\frac{\theta^2 + \alpha_1\theta + \alpha_0}{\theta(\theta + \beta)(\theta + \nu)(\theta^2 + \alpha^2)}$	$\frac{\alpha_0}{\alpha^2\beta\nu} + \frac{\left(\beta - \alpha_1 + \frac{\alpha_0}{\beta} \right) e^{-\beta t}}{(\beta - \nu)(\alpha^2 + \beta^2)} + \frac{\left(\nu - \alpha_1 + \frac{\alpha_0}{\nu} \right) e^{-\nu t}}{(\nu - \beta)(\alpha^2 + \nu^2)} + \frac{\sin(\alpha t - \phi)}{\alpha^2} \sqrt{\left(\frac{(\alpha^2 - \alpha_0)^2 + \alpha_1^2\alpha^2}{(\alpha^2 - \beta^2)^2} \right)}$ $\phi = \tan^{-1} \left(\frac{\alpha}{\beta} \right) + \tan^{-1} \left(\frac{\alpha}{\nu} \right) + \tan^{-1} \left(\frac{\alpha_0 - \alpha^2}{\alpha_1\alpha} \right)$
168	$\frac{\theta^2 + \alpha_1\theta + \alpha_0}{\theta^2(\theta + \beta)(\theta + \nu)(\theta^2 + \alpha^2)}$	$\frac{\alpha_1 + \alpha_0 \left(t - \frac{1}{\nu} - \frac{1}{\nu} \right)}{\alpha^2\beta\nu} + \frac{(\beta^2 - \alpha_1\beta + \alpha_0)e^{-\beta t}}{\beta^2(\nu - \beta)(\alpha^2 + \beta^2)} + \frac{(\nu^2 - \alpha_1\nu + \alpha_0)e^{-\nu t}}{\nu^2(\beta - \nu)(\alpha^2 + \nu^2)} + \frac{\cos(\alpha t + \phi)}{\alpha^2} \sqrt{\left(\frac{(\alpha^2 - \alpha_0)^2 + \alpha_1^2\alpha^2}{(\alpha^2 - \beta^2)^2} \right)}$ $\phi = \tan^{-1} \left(\frac{\nu}{\alpha} \right) + \tan^{-1} \left(\frac{\alpha_1\alpha}{\alpha_0 - \alpha^2} \right) - \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
169	$\frac{\theta^2 + \alpha_1\theta + \alpha_0}{(\theta^2 + \alpha^2)(\theta^2 + \beta^2)}$	$\frac{\cos(\alpha t + \phi_1)}{\beta^2 - \alpha^2} \sqrt{\left(\alpha_1^2 + \left(\frac{\alpha_0 - \alpha^2}{\alpha} \right)^2 \right)} + \frac{\cos(\beta t + \phi_2)}{\alpha^2 - \beta^2} \sqrt{\left(\alpha_1^2 + \left(\frac{\alpha_0 - \beta^2}{\beta} \right)^2 \right)}$ $\phi_1 = \tan^{-1} \left(\frac{\alpha^2 - \alpha_0}{\alpha_1\alpha} \right), \quad \phi_2 = \tan^{-1} \left(\frac{\beta^2 - \alpha_0}{\alpha_1\beta} \right)$

170	$\frac{s^3 + a_1s + a_0}{s[(s + \alpha)^2 + \beta^2]}$	$\frac{a_0}{\alpha^2 + \beta^2} - \frac{\varepsilon^{-\alpha t} \sin(\beta t + \phi)}{\beta} \sqrt{\frac{\beta^2(2\alpha - a_1)^2 + (\alpha^2 - \beta^2 + a_0 - a_1\alpha)^2}{\alpha^2 + \beta^2}},$ $\phi = \tan^{-1} \left(\frac{\beta}{\alpha} \right) + \tan^{-1} \left(\frac{\beta(a_1 - 2\alpha)}{\alpha^2 - \beta^2 + a_0 - a_1\alpha} \right)$
171	$\frac{s^2 + a_1s + a_0}{s^2[(s + \alpha)^2 + \beta^2]}$	$\frac{a_1 + a_0t}{\alpha^2 + \beta^2} - \frac{2a_0\alpha}{(\alpha^2 + \beta^2)^2} + \frac{\varepsilon^{-\alpha t} \sin(\beta t + \phi)}{\beta(\alpha^2 + \beta^2)} \sqrt{(\beta^2(2\alpha - a_1)^2 + (\alpha^2 - \beta^2 + a_0 - a_1\alpha)^2)},$ $\phi = 2 \tan^{-1} \left(\frac{\beta}{\alpha} \right) - \tan^{-1} \left(\frac{\beta(2\alpha - a_1)}{\alpha^2 - \beta^2 + a_0 - a_1\alpha} \right)$
172	$\frac{s^3 + a_1s + a_0}{(s + \nu)[(s + \alpha)^2 + \beta^2]}$	$\frac{(\nu^2 - a_1\nu + a_0)\varepsilon^{-\nu t}}{(\alpha - \nu)^2 + \beta^2} + \frac{\varepsilon^{-\alpha t} \sin(\beta t + \phi)}{\beta} \sqrt{\frac{\beta^2(2\alpha - a_1)^2 + (\alpha^2 - \beta^2 + a_0 - a_1\alpha)^2}{(\alpha - \nu)^2 + \beta^2}},$ $\phi = \tan^{-1} \left[\frac{(a_1 - 2\alpha)\beta}{\alpha^2 - \beta^2 + a_0 - a_1\alpha} \right] - \tan^{-1} \left(\frac{\beta}{\nu - \alpha} \right)$
173	$\frac{s^2 + a_1s + a_0}{s(s + \nu)[(s + \alpha)^2 + \beta^2]}$	$\frac{a_0}{(\alpha^2 + \beta^2)\nu} + \frac{(a_1\nu - a_0 - \nu^2)\varepsilon^{-\nu t}}{\nu[(\alpha - \nu)^2 + \beta^2]} + \frac{\varepsilon^{-\alpha t} \sin(\beta t + \phi)}{\beta} \sqrt{\frac{\beta^2(2\alpha - a_1)^2 + (\alpha^2 - \beta^2 - a_1\alpha + a_0)^2}{(\alpha^2 + \beta^2)(\alpha - \nu)^2 + \beta^2}},$ $\phi = \tan^{-1} \left(\frac{\beta}{\alpha} \right) + \tan^{-1} \left(\frac{\beta}{\alpha - \nu} \right) - \tan^{-1} \left(\frac{\beta(2\alpha - a_1)}{\alpha^2 - \beta^2 + a_0 - a_1\alpha} \right)$
174	$\frac{s^2 + a_1s + a_0}{s^2(s + \nu)[(s + \alpha)^2 + \beta^2]}$	$\frac{a_0 \left(t - \frac{1}{\nu} + \frac{a_1}{a_0} \right)}{v(\alpha^2 + \beta^2)} - \frac{2\alpha a_0}{\nu(\alpha^2 + \beta^2)^2} + \frac{(\nu^2 - a_1\nu + a_0)\varepsilon^{-\nu t}}{\nu^2(\alpha - \nu)^2 + \beta^2} + \frac{\varepsilon^{-\alpha t} \sin(\beta t + \phi)}{\beta(\alpha^2 + \beta^2)} \sqrt{\frac{\beta^2(2\alpha - a_1)^2 + (\alpha^2 - \beta^2 - a_1\alpha + a_0)^2}{(\alpha - \nu)^2 + \beta^2}}$ $\phi = \tan^{-1} \left[\frac{\beta(a_1 - 2\alpha)}{\alpha^2 - \beta^2 - a_1\alpha + a_0} \right] - \tan^{-1} \left(\frac{\beta}{\nu - \alpha} \right) + 2 \tan^{-1} \left(\frac{\beta}{\alpha} \right)$

No.	$F(s)$	$f(t)$
175	$\frac{s^2 + a_1 s + a_0}{(s^2 + \nu^2)(s + \alpha)^2 + \beta^2}$	$\frac{\varepsilon^{-\alpha t} \sin(\beta t + \phi_1)}{\beta} \cdot \sqrt{\frac{(\alpha^2 - \beta^2 - a_0 - a_1 \alpha)^2 + (2\alpha - a_1)^2 \beta^2}{(\alpha^2 + \beta^2 - \nu^2)^2 + (2\alpha\nu)^2}}$ $+ \frac{\sin(\nu t + \phi_2)}{\nu} \sqrt{\frac{(\nu^2 - a_0)^2 + a_1^2 \nu^2}{(\alpha^2 + \beta^2 - \nu^2)^2 + (2\alpha\nu)^2}}$ $\phi_1 = \tan^{-1} \left(\frac{2\alpha\beta}{\alpha^2 + \nu^2 - \beta^2} \right) + \tan^{-1} \left[\frac{\beta(\alpha_1 - 2\alpha)}{\alpha^2 - \beta^2 + a_0 - a_1 \alpha} \right],$ $\phi_2 = \tan^{-1} \left(\frac{a_1 \nu}{a_0 - \nu^2} \right) - \tan^{-1} \left(\frac{2\alpha\nu}{\alpha^2 + \beta^2 - \nu^2} \right).$
176	$\frac{s^2 + a_1 s + a_0}{s(s^2 + \nu^2)(s + \alpha)^2 + \beta^2}$	$\frac{a_0}{\nu^2(\alpha^2 + \beta^2)} - \frac{\varepsilon^{-\alpha t} \sin(\beta t + \phi_1)}{\beta} \sqrt{\frac{(\alpha^2 - \beta^2 + a_0 - a_1 \alpha)^2 + \beta^2(2\alpha - a_1)^2}{(\alpha^2 + \beta^2)(\alpha^2 + \beta^2 - \nu^2)^2 + (2\alpha\nu)^2}}$ $- \frac{\sin(\nu t + \phi_2)}{\nu^3} \sqrt{\frac{(\nu^2 - a_0)^2 + a_1^2 \nu^2}{(\alpha^2 + \beta^2 - \nu^2)^2 + (2\alpha\nu)^2}}$ $\phi_1 = \tan^{-1} \left(\frac{\beta}{\alpha} \right) - \tan^{-1} \left(\frac{\alpha^2 - \beta^2 + \nu^2}{2\alpha\beta} \right) + \tan^{-1} \left(\frac{\alpha^2 - \beta^2 + a_0 - a_1 \alpha}{\beta(2\alpha - a_1)} \right),$ $\phi_2 = \tan^{-1} \left(\frac{\alpha^2 + \beta^2 - \nu^2}{2\alpha\nu} \right) + \tan^{-1} \left(\frac{a_1 \nu}{a_0 - \nu^2} \right)$
177	$\frac{s^2 + a_1 s + a_0}{s(s + \alpha)^2}$	$\frac{a_0}{\alpha^2} + \left[\frac{(a_1 \alpha - a_0 - \alpha^2)t}{\alpha} + \frac{\alpha^2 - a_0}{\alpha^2} \right] \varepsilon^{-\alpha t}$
178	$\frac{s^2 + a_1 s + a_0}{s^2(s + \alpha)^2}$	$\frac{a_1 + a_0 t}{\alpha^2} - \frac{2a_0}{\alpha^2} + \frac{1}{\alpha^2} \left[\frac{2a_0}{\alpha} - a_1 + (a_1^2 + a_0 - a_1 \alpha) \right] \varepsilon^{-\alpha t}$
179	$\frac{s^2 + a_1 s + a_0}{(s + \beta)(s + \alpha)^2}$	$\frac{(\beta^2 + a_0 - a_1 \beta) \varepsilon^{-\beta t}}{(\alpha - \beta)^2} + \left[\frac{\alpha^2 - 2\alpha\beta - a_0 + a_1 \beta}{(\alpha - \beta)^2} + \frac{(\alpha^2 + a_0 - a_1 \alpha)t}{\beta - \alpha} \right] \varepsilon^{-\alpha t}$

180	$\frac{s^2 + a_1 e + a_0}{s(s + \beta)(e + \alpha)^2}$	$\frac{a_0}{\alpha^2 \beta} + \frac{(a_1 \beta - a_0 - \beta^2)e^{-\beta t}}{\beta(\alpha - \beta)^2} + \frac{e^{-\alpha t}}{\alpha(\alpha - \beta)} \left[(\alpha^2 - a_1 \alpha + a_0)t + \frac{\alpha^2(\beta - a_1) + a_0(2\alpha - \beta)}{\alpha(\alpha - \beta)} \right]$
181	$\frac{s^2 + a_1 e + a_0}{s^2(s + \beta)(e + \alpha)^2}$	$\frac{a_0}{\alpha^2 \beta} \left[\frac{a_1}{\alpha_0} - \frac{1}{\beta} - \frac{2}{\alpha} + t \right] + \frac{e^{-\alpha t}}{\alpha^2(\beta - \alpha)} \left[(\alpha^2 - a_1 \alpha + a_0)t + \frac{2a_0 \beta - \alpha(3a_0 + a_1 \beta) + \alpha^2(2a_1 - \alpha)}{\alpha(\beta - \alpha)} \right] + \dots + \frac{(\beta^2 - a_1 \beta + a_0)e^{-\beta t}}{\beta^2(\beta - \alpha)^2}$
182	$\frac{s^2 + a_1 e + a_0}{(e + \beta)(e + \nu)(e + \alpha)^2}$	$\frac{(\nu^2 - a_1 \nu + a_0)e^{-\nu t}}{(\beta - \nu)(\beta - \alpha)^2} + \frac{(\beta^2 - a_1 \beta + a_0)e^{-\beta t}}{(\nu - \beta)(\alpha - \beta)^2} + \frac{e^{-\alpha t}}{(\alpha - \nu)(\alpha - \beta)} \left[(\alpha^2 - a_1 \alpha + a_0)t + \frac{\nu - \beta}{(\alpha - \nu)(\alpha - \beta)} (\alpha^2 - a_1 \alpha - 2a_0) \right]$
183	$\frac{s^2 + a_1 e + a_0}{(e^2 + \beta^2)(e + \alpha)^2}$	$\frac{\sin(\beta t + \phi)}{\beta(\alpha^2 + \beta^2)} \sqrt{(\beta^2 - a_0)^2 + a_1^2 \beta^2} + \frac{e^{-\alpha t}}{\alpha^2 + \beta^2} \left[(\alpha^2 - a_1 \alpha + a_0)t + \frac{2\alpha(\beta^2 - a_0)^2 + a_1(\beta^2 - \alpha^2)}{(\alpha^2 + \beta^2)} \right]$ <p style="text-align: center;">$\phi = \tan^{-1} \left(\frac{a_1 \beta}{a_0 - \beta^2} \right) - 2 \tan^{-1} \frac{\beta}{\alpha}$</p>
184	$\frac{s^2 + a_1 e + a_0}{s(\alpha^2 + \beta^2)(e + \alpha)^2}$	$\frac{a_0}{\alpha^2 \beta^2} - \frac{\sin(\beta t + \phi) \sqrt{(\beta^2 a_1^2 + (\beta^2 - a_0)^2)}}{\beta^2(\alpha^2 + \beta^2)} - \left[\frac{\alpha^2(\alpha^2 - \beta^2) + a_0(\alpha^2 + \beta^2) + 2(\alpha_0 - a_1 \alpha)}{\alpha^2(\alpha^2 + \beta^2)^2} + \frac{(\alpha^2 - a_1 \alpha + a_0)t}{\alpha(\alpha^2 + \beta^2)} \right] \cdot e^{-\alpha t}$ <p style="text-align: center;">$\phi = \tan^{-1} \left(\frac{\alpha}{\beta} \right) - \tan^{-1} \left(\frac{\beta}{\alpha} \right) + \tan^{-1} \left(\frac{a_1 \beta}{a_0 - \beta^2} \right)$</p>

No.	$F(s)$	$f(t)$
185	$\frac{s^2 + a_1 s + a_0}{s^2(s^2 + \beta^2)(s + \alpha)^2}$	$\frac{a_0 t + a_1 - 2a_0/\alpha}{\alpha^2 \beta^2} + \left[\frac{(a_2^2 + \beta^2)(2a_0 - a_1\alpha) + 2\alpha^2(a_2^2 - a_1\alpha + a_0)}{\alpha^2(a_2^2 + \beta^2)^2} + \frac{(a_2^2 - a_1\alpha + a_0)t}{\alpha^2(a_2^2 + \beta^2)} \right] e^{-\alpha t}$ $+ \frac{\sqrt{(\beta^2 - a_0)^2 + a_1^2 \beta^2} \sin(\beta t + \phi)}{\beta^2(\alpha^2 + \beta^2)}$ $\phi = \tan^{-1} \left(\frac{a_1 \beta}{a_0 - \beta^2} \right) + 2 \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
186	$\frac{s^2 + a_1 s + a_0}{(s + \beta)^2(s + \alpha)^2 + \nu^2}$	$\frac{e^{-\alpha t} \sin(\nu t + \phi) \sqrt{\nu^2(a_1 - 2\alpha)^2 + (\alpha^2 - \nu^2 - a_1\alpha + a_0)^2}}{\nu(\nu^2 + (\alpha - \beta)^2)}$ $+ \left[\frac{(\beta^2 - a_1\beta + a_0)t + (a_1 - 2\beta)(\nu^2 + (\alpha - \beta)^2) - 2(\alpha - \beta)(\beta^2 - a_1\beta + a_0)}{\nu^2 + (\alpha - \beta)^2} \right] e^{-\beta t}$ $\phi = \tan^{-1} \left[\frac{\nu(a_1 - 2\alpha)}{\alpha^2 - \nu^2 - a_1\alpha + a_0} \right] - 2 \tan^{-1} \left[\frac{\nu}{\beta - \alpha} \right]$
187	$\frac{s^2 + a_1 s + a_0}{(s + \alpha)^2(s + \beta)^2}$	$\left[\frac{a_1(\alpha + \beta) - 2(\alpha\beta + a_0)}{(\beta - \alpha)^2} + \frac{(a_2^2 - a_1\alpha + a_0)t}{(\alpha - \beta)^2} \right] e^{-\alpha t}$ $+ \left[\frac{(\beta^2 - a_1\beta + a_0)t}{(\alpha - \beta)^2} - \frac{a_1(\alpha + \beta) - 2(\alpha\beta + a_0)}{(\beta - \alpha)^2} \right] e^{-\beta t}$
188	$\frac{s^2 + a_1 s + a_0}{s(s + \alpha)^2(s + \beta)^2}$	$\frac{a_0}{\alpha^2 \beta^2} + \left[\frac{(a_1\alpha - a_0 - \alpha^2)t}{\alpha(\alpha - \beta)^2} + \frac{2\alpha(a_2^2 - a_1\alpha + a_0) + (\alpha^2 - a_0)(\beta - \alpha)}{\alpha^2(\beta - \alpha)^2} \right] e^{-\alpha t}$ $+ \left[\frac{(a_1\beta - a_0 - \beta^2)t}{\beta(\beta - \alpha)^2} + \frac{2\beta(\beta^2 - a_1\beta + a_0) + (\beta^2 - a_0)(\alpha - \beta)}{\beta^2(\alpha - \beta)^2} \right] e^{-\beta t}$
189	$\frac{s^2 + a_1 s + a_0}{s^2(s + \alpha)^2(s + \beta)^2}$	$\frac{a_1 + a_0 t}{\alpha^2 \beta^2} - \frac{2a_0(\alpha + \beta)}{\alpha^2 \beta^2} + \left[\frac{(a_2^2 - a_1\alpha + a_0)t}{\alpha^2(\alpha - \beta)^2} + \frac{2\alpha(a_1\alpha - a_0 - \alpha^2) + (2a_0 - a_1\alpha)(\beta - \alpha)}{\alpha^2(\beta - \alpha)^2} \right] e^{-\alpha t}$ $+ \left[\frac{(\beta^2 - a_1\beta + a_0)t}{\beta^2(\alpha - \beta)^2} + \frac{2\beta(a_1\beta - a_0 - \beta^2) + (2a_0 - a_1\beta)(\alpha - \beta)}{\beta^2(\alpha - \beta)^2} \right] e^{-\beta t}$

190	$\frac{s^2 + a_1 s + a_0}{(s + \alpha)^2 + \beta^2}$	$\{[(\alpha^2 + \beta^2) + (a_0 - a_1\alpha) + (a_1 - 2\alpha_1\beta^2)] \sin \beta t + [(a_1\alpha - a_0) - (\alpha^2 - \beta^2)] \beta t \cos \beta t\} \frac{e^{-\alpha t}}{2\beta^2}$
191	$\frac{s^2 + a_1 s + a_0}{(s^2 + \alpha^2)^2}$	$\frac{1}{2\alpha^3} \{[a_0 + \alpha^2(1 + a_1 t)] \sin \alpha t + (\alpha^2 - a_0)\alpha t \cos \alpha t\}$
192	$\frac{s^2 + a_1 s + a_0}{s(s^2 + \alpha^2)^2}$	$\frac{a_0}{\alpha^4} - \frac{t \sin(\alpha t + \phi_1) \sqrt{[(\alpha^2 - a_0)^2 + a_1^2 \alpha^2]} - \cos(\alpha t + \phi_2) \sqrt{(a_1^2 \alpha^2 + 4a_0^2)}}{2\alpha^4}$, $\phi_1 = \tan^{-1} \left(\frac{a_1 \alpha}{a_0 - \alpha^2} \right)$, $\phi_2 = \tan^{-1} \left(\frac{a_1 \alpha}{2a_0} \right)$
193	$\frac{s^2 + a_1 s + a_0}{s^2(s^2 + \alpha^2)^2}$	$\frac{a_1 + a_0 t}{\alpha^4} + \frac{t \cos(\alpha t + \phi_1) \sqrt{[(\alpha^2 - a_0)^2 + a_1^2 \alpha^2]} - \sin(\alpha t + \phi_2) \sqrt{(\alpha^2 - 3a_0)^2 + 4a_1^2 \alpha^2}}{2\alpha^4}$, $\phi_1 = \tan^{-1} \left(\frac{a_1 \alpha}{a_0 - \alpha^2} \right)$, $\phi_2 = \tan^{-1} \left(\frac{2a_1 \alpha}{3a_0 - \alpha^2} \right)$
194	$\frac{s^2 + a_1 s + a_0}{(s + \alpha)^3}$	$\left[2 + (a_1 - 2\alpha)t + \frac{(\alpha^2 + a_1\alpha + a_0)t^2}{2} \right] e^{-\alpha t}$
195	$\frac{s^2 + a_1 s + a_0}{s(s + \alpha)^3}$	$\frac{a_0}{\alpha^3} - \frac{e^{-\alpha t}}{\alpha} \left[\frac{2a_0}{\alpha^2} + \frac{(a_0 + \alpha^2)t}{\alpha} + \frac{(\alpha^2 - a_1\alpha + a_0)t^2}{2} \right]$
196	$\frac{s^2 + a_1 s + a_0}{s^2(s + \alpha)^3}$	$\frac{a_1\alpha - 3a_0}{\alpha^4} + \frac{a_0 t}{\alpha^3} + \left[\frac{3a_0 - a_1\alpha}{\alpha^4} + \frac{(2a_0 - a_1\alpha)t}{\alpha^3} + \frac{(\alpha^2 - a_1\alpha + a_0)t^2}{2\alpha^3} \right] e^{-\alpha t}$
197	$\frac{s^3 + a_2 s^2 + a_1 s + a_0}{s^2(s + \alpha)(s + \beta)}$	$\frac{a_1 + a_0 t}{\alpha\beta} - \frac{a_0(\alpha + \beta)}{\alpha^2\beta^2} + \frac{1}{\alpha - \beta} \left[\left(\alpha + \frac{a_1}{\alpha} - a_2 - \frac{a_0}{\alpha^2} \right) e^{-\alpha t} - \left(\beta + \frac{a_1}{\beta} - a_2 - \frac{a_0}{\beta^2} \right) e^{-\beta t} \right]$
198	$\frac{s^3 + a_2 s^2 + a_1 s + a_0}{s(s + \alpha)(s + \beta)(s + \nu)}$	$\frac{a_0}{\alpha\beta\nu} + \frac{(\alpha^2 - a_2\alpha + a_1 - a_0)\alpha e^{-\alpha t}}{(\nu - \alpha)(\beta - \alpha)} + \frac{(\beta^2 - a_2\beta + a_1 - a_0)\beta e^{-\beta t}}{(\nu - \beta)(\alpha - \beta)} + \frac{(\nu^2 - a_2\nu + a_1 - a_0)\nu e^{-\nu t}}{(\beta - \nu)(\alpha - \nu)}$

No.	$F(e)$	$f(t)$
199	$\frac{e^2 + a_2 e^2 + a_1 e + a_0}{e^2(e^2 + \alpha^2)}$	$\frac{a_1 + a_2 e}{\alpha^2} - \frac{\sin(\alpha t + \phi) \sqrt{(a_2 \alpha - a_0/\alpha)^2 + (\alpha^2 - a_1)^2}}{\alpha^2}, \quad \phi = \tan^{-1} \left[\frac{\alpha(a_1 - \alpha^2)}{a_0 - a_2 \alpha^2} \right]$
200	$\frac{e^2 + a_2 e^2 + a_1 e + a_0}{e(e + \beta)(e^2 + \alpha^2)}$	$\frac{a_0}{\alpha^2 \beta} + \frac{(\beta^2 - a_2 \beta^2 + a_1 \beta - a_0) e^{-\beta t}}{\beta(\alpha^2 + \beta^2)} - \frac{\cos(\alpha t + \phi)}{\alpha^2} \sqrt{\frac{(a_2^2 \alpha^2 - a_1)^2 + (a_2 \alpha^2 - a_0)^2}{(\alpha^2 + \beta^2)}}$ $\phi = \tan^{-1} \left(\frac{a_1 - \alpha^2}{a_0/\alpha - a_2 \alpha} \right) - \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
201	$\frac{e^2 + a_2 e^2 + a_1 e + a_0}{e^2(e + \beta)(e^2 + \alpha^2)}$	$\frac{a_1 + a_2 e}{\alpha^2 \beta} + \frac{a_0 - a_1 \beta - \beta^2 + a_2 \beta^2 e^{-\beta t}}{\beta^2(\alpha^2 + \beta^2)} + \frac{\cos(\alpha t + \phi)}{\alpha^2} \sqrt{\frac{(a_2 \alpha - a_0/\alpha)^2 + (\alpha^2 - a_1)^2}{\alpha^2 + \beta^2}}$ $\phi = \tan^{-1} \left[\frac{\alpha(a_1 - \alpha^2)}{a_0 - a_2 \alpha^2} \right] + \tan^{-1} \left(\frac{\beta}{\alpha} \right)$
202	$\frac{e^2 + a_2 e^2 + a_1 e + a_0}{(e + \beta)(e + \gamma)(e^2 + \alpha^2)}$	$\frac{(\beta^2 - a_2 \alpha^2 + a_1 \beta - a_0) e^{-\beta t}}{(\beta - \gamma)(\alpha^2 + \beta^2)} + \frac{(\gamma^2 - a_2 \gamma^2 + a_1 \gamma - a_0) e^{-\gamma t}}{(\gamma - \beta)(\alpha^2 + \gamma^2)} + \frac{\sin(\alpha t + \phi)}{\alpha} \sqrt{\frac{\alpha^2(\alpha^2 - a_1)^2 + (a_2 \alpha^2 - a_0)^2}{(\alpha^2 + \beta^2)(\alpha^2 + \gamma^2)}}$ $\phi = \tan^{-1} \left[\frac{\alpha(a_1 - \alpha^2)}{a_0 - a_2 \alpha^2} \right] - \tan^{-1} \left(\frac{\alpha}{\beta} \right) - \tan^{-1} \left(\frac{\alpha}{\gamma} \right)$
203	$\frac{e^2 + a_2 e^2 + a_1 e + a_0}{(e^2 + \alpha^2)(e^2 + \beta^2)}$	$\frac{\cos(\beta t + \phi_1)}{\alpha^2 - \beta^2} \sqrt{(\beta^2 - a_1)^2 + \left(\frac{a_2 \beta^2 - a_0}{\beta} \right)^2} - \frac{\cos(\alpha t + \phi_2)}{\alpha^2 - \beta^2} \sqrt{(\alpha^2 - a_1)^2 + \left(\frac{a_2 \alpha^2 - a_0}{\alpha} \right)^2}$ $\phi_1 = \tan^{-1} \left[\frac{a_1 \beta^2 - a_0}{\beta(a_1 - \beta^2)} \right], \quad \phi_2 = \tan^{-1} \left[\frac{a_1 \alpha^2 - a_0}{\alpha(a_1 - \alpha^2)} \right]$
204	$\frac{e^2 + a_2 e^2 + a_1 e + a_0}{e^2(e + \alpha)^2}$	$\frac{a_1 + a_2 e}{\alpha^2} - \frac{2a_0}{\alpha^2} + \frac{e^{-\alpha t}}{\alpha^2} \left[\alpha^2 - a_1 + \frac{2a_0}{\alpha} + (a_0 - a_1 \alpha + a_2 \alpha^2 - \alpha^2) t \right]$

205	$\frac{\sigma^2 + a_2\sigma^2 + a_1\sigma + a_0}{s(s + \beta)(s + \alpha)^2}$	$\frac{a_0}{\alpha^2\beta} + \frac{(\beta^2 - a_2\beta^2 + a_1\beta - a_0)\varepsilon^{-\beta t}}{\beta(\alpha - \beta)^2}$ $+ \left[\frac{\alpha^4 - 2\beta\alpha^3 + \alpha^2(a_2\beta - a_1) + a_0(2\alpha - \beta)}{\alpha^2(\alpha - \beta)^2} + \frac{(\alpha^2 - a_2\alpha^2 + a_1\alpha - a_0)\varepsilon^{-\alpha t}}{\alpha(\beta - \alpha)} \right] \varepsilon^{-\alpha t}$
206	$\frac{\sigma^2 + a_2\sigma^2 + a_1\sigma + a_0}{s^2(s + \beta)(s + \alpha)^2}$	$\frac{a_0}{\alpha^2\beta} \left[\frac{a_1}{a_0} - \frac{2}{\alpha} - \frac{1}{\beta} + t \right] + \frac{(a_0 - a_1\beta + a_2\beta^2 - \beta^3)\varepsilon^{-\beta t}}{\beta^2(\alpha - \beta)^2}$ $+ \left[\frac{\alpha^2(\beta - a_1) + a_0(\beta - \alpha) - (a_1\alpha - a_0)(\beta - 2\alpha)}{\alpha^2(\alpha - \beta)^2} + \frac{(a_0 - a_2\alpha + a_1\alpha^2 - a_2^2)\varepsilon^{-\alpha t}}{\alpha^2(\beta - \alpha)} \right] \varepsilon^{-\alpha t}$
207	$\frac{\sigma^2 + a_2\sigma^2 + a_1\sigma + a_0}{(s^2 + \beta^2)(s + \alpha)^2}$	$\frac{\sin(\beta t + \phi)\sqrt{\{\beta^2(a_1 - \beta^2)\varepsilon^{\beta t} + (a_0 - a_2\beta^2)\varepsilon^{\beta t}\}}}{\beta(\alpha^2 + \beta^2)}$ $+ \frac{\varepsilon^{-\alpha t}}{\alpha^2 + \beta^2} \left[(a_0 - a_1\alpha + a_2\alpha^2 - \alpha^3)\varepsilon^t + \frac{(\alpha^4 + 3\beta^2\alpha^3 - a_1\alpha^2 + a_1\beta^2 + 2a_0\alpha - 2a_2\alpha\beta^2)}{(\alpha^2 + \beta^2)} \right]$ $\phi = \tan^{-1} \left[\frac{a_2\beta^2 - a_0}{\beta(a_1 - \beta^2)} \right] - \tan^{-1} \left(\frac{\beta}{\alpha} \right) + \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
208	$\frac{\sigma^2 + a_2\sigma^2 + a_1\sigma + a_0}{s(\sigma^2 + \beta^2)(s + \alpha)^2}$	$\frac{a_0}{\alpha^2\beta^2} + \frac{\varepsilon^{-\alpha t}}{\alpha(\alpha^2 + \beta^2)} \left[(\alpha^2 - a_2\alpha^2 + a_1\alpha - a_0)\varepsilon^t + \frac{2\alpha^2(a_1 - \beta^2) - \alpha^2(2a_0 + a_2\alpha^2 - a_2\beta^2) - a_0(\alpha^2 + \beta^2)}{\alpha(\alpha^2 + \beta^2)} \right]$ $+ \frac{\sin(\beta t + \phi)\sqrt{\{\beta^2(\beta^2 - a_1)\varepsilon^{\beta t} + (a_2\beta^2 - a_0)\varepsilon^{\beta t}\}}}{\beta^2(\alpha^2 + \beta^2)}$ $\phi = \tan^{-1} \left[\frac{\beta(\beta^2 - a_1)}{a_2\beta^2 - a_0} \right] - \tan^{-1} \left(\frac{\beta}{\alpha} \right) + \tan^{-1} \left(\frac{\alpha}{\beta} \right)$
209	$\frac{\sigma^2 + a_2\sigma^2 + a_1\sigma + a_0}{(s + \alpha)^2(s + \beta)^2}$	$\left[\frac{(a_0 - a_1\alpha + a_2\alpha^2 - \alpha^3)\varepsilon^t}{(\alpha - \beta)^2} + \frac{\alpha^2(\beta - \alpha) - 2a_2\alpha\beta + a_1(\alpha + \beta) - 2a_0}{(\beta - \alpha)^2} \right] \varepsilon^{-\alpha t}$ $+ \left[\frac{(a_0 - a_1\beta + a_2\beta^2 - \beta^3)\varepsilon^t}{(\alpha - \beta)^2} + \frac{\beta^2(3\alpha - \beta) - 2a_2\alpha\beta + a_1(\alpha + \beta) - 2a_0}{(\alpha - \beta)^2} \right] \varepsilon^{-\beta t}$

No.	$F(s)$	$f(t)$
210	$\frac{s^3 + a_2 s^2 + a_1 s + a_0}{s(s + \alpha)^2(s + \beta)^2}$	$\frac{a_0}{\alpha^2 \beta^2} + \left[\frac{(\alpha^3 - a_2 \alpha^2 + a_1 \alpha - a_0)t}{\alpha(\beta - \alpha)^3} + \frac{\alpha^2[a_2(\alpha + \beta) - 2(a_1 + \alpha\beta)] + a_0(3\alpha - \beta)}{\alpha^2(\beta - \alpha)^3} \right] \varepsilon^{-\alpha t}$ $+ \left[\frac{(\beta^3 - a_2 \beta^2 + a_1 \beta - a_0)t}{\beta(\alpha - \beta)^3} + \frac{\beta^2[a_2(\alpha + \beta) - 2(a_1 + \alpha\beta)] + a_0(3\beta - \alpha)}{\beta^2(\alpha - \beta)^3} \right] \varepsilon^{-\beta t}$
211	$\frac{s^3 + a_2 s^2 + a_1 s + a_0}{[(s + \alpha)^2 + \beta^2]^2}$	$\frac{\varepsilon^{-\alpha t} \sin \beta t}{2\beta^3} [(a_2 - \alpha)(\alpha^2 + \beta^2) - \alpha(a_1 + 2\beta^2) + (3\alpha^2 - \beta^2 - 2a_2\alpha + a_1)\beta^2 t + a_0]$ $+ \frac{\varepsilon^{-\alpha t} \cos \beta t}{2\beta^3} [2\beta^3 - (a_0 - a_1\alpha + a_2[\alpha^2 - \beta^2]) + \alpha(3\beta^2 - \alpha^2)]\beta t$
212	$\frac{s^3 + a_2 s^2 + a_1 s + a_0}{s^2(s^2 + \alpha^2)^2}$	$\frac{a_1 + a_0 t}{\alpha^4} - \frac{\sin(\alpha t + \phi_1)}{2\alpha^5} \sqrt{4a_1^2 \alpha^2 + (\alpha^2 a_2 - 3a_0)^2}$ $+ \frac{t \cos(\alpha t + \phi_2)}{2\alpha^4} \sqrt{(\alpha^2(\alpha^2 - a_1)^2 + (\alpha^2 a_2 - a_0)^2)}$ $\phi_1 = \tan^{-1} \left(\frac{2\alpha a_1}{3a_0 - \alpha^2 a_2} \right), \quad \phi_2 = \tan^{-1} \left(\frac{\alpha(a_1 - \alpha^2)}{a_0 - \alpha^2 a_2} \right)$
213	$\frac{s^3 + a_2 s^2 + a_1 s + a_0}{s(s + \alpha)^3}$	$\frac{a_0}{\alpha^3} + \left[\frac{(\alpha^3 - a_2 \alpha^2 + a_1 \alpha - a_0)\beta^2}{2\alpha} - \frac{(\alpha_0 - a_2 \alpha^2 + 2\alpha^3)t}{\alpha^2} - \frac{2(\alpha_0 - \alpha^3)}{\alpha^2} \right] \varepsilon^{-\alpha t}$
214	$\frac{s^3 + a_2 s^2 + a_1 s + a_0}{s^2(s + \alpha)^3}$	$\frac{a_1 + a_0 t}{\alpha^3} - \frac{3a_0}{\alpha^4} + \left[\frac{(6a_0 - 2\alpha a_1)}{\alpha^4} + \frac{(2a_0 - a_1 \alpha + \alpha^3)t}{\alpha^5} + \frac{(a_0 - a_1 \alpha + a_2 \alpha^2 - \alpha^3)t^2}{2\alpha^2} \right] \varepsilon^{-\alpha t}$
215	$\sqrt{(s - \alpha) - \varepsilon^{-\alpha t}}$	$\frac{e^{\beta t} - e^{\alpha t}}{2\sqrt{(\pi t^3)}}$
216	$\frac{\omega \left(\frac{\pi s}{\varepsilon^{\omega}} + \varepsilon - \frac{\pi s}{2\omega} \right)}{2(s^2 + \omega^2)}$	$ \sin \omega t $

217	$\frac{-\frac{a}{s}}{\varepsilon \frac{s}{s}}$	$J_0(2\sqrt{at})$
218	$\frac{-\frac{a}{s}}{\varepsilon \frac{s}{s}} \frac{1}{\sqrt{s}}$	$\frac{\cos 2\sqrt{at}}{\sqrt{\pi t}}$
219	$\frac{a}{\varepsilon^2} \frac{1}{\sqrt{s}}$	$\frac{\cosh 2\sqrt{at}}{\sqrt{\pi t}}$
220	$\ln \left(\frac{s + \alpha}{s + \beta} \right)$	$\frac{\varepsilon^{-\beta t} - \varepsilon^{-\alpha t}}{t}$
221	$\frac{\ln s}{s}$	$-0.5772 - \ln t$
222	$\frac{\ln s}{s^2 + 1}$	$Si(t) \cos t - Ci(t) \sin t$
223	$\frac{s \ln s}{s^2 + 1}$	$-Si(t) \sin t - Ci(t) \cos t$
224	$\ln \left(\frac{s^2 + a^2}{s^2} \right)$	$\frac{2(1 - \cos at)}{t}$
225	$\tan^{-1} \left(\frac{a}{s} \right)$	$\frac{\sin at}{t}$
226	ε^{-as}	$\delta(t - a)$

No.	$F(s)$	$f(t)$
227	$\frac{e^{-as}}{s}$	$U(t-a)$
228	$\frac{e^{-as}}{s^2}$	$(t-a)U(t-a)$
229	$\frac{e^{-as}}{(s+\alpha)}$	$e^{-\alpha(t-a)}U(t-a)$
230	$\frac{e^{-as}}{(s+\alpha)^2}$	$(t-a)e^{-\alpha(t-a)}U(t-a)$
231	$\frac{e^{-as}}{(s+\alpha)(s+\beta)}$	$\left[\frac{e^{-\alpha(t-a)} - e^{-\beta(t-a)}}{\beta - \alpha} \right] U(t-a)$
232	$\frac{1 - e^{-as}}{s}$	$U(t) - U(t-a)$
233	$\frac{(s+\alpha)e^{-as}}{\alpha s^2}$	$\left(t + \frac{1}{\alpha} - a \right) U(t-a)$
234	$\frac{e^{-as}}{s(s+\alpha)(s+\beta)}$	$\left[\frac{1}{\alpha\beta} - \frac{e^{-\alpha(t-a)}}{\alpha(\beta-\alpha)} - \frac{e^{-\beta(t-a)}}{\beta(\alpha-\beta)} \right] U(t-a)$

INDEX

- Abscissa of absolute convergence 53
- Acceleration caused by shock 180
- Active integrating networks 142
- Algebra 1
- Algebraic form of number 4
- Alternative derivation of Laplace integral 272
- Amplitude function 204
- Analog functions of s 279
- Area integration 21

- Back e.m.f. 174
- Band-pass filters 214
 - design 215
- Band rejection filter 218
- Basic $R-L-C$ relations 76
- Bessel polynomials 234
- Binomial coefficients 165
- Blanking sections of waveforms 195
- Borel's theorem 108
- Butterworth, filter 203
 - pole locations 208

- Capacity, parallel plate 14
- Cathode follower $R-C$ oscillator 131
- Circular integral 24, 35
- Clocks, time shifting 99, 112
- Closed form of series 274
- Coaxial cable capacity 12
- Coefficients, Fourier 40
 - square wave 45
- Complex, differentiation 101
 - functions 15
 - integration 20, 103
 - numbers 1, 3, 5
 - plane 3, 5
 - plane integration 23
 - plane translation 90
- Contraction of poles in s -plane 114
- Convergence factor 52
- Convolution theorem 106, 108
- Current, definition of 71, 173
 - in s -plane 168

- Decay factor 52
- Derivative transformation 66

- Determinants, expansion by minors 11
 - network 77, 117
- Diagram, pole-zero 19
- Dirac delta function 183
- Direct, Fourier transform 43
 - Laplace transform 55
- Discrete spectrum 46
- Displaced, ramp function 198
 - step function 50
- Dummy index of summation 275

- Euler's theorem 4, 40
- Even periodic functions 186
- Excitation function 72
- Exponential form of, number 4
 - Fourier series 40
- Exponentially decaying sinewaves 64

- Faltung integral 106
- Fictitious current 77
- Filter, cut-off 203
 - order 203
- Final value theorem 93
- Flat functions 203
- Flux, linkages 170, 176
 - transmission line 14
- Fourier, coefficients 40, 186
 - integral 46
 - integral of step function 50
 - series 37
 - series, complex conjugate form 41
 - transform, direct 43
 - transform, inverse 42
- Frequency normalization 201
- Frequency, spectrum 45
 - spectrum of rectangular pulse 49
- Function, complex 15
 - definition 5
 - periodic 37
 - of s 249

- General periodic wave 191
- Geographical planes 6
- Geometrical symmetry of filters 214

- Half-wave rectified sinewave 194, 197
 Harmonic, discrimination in oscillators 129
 distortion in oscillators 129
 square wave content 45
 Harmonics 37, 39, 45
 Higher order poles 86
 High-pass maximally flat functions 213
 Hyperbolic sine 278

 Imaginary exponents 60
 Impedance level 199
 Index of summation 275
 Induced back voltage 174
 Infinite series in closed form 274
 Initial, conditions 70, 75, 167
 current in an inductance 169
 value theorem 96
 Integral, around multiple poles 32
 around pole 23
 as area 21
 circular 24
 Fourier 46
 function of end points 22
 transform of 68
 Integration, as summation of residues 35
 complex plane 20, 22
 real 20
 Inverse Laplace transform 56, 72
 Iterative networks 164, 255

j-operator 3

 Kernel 84
 Keyed *R-F* carrier 195
 Kirchoff's law 73, 117

 Laplace, integral derived from series 272
 operator symbol 59
 transform 55
 transform used to sum infinite series 274
 Legendre polynomial filters 239
 Line transformation 8
 Linear-phase approximation 228
 Loop equations 77
 Lossless network models 284
 Low-pass, Butterworth filters 203
 R-C filters 159
 Mass-spring oscillating system 181
 Matched low-pass filters 219
 Maximally flat, functions 203, 205
 high-pass filters 213
 time-delay filters 225
 Maxwell's fictitious current 117
 Mercator projection 6
 Minors of determinants 118
 Multiple, loop circuits 117
 poles 16, 31
 Mutual, inductance 167, 173
 loop impedance 117
 Mutually coupled coils 174

 Negative numbers 2
 Network, equations 117
 synthesis 205
 Node equations 169
 Non-periodic waves 46, 47
 Non-tapered filters 160
 Normalization of functions 199
 Normalized, frequency 201
 high-pass filters 213
 Number of reactive elements in filter 204
 Numbers, variation in writing 4

 Operational amplifiers 145
 Order of filters 203

 Parametric variable 97, 107
 Partial fractions 83, 86
 Pascal's triangle 165, 265
 Periodic function 37
 Periodicity theorem 191
 Phase, angle and pole locations 66
 shift oscillator 126
 Point transformation 8
 Polar map projection 6
 Pole contraction in *s*-plane 114
 Pole locations for filters 208
 Poles of functions 16
 Pole-zero diagram 19
 Power series 272
 Pulsed periodic functions 195

Q of receiver 50

R-C cathode follower oscillator 131
R-C filter, for high voltage power supplies 245
 low-pass single section 159
 Reactance 116

- Real, integration 20
 - translation 98
- Rectangular, form of number 4
 - pulse 48, 180
- Rectified half sinewave 194, 197
- Relay damping 119
- Removing poles 32, 80
- Residue, definition 30
- Residues, of functions 27
 - of higher order poles 86
- Resistance-capacity voltage step-up networks 132
- Response function 72
- Rotation, vector 2

- Sampling with delta functions 185
- Sawtooth pulse 194
- Scale change theorem 112
- Second-order Butterworth function 207
- Sectioning time functions 105
- Selective variable 107
- Self-impedance of loops 117
- Series, derivation of Laplace integral 272
 - Fourier 37
 - in closed form 274
- Shifting in time domain 98
- Shock spectrum computer 180
- Single section, low-pass filter 159
 - R - C oscillator 139
- Spectrum, discrete 46
 - rectangular pulse 48
 - square wave 43, 45
- s -plane 6
 - s -plane translation 90
- Square wave, coefficients 45
- Step function 50
- Surface, complex functions 15, 22
- Symbol for Laplace operator 59
- Synthesis of, networks 205
 - third-order maximally flat function 211
- Tabular method 261
- Tchebycheff filters 239
- Third-order Butterworth filter 211
- Three-section low-pass filter 162
- Time function as summation of residues 83
- Transcendental functions of s 83
- Transfer function 72
 - normalization 199
 - odd and even parts 288
- Transformation, derivative 66
 - integral 68
 - line 8
 - point 8
 - regional 12
- Transformed, battery 170
 - current and voltage 168
 - impedances 76
- Transient solutions 167, 171
- Translation in time domain 98
- Transmission line, capacity of 12
- Two-section R - C filter 160

- Unilateral Fourier integral transform 54
- Unit step function 50
- Unit vector 2

- Vector, as complex number 3
 - rotation 2
- Vibrating reed accelerometer 181

- WESSEL, CASPER 2
- Wien-bridge oscillator 122
- w -plane 7

- Zeros of functions 18
- z -plane 5

OTHER TITLES IN THE SERIES

- Vol. 1 *Signal Noise and Resolution in Nuclear Counter Amplifiers*
by A. B. GILLESPIE
- Vol. 2 *Scintillation Counters*
by J. B. BIRKS
- Vol. 3 *Probability and Information Theory with Applications to Radar*
by P. M. WOODWARD
- Vol. 4 *Physics and Applications of Secondary Electron Emission*
by H. BRUINING
- Vol. 5 *Millimicrosecond Pulse Techniques* (2nd Edition)
by I. A. D. LEWIS and F. H. WELLS
- Vol. 6 *Introduction to Electronic Analogue Computers* (2nd Edition)
by C. A. A. WASS and K. C. GARNER
- Vol. 7 *Scattering and Diffraction of Radio Waves*
by J. R. MENTZER
- Vol. 8 *Space Charge Waves and Slow Electromagnetic Waves*
by A. H. W. BECK
- Vol. 9 *Statistical Theory of Signal Detection*
by C. W. HELSTROM
- Vol. 11 *Frequency Modulation Theory—Application to Microwave Links*
by J. FAGOT and PH. MAGNE
- Vol. 12 *Theory of Microwave Valves*
by S. D. GVOZDOVER
- Vol. 13 *Electronic Computers*
by A. I. KITOV and N. A. KRINITSKII
- Vol. 14 *Topics in Engineering Logic*
by M. NADLER
- Vol. 15 *Environmental Testing Techniques for Electronics and Materials*
by G. W. A. DUMMER and N. B. GRIFFIN
- Vol. 16 *Fundamentals of Microwave Electronics*
by V. N. SHEVCHIK
- Vol. 17 *Static Electromagnetic Frequency Changers*
by L. L. ROZHANSKII
- Vol. 18 *Problems in the Design and Development 750 MW Turbogenerators*
by V. P. ANEMPODISTOV, E. G. KASHARSKII and I. D. URUSOV

- Vol. 19 *Controlled-Delay Devices*
by S. A. DOGANOVSKII and V. A. IVANOV
- Vol. 20 *High Sensitivity Counting Techniques*
by D. E. WATT and D. RAMSDEN
- Vol. 21 *Asynchronized Synchronous Machines*
by M. M. BOTVINNIK
- Vol. 22 *Sampling Systems Theory and Its Application, Vol. 1*
by YA. Z. TSYPKIN
- Vol. 23 *Sampling Systems Theory and Its Application, Vol. 2*
by YA. Z. TSYPKIN
- Vol. 24 *Transient Phenomena in Electrical Power Systems*
by V. A. VENIKOV
- Vol. 25 *Digital Differential Analysers*
by A. V. SHLEIKO
- Vol. 26 *The Use of Ferrites at Microwave Frequencies*
by L. THOUREL
- Vol. 27 *The Theory and Practice of Scintillation Counting*
by J. B. BIRKS
- Vol. 28 *Energetic Processes in Follow-up Electrical Control Systems*
by A. A. BULGAROV
- Vol. 29 *Excitation Control*
by G. M. ULANOV
- Vol. 30 *Electrical Analogues of Pin-Jointed Systems*
by K. K. KEROPYAN
- Vol. 31 *Electromagnetic Clutches and Couplings*
by T. M. VOROB'YEVA
- Vol. 32 *Elements of Theoretical Mechanics for Electronic Engineers*
by F. BULTOT
- Vol. 33 *Transient Phenomena in Electrical Power Systems—Problems and Illustrations*
by V. A. VENIKOV
- Vol. 34 *Wave and Oscillatory Phenomena in Electron Beams at Microwave Frequencies*
by V. N. SHEVCHIK, G. N. SHVEDOV and A. V. SOBOLEVA
- Vol. 35 *Modulation, Resolution Signal Processing in Radar, Sonar and Related Systems*
by R. BENJAMIN
- Vol. 36 *Basic Matrix Analysis and Synthesis*
by G. ZELINGER